

# Mikroelektronische Schaltungen und Systeme

Lect. 4


## Differential Amplifiers



Prof. Dr.-Ing. Ahmet Cagri Ulusoy  
Institut für Technik der Informationsverarbeitung (ITIV)


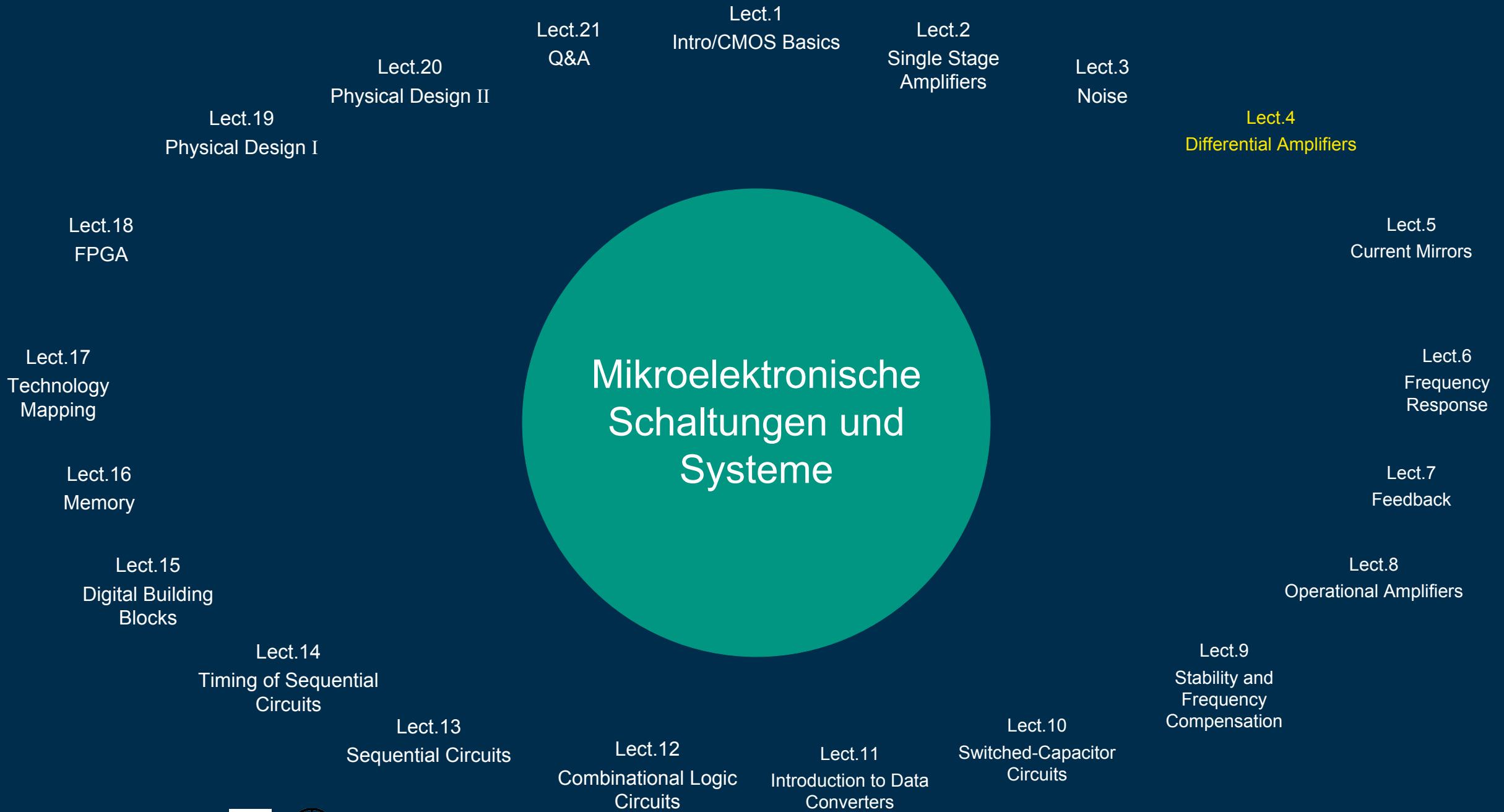
# Mikroelektronische Schaltungen und Systeme









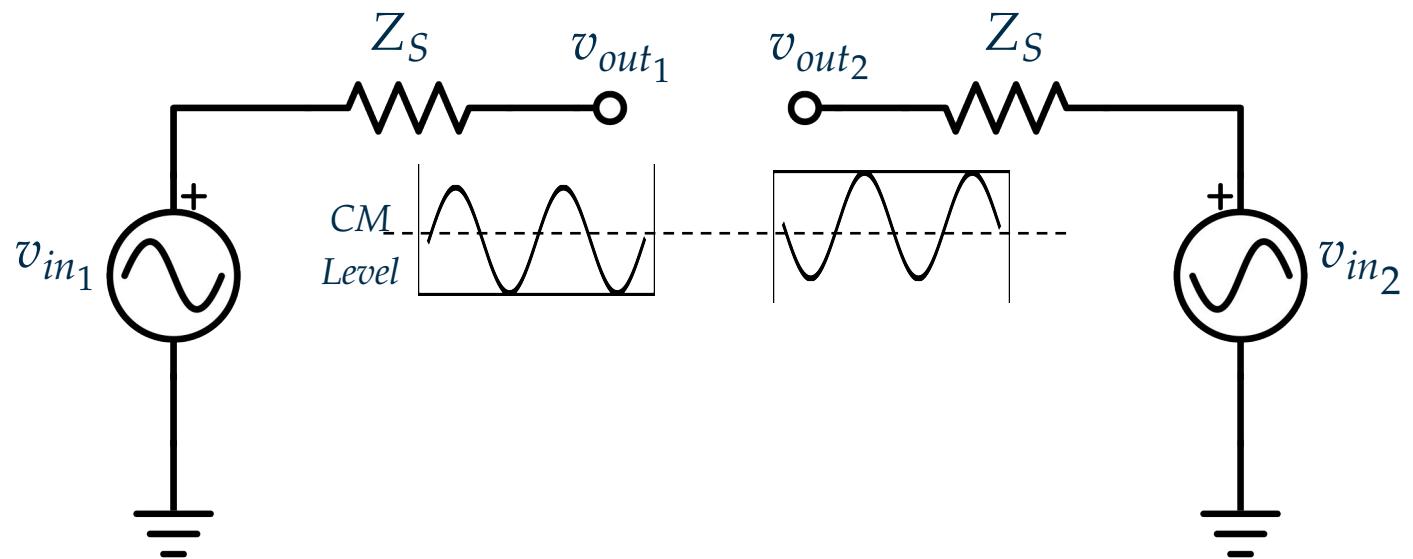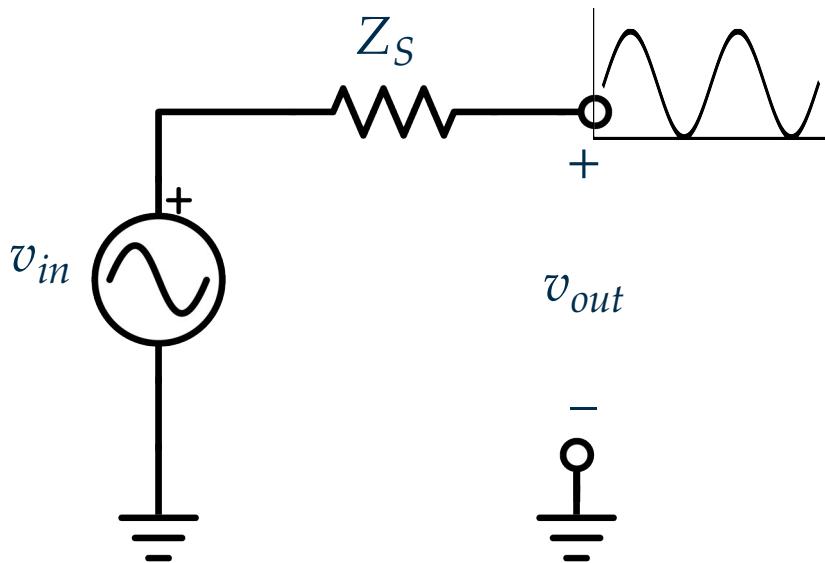
# Differential Operation

- **Single-Ended Signal:** Measured with respect to a fixed potential, usually ground.
- **Differential Signal:** Measured between two nodes (e.g.  $v_{out_1}$ ,  $v_{out_2}$ ) that have equal and opposite excursions around a "common-mode" (CM) level.




# Differential Operation

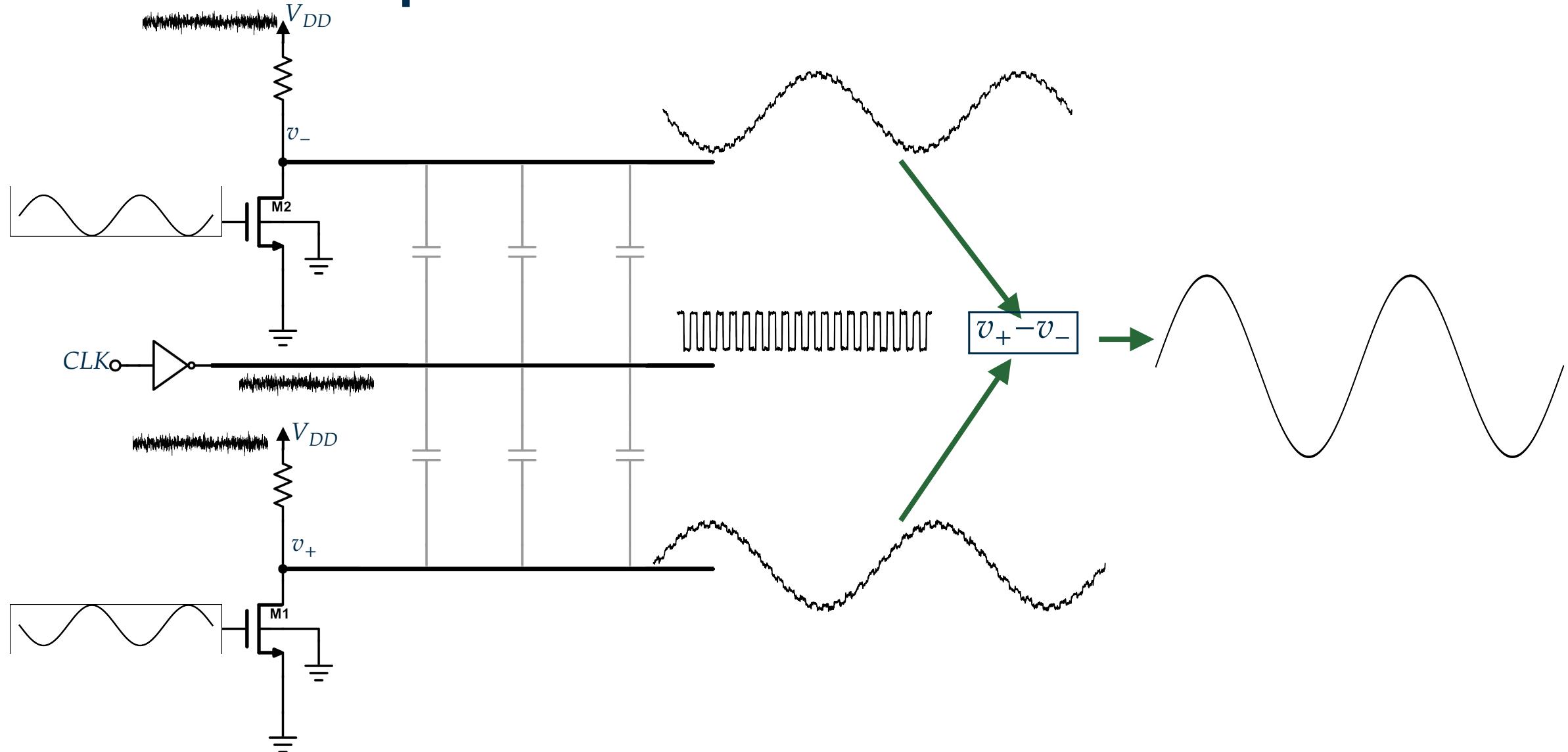


# Differential Operation
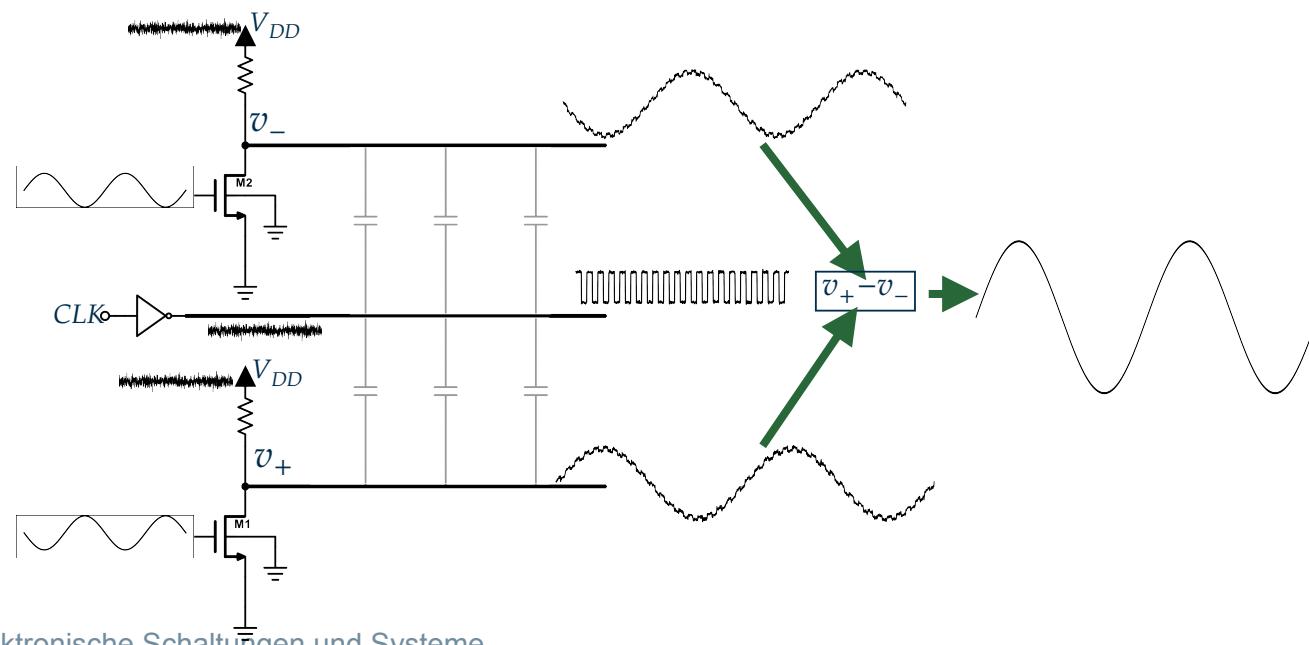
## Why Differential?

- A single-ended signal is highly sensitive to noise or interference (e.g., a clock line) coupling onto it. The amplifier can't distinguish the noise from the signal.
- Differential lines are physically close. The interference couples equally to both lines as a common-mode signal.
- A differential amplifier amplifies only the difference between the lines, rejecting the common-mode noise.






# Basic Differential Pair



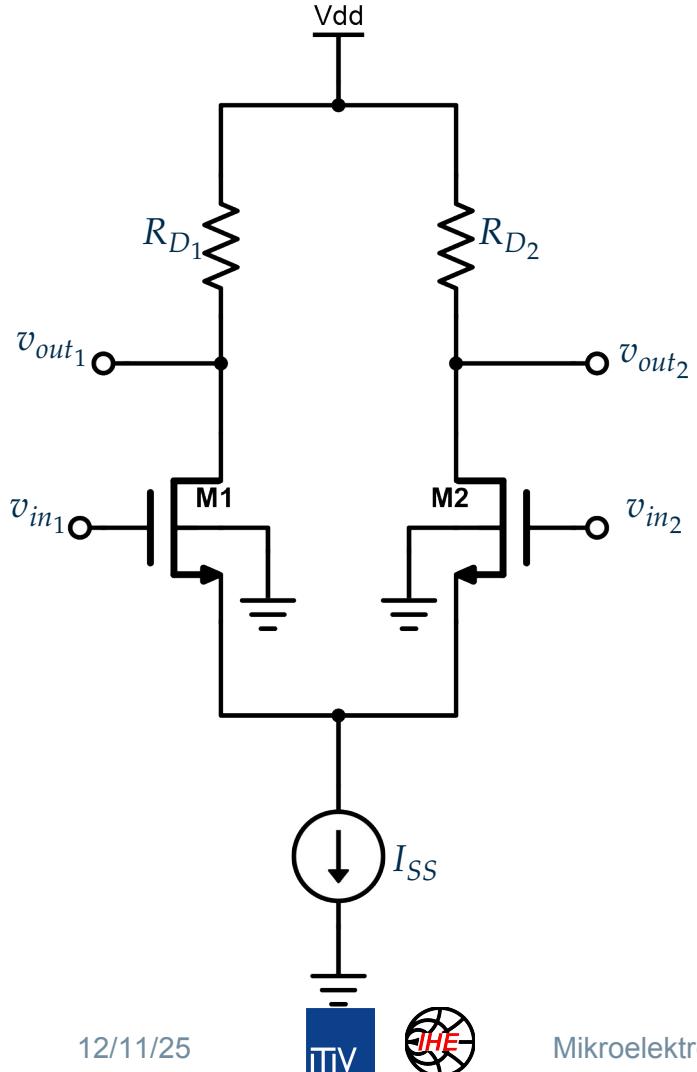


- Two identical single-ended CS amplifiers with differential inputs and a common-mode level are utilized to form a differential pair.
- The output is also differential and has its own common-mode level.
- This topology offers improved noise rejection and larger output swing. However, variations in the input common-mode level can degrade the common-mode rejection ratio (CMRR) and impact overall circuit performance.


# Basic Differential Pair

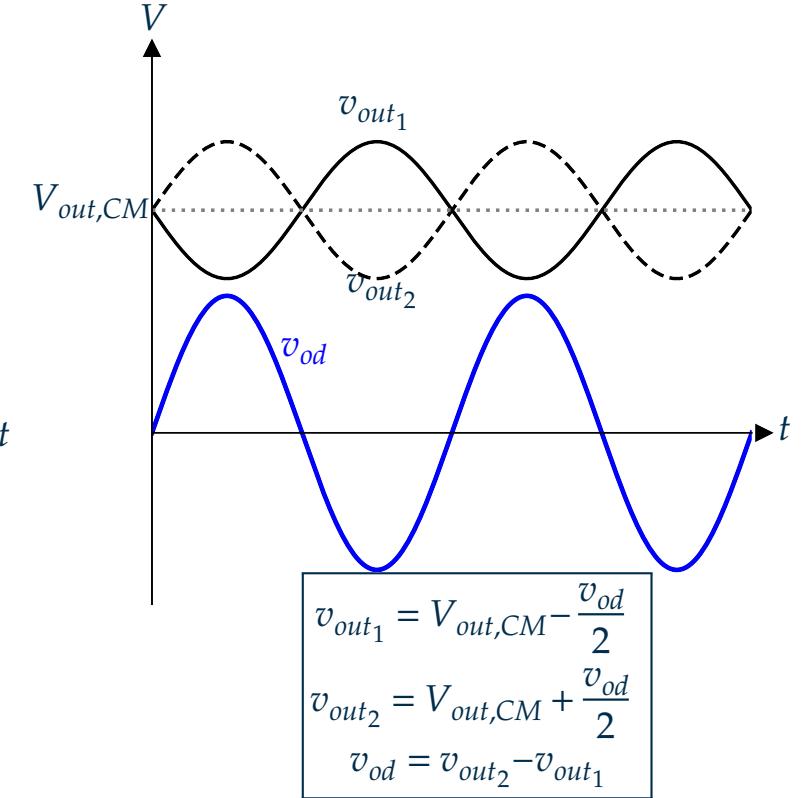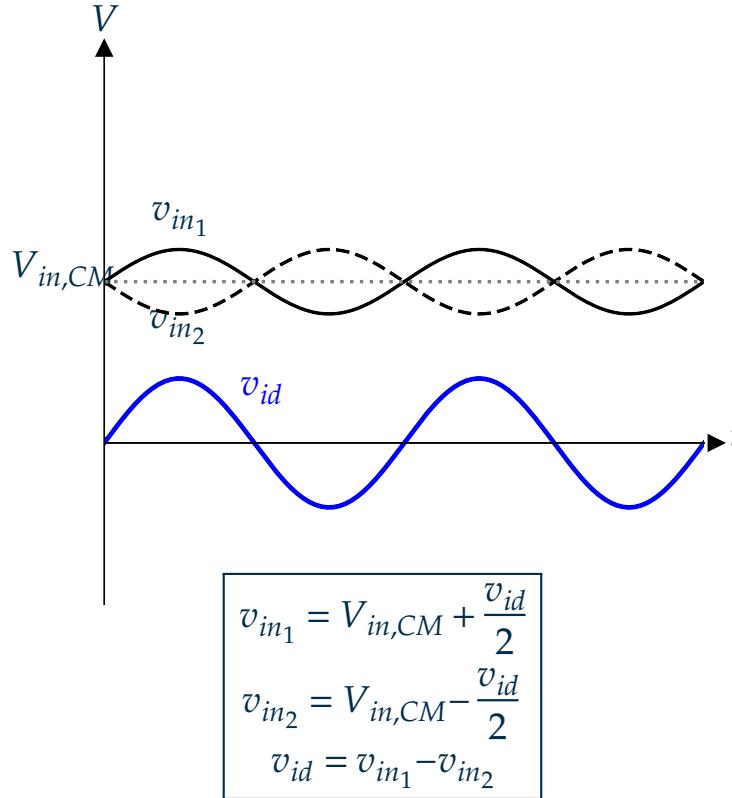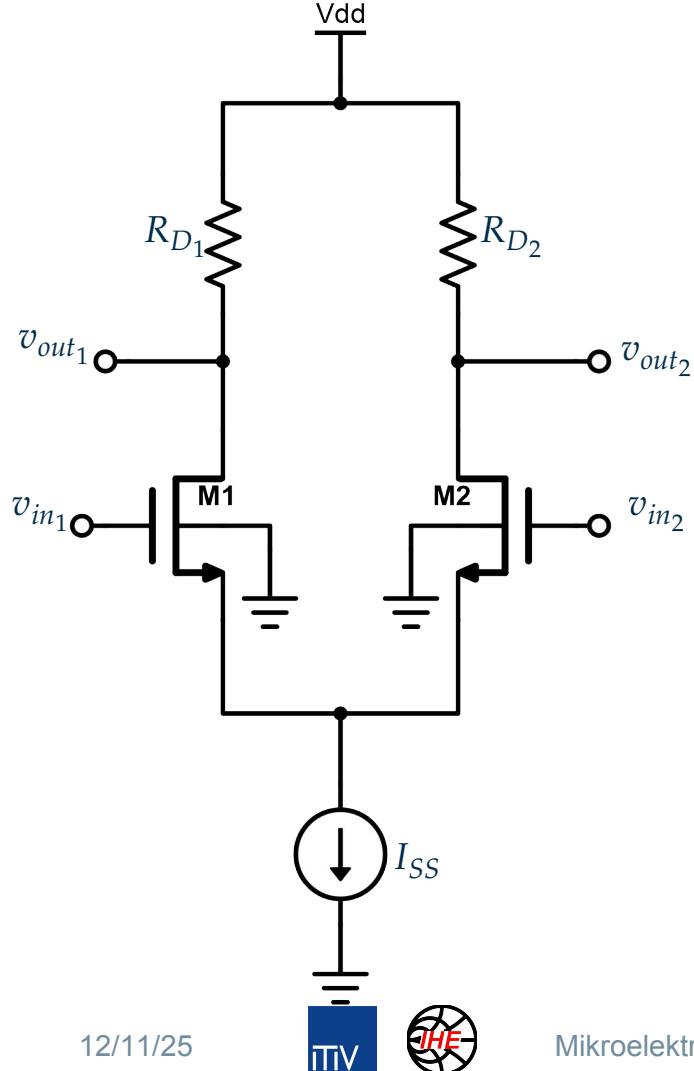

# Basic Differential Pair

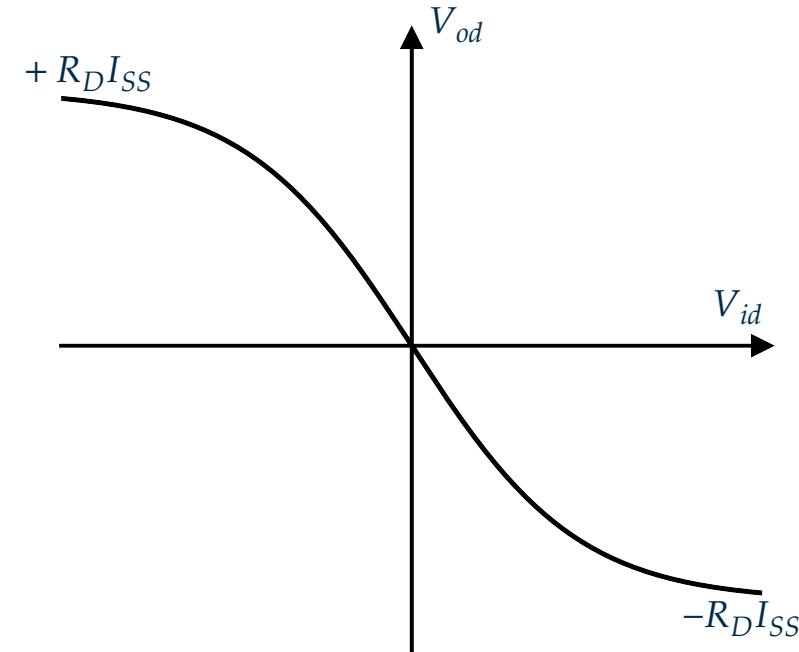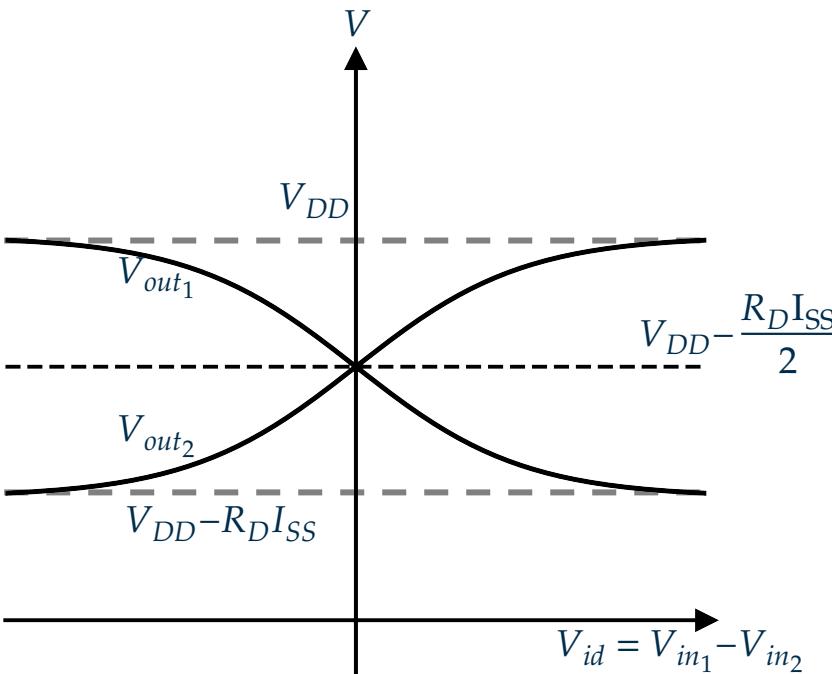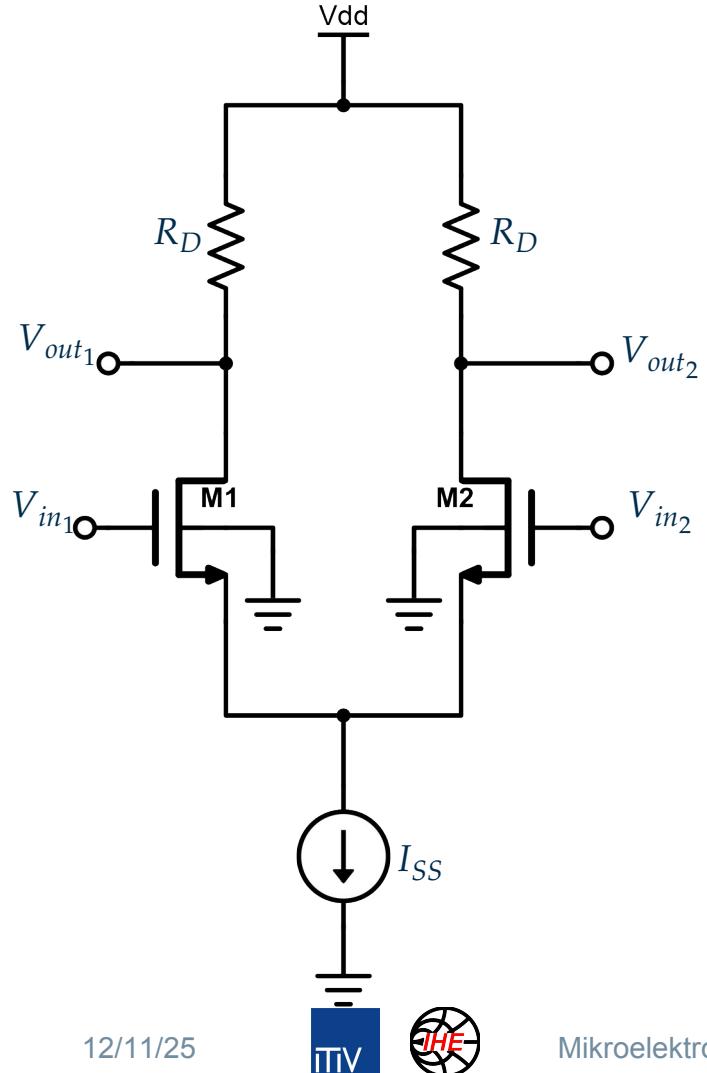

# Voltage Swing Boundaries

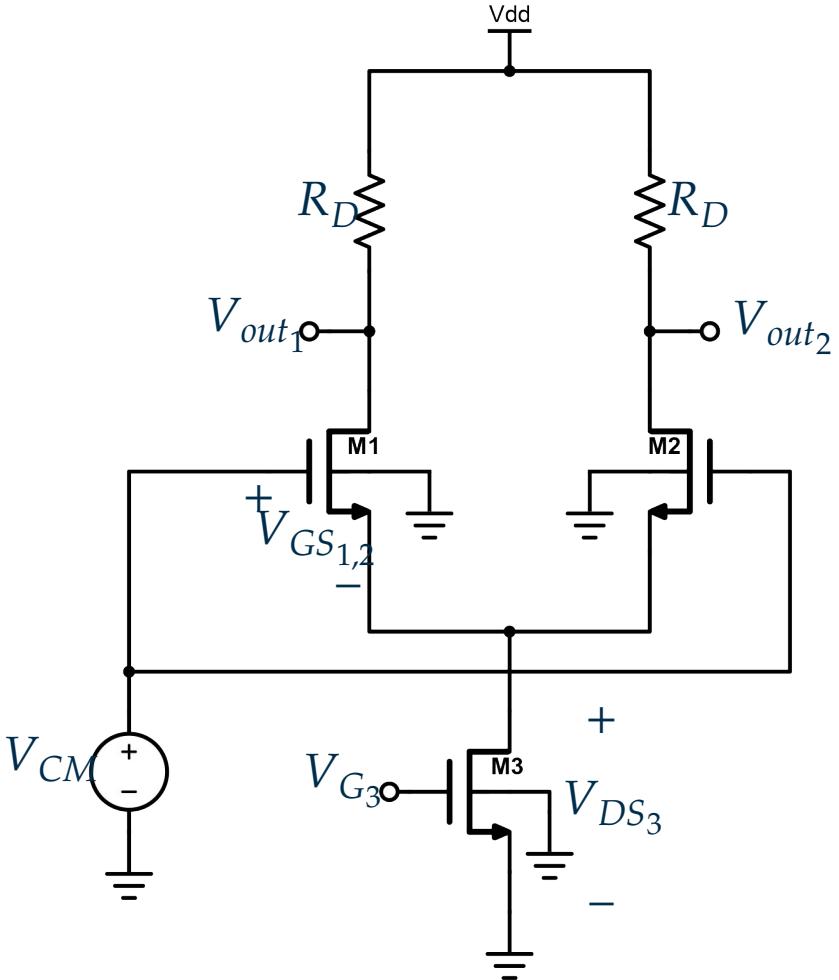


$$V_{DS_3} = V_{GS_3} - V_{TH_3}$$

$$V_{CM} \geq V_{DS_3} + V_{GS_1}$$

$$V_{CM} \geq V_{GS_{1,2}} + (V_{GS_3} - V_{TH_3})$$

# Voltage Swing Boundaries

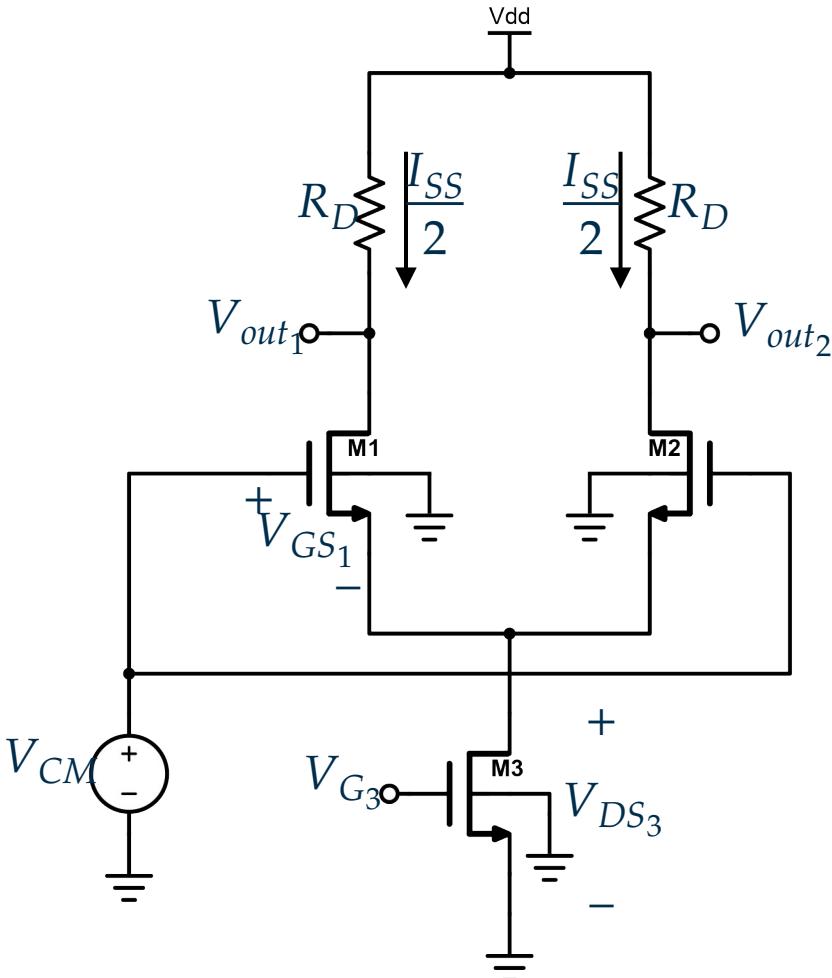

$$V_{out_1} = V_{DD} - \frac{I_{SS}}{2} R_D, \quad V_{CM} = V_{DS_3} + V_{GS_1}$$


$$V_{out_1} - V_{DS_3} \geq V_{GS_1} - V_{TH_1}$$

$$V_{DD} - \frac{I_{SS}}{2} R_D \geq V_{CM} - V_{TH_1}$$

$$V_{CM} \leq V_{TH_1} + V_{DD} - \frac{I_{SS}}{2} R_D$$


$$V_{GS_1} + (V_{GS_3} - V_{TH_3}) \leq V_{CM} \leq V_{TH_1} + V_{DD} - \frac{I_{SS}}{2} R_D$$

# Large Signal Analysis

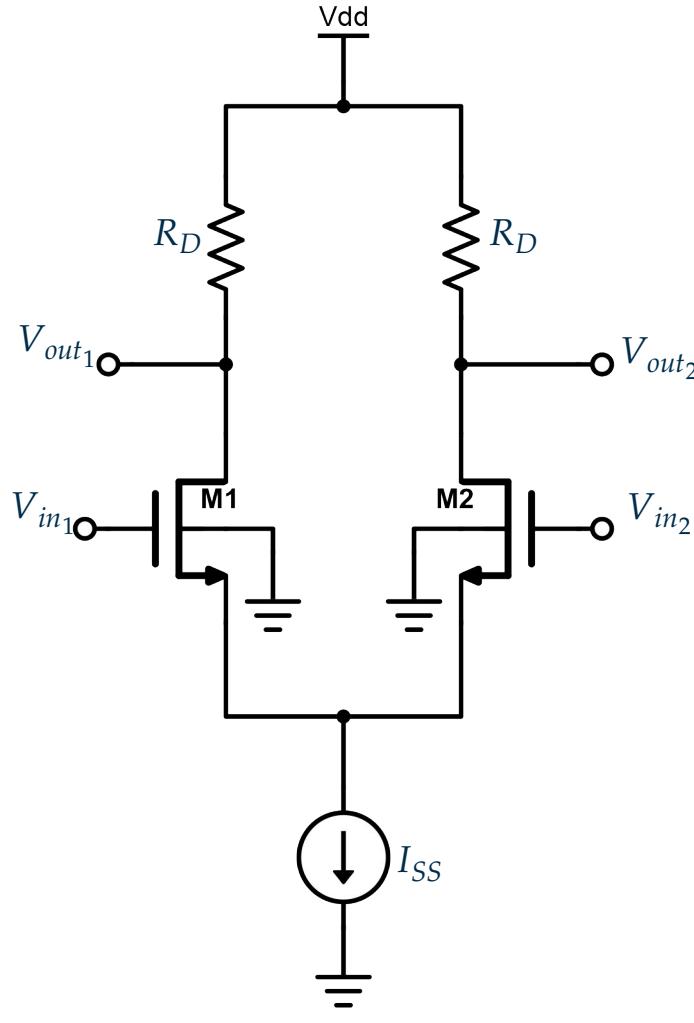

- $(V_{GS} - V_{TH})^2 = \frac{I_D}{\frac{1}{2}\mu_n C_{ox} \frac{W}{L}} \rightarrow V_{GS} = \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} + V_{TH}$
- $V_{in_1} - V_{in_2} = \sqrt{\frac{2I_{D1}}{\mu_n C_{ox} \frac{W}{L}}} - \sqrt{\frac{2I_{D2}}{\mu_n C_{ox} \frac{W}{L}}}$
- $(V_{in_1} - V_{in_2})^2 = \frac{2}{\mu_n C_{ox} \frac{W}{L}} (I_{SS} - 2 \sqrt{I_{D1} I_{D2}})$
- $\frac{1}{2}\mu_n C_{ox} \frac{W}{L} (V_{in_1} - V_{in_2})^2 - I_{SS} = -2 \sqrt{I_{D1} I_{D2}}$
- $(I_{D1} - I_{D2})^2 = -\frac{1}{4} \left( \mu_n C_{ox} \frac{W}{L} \right)^2 (V_{in_1} - V_{in_2})^4 + I_{SS} \mu_n C_{ox} \frac{W}{L} (V_{in_1} - V_{in_2})^2$
- $I_{D1} - I_{D2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in_1} - V_{in_2}) \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{in_1} - V_{in_2})^2}$
- $\frac{\partial \Delta I_D}{\partial \Delta V_{in}} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \frac{\frac{4I_{SS}}{\mu_n C_{ox} W/L} - 2\Delta V_{in}^2}{\sqrt{\frac{4I_{SS}}{\mu_n C_{ox} W/L} - \Delta V_{in}^2}}$
- For  $\Delta V_{in} = 0$ ,  $G_m = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}}$
- $|A_d| = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS} R_D}$
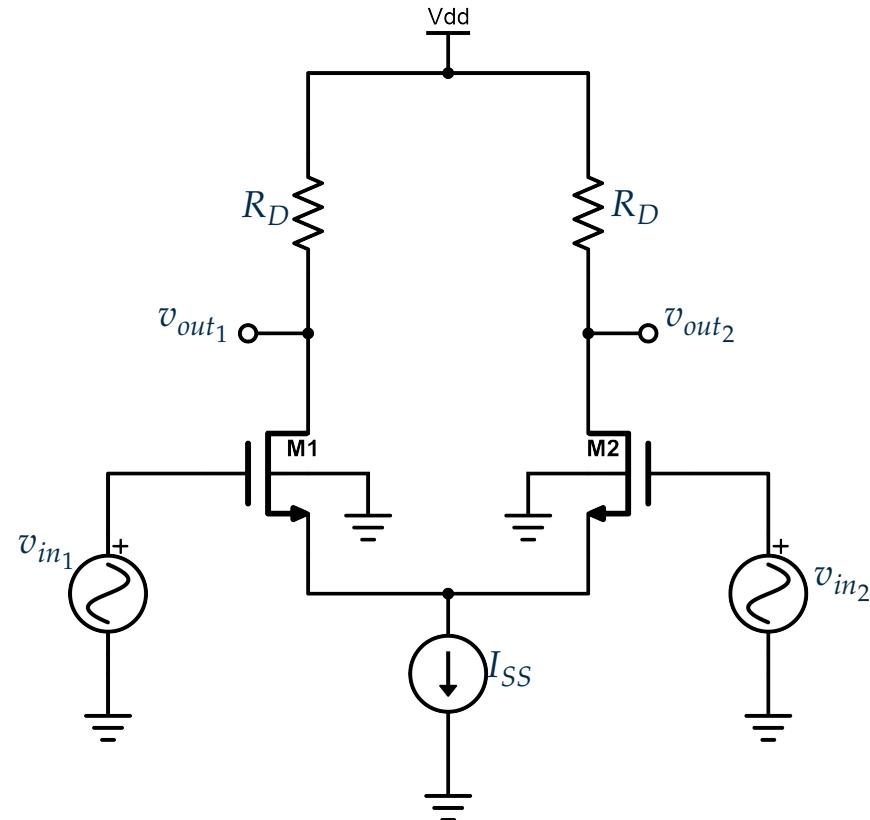
# Differential Amplifier Small-Signal Analysis




- Small signals  $v_{in_1}$  and  $v_{in_2}$  are applied as input.
- M1 and M2 are saturated.
- Two methods will be introduced for gain analysis.

# Differential Amplifier Small-Signal Analysis

$$g_{m_{eff}} = \frac{g_m}{1 + g_m R_S}$$

**Superposition (Only  $v_{in_1}$ )**

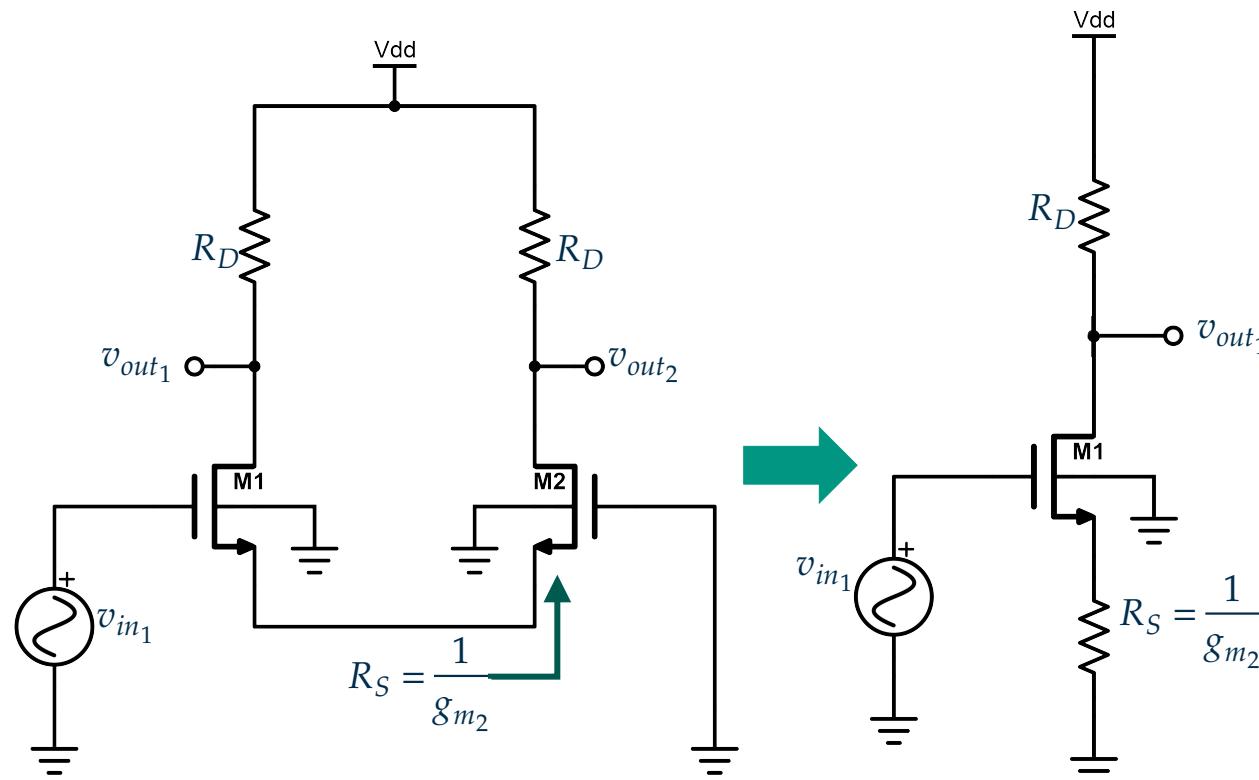

$$\frac{v_{out_1}}{v_{in_1}} = -\frac{R_D}{\frac{1}{g_{m_1}} + \frac{1}{g_{m_2}}}, \quad \frac{v_{out_2}}{v_{in_1}} = \frac{R_D}{\frac{1}{g_{m_2}} + \frac{1}{g_{m_1}}}$$

$$(v_{out_1} - v_{out_2}) \mid_{\text{due to } v_{in_1}} = -\frac{2R_D}{\frac{1}{g_{m_1}} + \frac{1}{g_{m_2}}} v_{in_1}$$

Due to the symmetry, the effect of  $v_{in_2}$  at the output ports is identical to that of  $v_{in_1}$  except for a change in polarities.

$$(v_{out_1} - v_{out_2}) \mid_{\text{due to } v_{in_2}} = \frac{2R_D}{\frac{1}{g_{m_1}} + \frac{1}{g_{m_2}}} v_{in_2}$$


$$\frac{v_{out_1} - v_{out_2}}{v_{in_1} - v_{in_2}} = -\frac{2R_D}{\frac{1}{g_{m_1}} + \frac{1}{g_{m_2}}}$$

For  $g_m = g_{m_1} = g_{m_2}$


$$\frac{v_{out_1} - v_{out_2}}{v_{in_1} - v_{in_2}} = -g_m R_D$$

# Differential Amplifier Small-Signal Analysis

## Half Circuit Analysis

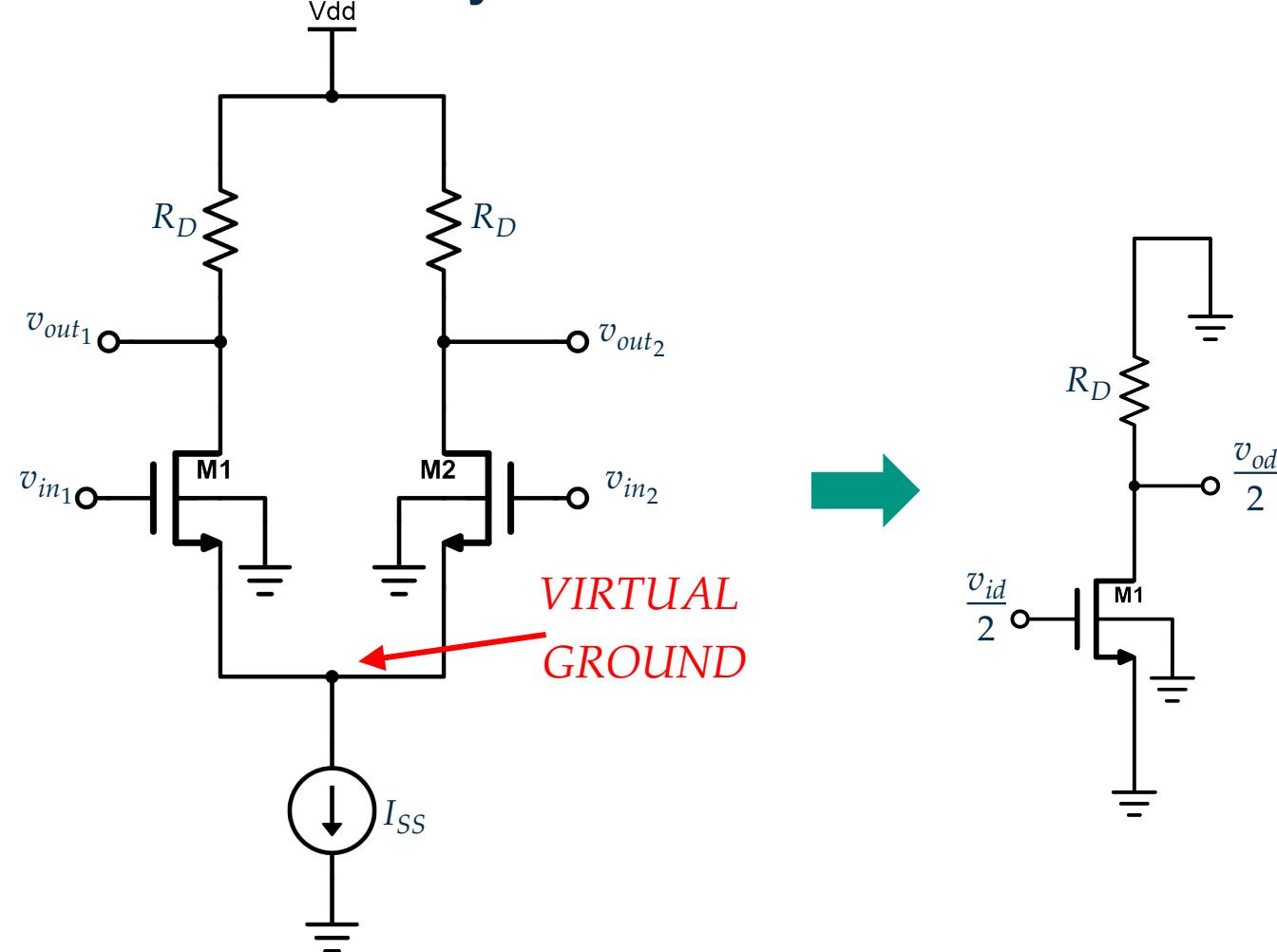

# Common-Mode Response

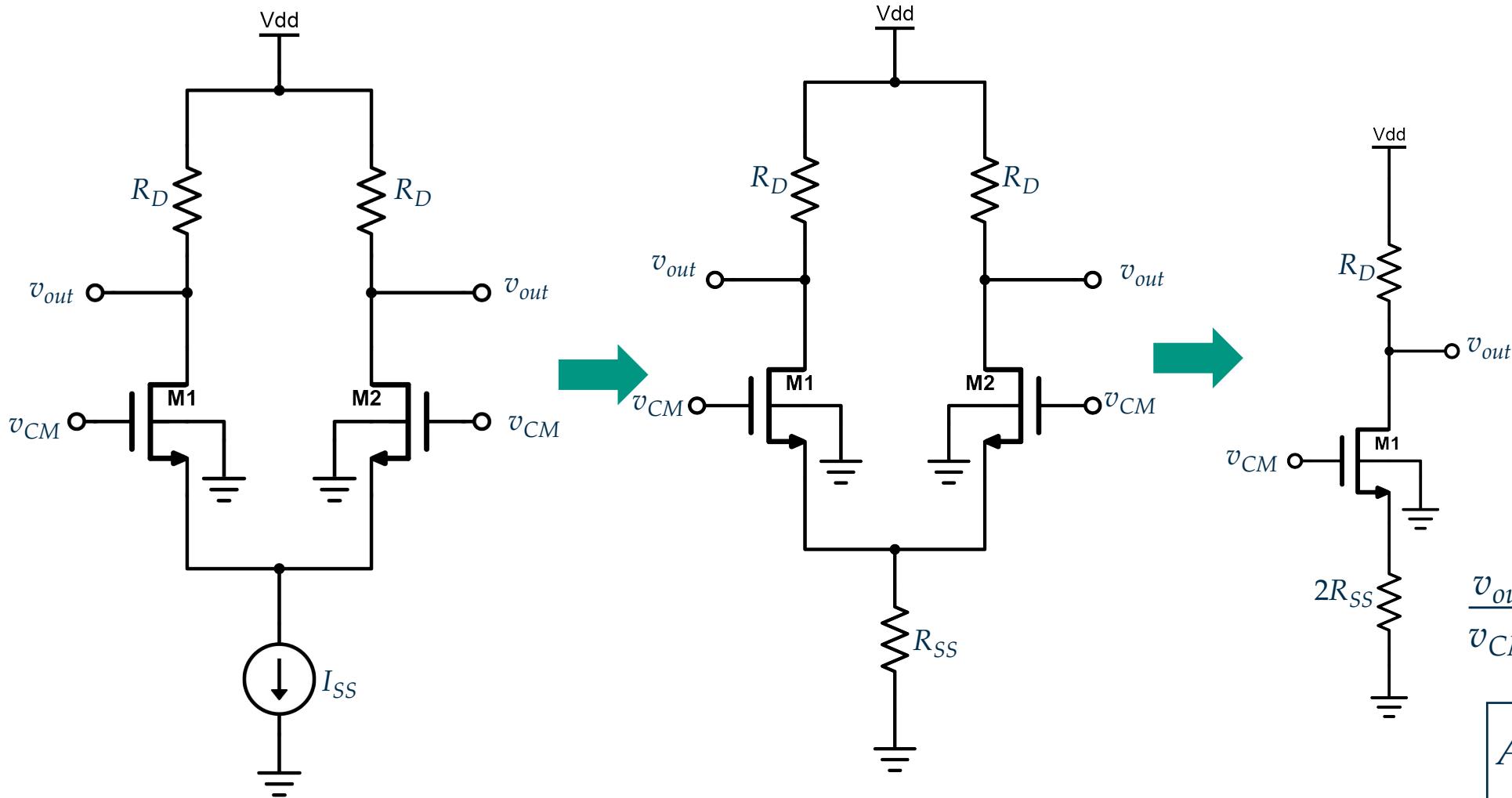


$$\frac{v_{out}}{v_{CM}} = -\frac{g_m}{1 + g_m 2R_{SS}} R_D$$

$$A_{cm} = \frac{v_{out}}{v_{CM}} \approx -\frac{R_D}{2R_{SS}}$$

# Common-Mode Response

## $R_D$ Mismatch

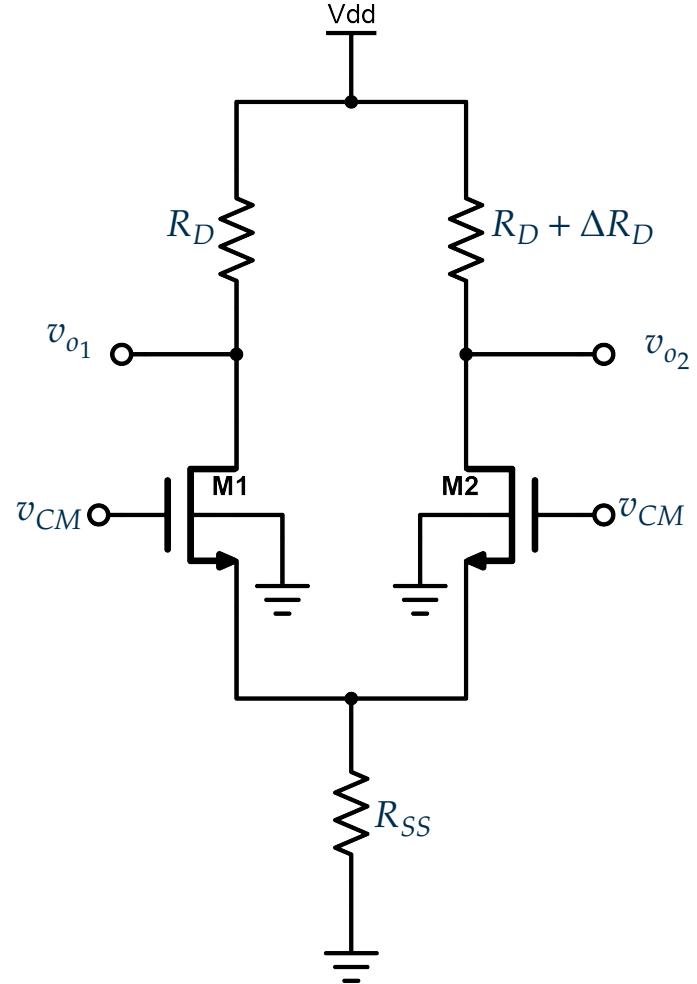

$$v_{o_1} = -\frac{R_D}{2R_{SS}} v_{CM}$$

$$v_{o_2} = -\frac{R_D + \Delta R_D}{2R_{SS}} v_{CM}$$

$$v_{o_d} = v_{o_2} - v_{o_1} = -\frac{\Delta R_D}{2R_{SS}} v_{CM}$$


$$A_{cm} = \frac{v_{o_d}}{v_{CM}} = -\frac{\Delta R_D}{2R_{SS}} = -\left(\frac{R_D}{2R_{SS}}\right)\left(\frac{\Delta R_D}{R_D}\right)$$

# Common-Mode Rejection Ratio (CMRR)

$$CMRR = \frac{\text{Differential Gain}}{\text{Common-Mode Gain}} = \frac{|A_d|}{|A_{cm}|} \approx \frac{g_m R_D}{\frac{R_D}{2R_{SS}}} = 2g_m R_{SS}$$
$$CMRR(dB) = 20 \log \left( \frac{|A_d|}{|A_{cm}|} \right)$$

# Differential Pair with MOS Loads

## Diode-Connected Load

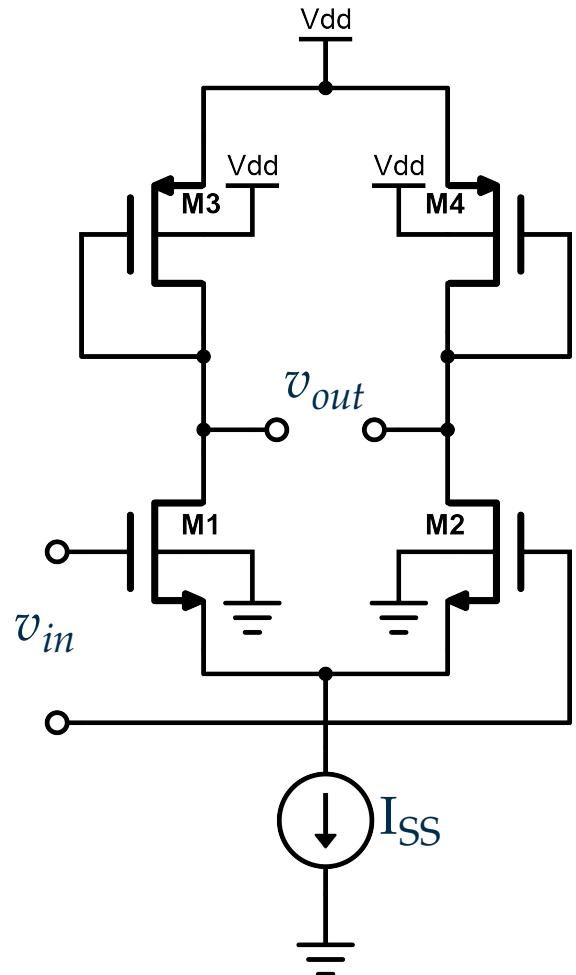


$$A_d = \frac{v_{out}}{v_{in}} = -g_{mN} \left( \frac{1}{g_{mP}} \parallel r_{oN} \parallel r_{oP} \right)$$

- N and P denote NMOS and PMOS, respectively.

$$A_d = \frac{v_{out}}{v_{in}} \approx -\frac{g_{mN}}{g_{mP}} = -\sqrt{\frac{\mu_n \left(\frac{W}{L}\right)_N}{\mu_p \left(\frac{W}{L}\right)_P}}$$

# Differential Pair with MOS Loads


## Current-Source Load

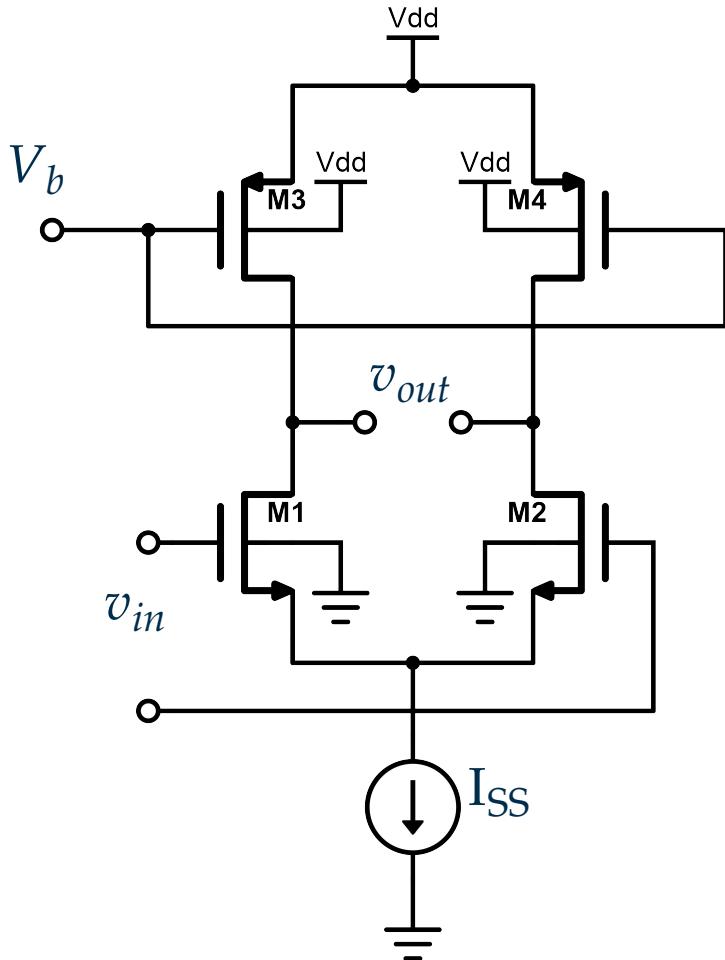

$$A_d = \frac{v_{out}}{v_{in}} = -g_m N (r_{oN} \parallel r_{oP})$$


# Differential Pair with MOS Loads

## Self-Biased Load

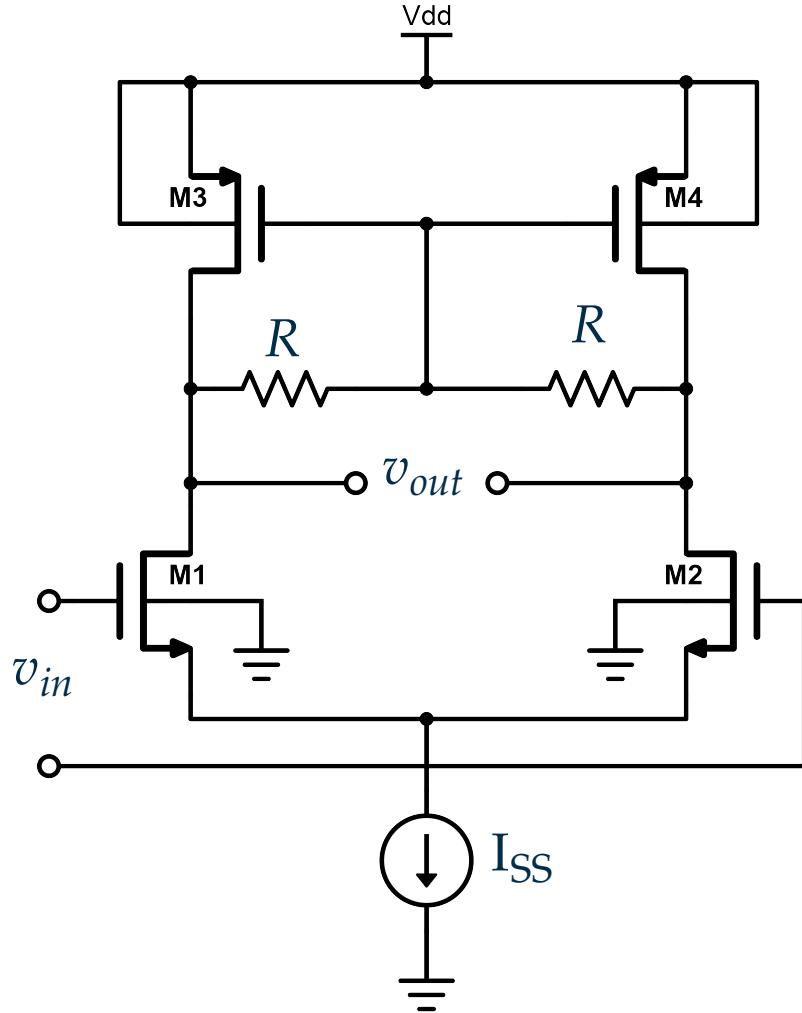

$$A_d = \frac{v_{out}}{v_{in}} = -g_m (r_{o1} \parallel R \parallel r_{o3})$$

# Cascode Differential Pair

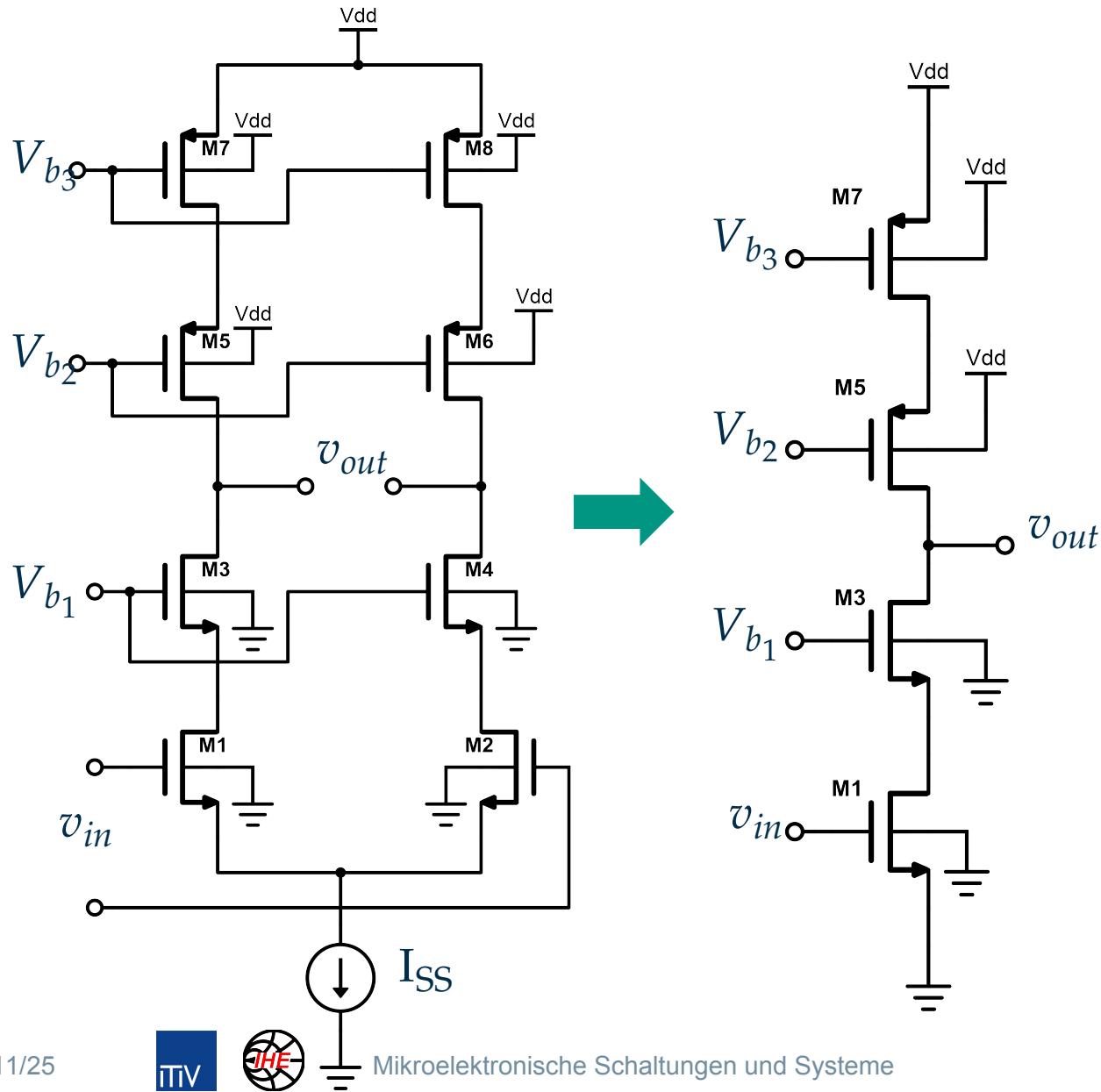

$$|A_d| \approx g_{m_1} [(g_{m_3} r_{o_3} r_{o_1}) \parallel (g_{m_5} r_{o_5} r_{o_7})]$$