

# Mikroelektronische Schaltungen und Systeme

## Lect.6 Frequency Response

Prof. Dr.-Ing. Ahmet Cagri Ulusoy  
Institut für Hochfrequenztechnik und Elektronik (IHE)



# Mikroelektronische Schaltungen und Systeme

Lect.1

Intro/CMOS Basics

Lect.2

Single Stage  
Amplifiers

Lect.3

Noise

Lect.4

Differential  
Amplifiers

Lect.5

Current Sources

Lect.6

Frequency  
Response

Lect.7

Feedback

Lect.8

Operational Amplifiers

Lect.9

Stability and  
Frequency  
Compensation

Lect.10

Switched-Capacitor  
Circuits

Lect.11

Introduction to Data  
Converters

Lect.12

Combinational Logic  
Circuits

Lect.13

Sequential Circuits

Lect.14

Timing of Sequential  
Circuits

Lect.15

Digital Building  
Blocks

Lect.16

Memory

Lect.17

Technology  
Mapping

Lect.18

FPGA

Lect.19

Physical Design I

Lect.20

Physical Design II


Lect.21

Q&A






# Introduction

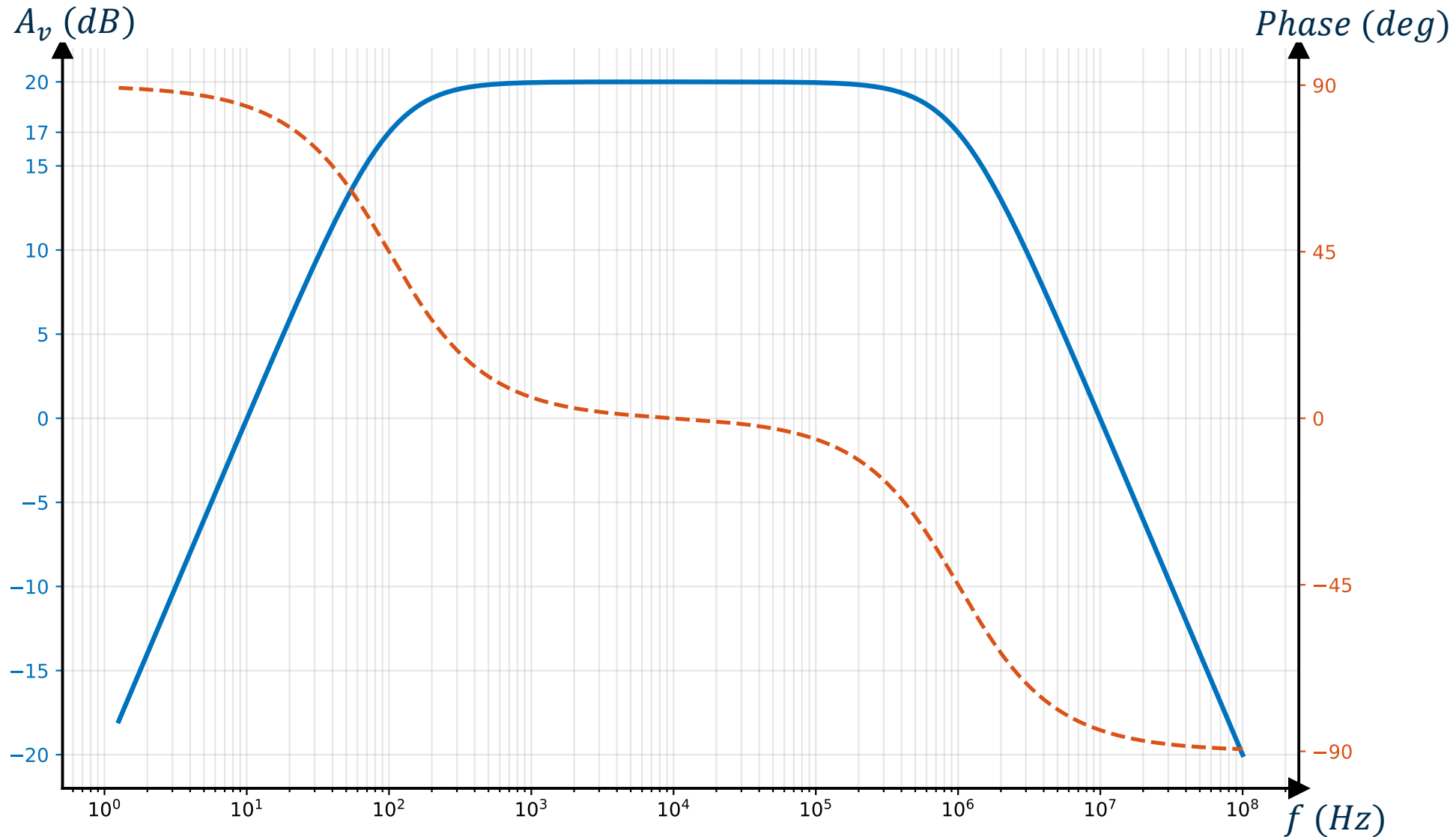

# Introduction

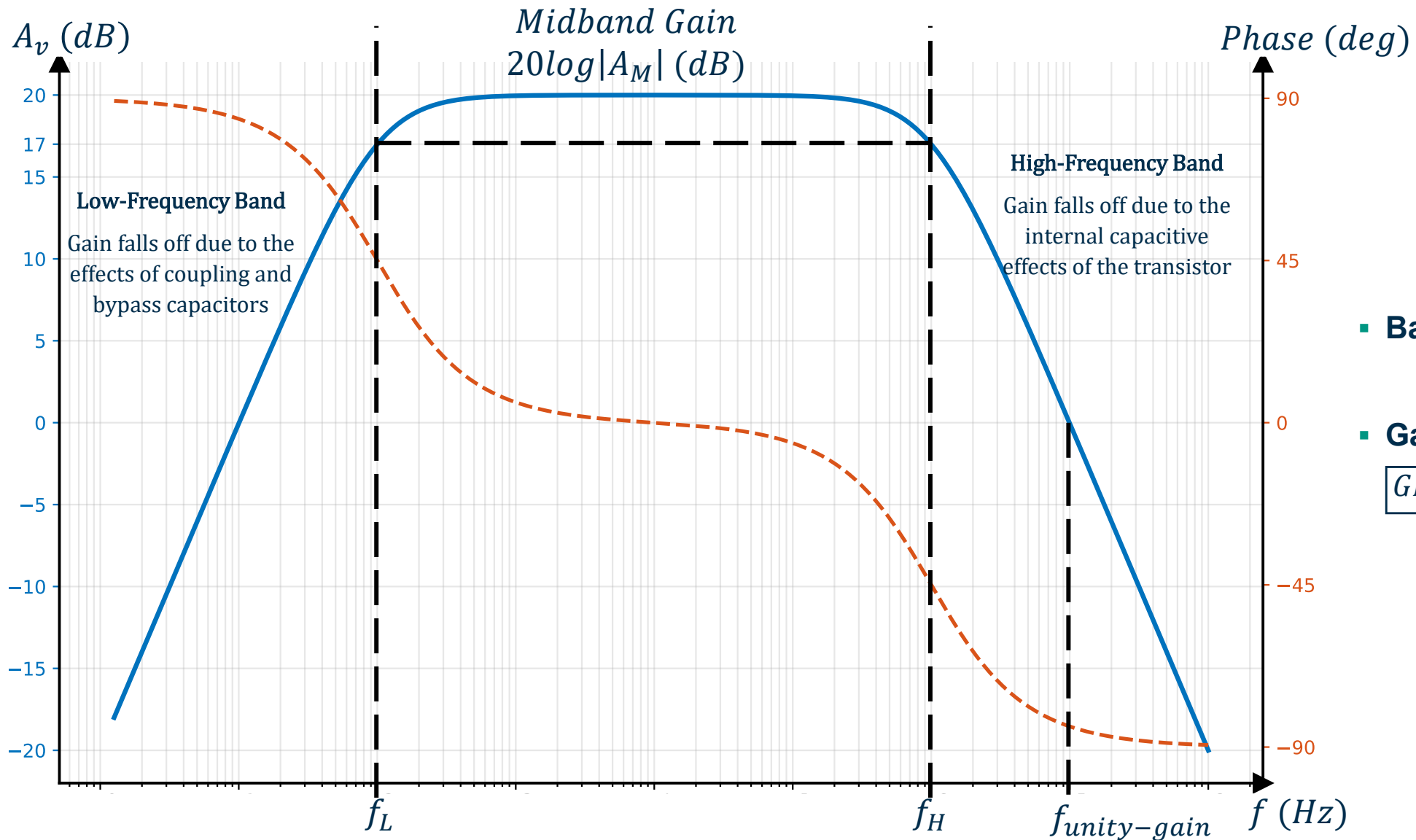

- **Bandwidth:**

$$BW = f_H - f_L$$

- **Gain-Bandwidth Product:**

$$GBW = |A_M|BW \approx f_{unity-gain}$$

# Transfer Function

- The transfer function of a circuit at steady state can be written as:



$$A(j\omega) = a_0 \frac{\left(1 + \frac{j\omega}{\omega_{z_1}}\right) \left(1 + \frac{j\omega}{\omega_{z_2}}\right) \dots \left(1 + \frac{j\omega}{\omega_{z_n}}\right)}{\left(1 + \frac{j\omega}{\omega_{p_1}}\right) \left(1 + \frac{j\omega}{\omega_{p_2}}\right) \dots \left(1 + \frac{j\omega}{\omega_{p_m}}\right)}$$

**Poles:** Magnitude: -3-dB, -20dB/decade, Phase: -45° asymptotically -90°

**Zeros:** Magnitude: +3-dB, +20dB/decade, Phase: +45° asymptotically +90°

**Dominant Pole Approximation:** The frequency points are far enough apart (sufficiently separated) that the poles and zeros can be considered separately.

# MOSFET Parasitic Capacitances

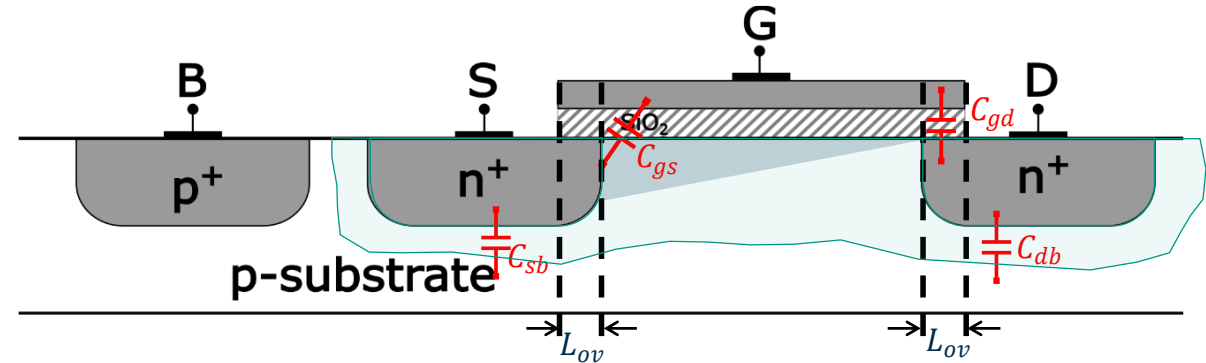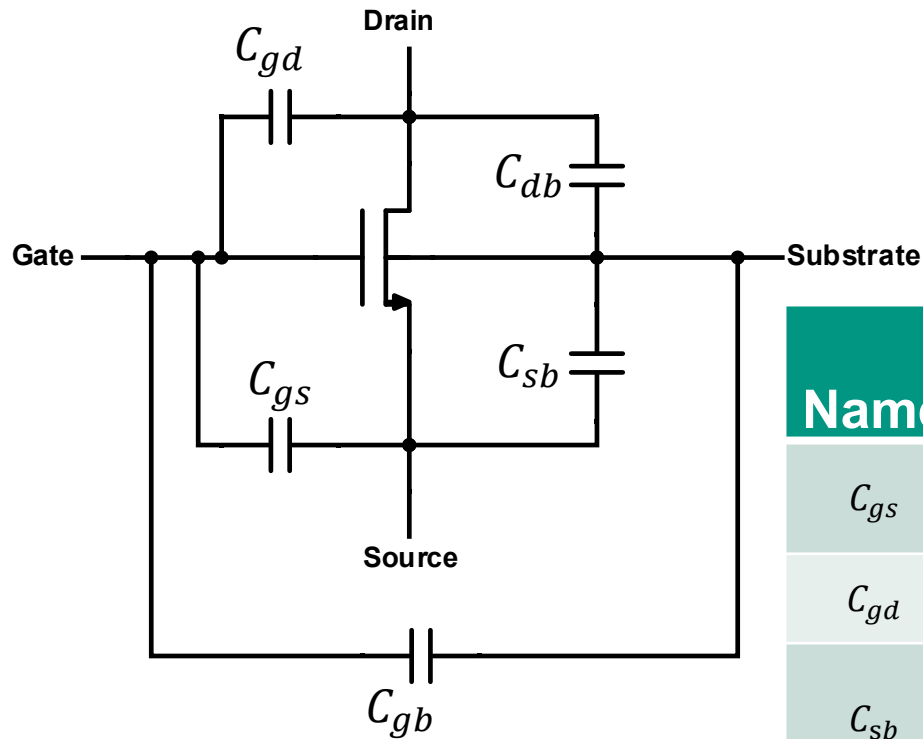


Name	Value in Saturation	Value in Triode
$C_{gs}$	$\frac{2}{3}WLC_{ox} + WL_{ov}C_{ox}$	$\frac{1}{2}WLC_{ox} + WL_{ov}C_{ox}$
$C_{gd}$	$WL_{ov}C_{ox}$	$\frac{1}{2}WLC_{ox} + WL_{ov}C_{ox}$
$C_{sb}$	$\frac{C_{sb0}}{\sqrt{1 + \frac{V_{SB}}{\phi_0}}}$	$\frac{C_{sb0}}{\sqrt{1 + \frac{V_{SB}}{\phi_0}}}$
$C_{db}$	$\frac{C_{db0}}{\sqrt{1 + \frac{V_{DB}}{\phi_0}}}$	$\frac{C_{db0}}{\sqrt{1 + \frac{V_{DB}}{\phi_0}}}$
$C_{gb}$	Omitted	Omitted


- $L_{ov}$ : Overlap length
- $C_{sb0}$ : The value of  $C_{sb}$  at zero body-source bias.
- $C_{db0}$ : The capacitance value at zero reverse-bias voltage.
- $\phi_0$ : Built-in junction potential


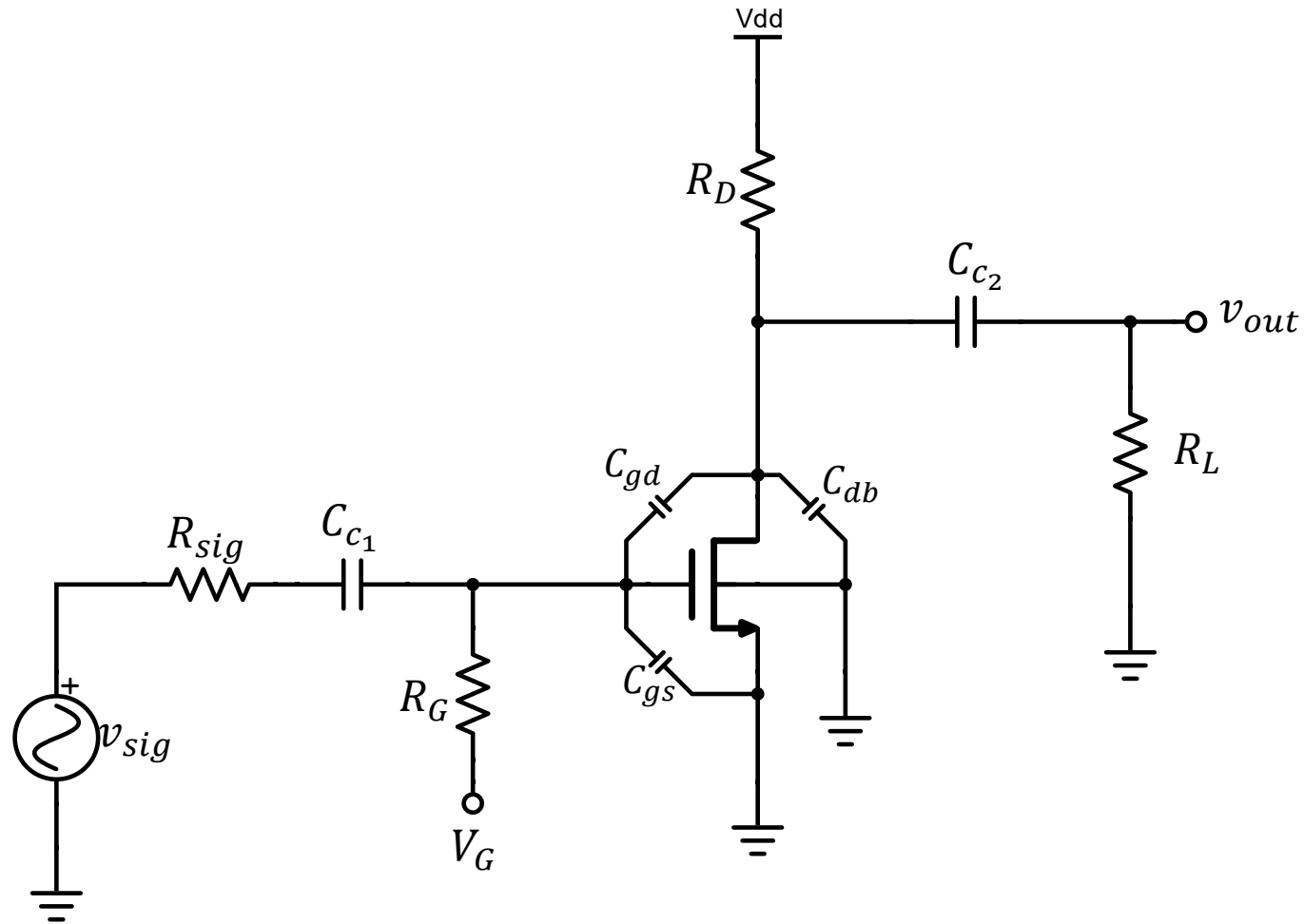
# Common-Source Amplifier with DC-Decoupling and Parasitic Capacitors




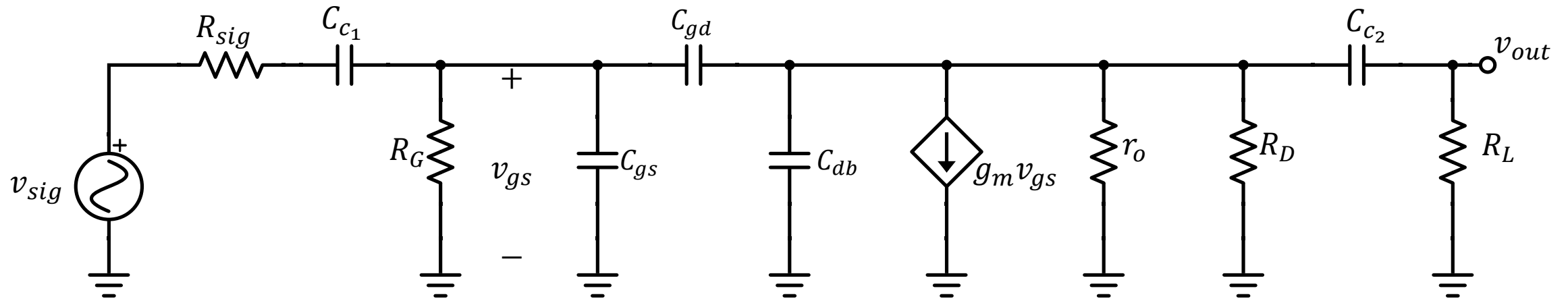
# Common-Source Amplifier with DC-Decoupling and Parasitic Capacitors



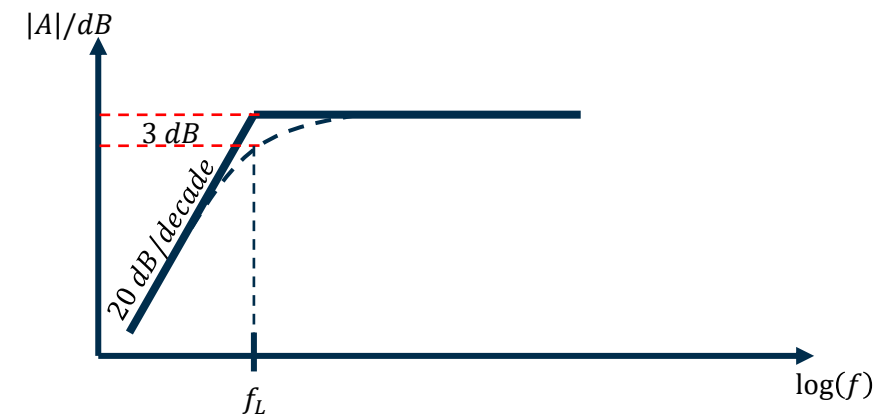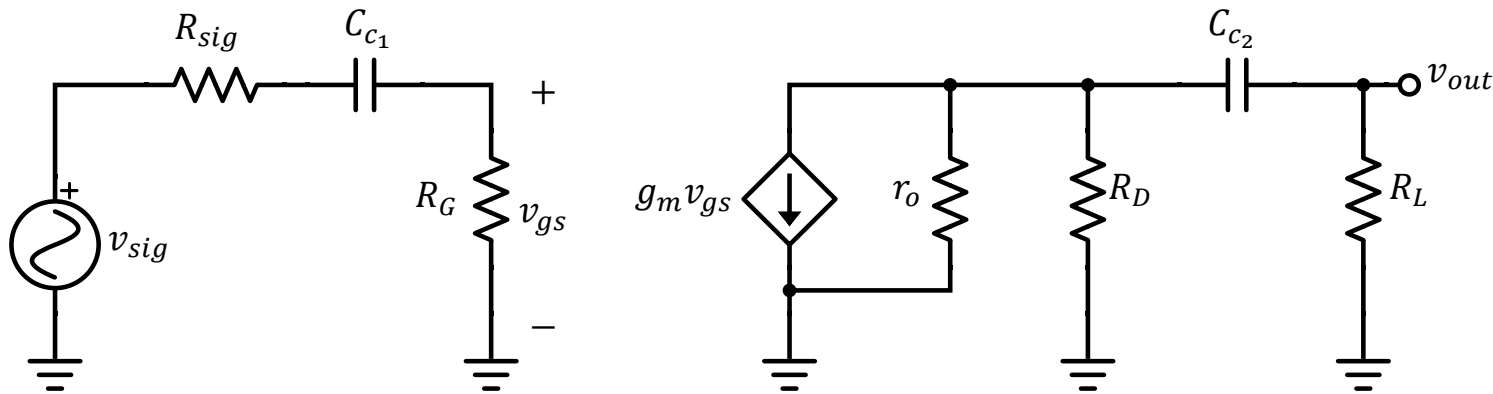
# Common-Source Amplifier Low-Frequency Response

- $C_{coupling} \gg C_{parasitics} \rightarrow \frac{1}{j\omega C_{parasitics}} \gg \frac{1}{j\omega C_{coupling}}$
- Parasitic capacitances are treated as open circuit in low-frequency analysis.



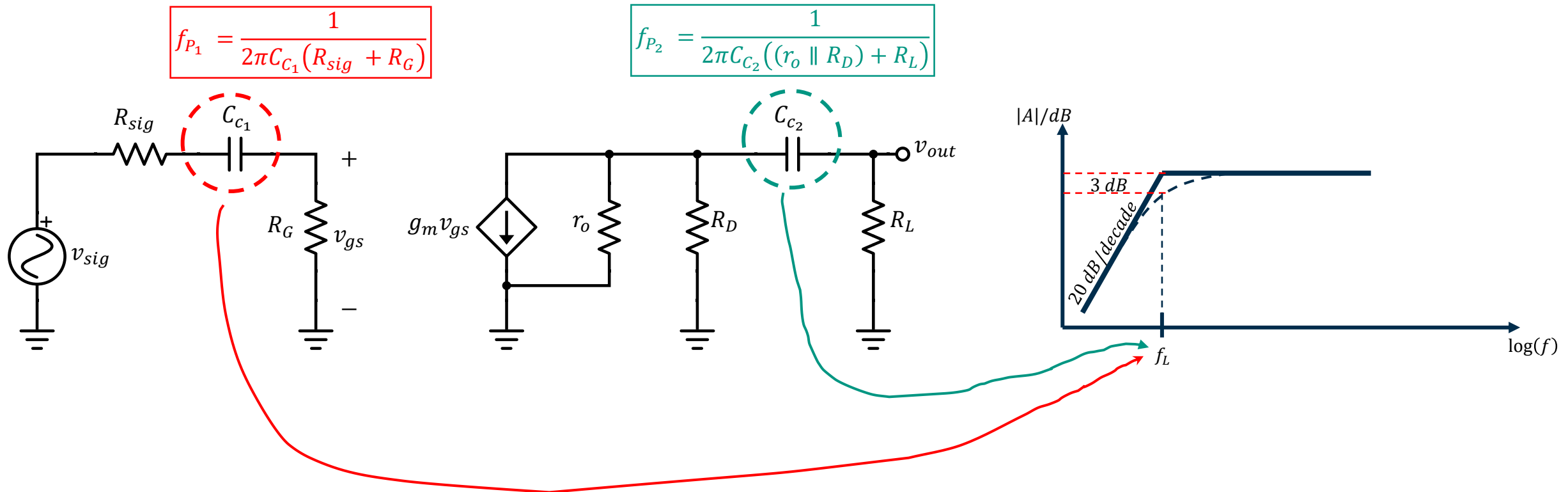
# Common-Source Amplifier Low-Frequency Response

- One of the coupling capacitors dominate and determine the low-frequency corner.





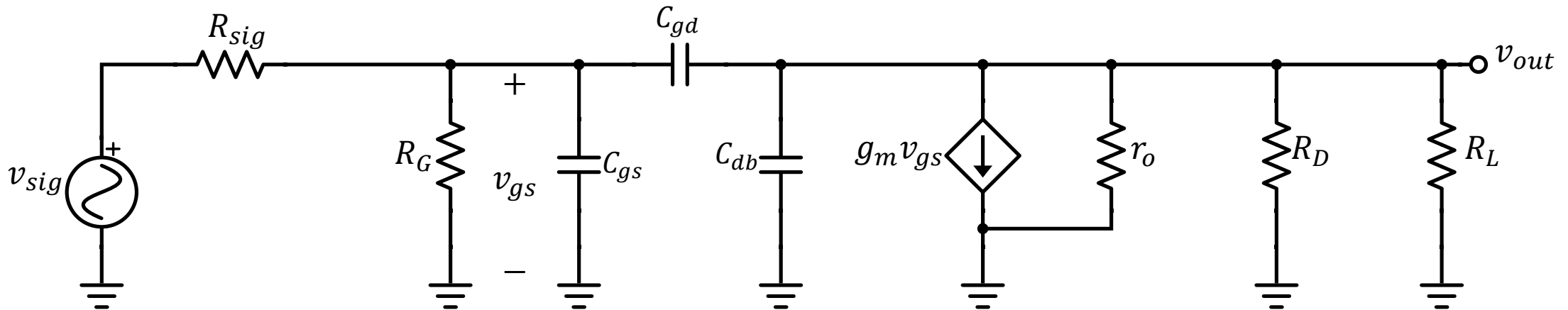
# Common-Source Amplifier High-Frequency Response


- $C_{coupling} \gg C_{parasitics} \rightarrow \frac{1}{j\omega C_{coupling}} \rightarrow 0$  at high  $\omega$ .
- Coupling capacitances are treated as short circuit in high-frequency analysis.



# Miller's Theorem

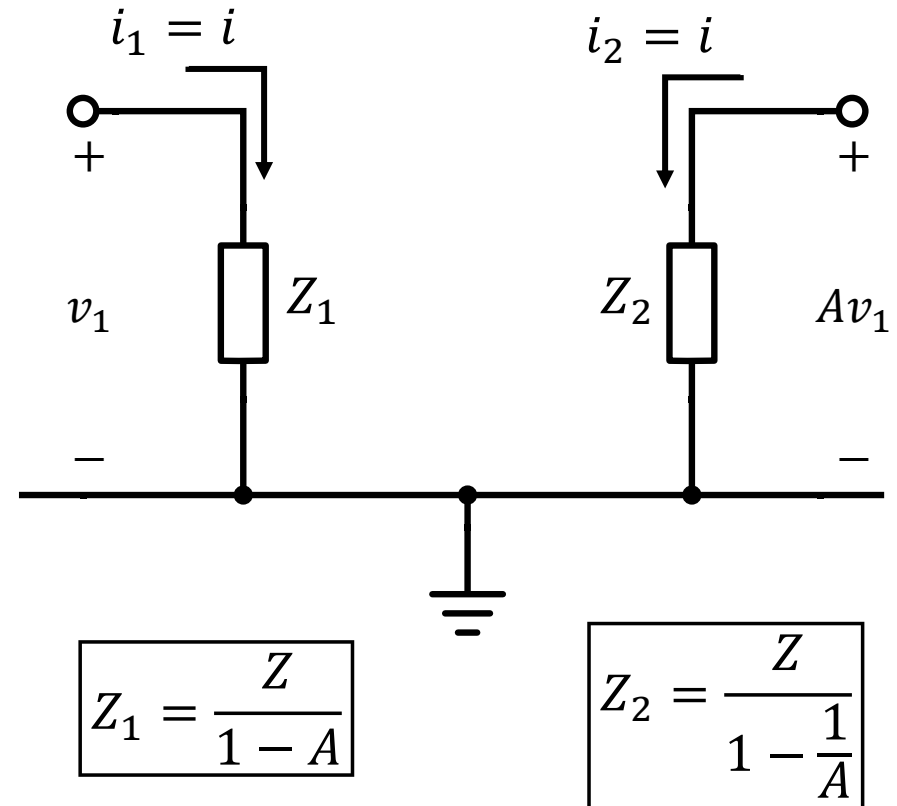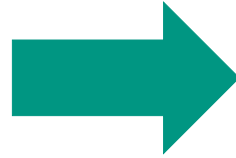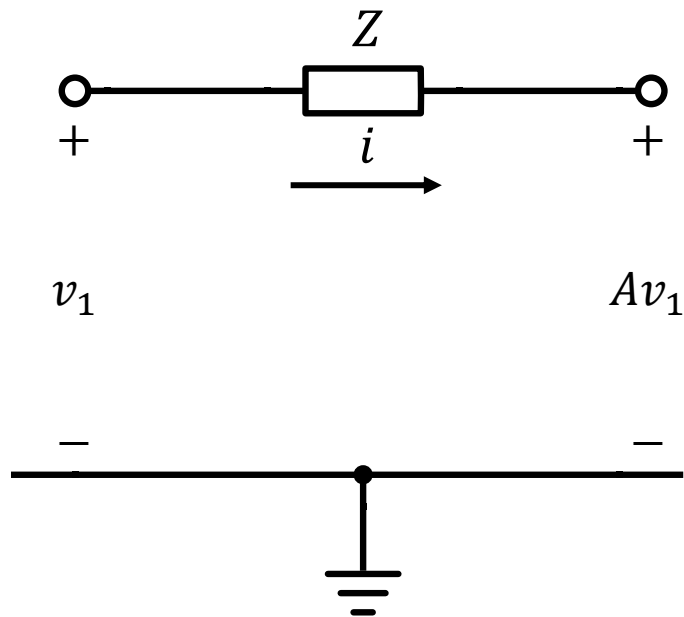

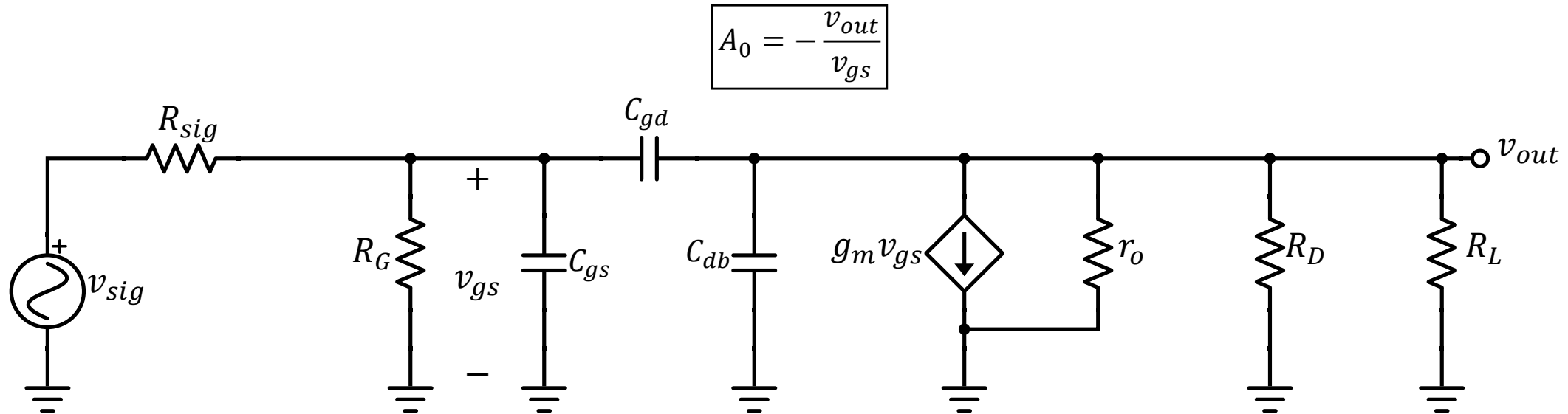
# Miller's Theorem Applied in CS Amplifier




# Miller's Theorem Applied in CS Amplifier

$$A_0 = -\frac{v_{out}}{v_{gs}}$$

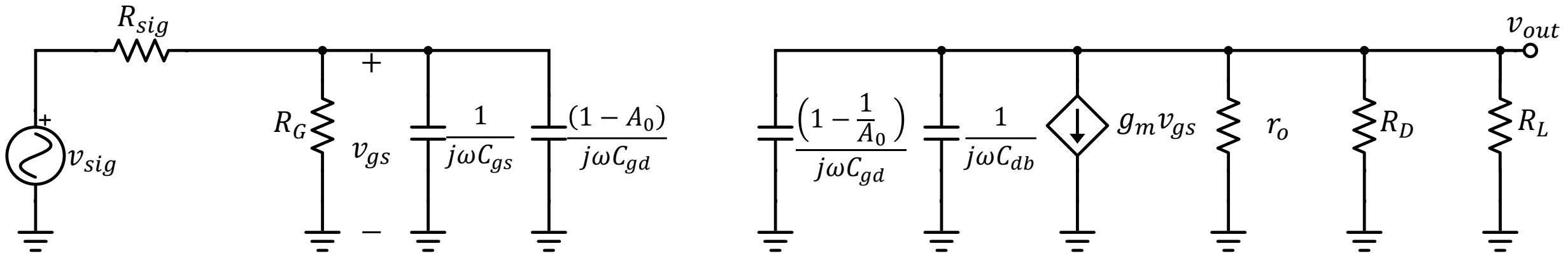



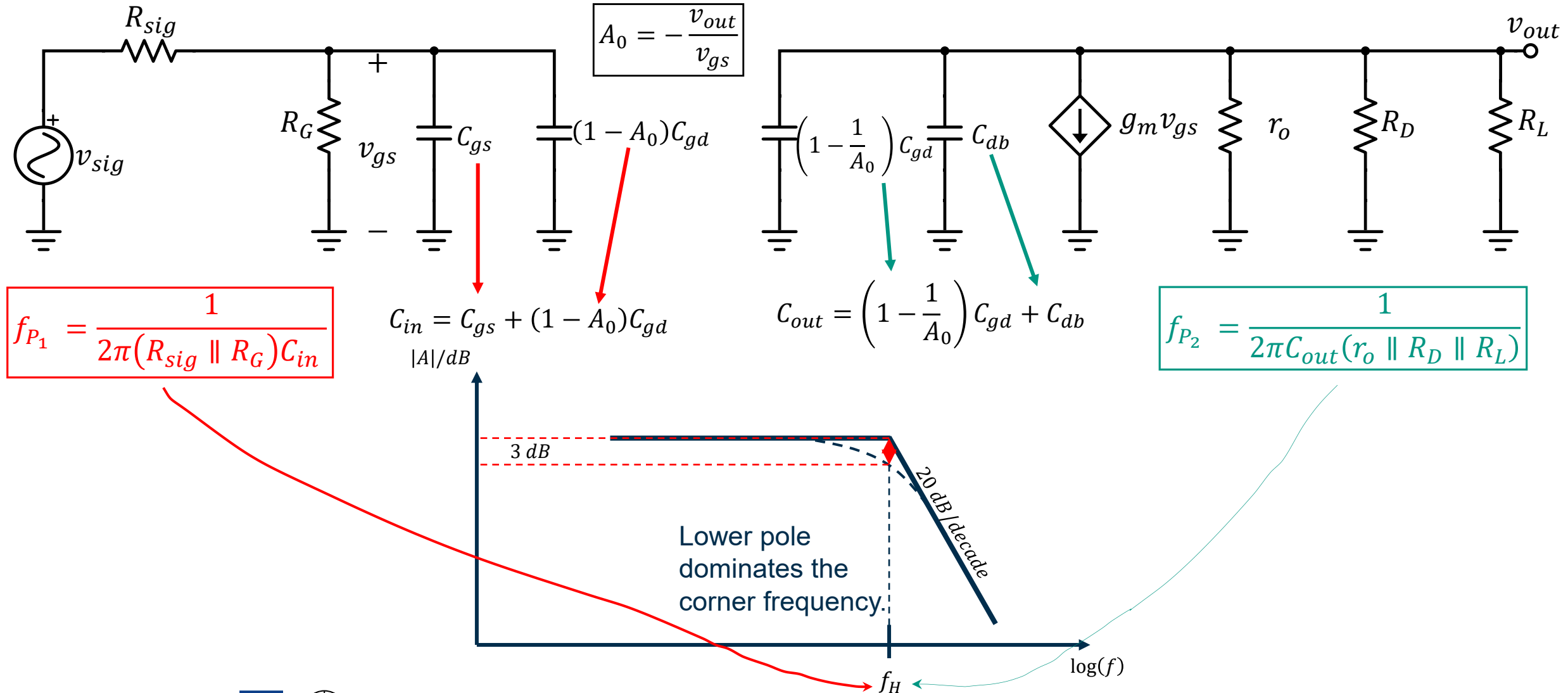
# Miller's Theorem Applied in CS Amplifier


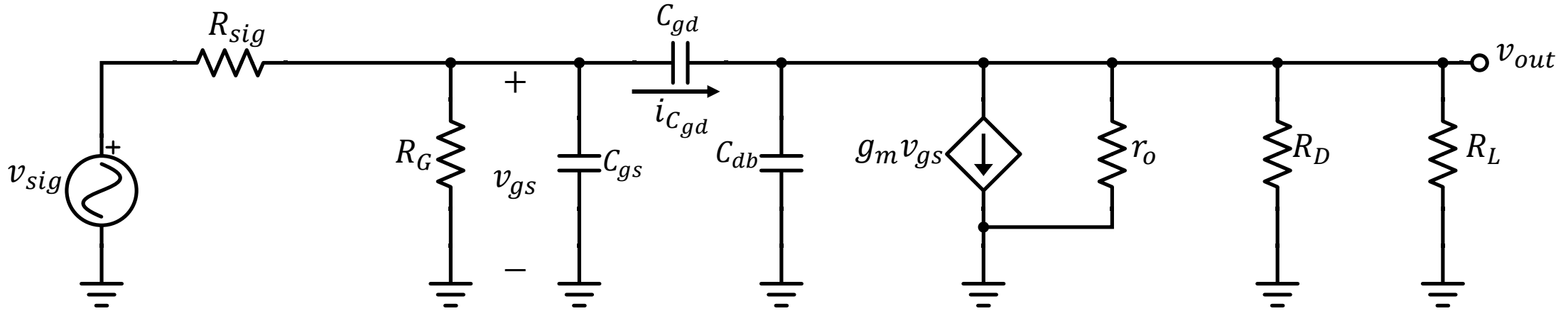
# Common-Source Amplifier Calculation of Zero





Consider  $R_{sig} = 0 \rightarrow v_{gs} = v_{sig}$

- $R_{out} = r_o \parallel R_D \parallel R_L$
- $i_{C_{gd}} = sC_{gd}(v_{sig} - v_{out}) = \frac{v_{out}}{R_{out}} + v_{out}(sC_{db}) + g_mv_{sig}$
- $v_{sig}(sC_{gd} - g_m) = v_{out}\left(\frac{1}{R_{out}} + s(C_{db} + C_{gd})\right)$
- $C_{out} = C_{db} + C_{gd}$
- $\frac{v_{out}}{v_{sig}} = \frac{(sC_{gd} - g_m)R_{out}}{1 + sR_{out}C_{out}}$

$$\frac{v_{out}}{v_{sig}} = - \frac{g_m R_{out} \left(1 - \frac{sC_{gd}}{g_m}\right)}{1 + sR_{out}C_{out}}$$


$$f_z = \frac{g_m}{2\pi C_{gd}}$$
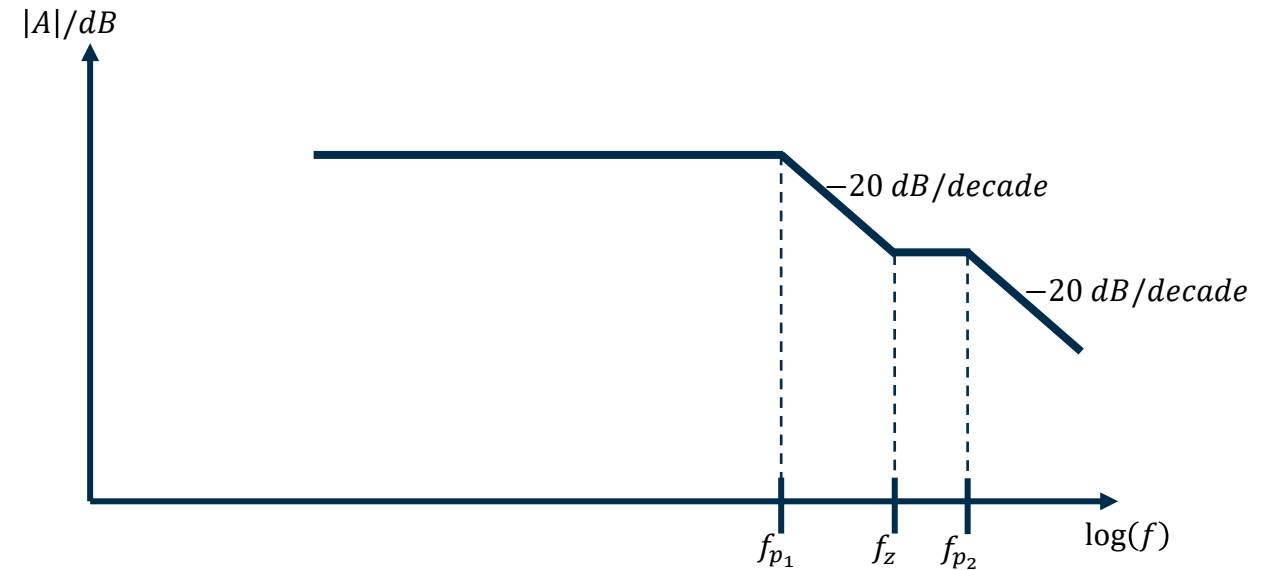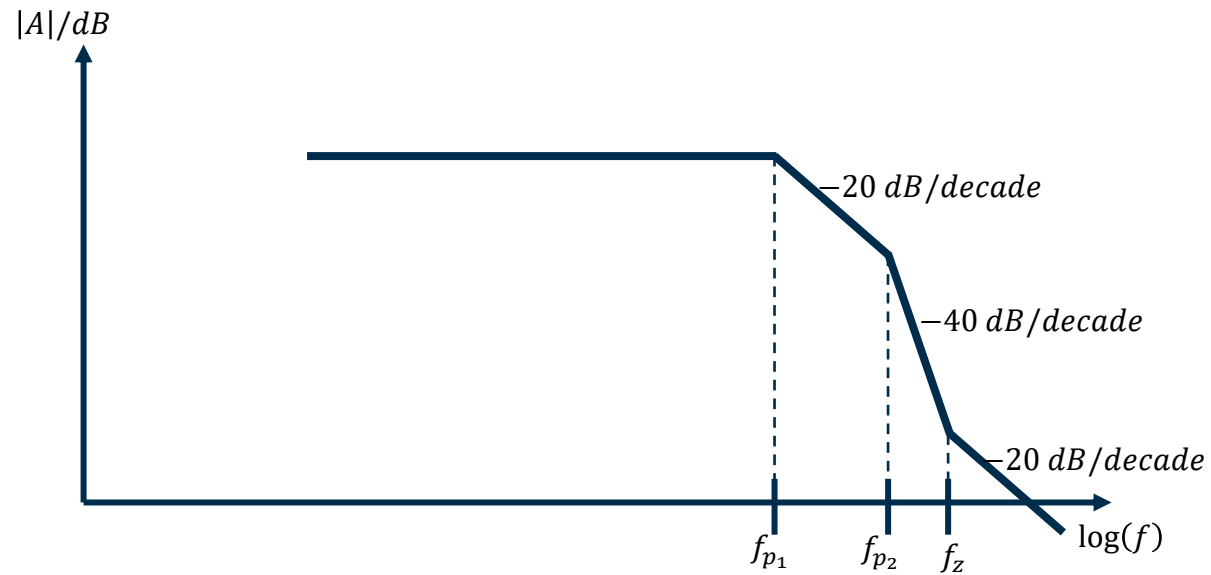
# Rough Drawing of Poles and Zero on Bode Plot


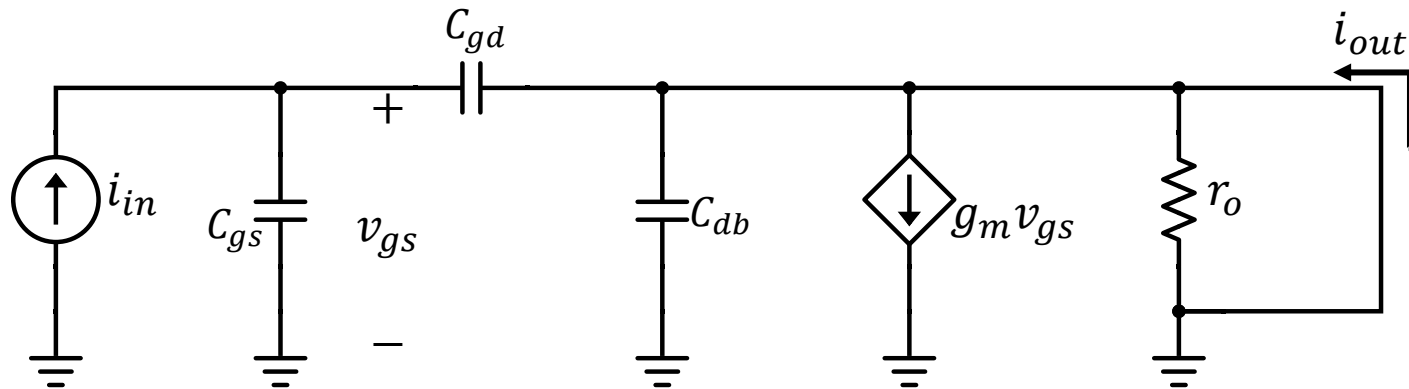
# Unity Gain (Transition) Frequency $f_T$

- The transition frequency is the frequency at which the short-circuit current gain of the common-source configuration becomes unity.
- This intrinsic device parameter is key to understanding the device's maximum speed capability and its fundamental high-frequency limitation.



$$\begin{aligned} i_{out} &\approx g_m v_{gs} \\ v_{gs} &= \frac{i_{in}}{j\omega(C_{gs} + C_{gd})} \\ \frac{i_{out}}{i_{in}} &= \frac{g_m}{j\omega(C_{gs} + C_{gd})} \\ \left| \frac{i_{out}}{i_{in}} \right| &= \frac{g_m}{\omega(C_{gs} + C_{gd})} = 1 \rightarrow \omega_T = 2\pi f_T = \frac{g_m}{C_{gs} + C_{gd}} \end{aligned}$$

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

# The Method of Open-Circuit Time Constants

- It is not always a simple matter to determine the poles and zeros by quick hand analysis. In such cases an approximate value for 3-dB frequency  $f_h$  can be obtained by using the method of open-circuit time constants. This method allows you to estimate the bandwidth by analyzing the interaction of each capacitor with the circuit resistance individually.

# The Method of Open-Circuit Time Constants

- Assume a system with two poles and two zeros

$$A(s) = \frac{\left(1 + \frac{s}{\omega_{z_1}}\right)\left(1 + \frac{s}{\omega_{z_2}}\right)}{\left(1 + \frac{s}{\omega_{p_1}}\right)\left(1 + \frac{s}{\omega_{p_2}}\right)} = \frac{\left(1 + s\left(\frac{1}{\omega_{z_1}} + \frac{1}{\omega_{z_2}}\right) + \frac{s^2}{\omega_{z_1}\omega_{z_2}}\right)}{\left(1 + s\left(\frac{1}{\omega_{p_1}} + \frac{1}{\omega_{p_2}}\right) + \frac{s^2}{\omega_{p_1}\omega_{p_2}}\right)} = \frac{(1 + a_1s + a_2s^2)}{1 + b_1s + b_2s^2}$$

- $b_1$  is the sum of the reciprocal of pole frequencies or the sum of time constants.

$$b_1 = \frac{1}{\omega_{p_1}} + \frac{1}{\omega_{p_2}} = \frac{1}{2\pi f_{p_1}} + \frac{1}{2\pi f_{p_2}} = \tau_{pole_1} + \tau_{pole_2} = \tau_{C_1} + \tau_{C_2}$$

$$\tau_{C_{1,2}} \neq \tau_{pole_{1,2}}$$

# The Method of Open-Circuit Time Constants

- Assume a system with two poles and two zeros

$$A(s) = \frac{\left(1 + \frac{s}{\omega_{z_1}}\right)\left(1 + \frac{s}{\omega_{z_2}}\right)}{\left(1 + \frac{s}{\omega_{p_1}}\right)\left(1 + \frac{s}{\omega_{p_2}}\right)} = \frac{\left(1 + s\left(\frac{1}{\omega_{z_1}} + \frac{1}{\omega_{z_2}}\right) + \frac{s^2}{\omega_{z_1}\omega_{z_2}}\right)}{\left(1 + s\left(\frac{1}{\omega_{p_1}} + \frac{1}{\omega_{p_2}}\right) + \frac{s^2}{\omega_{p_1}\omega_{p_2}}\right)} = \frac{(1 + a_1s + a_2s^2)}{1 + b_1s + b_2s^2}$$

- $b_1$  is the sum of the reciprocal of pole frequencies or the sum of time constants.

$$b_1 = \frac{1}{\omega_{p_1}} + \frac{1}{\omega_{p_2}} = \frac{1}{2\pi f_{p_1}} + \frac{1}{2\pi f_{p_2}} = \tau_{pole_1} + \tau_{pole_2} = \tau_{C_1} + \tau_{C_2} \approx \frac{1}{2\pi f_H}$$

- Dominant pole approximation

# The Method of Open-Circuit Time Constants

- The result can be expanded to multiple poles:

$$b_1 = \frac{1}{\omega_{p_1}} + \frac{1}{\omega_{p_2}} + \dots + \frac{1}{\omega_{p_m}} = \sum_{k=1}^m \tau_{C_k} \approx \frac{1}{2\pi f_H}$$


- The lowest-frequency pole normally dominates the result; however, even when the poles are close to each other, the OCTC method still provides a good approximation of the 3-dB corner frequency.

$$f_H = \left( \frac{1}{f_{p_1}} + \frac{1}{f_{p_2}} + \dots + \frac{1}{f_{p_m}} \right)^{-1}$$



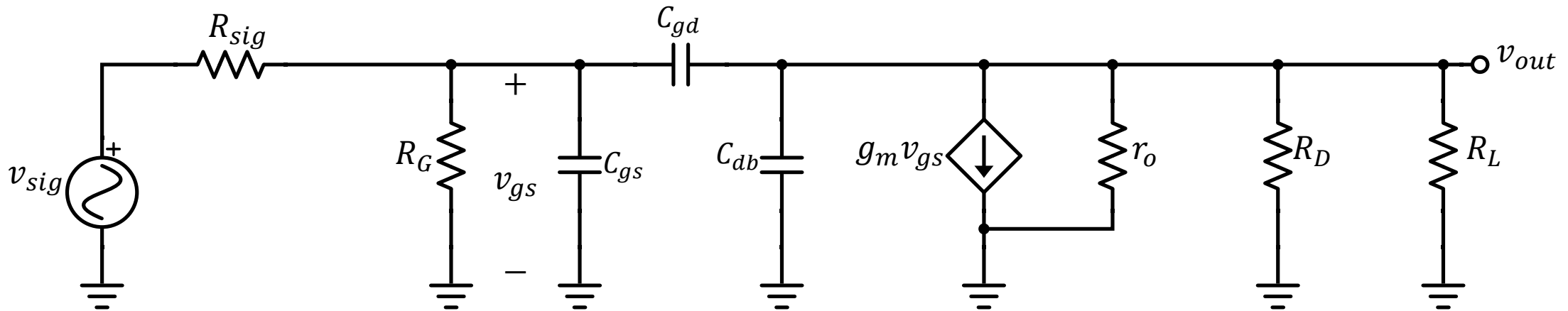
# Application of the OCTC to the CS Amplifier

- We set  $v_{sig} = 0$  and consider each of the three capacitances at a time, setting the other two open-circuit.



# Application of the OCTC to the CS Amplifier

CGS:

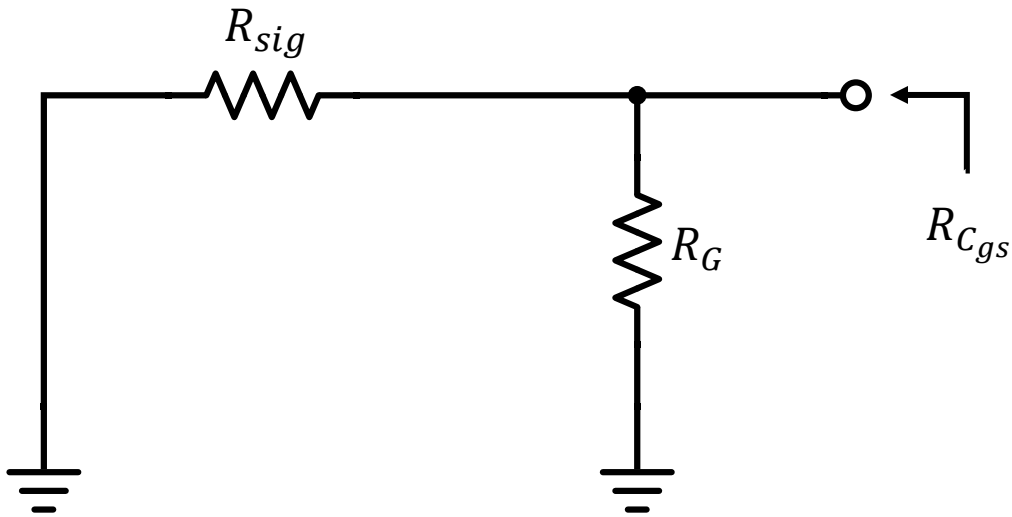

$$R_{Cgs} = R_{sig} \parallel R_G$$

$\frac{1}{\tau_1} = \frac{1}{R_{Cgs} C_{gs}} = \frac{1}{(R_{sig} \parallel R_G) C_{gs}}$
------------------------------------------------------------------------------------------

# Application of the OCTC to the CS Amplifier

**Example:**  $C_{GS} = 100 \text{ fF}$ ,  $C_{GD} = 10 \text{ fF}$ ,  $g_m = 100 \text{ mS}$ ,  $R_{sig} = 75 \text{ } \Omega$ ,  $r_o = 10 \text{ k}\Omega$ ,  $R_G = 1 \text{ M}\Omega$ ,  $R_D = 500 \text{ } \Omega$ ,  $R_L = 250 \text{ } \Omega$


$$R_{C_{gs}} = R_{sig} \parallel R_G$$

$\frac{1}{\tau_1} = \frac{1}{R_{C_{gs}} C_{gs}} = \frac{1}{(R_{sig} \parallel R_G) C_{gs}}$
---------------------------------------------------------------------------------------------

$$\tau_1 = 7.5 \text{ psec}$$

# Application of the OCTC to the CS Amplifier

## CGD

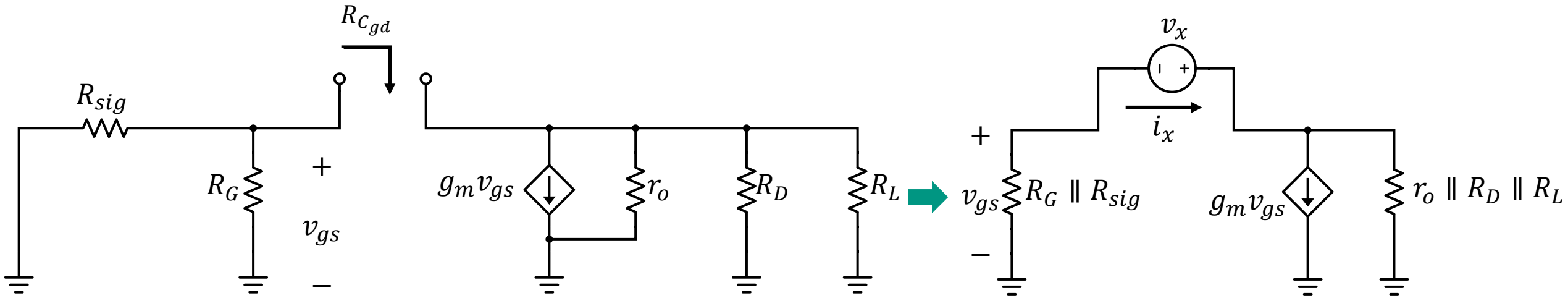

$$R'_{sig} = R_G \parallel R_{sig}$$

$$R'_L = r_o \parallel R_D \parallel R_L$$

$$R_{C_{gd}} = \frac{v_x}{i_x} = R'_{sig}(1 + g_m R'_L) + R'_L$$

$$\frac{1}{\tau_2} = \frac{1}{R_{C_{gd}} C_{gd}} = \frac{1}{(R'_{sig}(1 + g_m R'_L) + R'_L) C_{gd}}$$

# Application of the OCTC to the CS Amplifier

**Example:**  $C_{GS} = 100 \text{ fF}$ ,  $C_{GD} = 10 \text{ fF}$ ,  $g_m = 100 \text{ mS}$ ,  $R_{sig} = 75 \text{ } \Omega$ ,  $r_o = 10 \text{ k}\Omega$ ,  $R_G = 1 \text{ M}\Omega$ ,  $R_D = 500 \text{ } \Omega$ ,  $R_L = 250 \text{ } \Omega$

$$R'_{sig} = R_G \parallel R_{sig} = 75 \text{ } \Omega$$

$$R'_L = r_o \parallel R_D \parallel R_L = 163 \text{ } \Omega$$

$$R_{C_{gd}} = \frac{v_x}{i_x} = R'_{sig}(1 + g_m R'_L) + R'_L = 1460 \text{ } \Omega$$


$$\boxed{\frac{1}{\tau_2} = \frac{1}{R_{C_{gd}} C_{gd}} = \frac{1}{(R'_{sig}(1 + g_m R'_L) + R'_L) C_{gd}}}$$

$$\tau_2 = 14.6 \text{ psec}$$

# Application of the OCTC to the CS Amplifier

## CDB

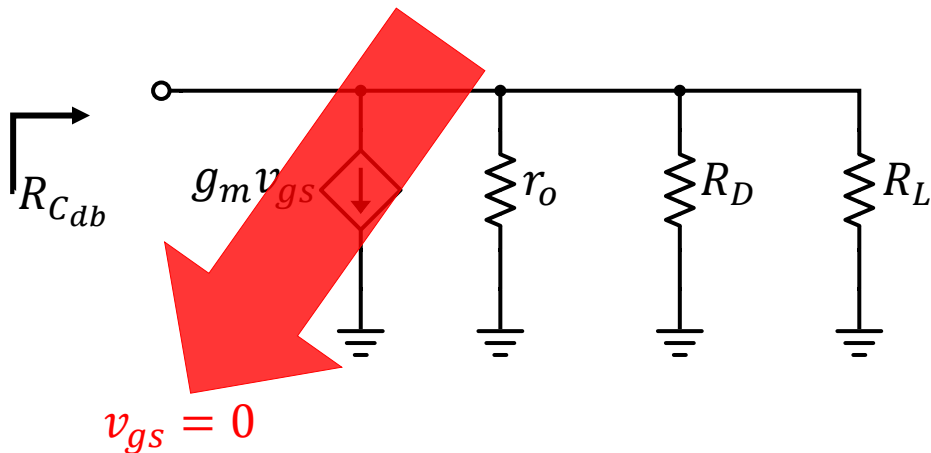**Example:**  $C_{GS} = 100 \text{ fF}$ ,  $C_{GD} = 10 \text{ fF}$ ,  $C_{DB} = 10 \text{ fF}$ ,  $g_m = 100 \text{ mS}$ ,  $R_{sig} = 75 \text{ } \Omega$ ,  $r_o = 10 \text{ k}\Omega$ ,  $R_G = 1 \text{ M}\Omega$ ,  $R_D = 500 \text{ } \Omega$ ,  $R_L = 250 \text{ } \Omega$




$$R_{Cdb} = r_o \parallel R_D \parallel R_L = \mathbf{163 \text{ } \Omega}$$

$\frac{1}{\tau_3} = \frac{1}{R_{Cdb} C_{db}} = \frac{1}{(r_o \parallel R_D \parallel R_L) C_{db}}$
----------------------------------------------------------------------------------------------------

$$\tau_3 = 1.63 \text{ psec}$$
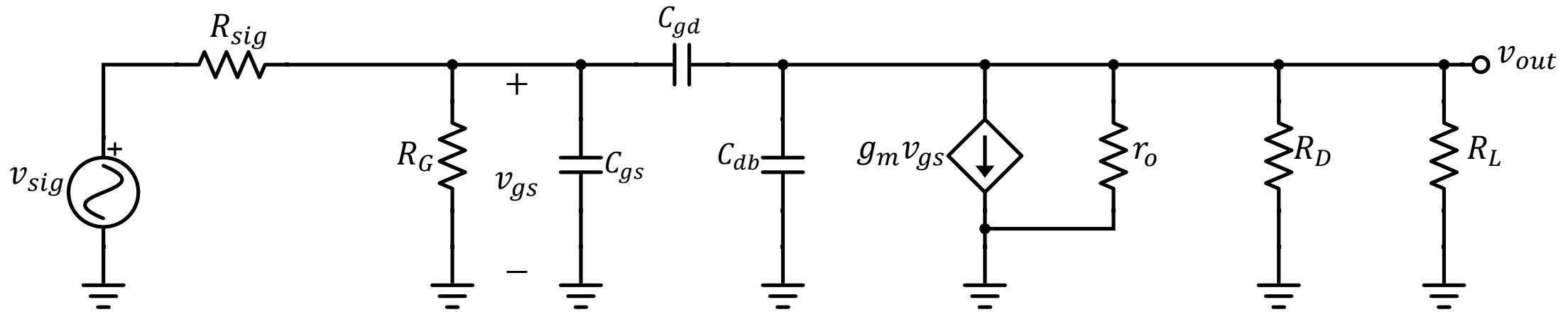
# Application of the OCTC to the CS Amplifier




$$f_H = \frac{1}{2\pi(\tau_1 + \tau_2 + \tau_3)}$$

$$f_H = \frac{1}{2\pi \left[ (R_{sig} \parallel R_G) C_{gs} + R_{C_{gd}} C_{gd} + (r_o \parallel R_D \parallel R_L) C_{db} \right]}$$

$$R_{C_{gd}} = R'_{sig}(1 + g_m R'_L) + R'_L$$
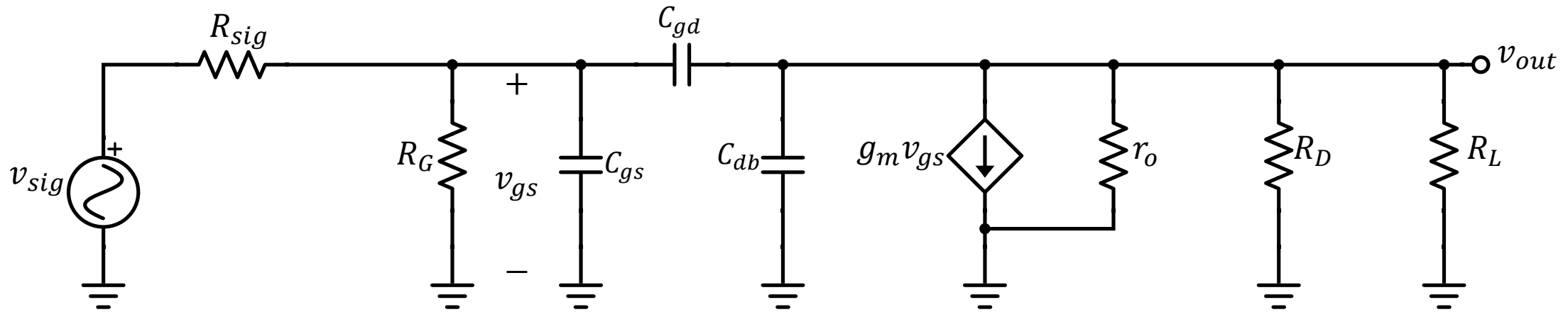
# Application of the OCTC to the CS Amplifier




$$f_H = \frac{1}{2\pi(\tau_1 + \tau_2 + \tau_3)} = \frac{1}{2\pi(23.73 \text{ psec})} = 6.7 \text{ GHz}$$

$$f_H = \frac{1}{2\pi \left[ (R_{sig} \parallel R_G) C_{gs} + R_{C_{gd}} C_{gd} + (r_o \parallel R_D \parallel R_L) C_{db} \right]}$$

$$R_{C_{gd}} = R'_{sig}(1 + g_m R'_L) + R'_L$$



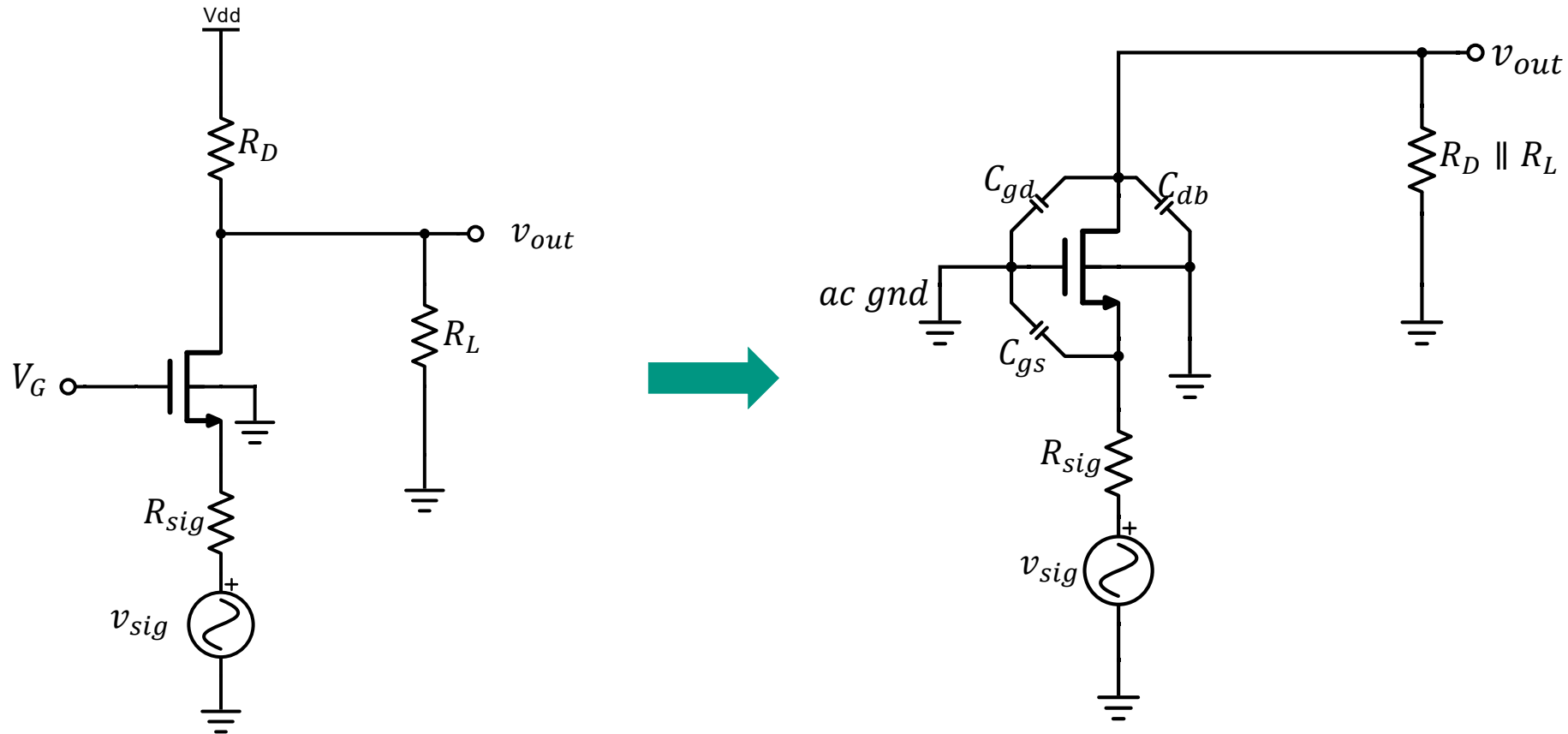
# Common-Gate Amplifier High-Frequency Response




# Common-Gate Amplifier High-Frequency Response

## Small-Signal Equivalent

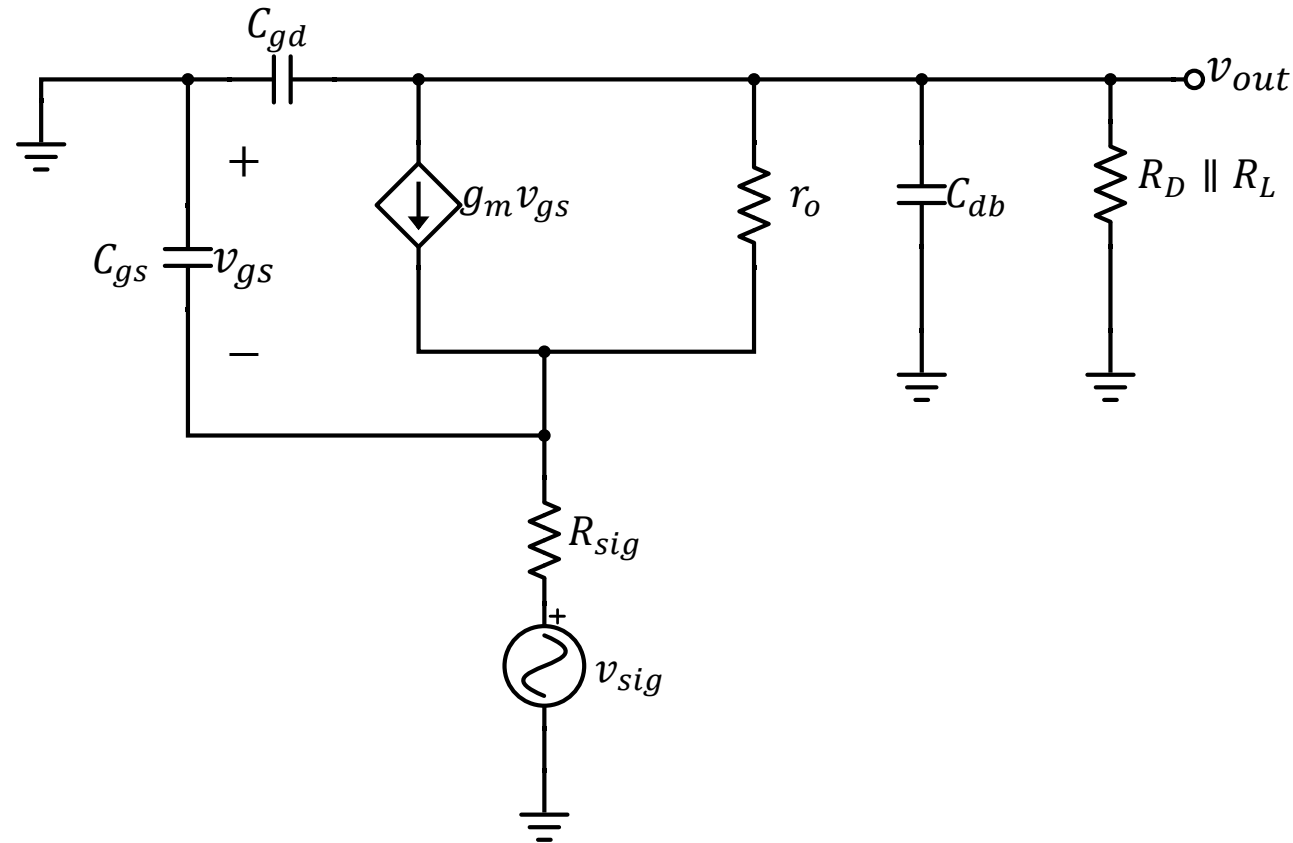

# Common-Gate Amplifier High-Frequency Response


## Small-Signal Equivalent Simplified

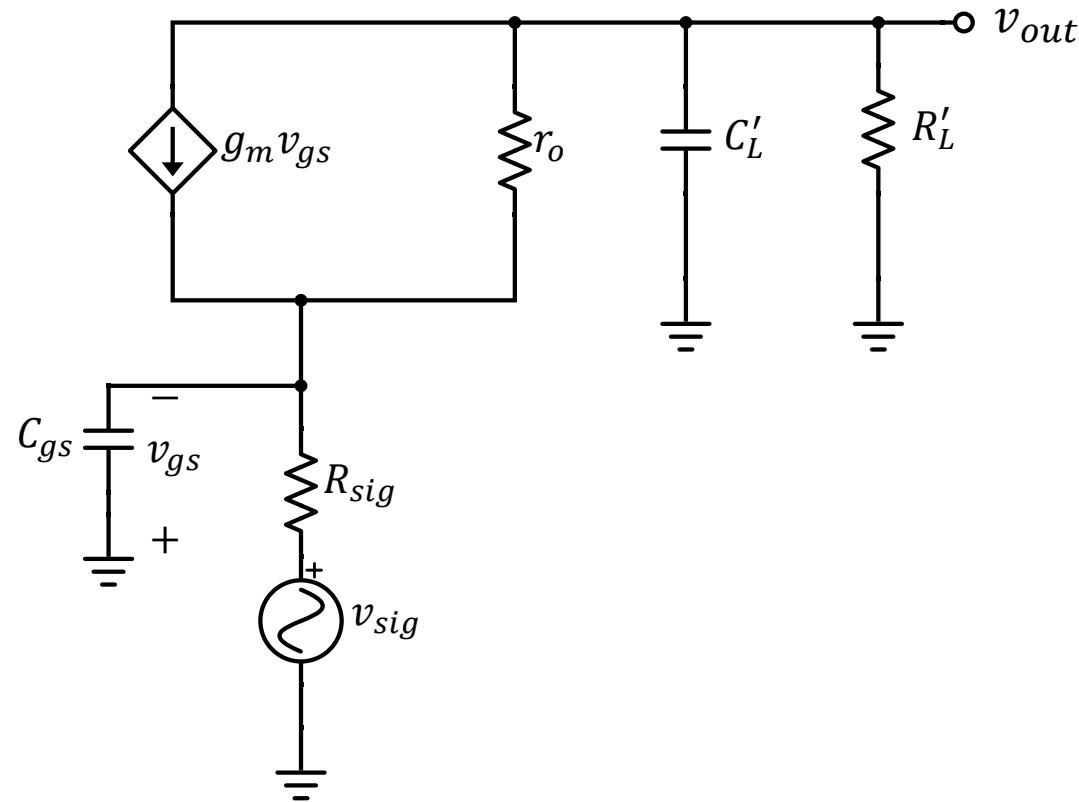

$$C'_L = C_{gd} + C_{db}$$
$$R'_L = R_D \parallel R_L$$

# Common-Gate Amplifier High-Frequency Response


## Open-Circuit Time Constants

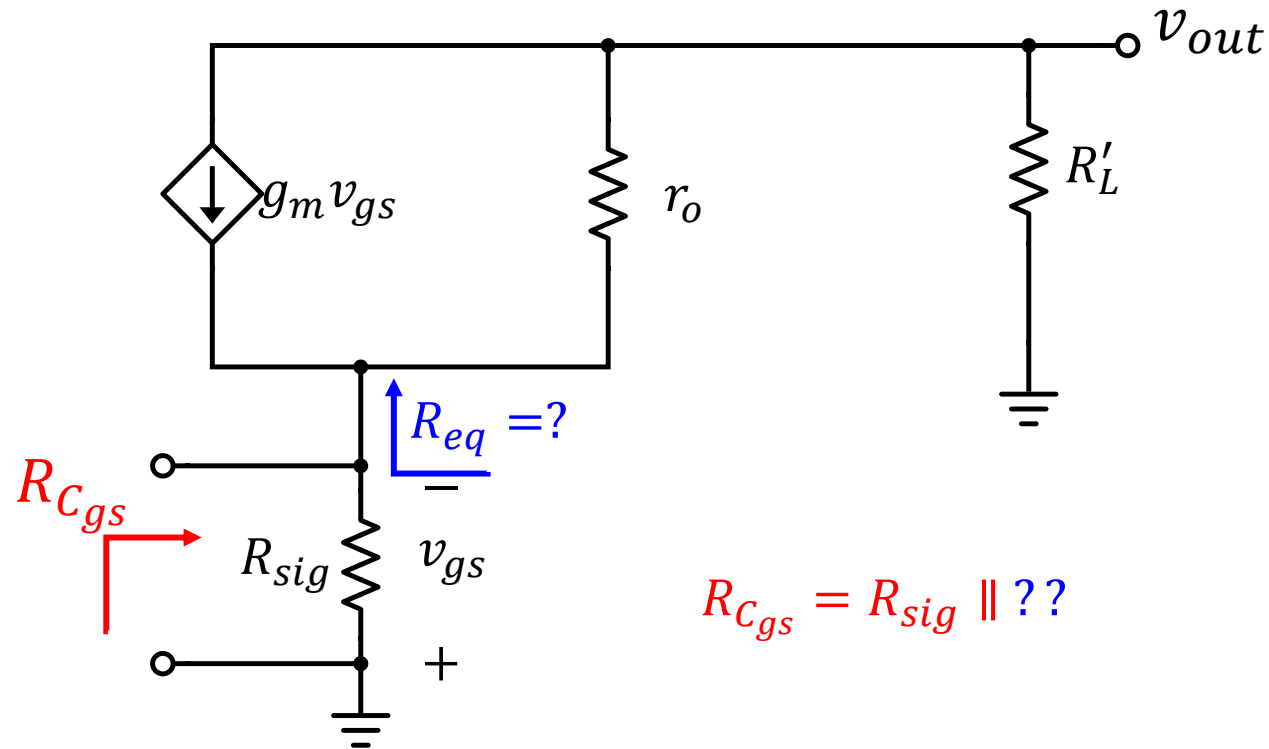

$$C'_L = C_{gd} + C_{db}$$
$$R'_L = R_D \parallel R_L$$

# Common-Gate Amplifier High-Frequency Response

## Open-Circuit Time Constants

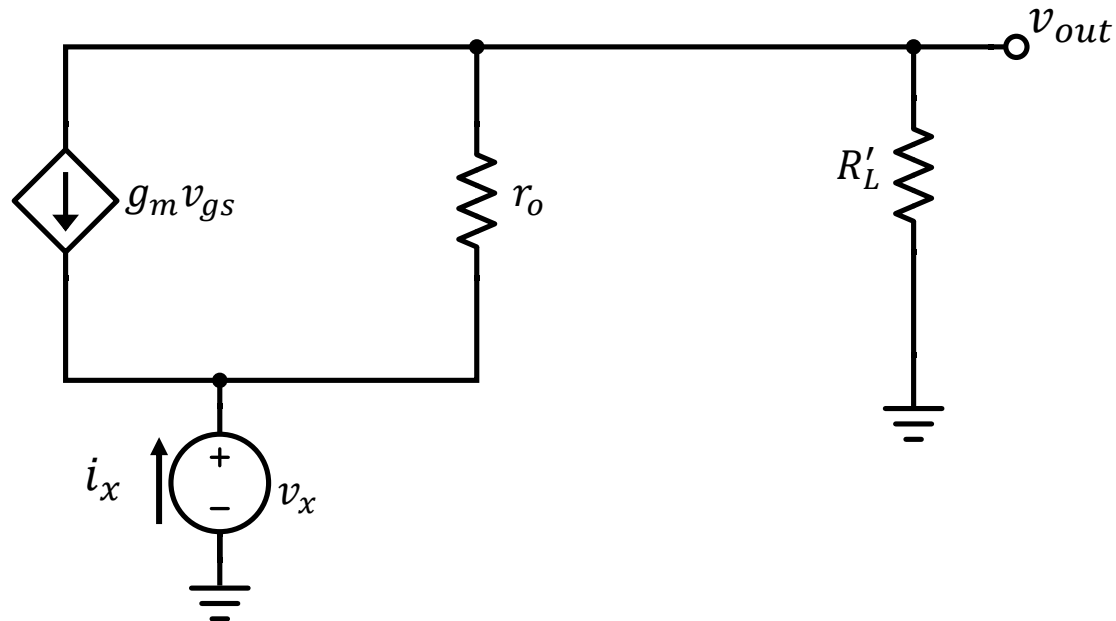

$$R_{eq} = \frac{v_x}{i_x} = \frac{R'_L \left( \frac{1}{g_m} \parallel r_o \right)}{R'_L \parallel r_o} = \frac{r_o + R'_L}{1 + g_m r_o}$$

$$C'_L = C_{gd} + C_{db}$$

$$R'_L = R_D \parallel R_L$$

$$R_{C_{gs}} = R_{sig} \parallel R_{eq}$$

$$\frac{1}{\tau_1} = \frac{1}{2\pi \left[ R_{sig} \parallel \left( \frac{r_o + R'_L}{1 + g_m r_o} \right) \right] C_{gs}}$$

$$\text{For } R'_L \ll r_o, \frac{1}{g_m} \ll r_o:$$

$$\frac{1}{\tau_1} = \frac{1}{(R_{sig} \parallel 1/g_m) C_{gs}}$$

# Common-Gate Amplifier High-Frequency Response

## Open-Circuit Time Constants

**Example:**  $C_{GS} = 100 \text{ fF}$ ,  $C_{GD} = 10 \text{ fF}$ ,  $C_{DB} = 10 \text{ fF}$ ,  $g_m = 100 \text{ mS}$ ,  $R_{sig} = 75 \text{ } \Omega$ ,  $r_o = 10 \text{ k}\Omega$ ,  $R_G = 1 \text{ M}\Omega$ ,  $R_D = 500 \text{ } \Omega$ ,  $R_L = 250 \text{ } \Omega$

$$R_{sig} \parallel \frac{1}{g_m} = 8.8 \text{ } \Omega$$

$$R_{sig} \parallel \left( \frac{r_o + R'_L}{1 + g_m r_o} \right) = 8.945 \text{ } \Omega$$

$$\tau_1 = 0.88 \text{ psec}$$

$$R_{eq} = \frac{v_x}{i_x} = \frac{R'_L \left( \frac{1}{g_m} \parallel r_o \right)}{R'_L \parallel r_o} = \frac{r_o + R'_L}{1 + g_m r_o}$$

$C'_L = C_{gd} + C_{db}$   
 $R'_L = R_D \parallel R_L$


$$R_{C_{gs}} = R_{sig} \parallel R_{eq}$$

$$\frac{1}{\tau_1} = \frac{1}{2\pi \left[ R_{sig} \parallel \left( \frac{r_o + R'_L}{1 + g_m r_o} \right) \right] C_{gs}}$$

For  $R'_L \ll r_o$ ,  $\frac{1}{g_m} \ll r_o$ :

$$\frac{1}{\tau_1} = \frac{1}{(R_{sig} \parallel 1/g_m) C_{gs}}$$
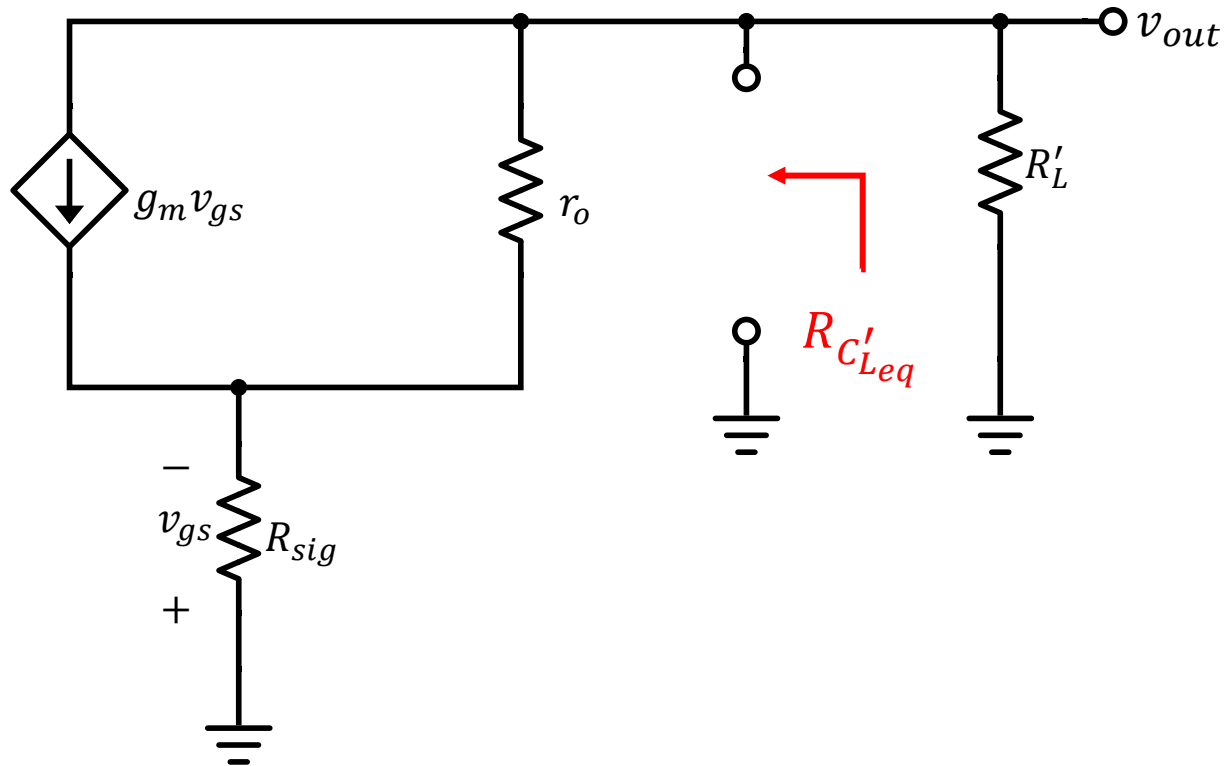
# Common-Gate Amplifier High-Frequency Response



$$R'_{CLeq} = g_m R_{sig} r_o + R_{sig} + r_o \approx g_m R_{sig} r_o \quad C'_L = C_{gd} + C_{db}$$


$$R'_L = R_D \parallel R_L$$

(Recall Cascode analysis)

$$\frac{1}{\tau_2} = \frac{1}{(R'_L \parallel g_m R_{sig} r_o) C'_L}$$

# Common-Gate Amplifier High-Frequency Response

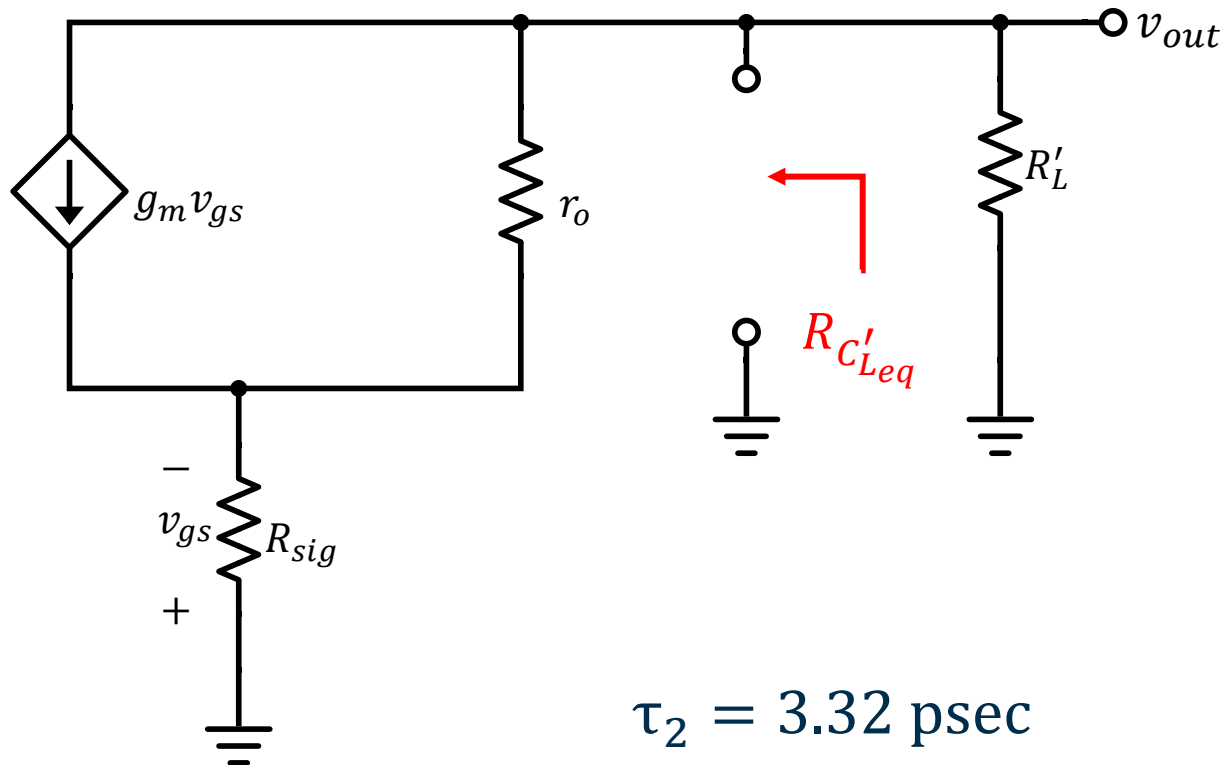**Example:**  $C_{GS} = 100 \text{ fF}$ ,  $C_{GD} = 10 \text{ fF}$ ,  $C_{DB} = 10 \text{ fF}$ ,  $g_m = 100 \text{ mS}$ ,  $R_{sig} = 75 \text{ } \Omega$ ,  $r_o = 10 \text{ k}\Omega$ ,  $R_G = 1 \text{ M}\Omega$ ,  $R_D = 500 \text{ } \Omega$ ,  $R_L = 250 \text{ } \Omega$



$$R'_{CLeq} = g_m R_{sig} r_o + R_{sig} + r_o \approx g_m R_{sig} r_o$$

(Recall Cascode analysis)

$$C'_L = C_{gd} + C_{db}$$

$$R'_L = R_D \parallel R_L$$


$$\frac{1}{\tau_2} = \frac{1}{(R'_L \parallel g_m R_{sig} r_o) C'_L}$$

166  $\Omega$       75 k $\Omega$

165.6  $\Omega$


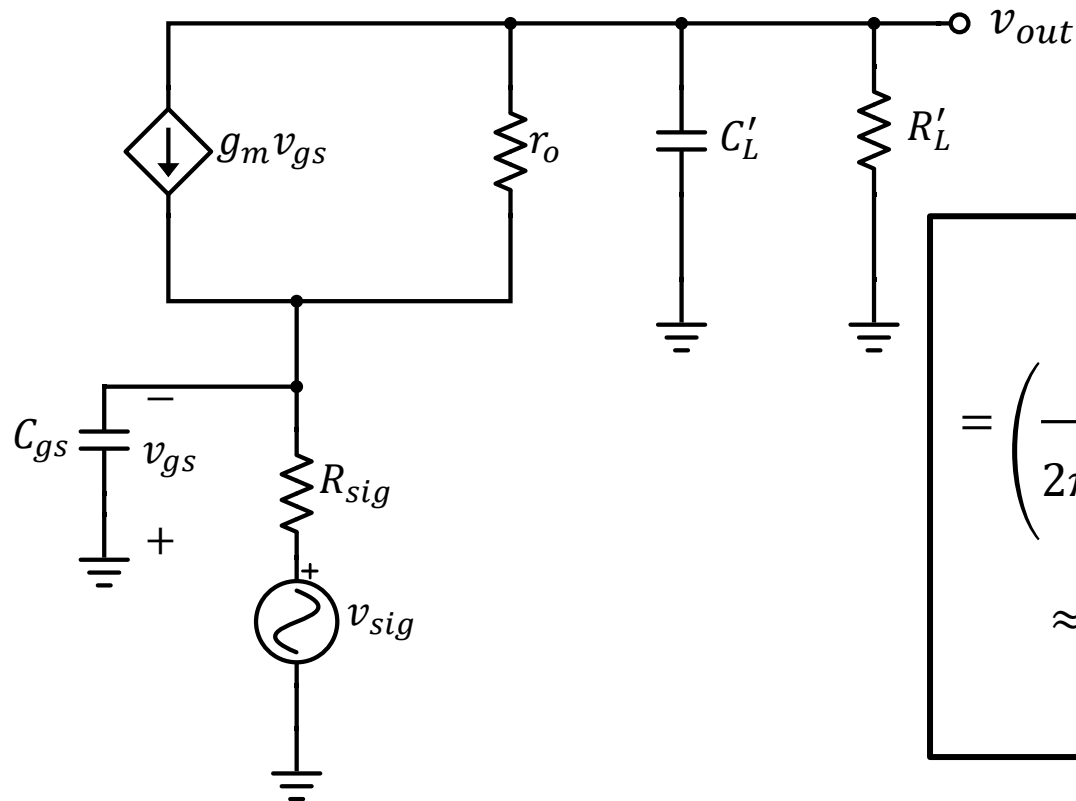
# Common-Gate Amplifier High-Frequency Response



$$C'_L = C_{gd} + C_{db}$$


$$R'_L = R_D \parallel R_L$$

$$f_H = \frac{1}{2\pi(\tau_1 + \tau_2)} = \mathbf{37.8 \text{ GHz}}$$

$$= \left( \frac{1}{2\pi \left[ R_{sig} \parallel \left( \frac{r_o + R'_L}{1 + g_m r_o} \right) \right] C_{gs}} + \frac{1}{2\pi (R'_L \parallel g_m R_{sig} r_o) C'_L} \right)^{-1}$$

$$\approx \left( \frac{1}{2\pi \left[ R_{sig} \parallel \frac{1}{g_m} \right] C_{gs}} + \frac{1}{2\pi (R'_L \parallel g_m R_{sig} r_o) C'_L} \right)^{-1}$$

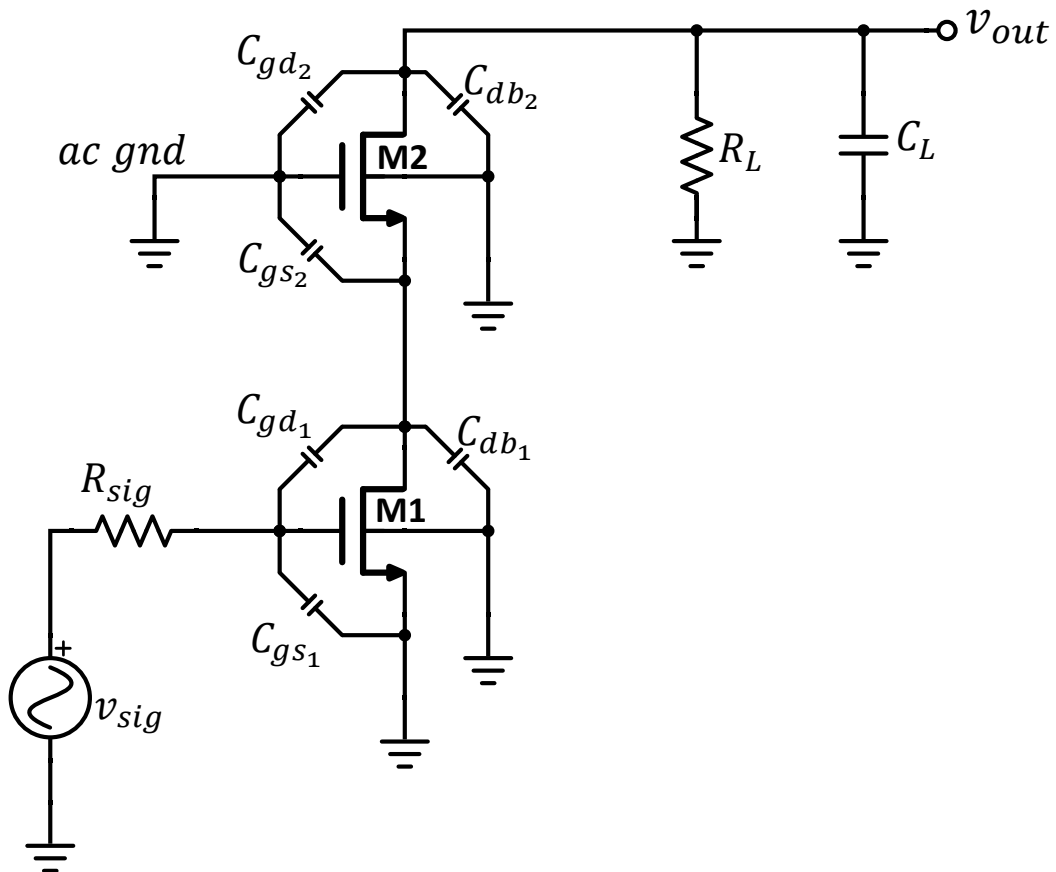
# Cascode Amplifier High-Frequency Response



# Cascode Amplifier High-Frequency Response

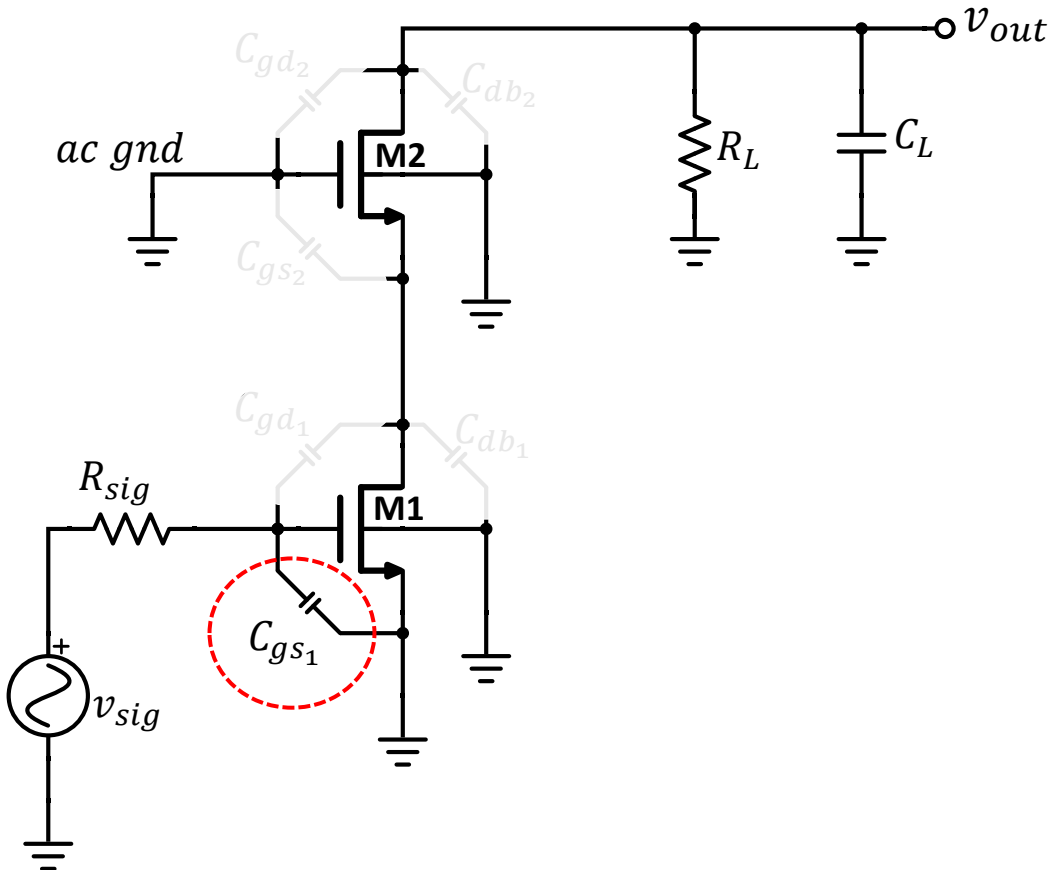**Example:**  $C_{GS} = 100 \text{ fF}$ ,  $C_{GD} = 10 \text{ fF}$ ,  $C_{DB} = 10 \text{ fF}$ ,  $g_m = 100 \text{ mS}$ ,  $R_{sig} = 75 \text{ } \Omega$ ,  $r_o = 10 \text{ k}\Omega$ ,  $R_G = 1 \text{ M}\Omega$ ,  $R_D = 500 \text{ } \Omega$ ,  $R_L = 250 \text{ } \Omega$


- $C_{gs_1}$  sees a resistance  $R_{sig}$ .



$$\frac{1}{\tau_1} = \frac{1}{R_{sig} C_{gs_1}}$$

$$\tau_1 = 7.5 \text{ psec}$$
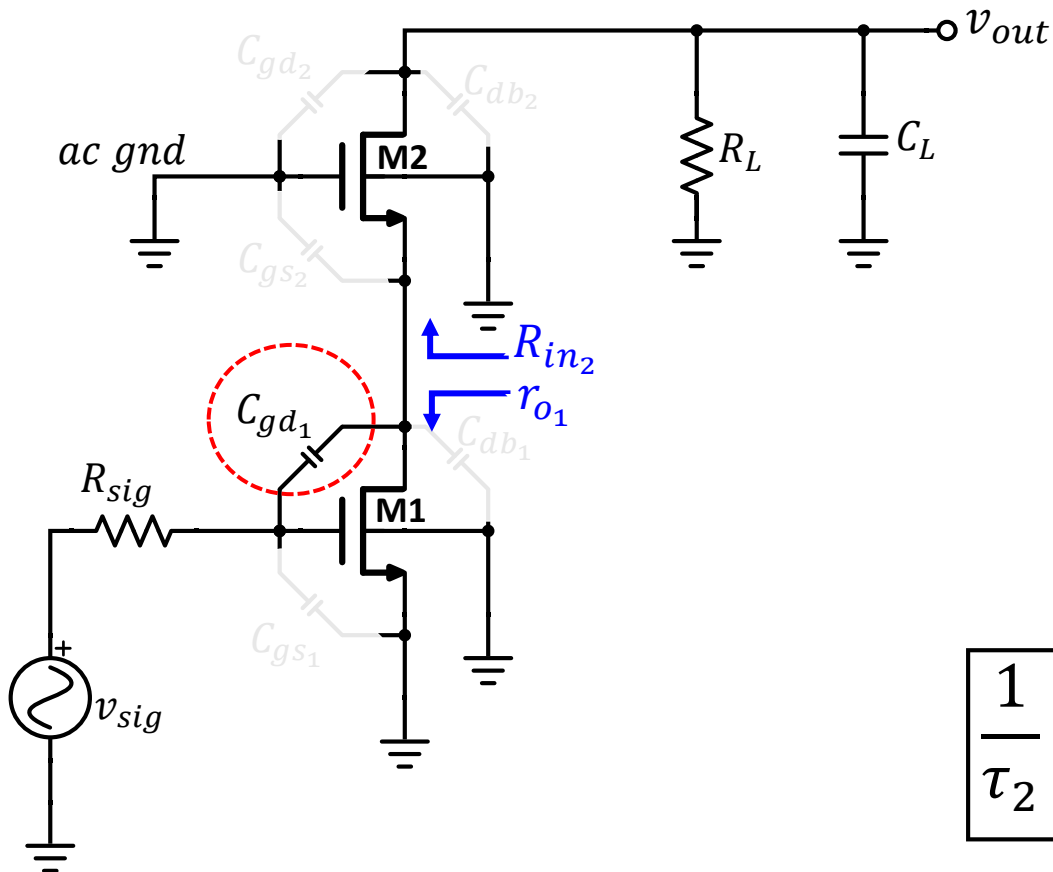
# Cascode Amplifier High-Frequency Response



- $C_{gd1}$  sees a resistance  $R_{gd1}$ , which can be obtained by adapting the formula derived in OCTC analysis of CS amplifier.

$$R_{gd1} = g_{m1} R_{d1} R_{sig} + R_{sig} + R_{d1}$$

$$R_{d1} = r_{o1} \parallel R_{in2}$$


- $R_{in2}$  was derived in CG amplifier analysis:

$$R_{in2} = \frac{r_{o2} + R_L}{1 + g_{m2} r_{o2}}$$

$$\frac{1}{\tau_2} = \frac{1}{R_{gd1} C_{gd1}} = \frac{1}{(g_{m1} R_{d1} R_{sig} + R_{sig} + R_{d1}) C_{gd1}}$$

# Cascode Amplifier High-Frequency Response

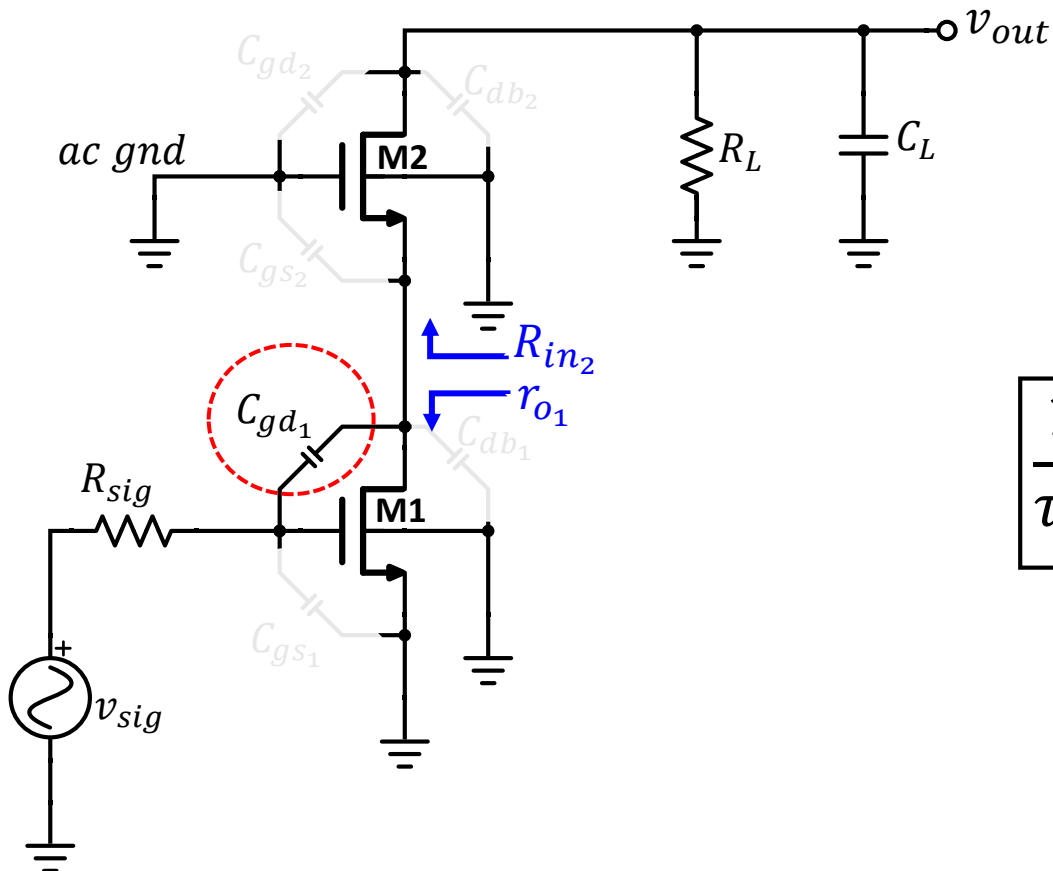**Example:**  $C_{GS} = 100 \text{ fF}$ ,  $C_{GD} = 10 \text{ fF}$ ,  $C_{DB} = 10 \text{ fF}$ ,  $g_m = 100 \text{ mS}$ ,  $R_{sig} = 75 \text{ } \Omega$ ,  $r_o = 10 \text{ k}\Omega$ ,  $R_G = 1 \text{ M}\Omega$ ,  $R_L = 166 \text{ } \Omega$



$$R_{gd1} = g_{m1} R_{d1} R_{sig} + R_{sig} + R_{d1}$$


$$R_{d1} = r_{o1} \parallel R_{in2} = 10.09 \text{ } \Omega$$

$$R_{in2} = \frac{r_{o2} + R_L}{1 + g_{m2} r_{o2}} = 10.1 \text{ } \Omega$$

$$\frac{1}{\tau_2} = \frac{1}{R_{gd1} C_{gd1}} = \frac{1}{(g_{m1} R_{d1} R_{sig} + R_{sig} + R_{d1}) C_{gd1}}$$

$$\tau_2 = 1.6 \text{ psec}$$
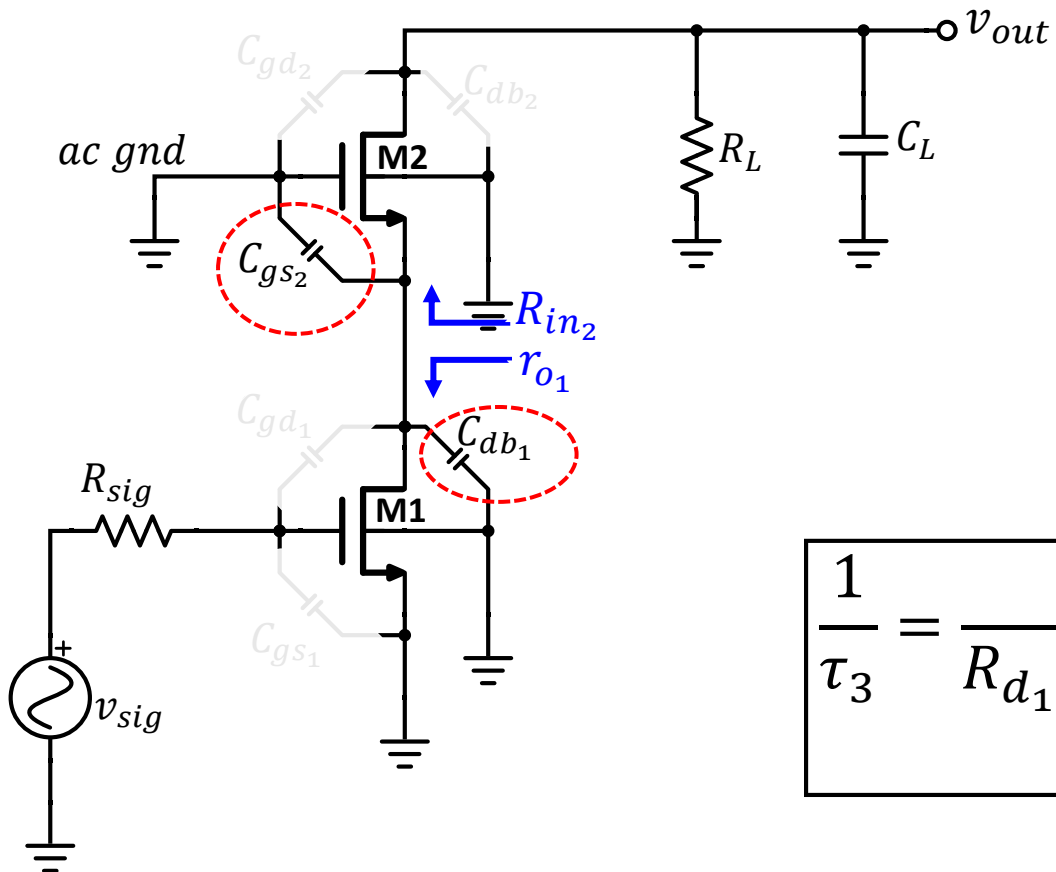
# Cascode Amplifier High-Frequency Response



- Capacitance  $(C_{db_1} + C_{gs_2})$  sees  $R_{d_1}$ .
- $R_{d_1}$  was determined in previous slide as given:


$$R_{d_1} = r_{o_1} \parallel R_{in_2} = r_{o_1} \parallel \frac{r_{o_2} + R_L}{1 + g_{m_2} r_{o_2}}$$

$$\tau_3 = 0.2 \text{ psec}$$

$$\frac{1}{\tau_3} = \frac{1}{R_{d_1} (C_{db_1} + C_{gs_2})} = \frac{1}{\left( r_{o_1} \parallel \frac{r_{o_2} + R_L}{1 + g_{m_2} r_{o_2}} \right) (C_{db_1} + C_{gs_2})}$$

# Cascode Amplifier High-Frequency Response

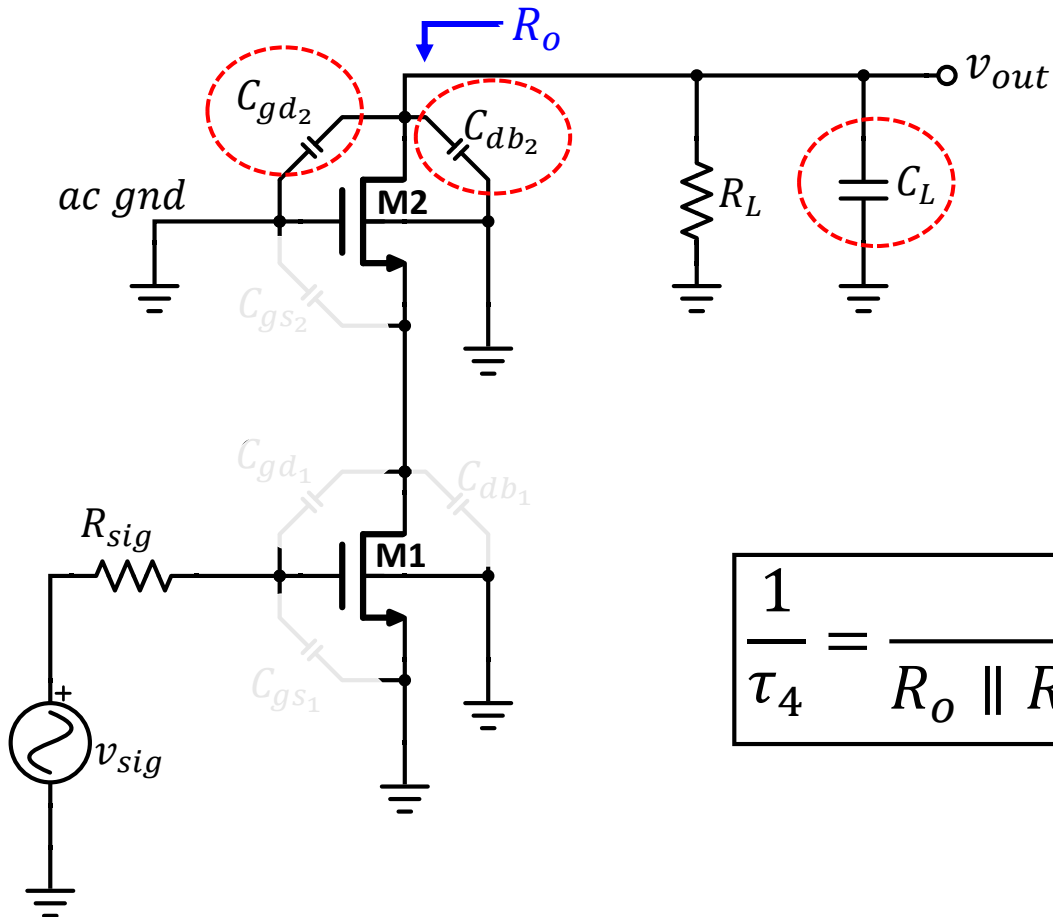**Example:**  $C_{GS} = 100 \text{ fF}$ ,  $C_{GD} = 10 \text{ fF}$ ,  $C_{DB} = 10 \text{ fF}$ ,  $g_m = 100 \text{ mS}$ ,  $R_{sig} = 75 \text{ } \Omega$ ,  $r_o = 10 \text{ k}\Omega$ ,  $R_G = 1 \text{ M}\Omega$ ,  $R_L = 166 \text{ } \Omega$ ,  $C_L = 0$




- Capacitance  $(C_L + C_{gd_2} + C_{db_2})$  see a resistance  $(R_L \parallel R_o)$ .
- $R_o$  is the output resistance of the cascode amplifier, given by:

$$R_o = g_{m_2} r_{o_2} r_{o_1} + r_{o_1} + r_{o_2} \approx g_{m_2} r_{o_2} r_{o_1}$$

$$\frac{1}{\tau_4} = \frac{1}{R_o \parallel R_L (C_L + C_{gd_2} + C_{db_2})} \approx \frac{1}{R_L (C_L + C_{gd_2} + C_{db_2})}$$

$$\tau_4 = 3.32 \text{ psec}$$
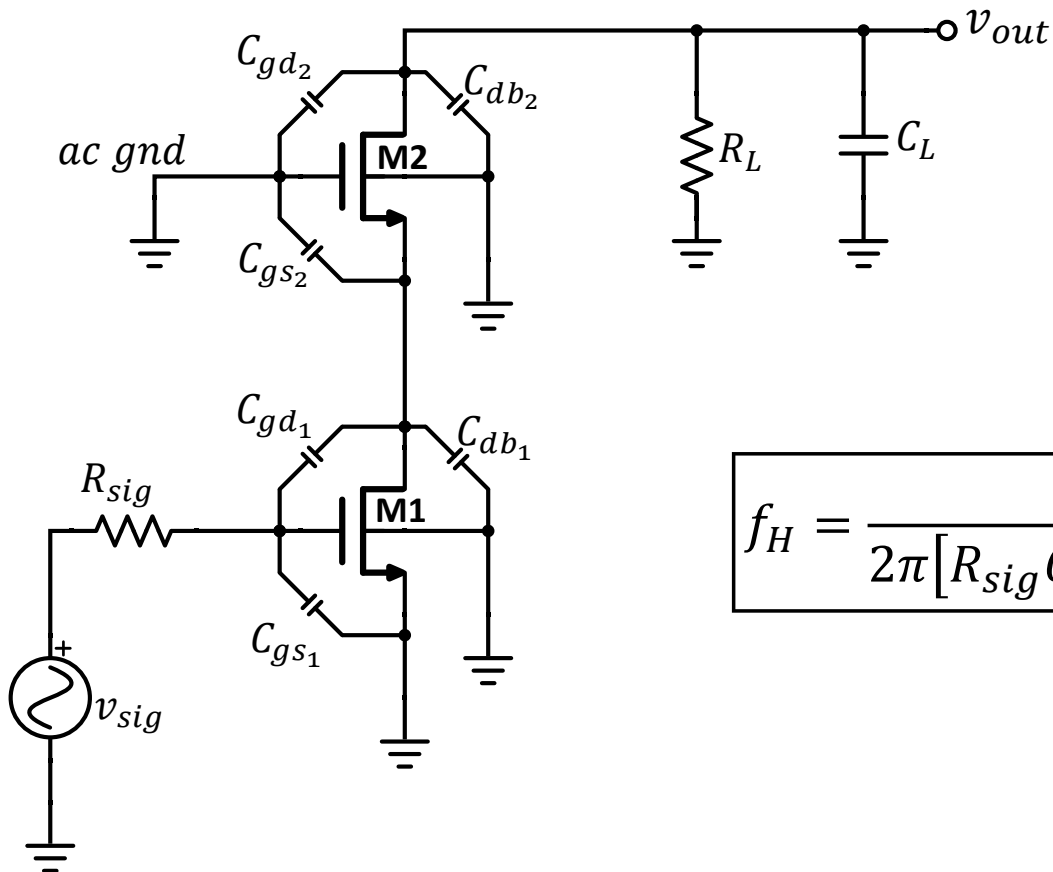
# Cascode Amplifier High-Frequency Response




$$f_H = \frac{1}{2\pi(\tau_1 + \tau_2 + \tau_3 + \tau_4)} = 12.6 \text{ GHz}$$

$$f_H = \frac{1}{2\pi[R_{sig}C_{gs1} + R_{gd1}C_{gd1} + R_{d1}(C_{db1} + C_{gs2}) + R_o(C_L + C_{gd2} + C_{db2})]}$$


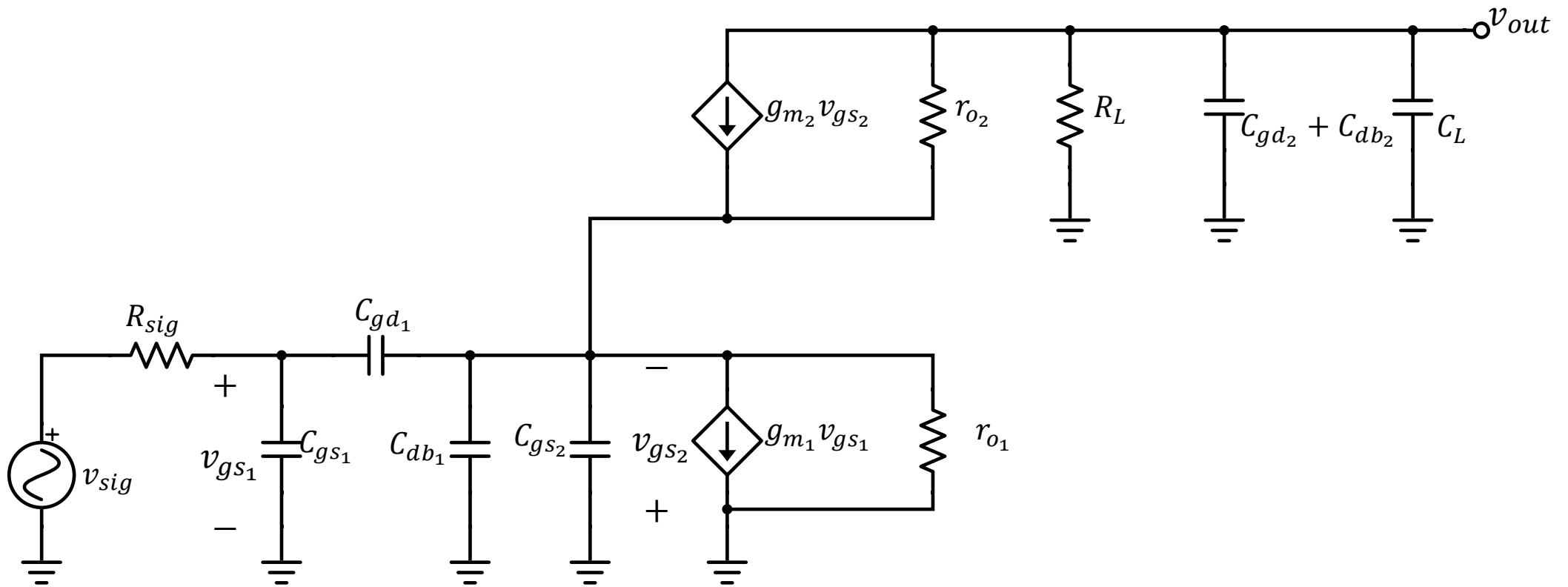
# Cascode Amplifier High-Frequency Response Small-Signal Model



# 2<sup>nd</sup> Order Amplifiers

- For the Cascode example: we have seen that the OCTC at input ( $\tau_1 = 7.5$  psec) and output ( $\tau_4 = 3.3$  psec) comparable in magnitude
- Due to good isolation between input and output, these indeed can be seen as independent pole frequencies → Dominant pole approximation does not hold
- In many cases, we need to handle such circuits not as a first-order but as a second-order system with certain implications – this will be revisited in topic: Feedback and Stability

# 2<sup>nd</sup> Order Amplifiers

- The second-order system will be described with characteristic equation in the denominator

$$s^2 + s \frac{\omega_0}{Q} + \omega_0^2 = 0$$

- In case of dominant pole, e.g.  $\frac{1}{\omega_{p_2}} \approx 0$

$$1 + s \left( \frac{1}{\omega_{p_1}} + \frac{1}{\omega_{p_2}} \right) + \frac{s^2}{\omega_1 \omega_{p_2}}$$

# 2<sup>nd</sup> Order Amplifiers

- The second-order system will be described with characteristic equation in the denominator

$$s^2 + s \frac{\omega_0}{Q} + \omega_0^2 = 0$$

- $s$ , the Laplace parameter with  $s = \sigma + j\omega$
- $Q$  quality factor ( $\frac{1}{2Q} = \zeta$ , damping factor), and  $\omega_0$  the (complex conjugate) pole frequency

# 2<sup>nd</sup> Order Amplifiers

- The second-order amplifier behaviour

