

# Mikroelektronische Schaltungen und Systeme

## Lect.7 Feedback

Prof. Dr.-Ing. Ahmet Cagri Ulusoy  
Institut für Hochfrequenztechnik und Elektronik (IHE)



# Mikroelektronische Schaltungen und Systeme

Lect.1

Intro/CMOS Basics

Lect.2

Single Stage  
Amplifiers

Lect.3

Noise

Lect.4

Differential  
Amplifiers

Lect.5

Current Sources

Lect.6

Frequency  
Response

Lect.7

Feedback

Lect.8

Operational Amplifiers

Lect.9

Stability and  
Frequency  
Compensation

Lect.10

Switched-Capacitor  
Circuits

Lect.11

Introduction to Data  
Converters

Lect.12

Combinational Logic  
Circuits

Lect.13

Sequential Circuits

Lect.14

Timing of Sequential  
Circuits

Lect.15

Digital Building  
Blocks

Lect.16

Memory

Lect.17

Technology  
Mapping

Lect.18

FPGA

Lect.19

Physical Design I

Lect.20

Physical Design II

Lect.21

Q&A






# Introduction

- Microelectronic circuits are rarely used in „open loop“, they typically contain some kind of feedback mechanism to:
  - Adjust the gain
  - Adjust input/output impedances to desired values
  - Linearize/stabilize the circuit
  - Robustness against PVT
- All circuits also include unintentional feedback (e.g., Miller capacitance)
- In classic text book approach, feedback is analyzed from a system theoretical perspective
- We will start with this, but we will introduce a more intuitive approach to feedback analysis
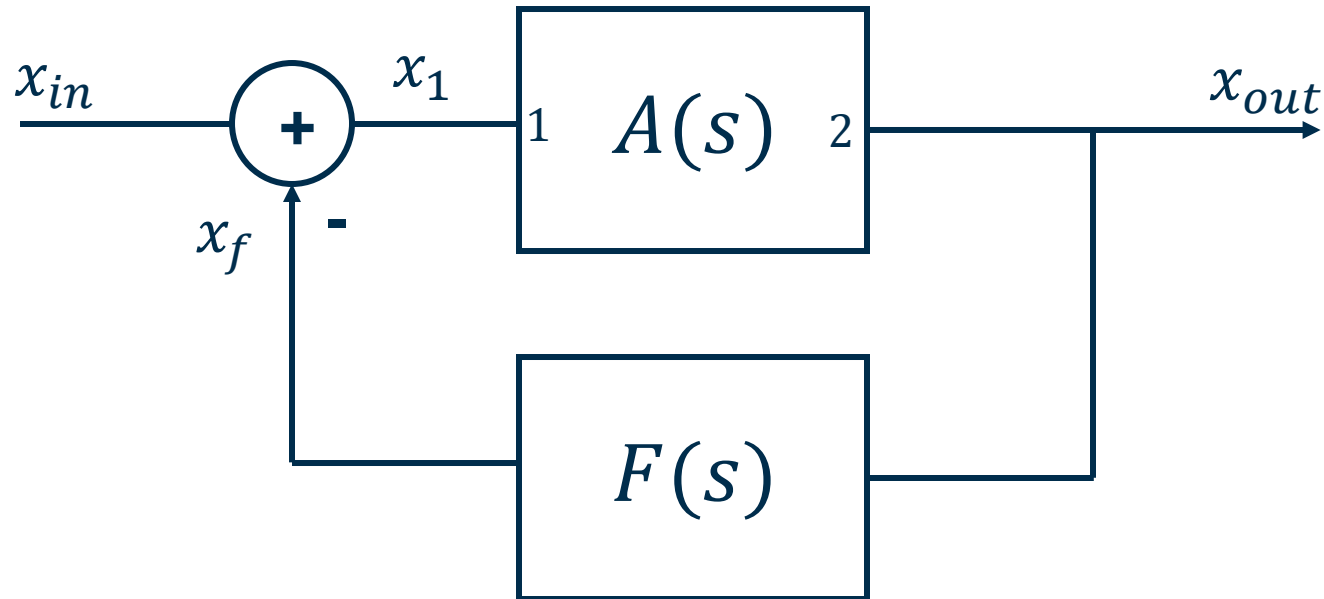
# Feedback System

- A general representation of a feedback system looks as following:



- Here,  $x_{in}, x_{out}$  could be voltages, currents or a mix of voltage and current

# Feedback System

- This representation leads to classic feedback expression (in steady state for voltage signals):

$$v_2 = v_{out} = v_1 A(j\omega)$$

$$v_1 = v_{in} - v_f = v_{in} - v_{out} F(j\omega)$$

$$\frac{v_{out}}{v_{in}} = \frac{A(j\omega)}{1 + A(j\omega)F(j\omega)}$$


# Feedback System

- The challenge in circuit design with feedback is to properly draw the boundaries between  $A$  and  $F$  circuits in a way that the general expressions from previous slide hold, and any loading affect between the two circuits are taken into account
- For this purpose, we try to identify the feedback mechanism, and try to fit parts of the circuit to appropriate boxes
- These „boxes“ are two-port representations of portions of the circuits


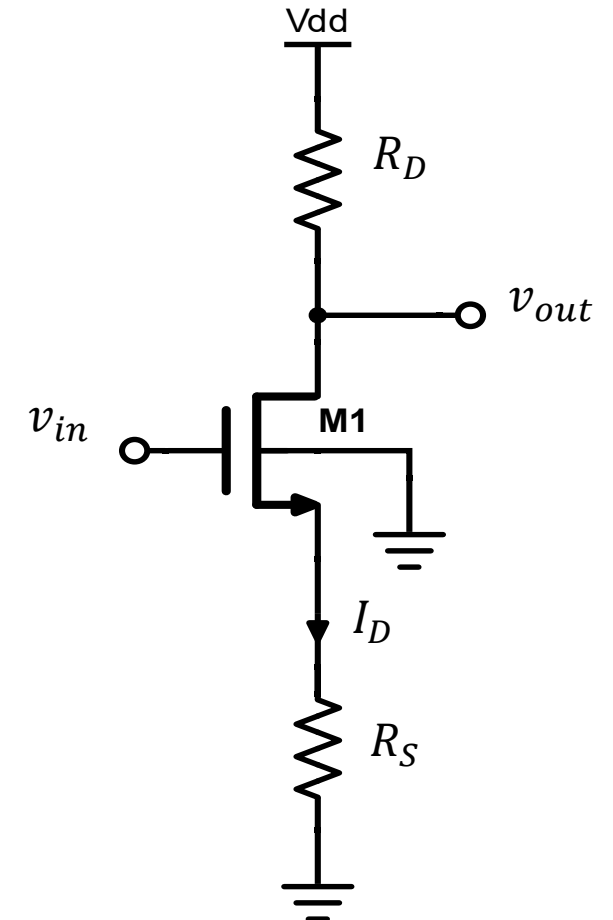
# Common-Source Amplifier with Source Degeneration


- We start with a simple example, CS stage with source degeneration:
- **First:** identify the feedback mechanism


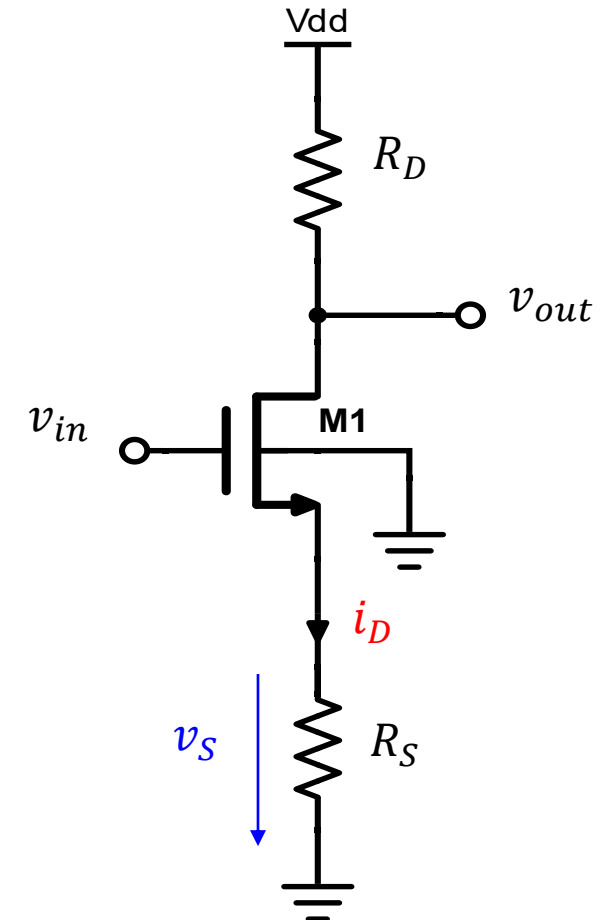
# Common-Source Amplifier with Source Degeneration

- We start with a simple example, CS stage with source degeneration:
- **First:** identify the feedback mechanism
  - The current at the output  $i_D$  generates a voltage across  $R_S$ , which generates a feedback voltage that is subtracted from  $v_{in}$
  - It is a negative feedback
  - It samples **current** at the **output** and feeds back **voltage** to the **input**


$$v_{GS} = v_{in} - v_S = v_{in} - i_D R_S$$



# Common-Source Amplifier with Source Degeneration

- Here, the *A-circuit* is a common source amplifier, with voltage as input signal and current as output signal, ideally modelled with its **y-parameters**
- The *F-circuit* is the feedback resistor, that takes current as input, and voltage as output, ideally modelled with its **z-parameters**

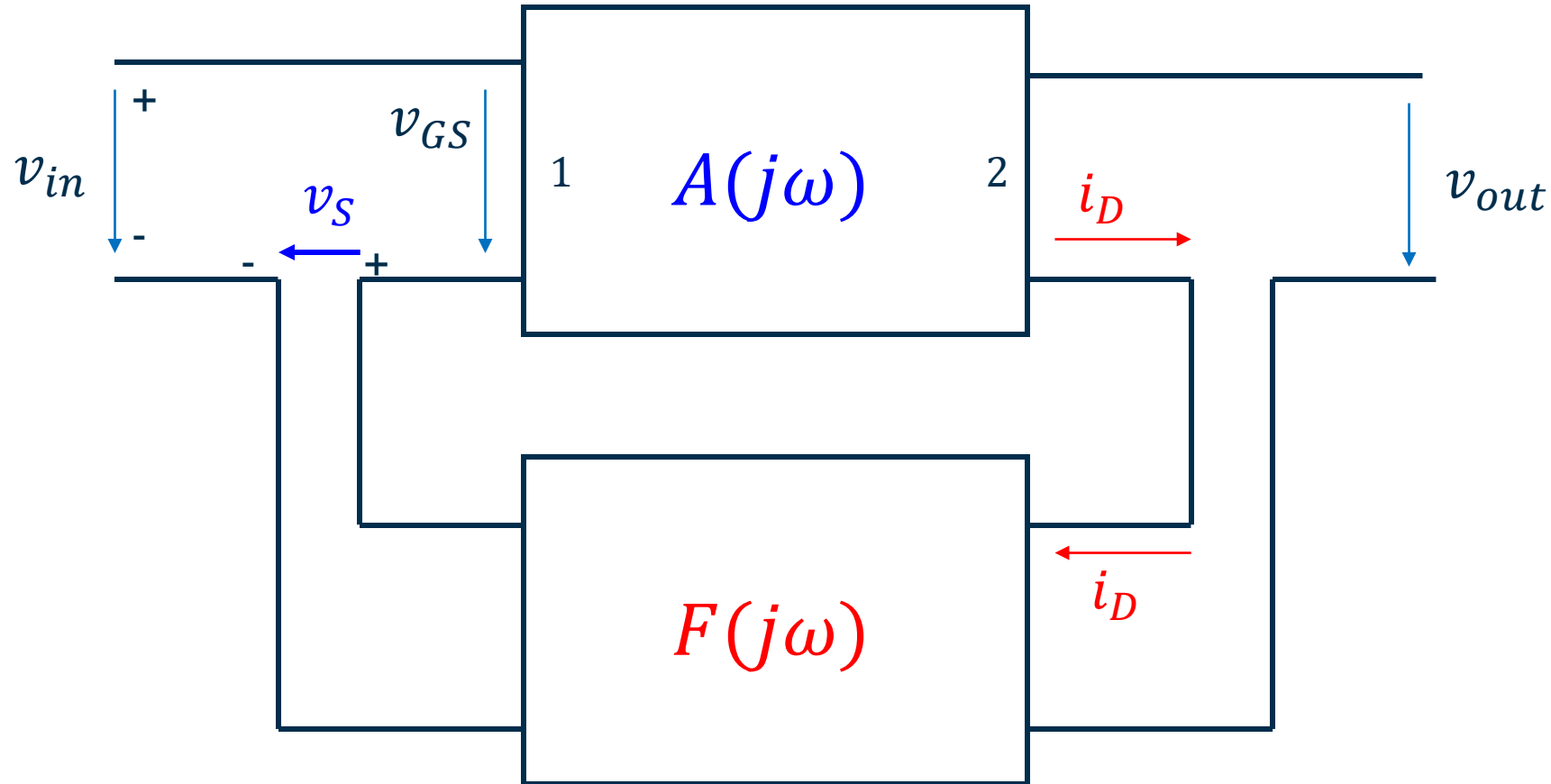
# Common-Source Amplifier with Source Degeneration



# Common-Source Amplifier with Source Degeneration

$$i_1 = y_{11}v_1 + y_{12}v_2$$


$$i_2 = y_{21}v_1 + y_{22}v_2$$

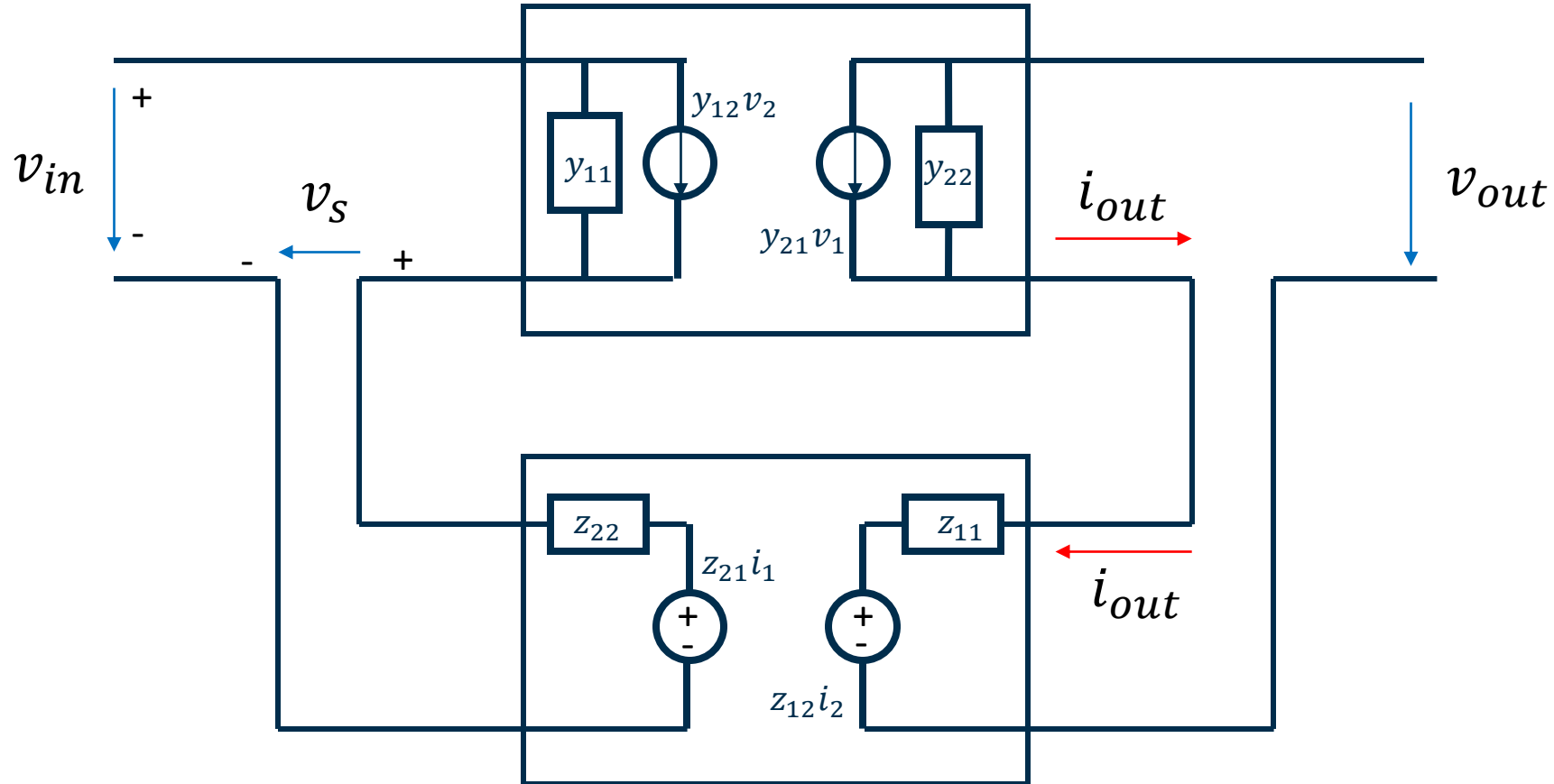


$$v_1 = z_{11}i_1 + z_{12}i_2$$

$$v_2 = z_{21}i_1 + z_{22}i_2$$
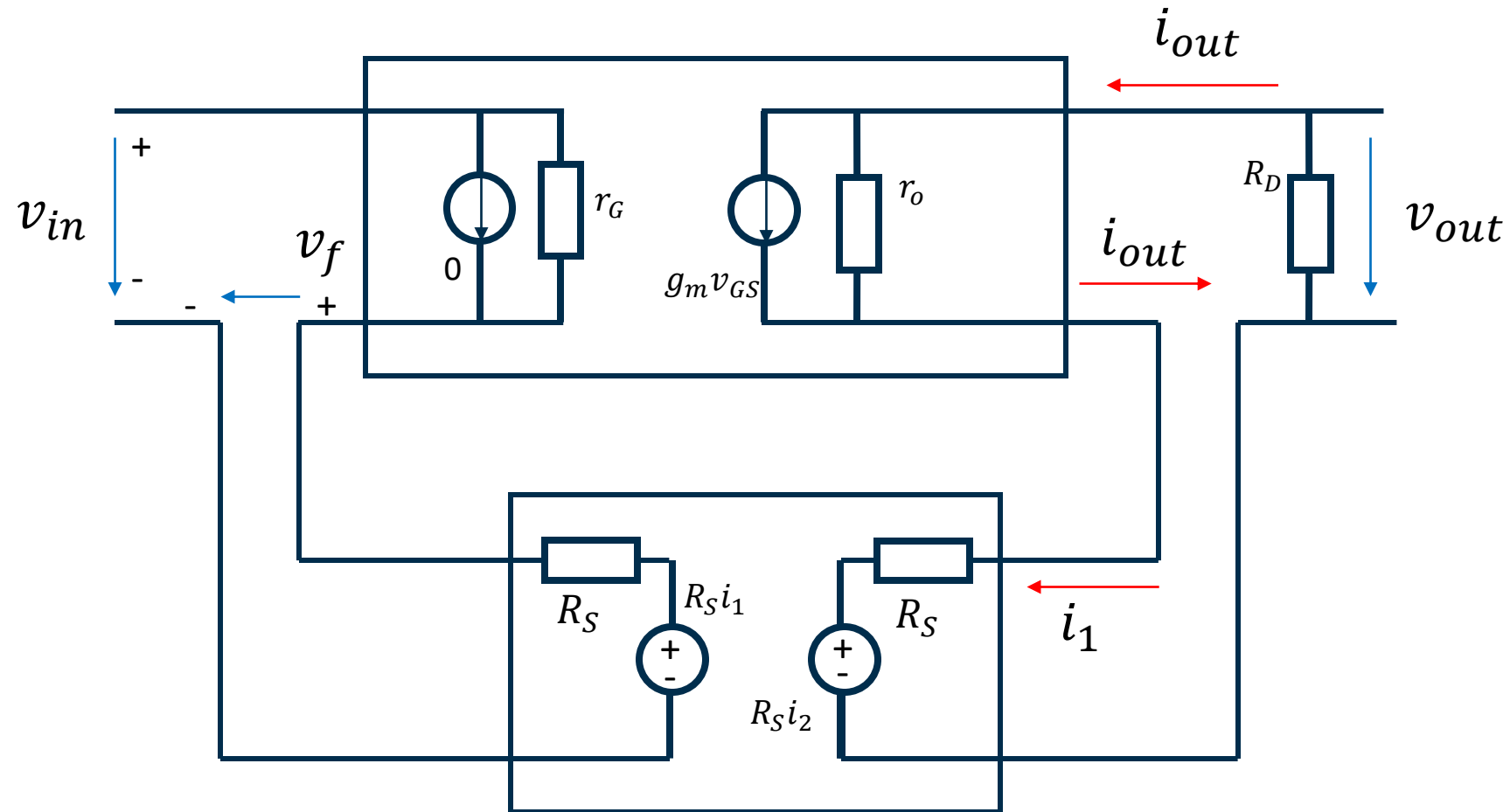
# Common-Source Amplifier with Source Degeneration



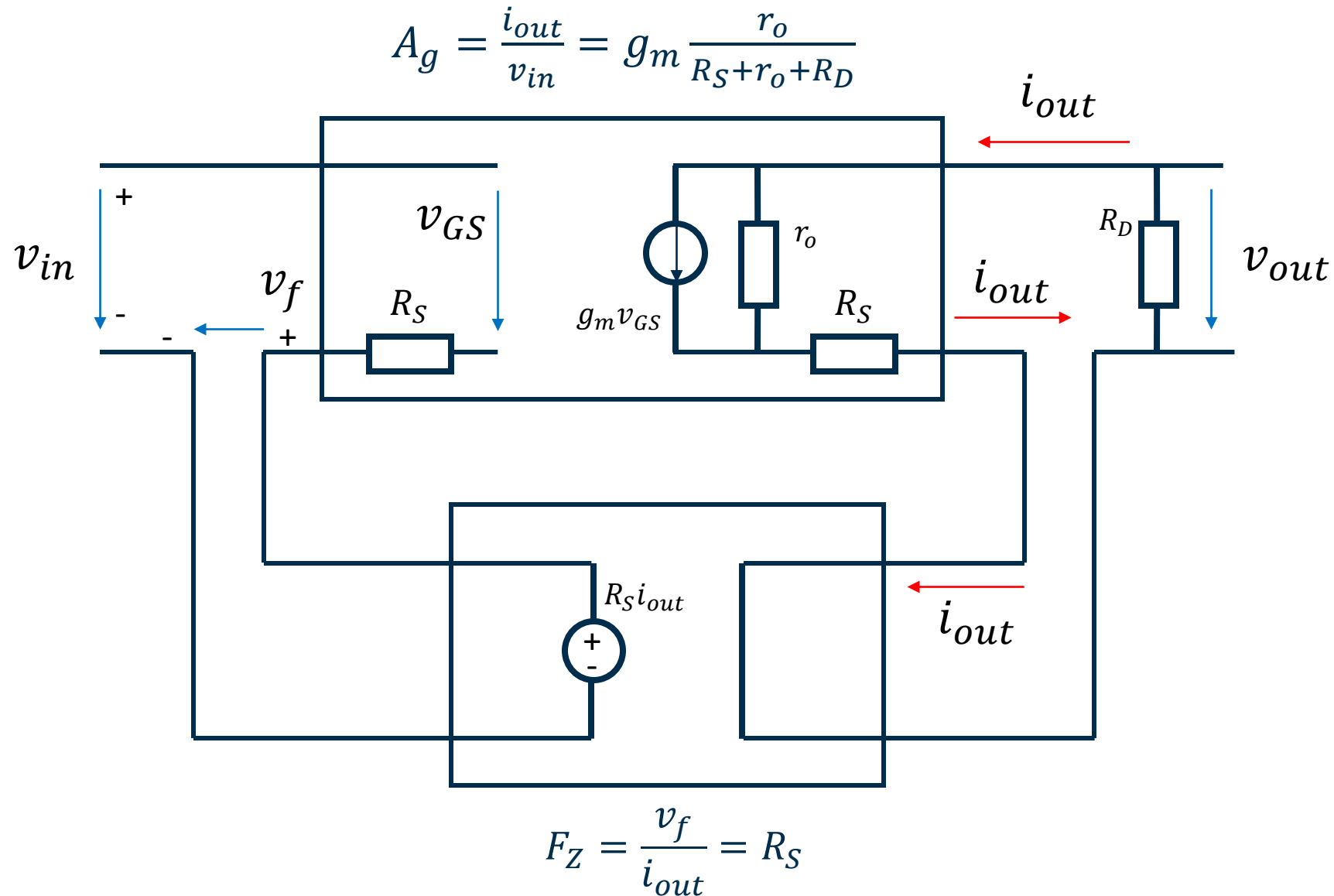
# Common-Source Amplifier with Source Degeneration


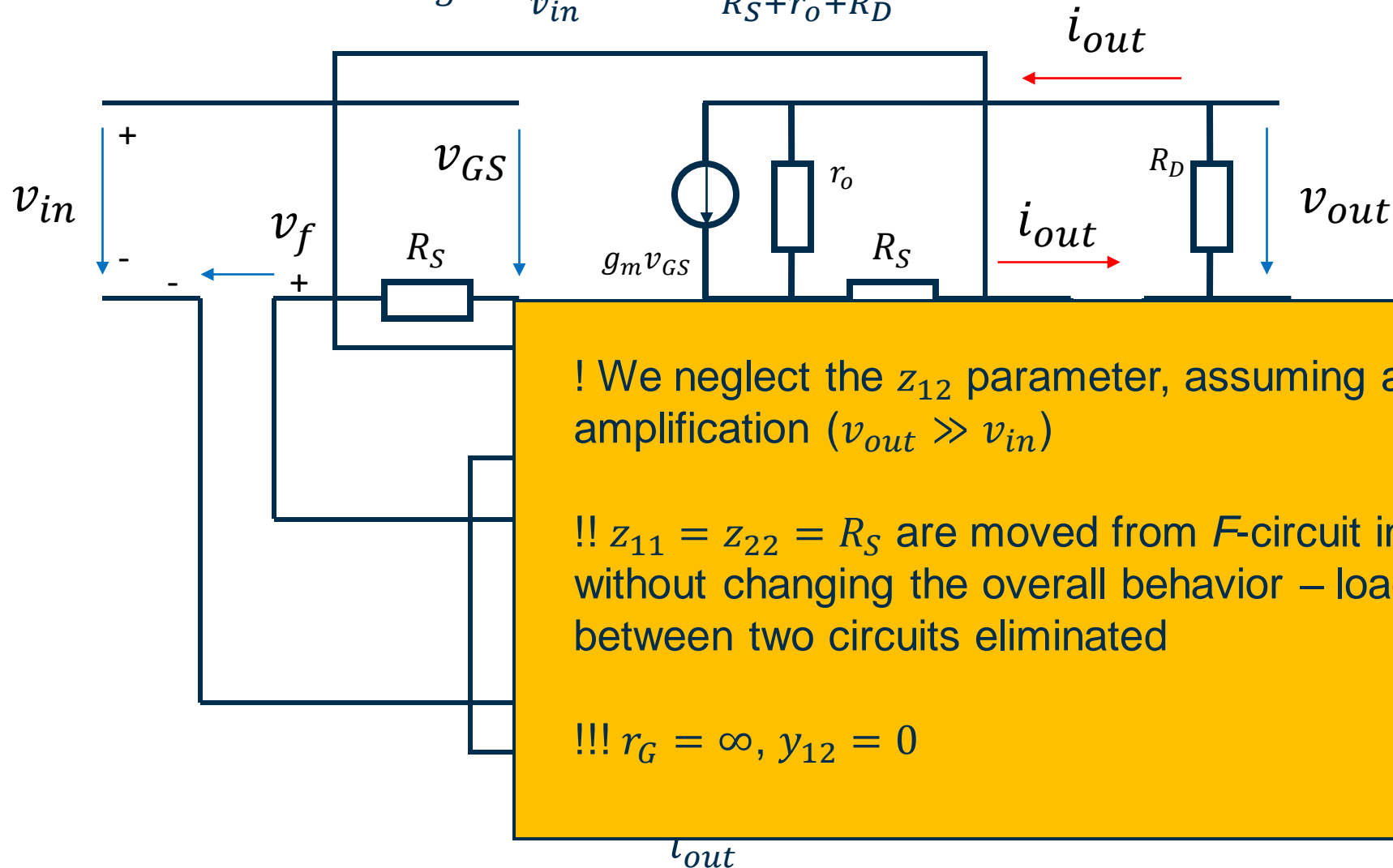
# Common-Source Amplifier with Source Degeneration

$$A_g = \frac{i_{out}}{v_{in}} = g_m \frac{r_o}{R_S + r_o + R_D}$$



! We neglect the  $z_{12}$  parameter, assuming a large voltage amplification ( $v_{out} \gg v_{in}$ )

!!  $z_{11} = z_{22} = R_S$  are moved from  $F$ -circuit into  $A$ -circuit without changing the overall behavior – loading effects between two circuits eliminated

!!!  $r_G = \infty, y_{12} = 0$



# Common-Source Amplifier with Source Degeneration

- Closed Loop Gain:

$$A_{gf} = \frac{i_{out}}{v_{in}} = \frac{A_g}{1 + A_g F_z} = \frac{r_o}{R_S + r_o + R_D} \frac{g_m}{1 + g_m \frac{r_o R_S}{R_S + r_o + R_D}}$$

- Closed Loop Voltage Gain:

$$A_{vf} = \frac{v_{out}}{v_{in}} = -\frac{A_g}{1 + A_g F_z} \times R_D = -\frac{r_o}{R_S + r_o + R_D} \frac{g_m R_D}{1 + g_m \frac{r_o R_S}{R_S + r_o + R_D}}$$

# Common-Source Amplifier with Source Degeneration

- Closed Loop Gain:

$$A_{gf} = \frac{i_{out}}{v_{in}} = \frac{A_g}{1 + A_g F_z} = \frac{r_o}{R_S + r_o + R_D} \frac{g_m}{1 + g_m \frac{r_o R_S}{R_S + r_o + R_D}}$$

- Closed Loop Voltage Gain:

$$A_{vf} = \frac{v_{out}}{v_{in}} = - \frac{A_g}{1 + A_g F_z} \times R_D = - \frac{\cancel{r_o}}{\cancel{R_S + r_o + R_D}} \frac{g_m R_D}{\cancel{X} + g_m \frac{\cancel{r_o} R_S}{\cancel{R_S + r_o + R_D}}} \approx - \frac{R_D}{R_S}$$

for  $r_o \gg R_S, R_D$

# Feedback Types

	A-input	A-output	$Z_{in}$	$Z_{out}$
series-series	voltage	current	$Z_i(1 + AF)$	$Z_o(1 + AF)$
series-shunt	voltage	voltage	$Z_i(1 + AF)$	$Z_o/(1 + AF)$
shunt-series	current	current	$Z_i/(1 + AF)$	$Z_o(1 + AF)$
shunt-shunt	current	voltage	$Z_i/(1 + AF)$	$Z_o/(1 + AF)$


# Feedback Analysis using Asymptotic Gain Function

- Instead of such a formal analysis, we would like to use a more intuitive approach, namely, the asymptotic gain
- In this case we consider the extreme case for the feedback analysis, asking ourselves what happens if our feedback circuit is „ideal“, having an *A-circuit* with an infinitely high amplification

$$\frac{v_{out}}{v_{in}} = \frac{A}{1 + AF} \bigg|_{A \rightarrow \infty} = \frac{1}{F}$$


# Example

- Consider following feedback circuit:

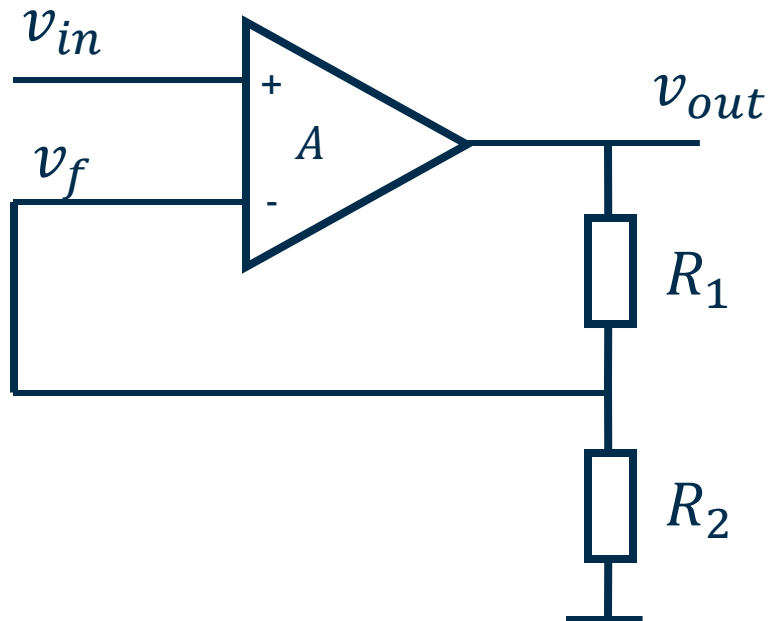

# Example

- Consider following feedback circuit:

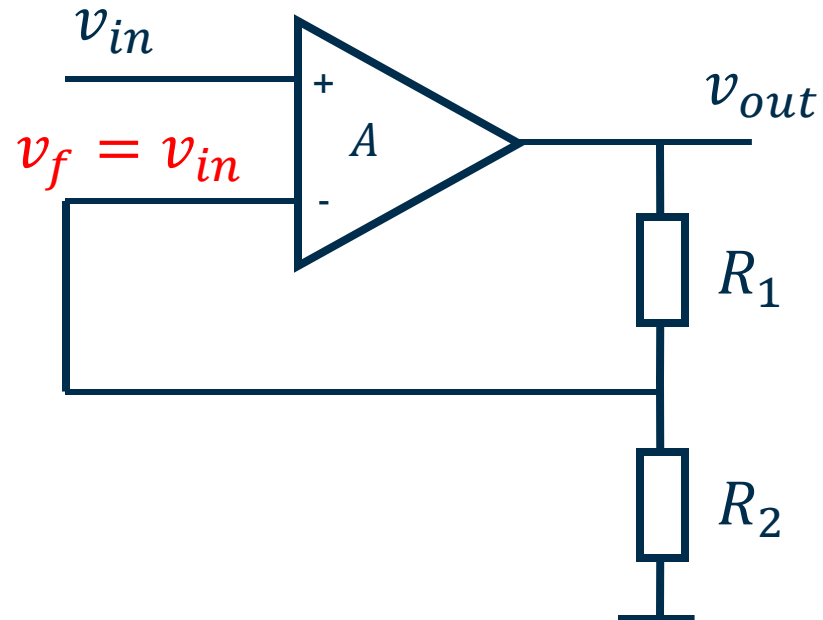


$$\frac{v_{out}R_2}{R_1 + R_2} = v_{in}$$
$$H_{\infty} = \left. \frac{v_{out}}{v_{in}} \right|_{A=\infty} = 1 + \frac{R_1}{R_2}$$

OPAMP is ideal:  $A \rightarrow \infty$

# Example

- Consider following feedback circuit:

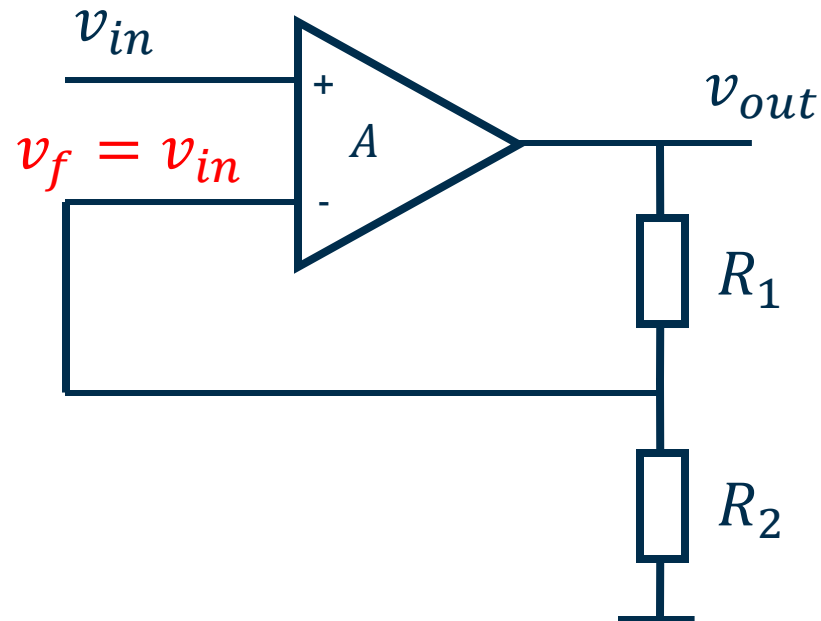

OPAMP is ideal:  $A \rightarrow \infty$


$$\frac{v_{out}R_2}{R_1 + R_2} = v_{in}$$

$$H_{\infty} = \left. \frac{v_{out}}{v_{in}} \right|_{A=\infty} = 1 + \frac{R_1}{R_2}$$

- If we want an amplifier with a gain of 10, chose  $R_1 = 9 \text{ k}\Omega$  and  $R_2 = 1 \text{ k}\Omega$

# Common-Source Amplifier with Source Degeneration


- Let's revisit previous circuit:

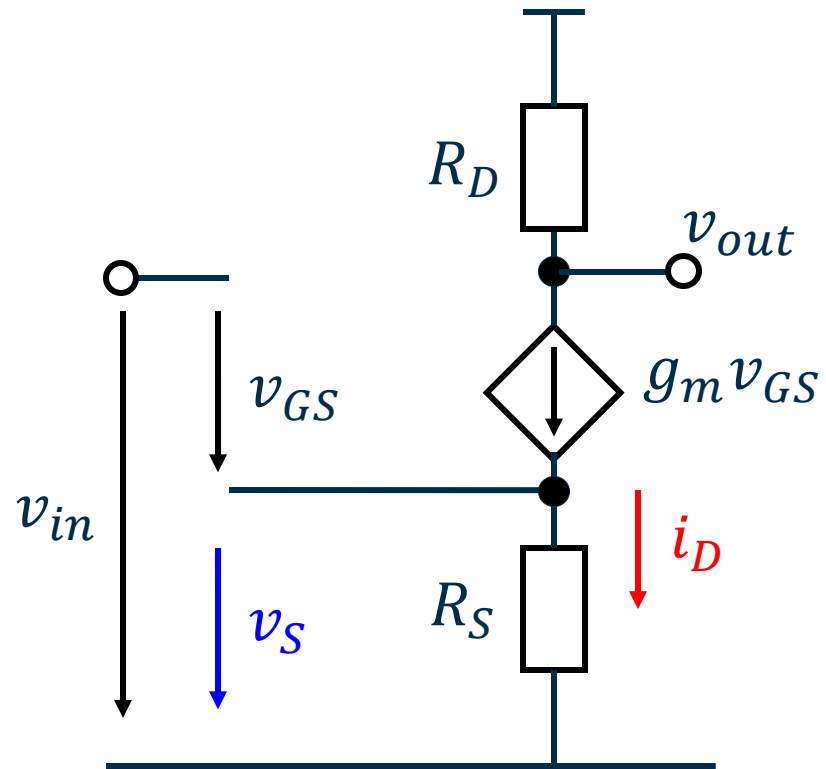



# Common-Source Amplifier with Source Degeneration

- Let's revisit previous circuit:

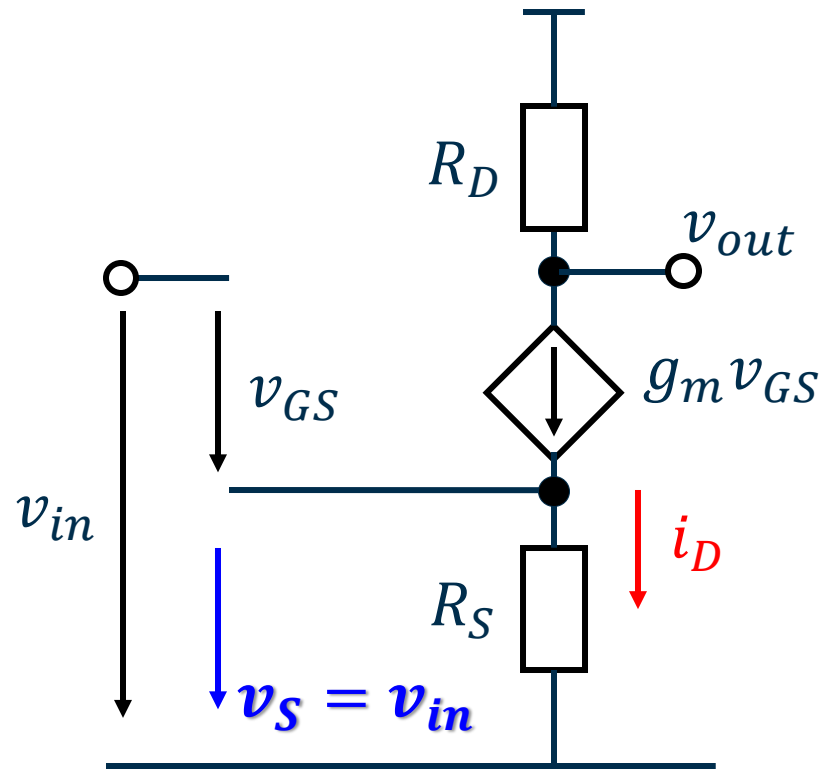

MOSFET ideal:  $g_m \rightarrow \infty$


$$i_{out} = i_D = \frac{v_{in}}{R_S}$$

$$v_{out} = -i_{out} R_D = -\frac{v_{in}}{R_S} R_D$$

$$\frac{v_{out}}{v_{in}} = -\frac{R_D}{R_S}$$
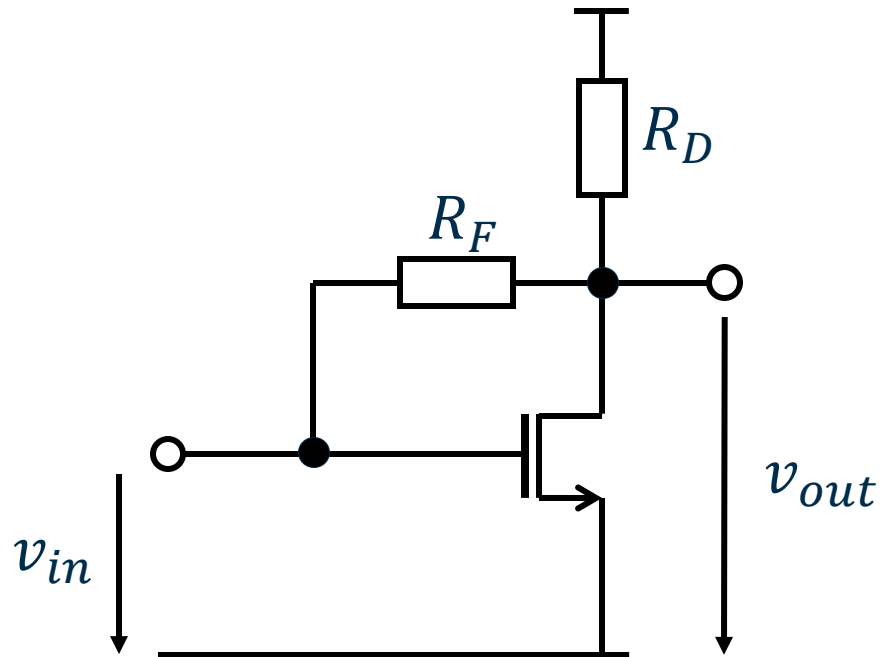
# Common-Source with Shunt Feedback


- Let's consider a second common feedback circuit:


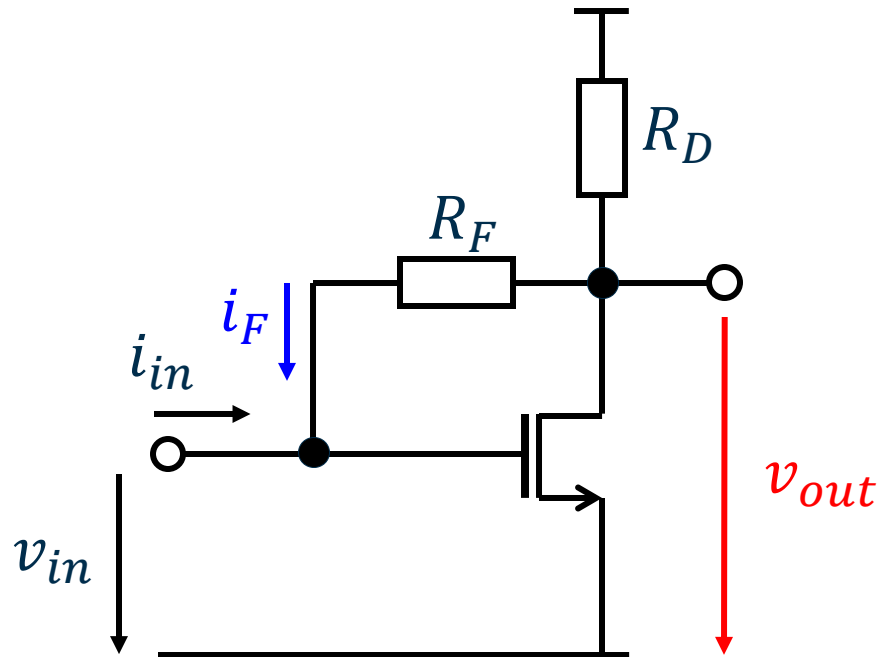
# Common-Source with Shunt Feedback

- Let's consider a second common feedback circuit:

! The feedback circuit samples voltage and feeds current back to the input




# Common-Source with Shunt Feedback

- Let's consider a second common feedback circuit:

! The feedback circuit samples voltage and feeds current back to the input

MOSFET ideal:  $g_m \rightarrow \infty$

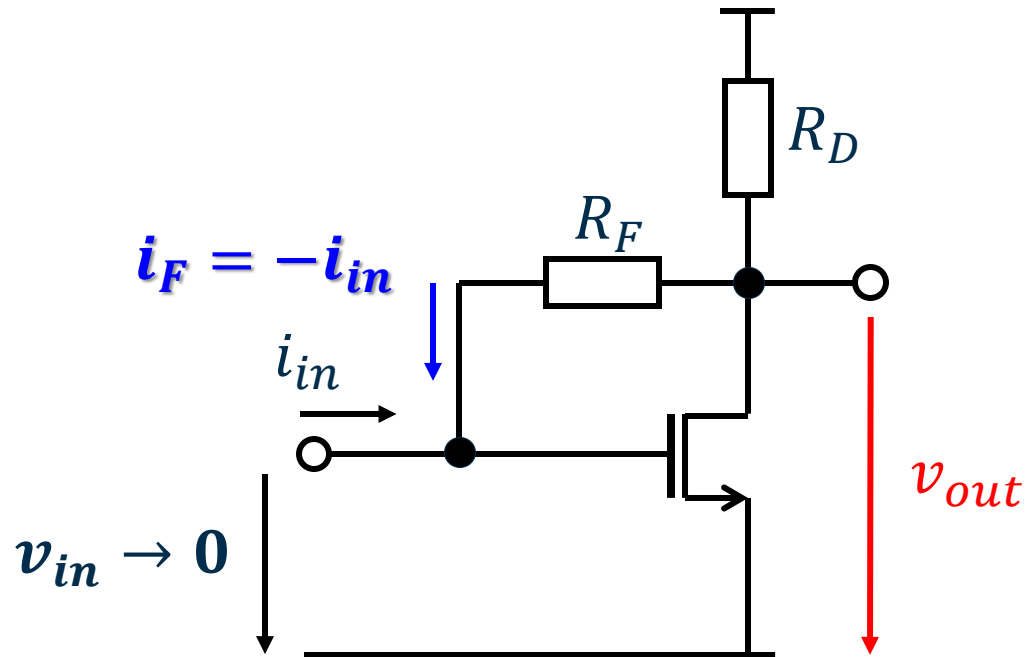


$$v_{out} - v_{in}^0 = -i_{in} R_F$$

$$v_{out}/i_{in} = -R_F$$

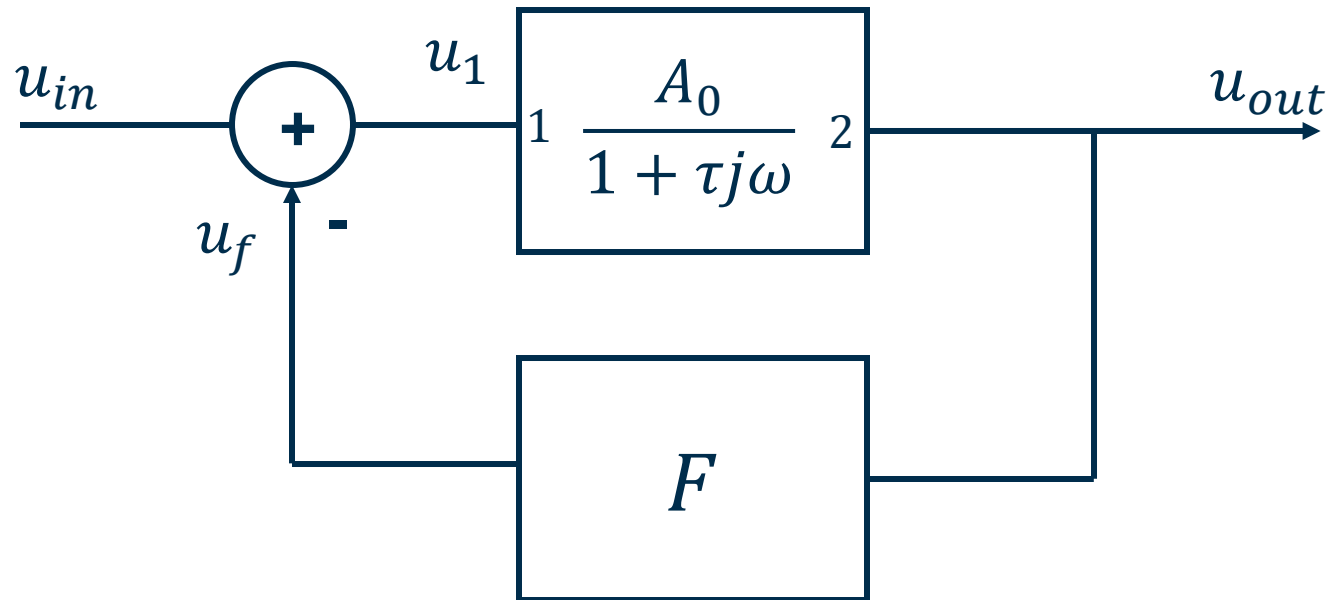
# Effects of Feedback

- Frequency response can be modified to achieve desired response:



# Effects of Feedback


- Frequency response can be modified:

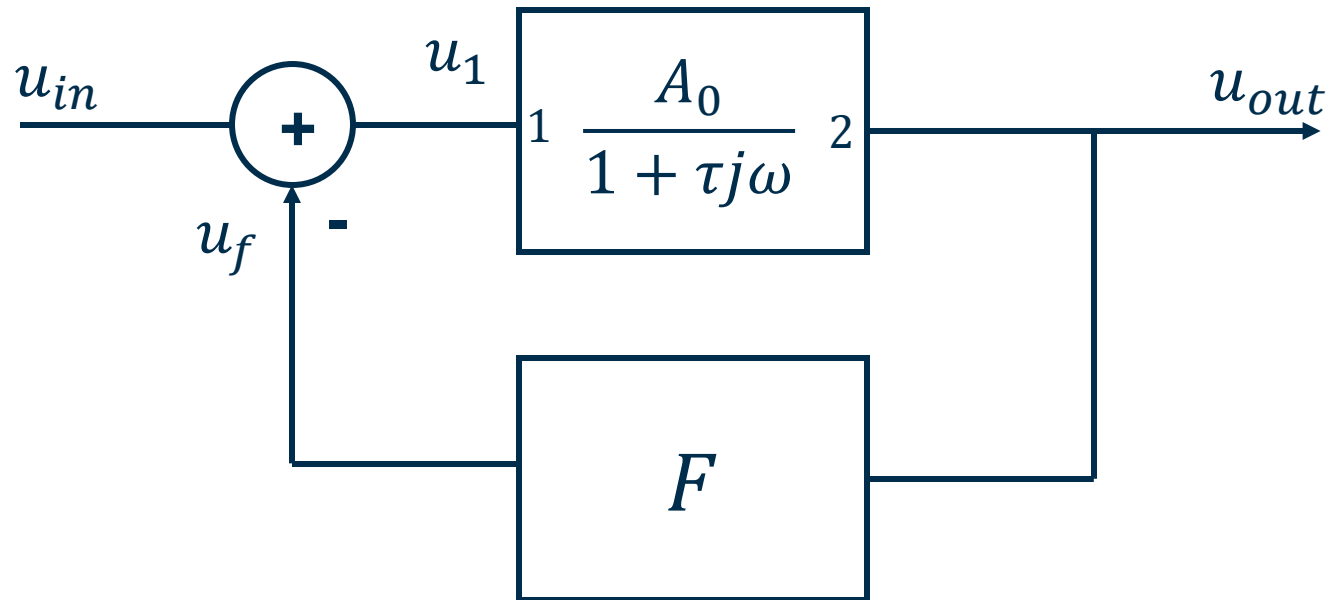

$$H(j\omega) = \frac{A(j\omega)}{1 + A(j\omega)F} = \frac{A_0}{1 + A_0F + \tau j\omega} = \frac{A_0}{1 + A_0F} \frac{1}{1 + \frac{\tau}{1 + A_0F} j\omega}$$

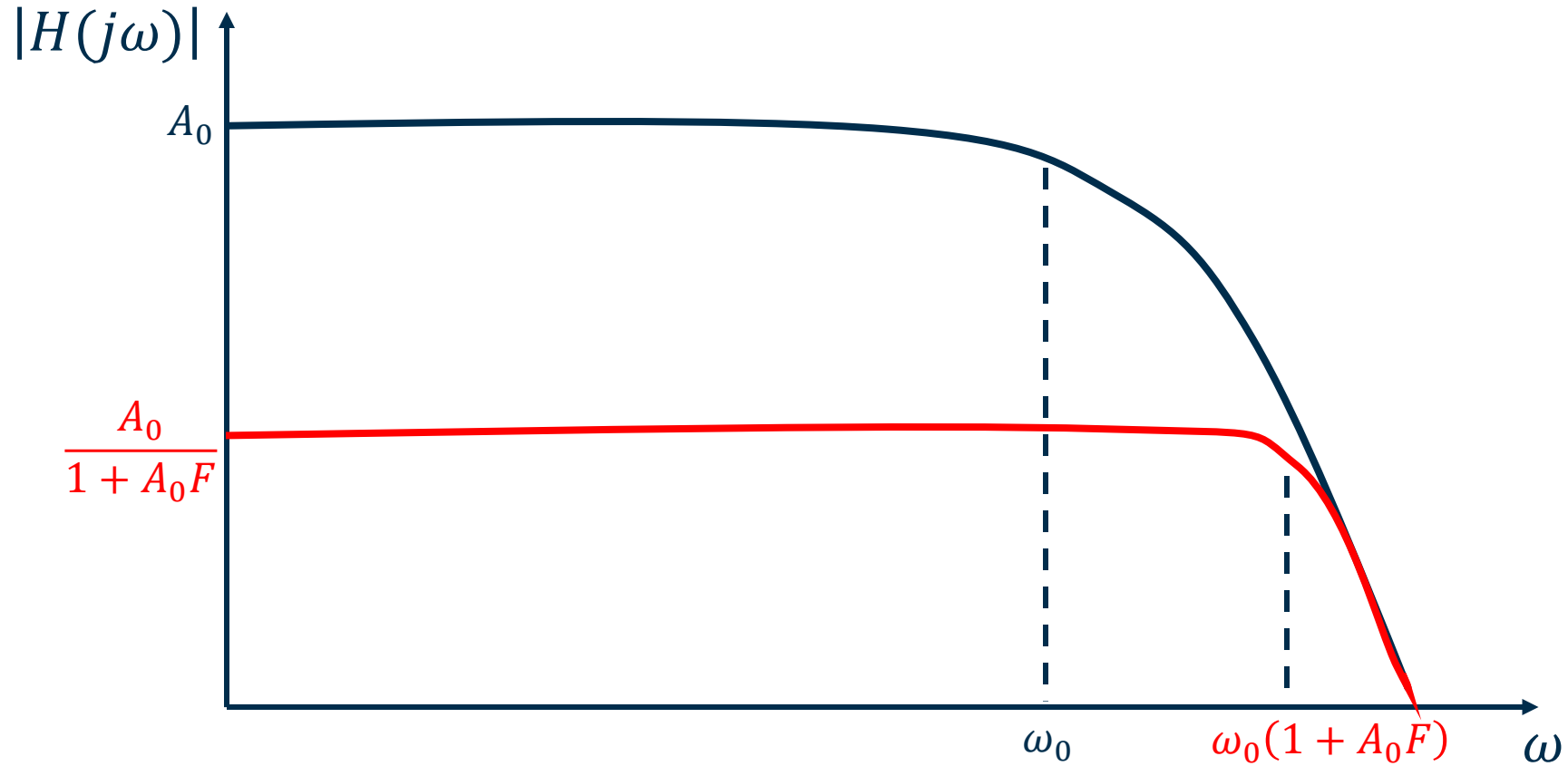
# Effects of Feedback

- Frequency response with negative feedback:


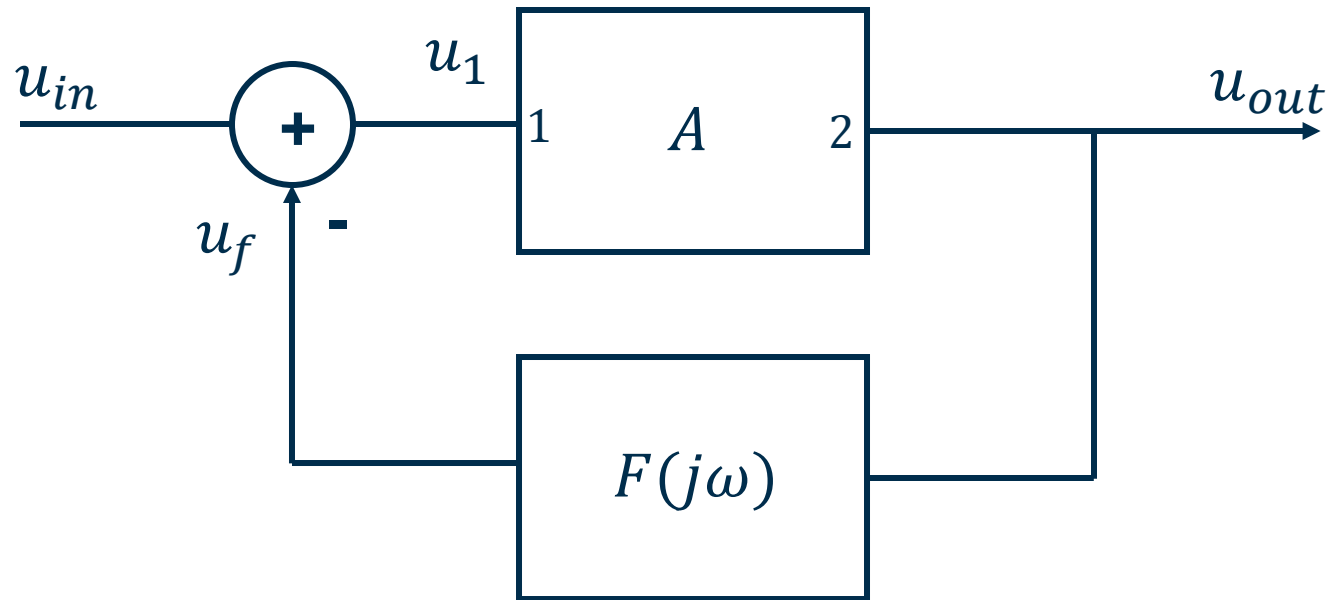
# Effects of Feedback

- Frequency response can be modified, but the situation is different when the frequency dependency in the feedback circuit:






# Effects of Feedback

- RC-Feedback:


- This a high-pass feedback circuit, but:

$$\frac{v_{out}}{v_{in}} = \frac{A}{1 + AF} \bigg|_{A \rightarrow \infty} = \frac{1}{F}$$

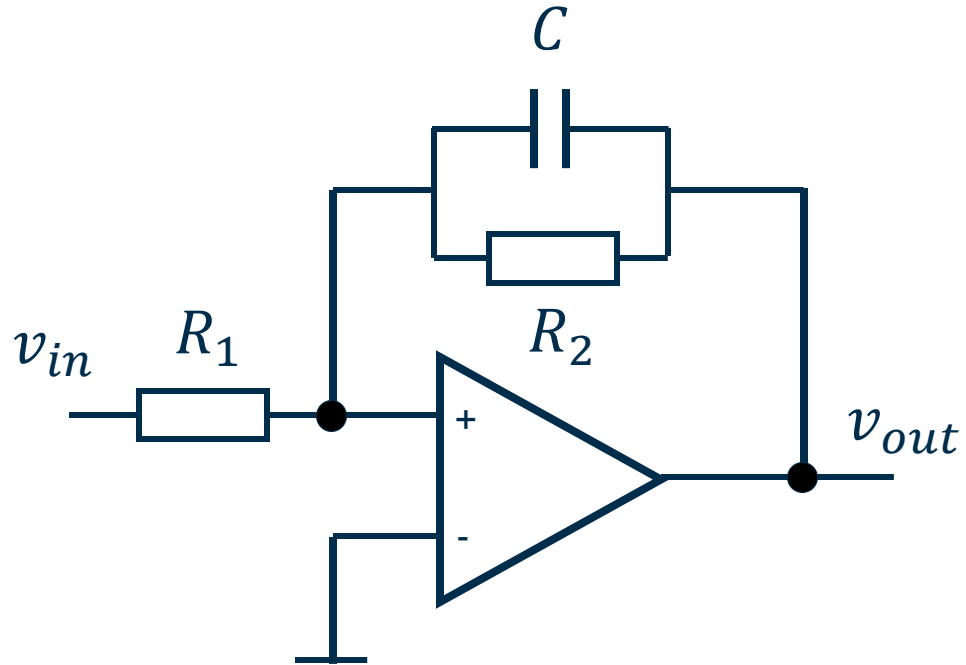

# Effects of Feedback

- RC-Feedback:

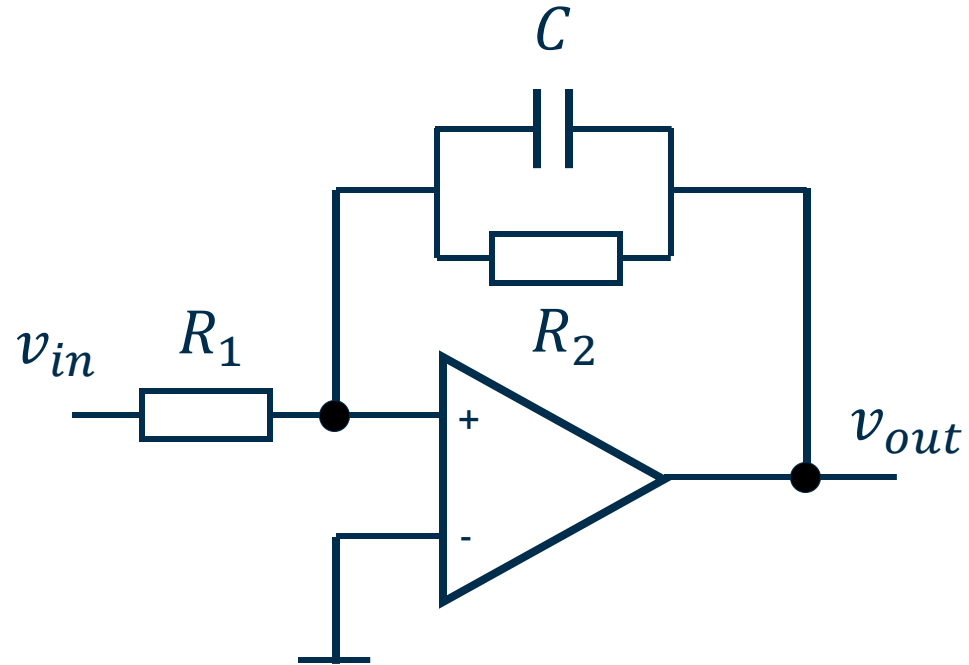

- This a high-pass feedback circuit, but:

$$\frac{v_{out}}{v_{in}} = \frac{A}{1 + AF} \bigg|_{A \rightarrow \infty} = \frac{1}{F}$$

$$\frac{v_{in}}{R_1} = - \frac{v_{out}}{\frac{R_2}{1 + j\omega R_2 C}}$$

$$H_{\infty} = \frac{v_{out}}{v_{in}} \bigg|_{A=\infty} = - \frac{R_2}{R_1} \frac{1}{1 + j\omega R_2 C}$$

- Which is a lowpass function!

# Asymptotic Transfer Function


- Now we would like to move towards acquiring the complete transfer function starting from the idealized case:

$$H = H_{\infty} \frac{T}{1 + T} + H_0 \frac{1}{1 + T}$$

$$H_{\infty} = H \Big|_{A \rightarrow \infty} \quad H_0 = H \Big|_{A \rightarrow 0} \quad T: \text{return ratio}$$
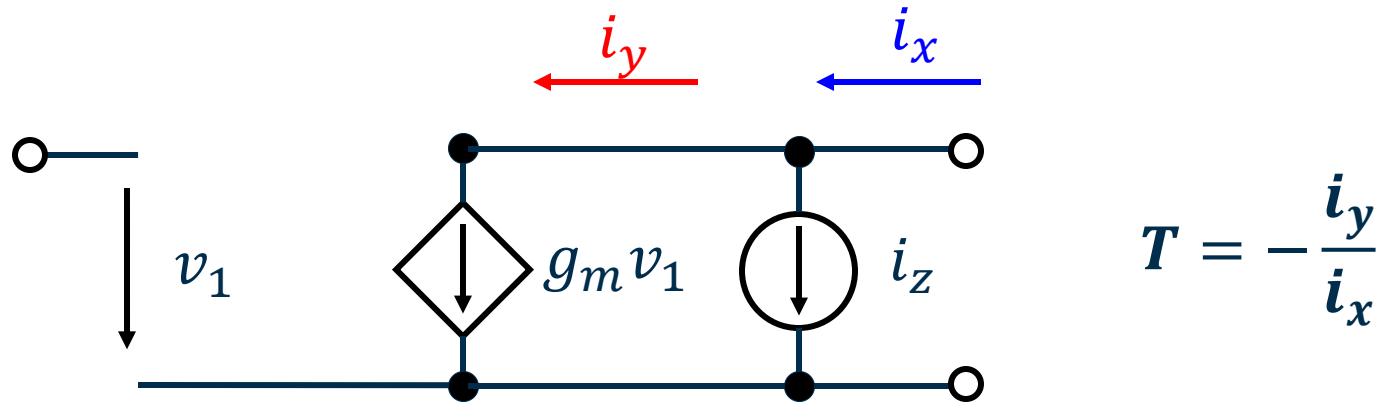
# Return Ratio


- The return ratio  $T$  is part of the controlled source signal that returns upon itself through the feedback, and corrects for the factor  $A \neq \infty$



- Other sources are eliminated from the circuit, the quantities could be voltages or currents (they need to be of the same type)
- In this example  $i_z$  is only included so that  $i_x \neq i_y$ , and does not influence the calculation of  $T$


# Common-Source Amplifier with Source Degeneration

- Let's return to our example

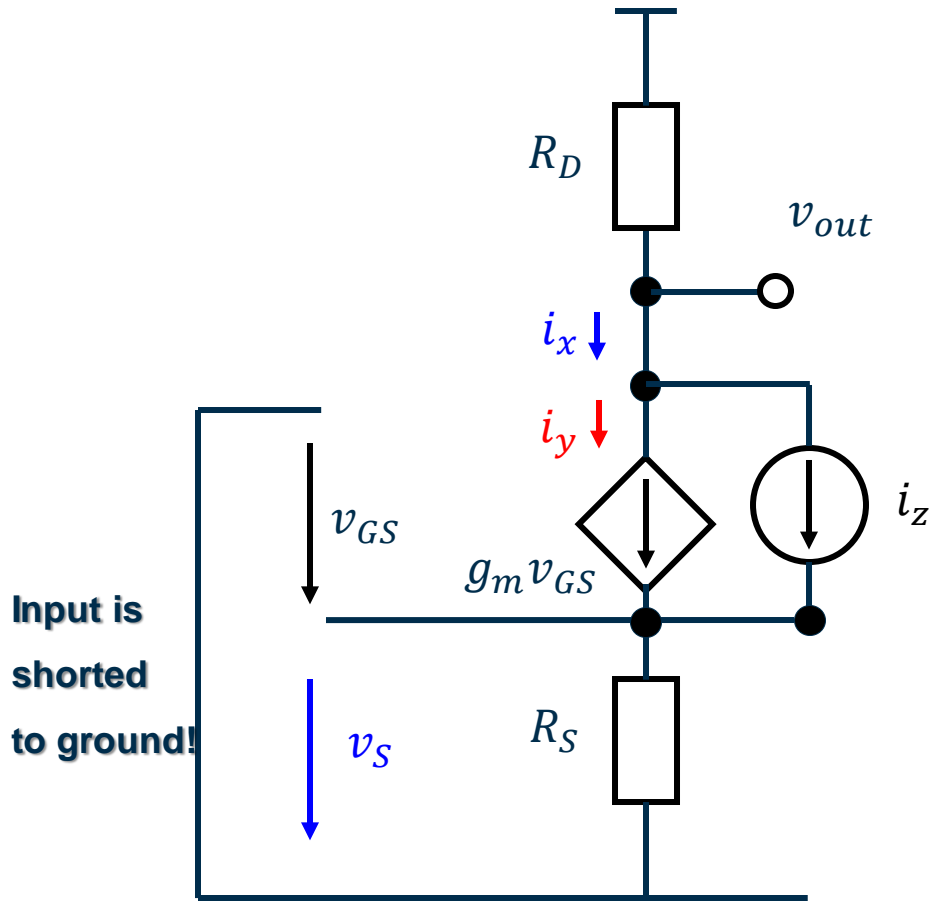

# Common-Source Amplifier with Source Degeneration

- Let's return to our example

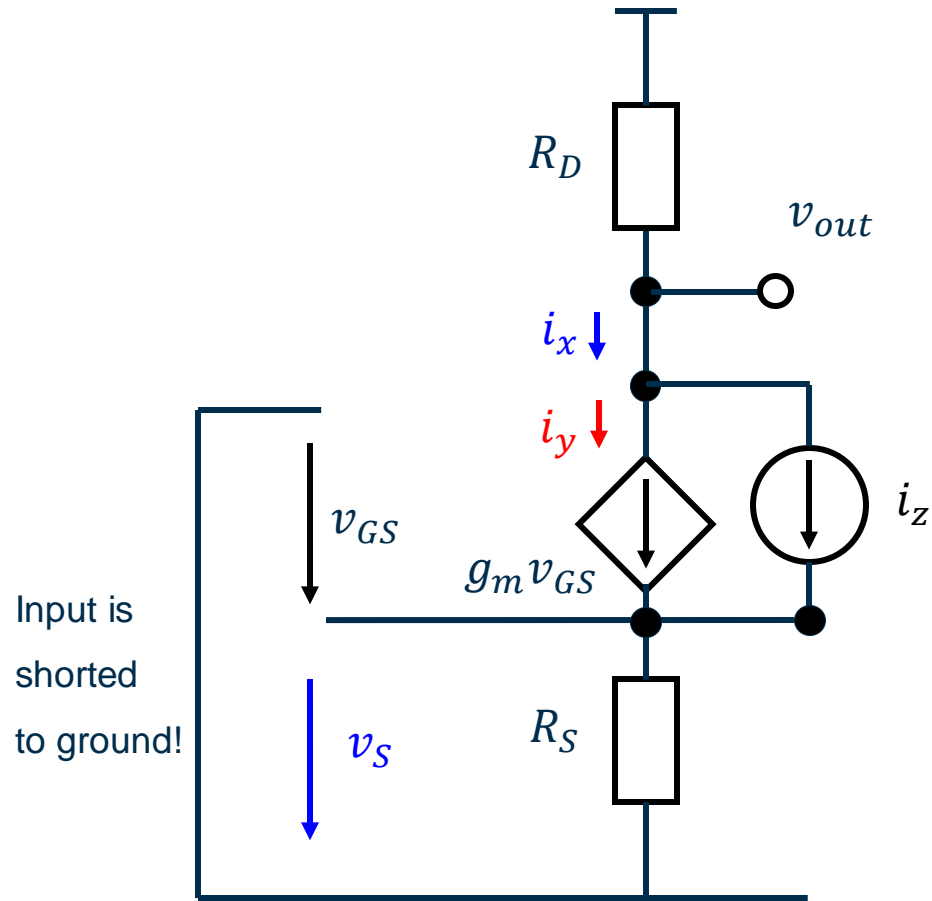


$$i_x R_S = -v_{GS}$$

$$i_y = -i_x g_m R_S$$

$$T = -\frac{i_y}{i_x} = g_m R_S$$

# Common-Source Amplifier with Source Degeneration

- Let's return to our example

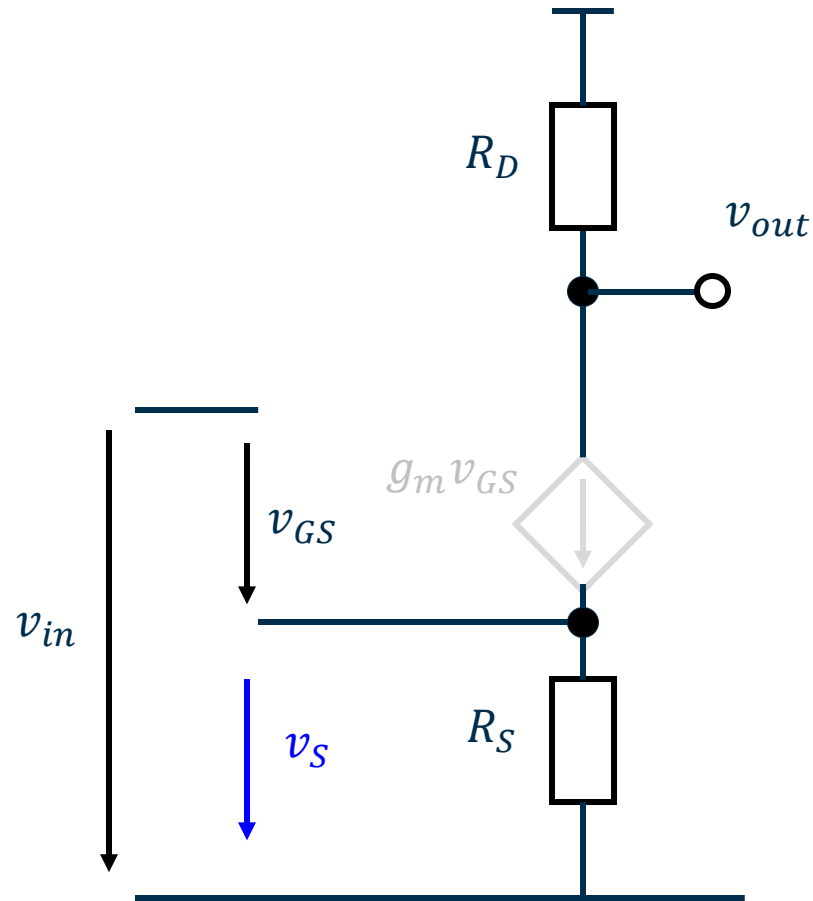

$$H_0 = H \Big|_{A \rightarrow 0} = 0$$


# Common-Source Amplifier with Source Degeneration

$$H = H_{\infty} \frac{T}{1 + T} + H_0 \frac{1}{1 + T}$$

$$H = -\frac{R_D}{R_S} \frac{g_m R_S}{1 + g_m R_S} = -\frac{g_m R_D}{1 + g_m R_S}$$



# Common-Source with Shunt Feedback

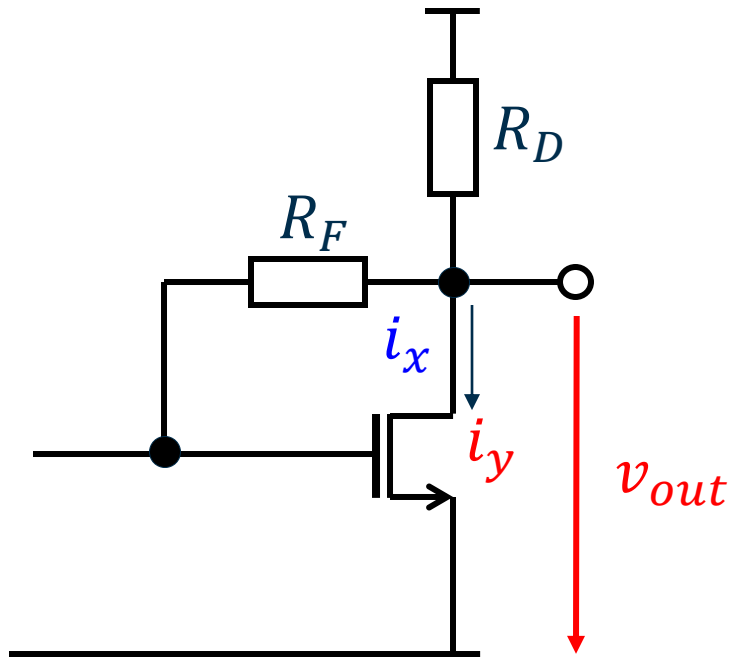


$$v_{out} = v_{in}$$

$$\frac{v_{in} - v_{out}}{R_F} - \frac{v_{out}}{R_D} = i_x$$

$$g_m v_{in} = i_y$$

$$T = -\frac{i_y}{i_x} = g_m R_D$$

# Common-Source with Shunt Feedback

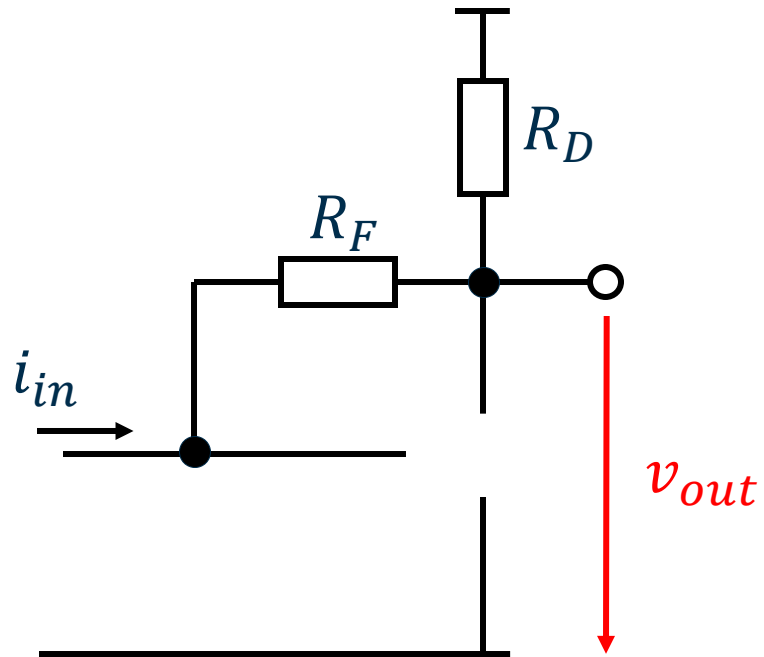

$$H_0 = H \Big|_{A \rightarrow 0} = -R_D$$

# Common-Source Amplifier with Source Degeneration

$$H = H_{\infty} \frac{T}{1 + T} + H_0 \frac{1}{1 + T}$$

$$H = -R_F \frac{g_m R_D}{1 + g_m R_D} - R_D \frac{1}{1 + g_m R_D}$$

$$H = -\frac{g_m R_D R_F + R_D}{1 + g_m R_D}$$


# Input/Output Impedances, Blackman's Formula

- The input and output impedances can be calculated using return ratio under open/short terminations at the port of interest

$$Z = Z_0 \frac{1 + T_{short}}{1 + T_{open}}$$

- $Z_0$  corresponds to the port impedance for  $H_0$  case

# Source Degenerated Amplifier

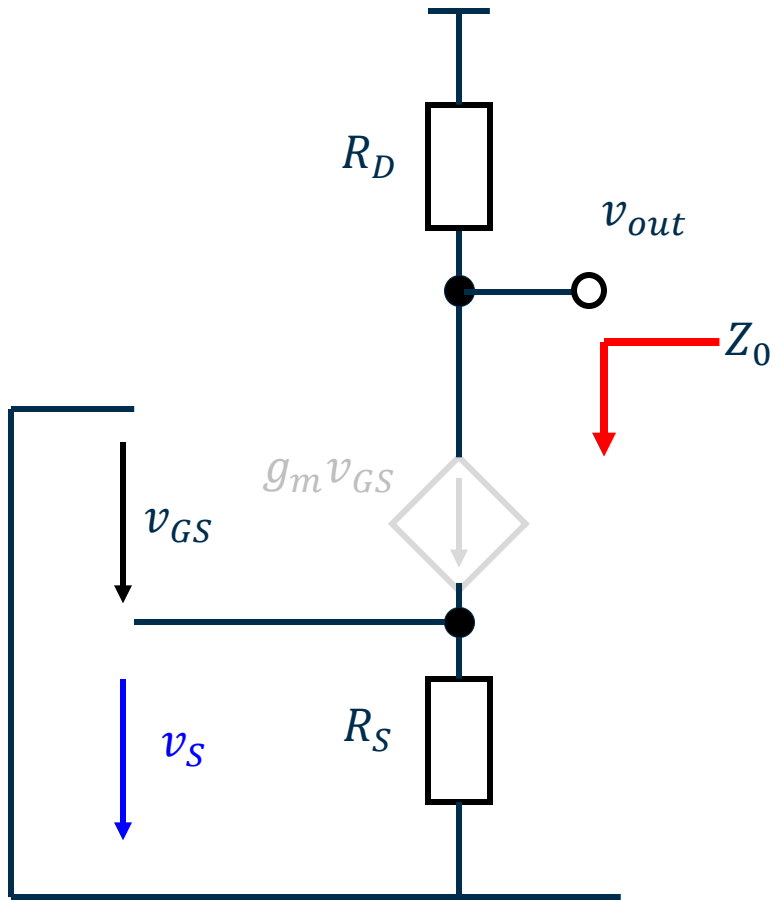


$$Z_0 = r_o$$

! Without channel length modulation  $z_{out} = \infty$

!! We are also not considering  $R_D$  in the circuit, because it will be just in parallel to whatever we find looking into the amplifier

# Common-Source Amplifier with Source Degeneration


## ■ $T_{short}$

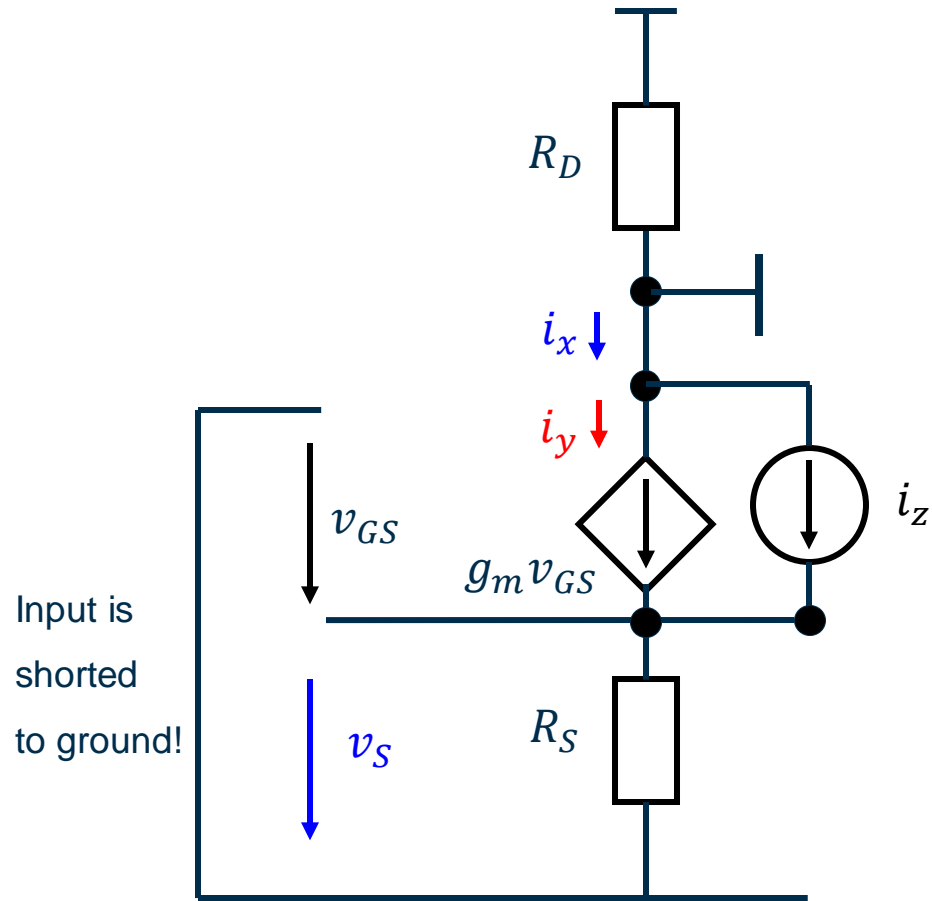

$$T_{short} = T = -\frac{i_y}{i_x} = g_m R_S$$

# Common-Source Amplifier with Source Degeneration

## ■ $T_{short}$

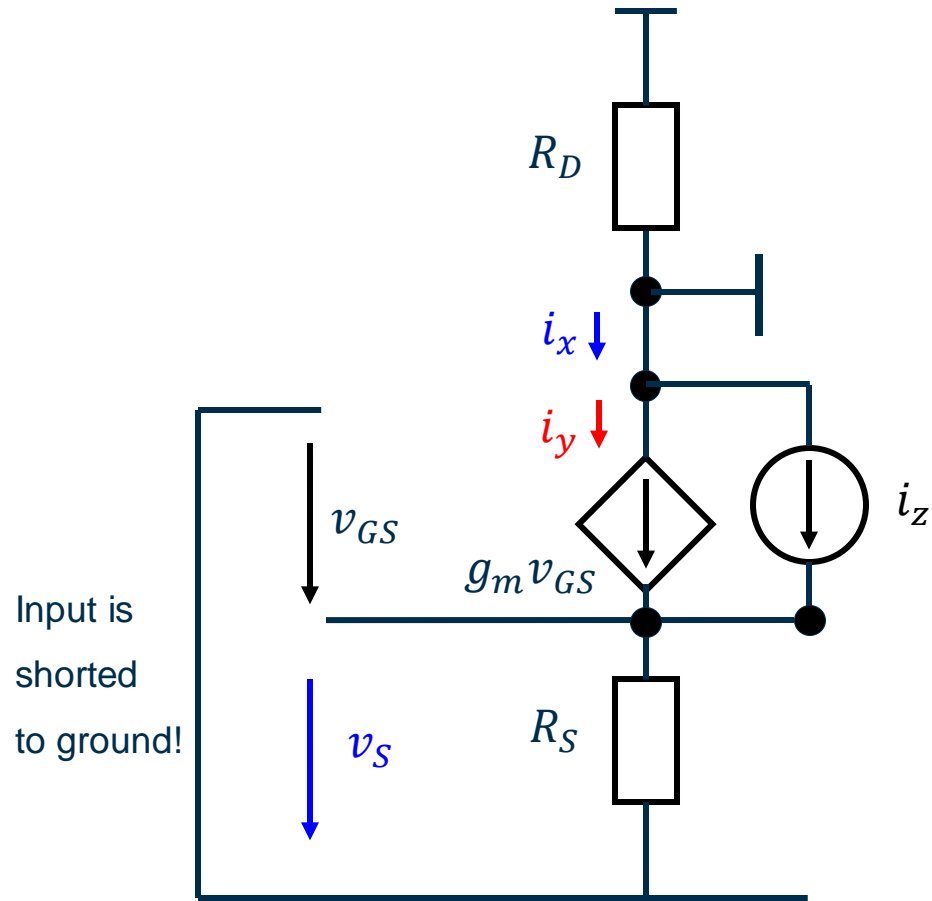

$$T_{short} = T = -\frac{i_y}{i_x} = g_m R_S$$

$$T_{open} = 0 \text{ (no } R_D \text{)}$$

# Common-Source Amplifier with Source Degeneration


$$Z = Z_0 \frac{1 + T_{short}}{1 + T_{open}}$$

$$Z = r_o \frac{1 + g_m R_S}{1 + 0} = r_o + g_m r_o R_S$$

! cascode expression that we been seeing very often



# Common-Source with Shunt Feedback

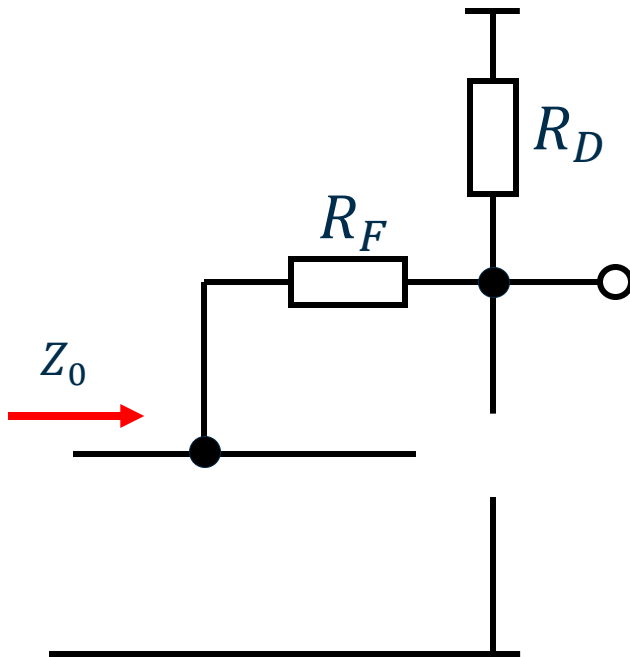


$$Z_0 = R_F + R_D$$

# Common-Source with Shunt Feedback

- $T_{short}$

$$T_{short} = 0$$

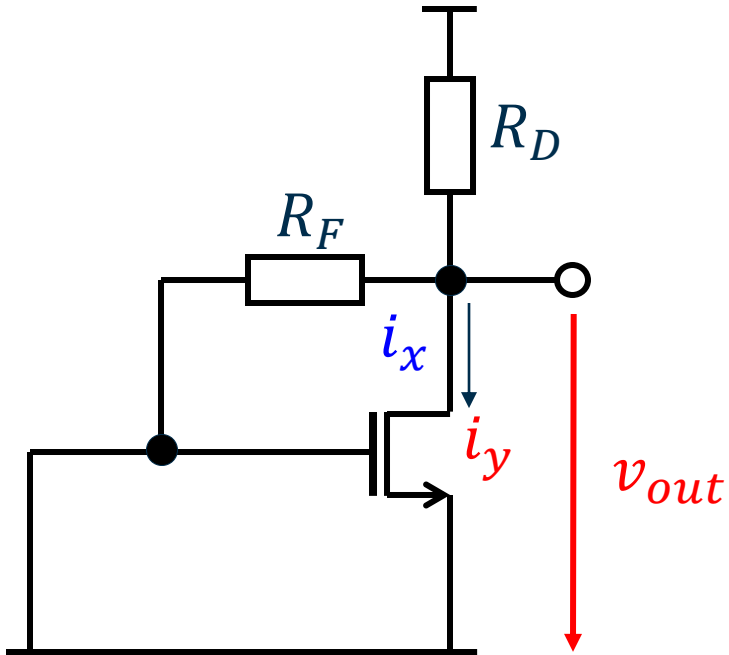


# Common-Source with Shunt Feedback

- $T_{short}$

$$T_{short} = 0$$

$$T_{open} = T = g_m R_D$$

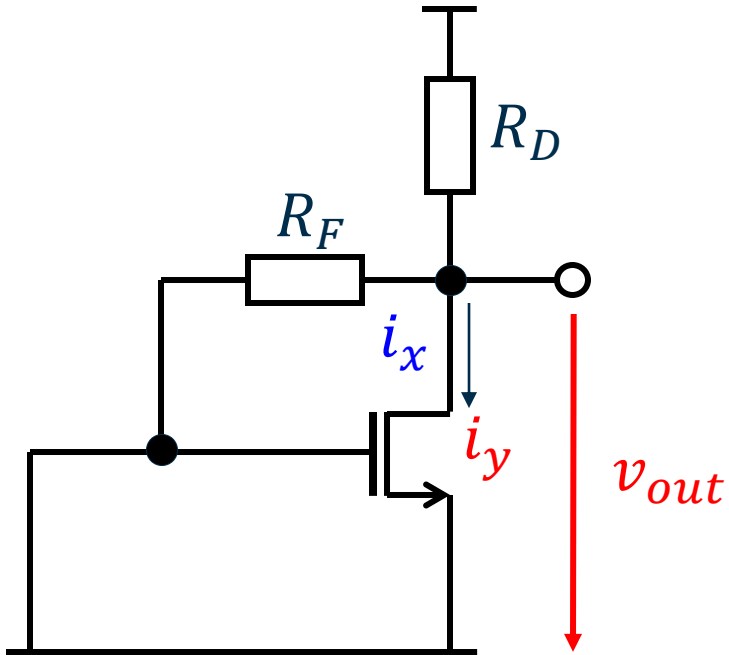

# Common-Source Amplifier with Shunt Feedback

$$Z = Z_0 \frac{1 + T_{short}}{1 + T_{open}}$$

$$Z = (R_F + R_D) \frac{1 + 0}{1 + g_m R_D} = \frac{R_F}{1 + g_m R_D} + \frac{R_D}{1 + g_m R_D}$$

# Common-Source Amplifier with Shunt Feedback

$$Z = Z_0 \frac{1 + T_{short}}{1 + T_{open}}$$


$$Z = (R_F + R_D) \frac{1 + 0}{1 + g_m R_D} = \frac{R_F}{1 + g_m R_D} + \frac{R_D}{1 + g_m R_D} \overset{\sim \frac{1}{g_m}}{\quad}$$



Dominant expression
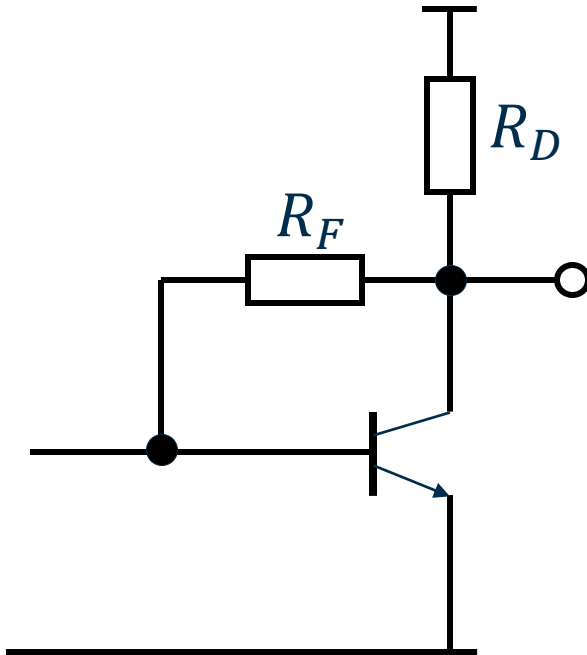
# Simulations


$$R_D = 5k\Omega, I_C = 0.5 \text{ mA}, g_m = 0.015 \text{ S}$$



- No feedback:  $\frac{v_{out}}{v_{in}} = 76$   $r_{in} = 2470 \Omega$
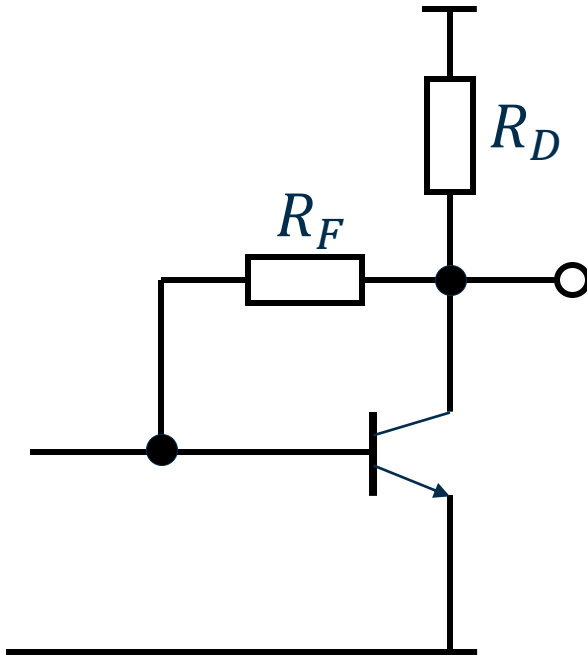
# Simulations


$$R_D = 5k\Omega, I_C = 0.5 \text{ mA}, g_m = 0.015 \text{ S}$$



- No feedback:  $\frac{v_{out}}{v_{in}} = 76$   $r_{in} = 2470 \Omega$
- $R_F = 50k \Omega$ :  $\frac{v_{out}}{i_{in}} = 39200$  (calculated 48700)  
 $R_{in} = 563 \Omega$  (calculated 550  $\Omega$ )
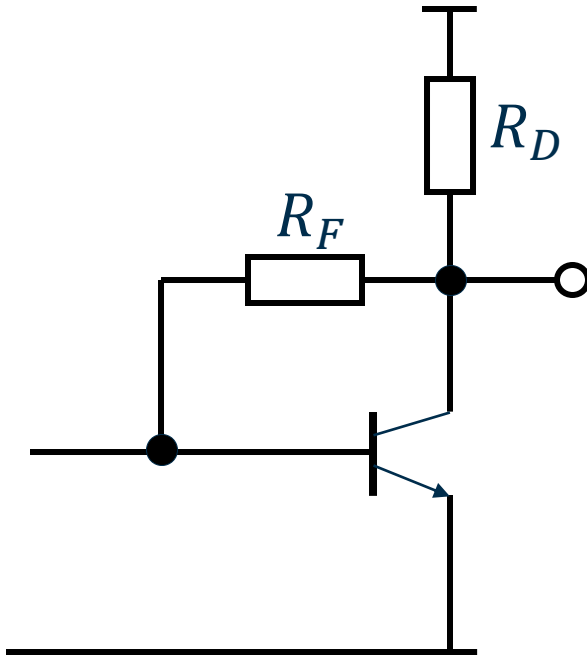
# Simulations

$$R_D = 5k\Omega, I_C = 0.5 \text{ mA}, g_m = 0.015 \text{ S}$$



- No feedback:  $\frac{v_{out}}{v_{in}} = 76$   $r_{in} = 2470 \Omega$
- $R_F = 50k \Omega$ :  $\frac{v_{out}}{i_{in}} = 39200$  (calculated 48700)  
 $R_{in} = 563 \Omega$  (calculated 550  $\Omega$ )
- $R_F = 5k \Omega$ :  $\frac{v_{out}}{i_{in}} = 4658$  (calculated 4935)  
 $R_{in} = 123 \Omega$  (calculated 123  $\Omega$ )




# Loop Gain

- We can see that the loop gain  $AF$  has significant importance in the feedback circuit – there is also a practical way to calculate this important parameter!
- To calculate the loop gain, we can break the feedback loop at any point, and calculate corresponding voltage and current gains; the loop gain will be:

$$\frac{1}{AF} = \frac{1}{A_{vop}} + \frac{1}{H_{os}}$$

# Common-Source with Shunt Feedback


- Loop gain calculation

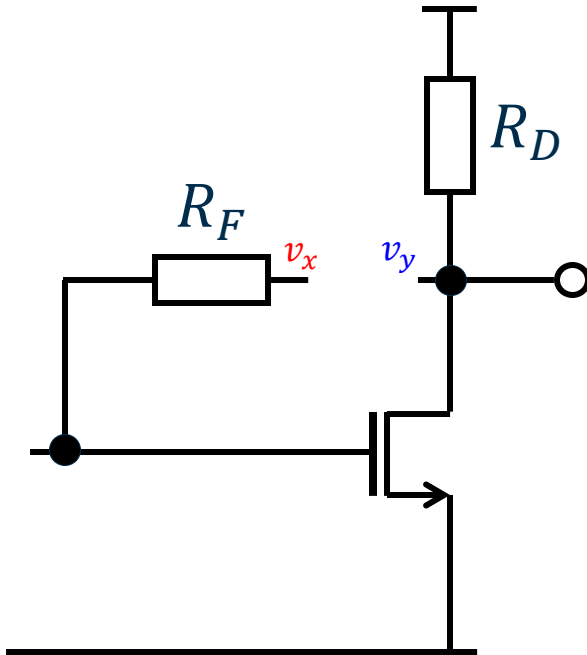

$$A_{vop} = - \left. \frac{v_y}{v_x} \right|_{i_y=0} = g_m R_D$$

# Common-Source with Shunt Feedback

- Loop gain calculation

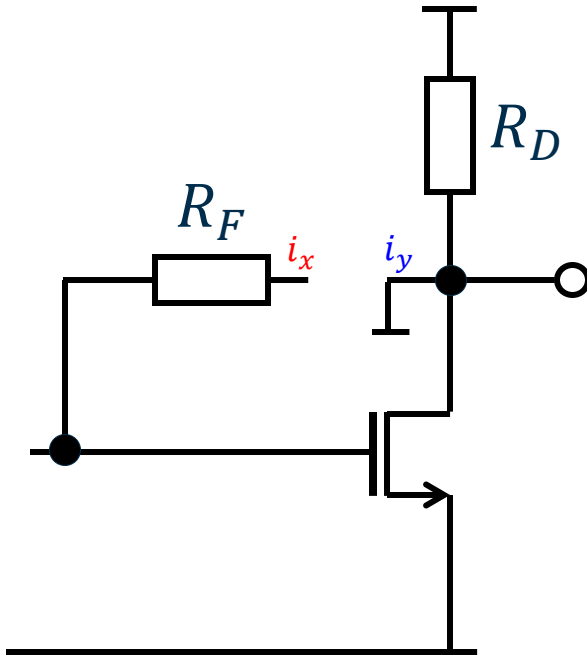


$$H_{os} = -\frac{i_y}{i_x} \Big|_{v_y=0} = \infty$$

$$AF = g_m R_D$$

# Common-Source Amplifier with Source Degeneration

- Loop gain calculation

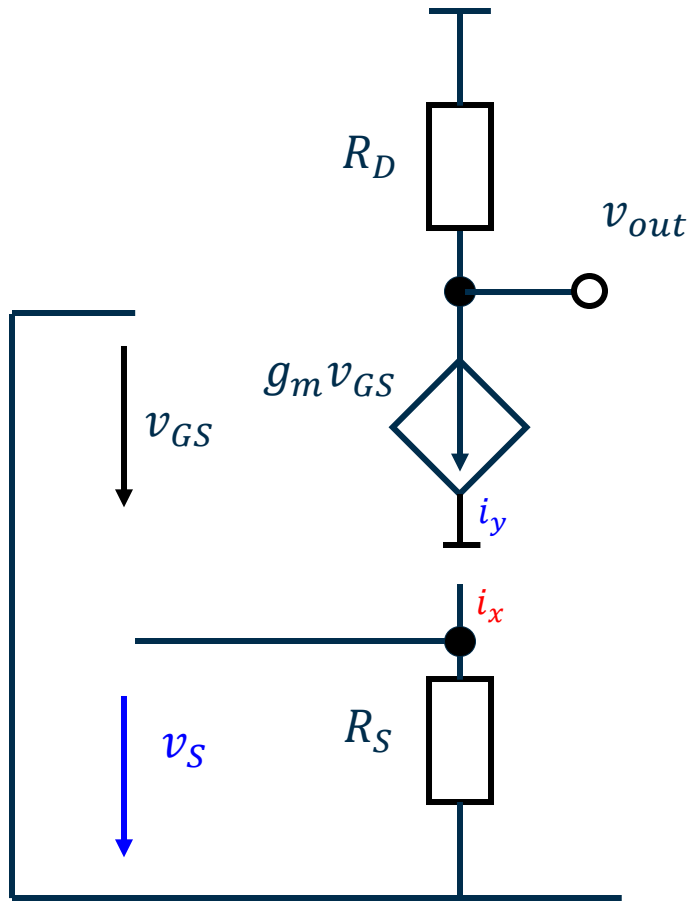


$$A_{vop} = -\frac{v_y}{v_x} \Big|_{i_y=0} = \infty$$


$$H_{os} = -\frac{i_y}{i_x} \Big|_{v_y=0} = g_m R_S$$

$$AF = g_m R_S$$
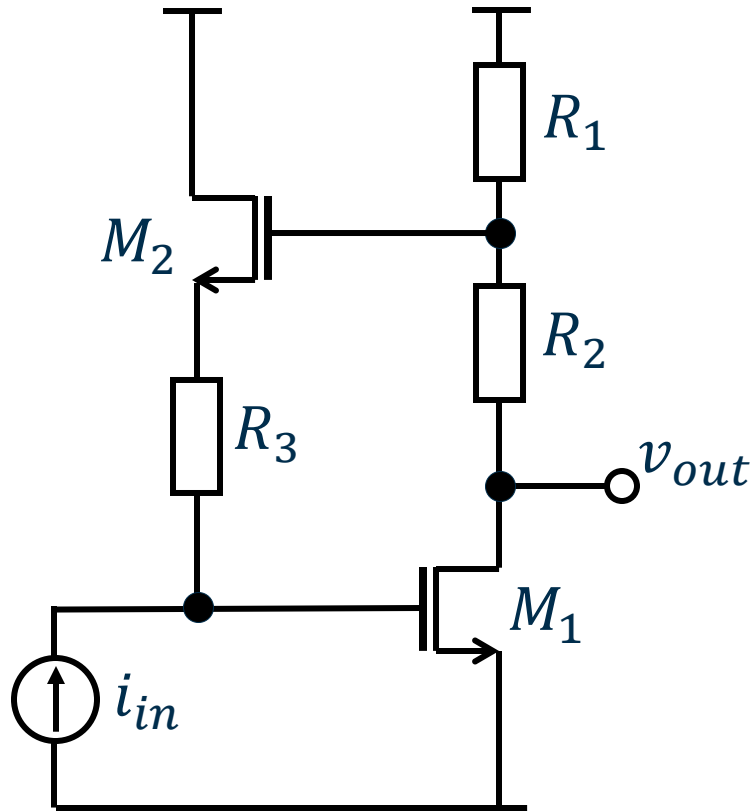
# Advanced Example: Cherry-Hooper Amplifier



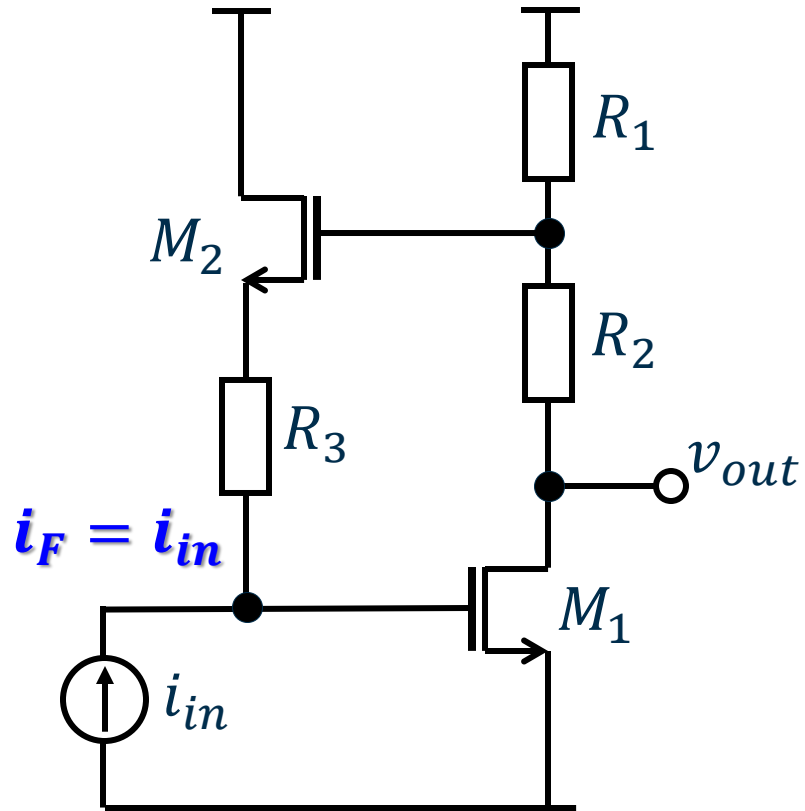
# Advanced Example: Cherry-Hooper Amplifier



$$H_{\infty} = \left. \frac{v_{out}}{i_{in}} \right|_{g_{m1}=\infty} = \left( R_3 + \frac{1}{g_{m2}} \right) \left( 1 + \frac{R_2}{R_1} \right)$$

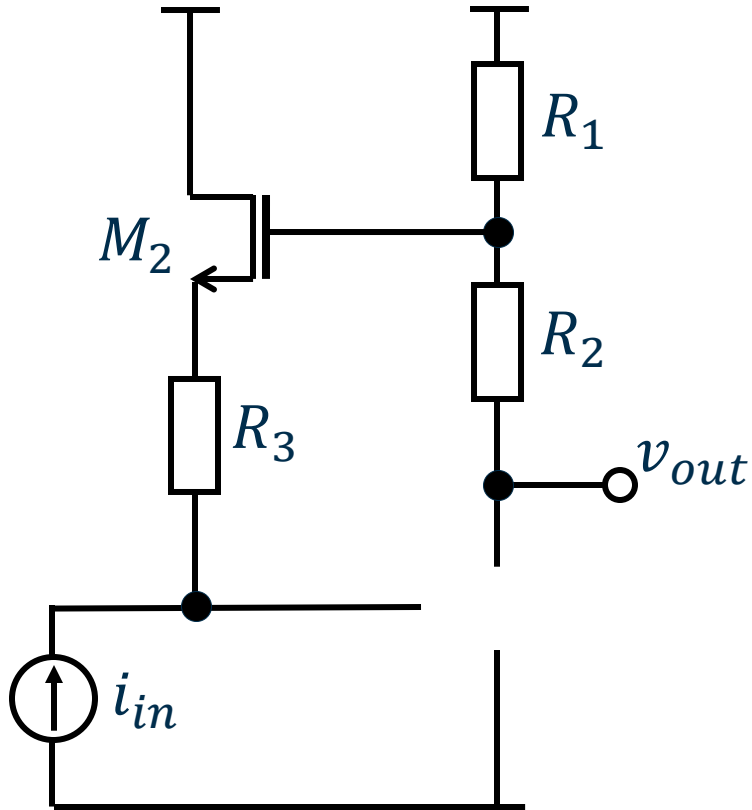
# Advanced Example: Cherry-Hooper Amplifier



$$H_{\infty} = \left. \frac{v_{out}}{i_{in}} \right|_{g_{m1}=\infty} = - \left( R_3 + \frac{1}{g_{m2}} \right) \left( 1 + \frac{R_2}{R_1} \right)$$

$$H_0 = \left. \frac{v_{out}}{i_{in}} \right|_{g_{m1}=0} = 0$$
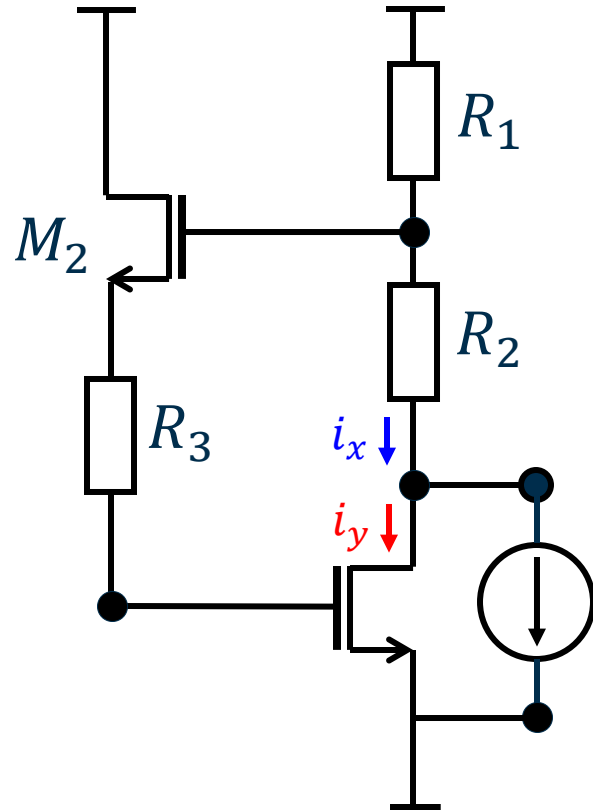
# Advanced Example: Cherry-Hooper Amplifier




$$i_x R_1 = v_{G2} = v_{G1} \quad (\text{M2 is common drain})$$

$$T = -\frac{i_y}{i_x} = g_{m1} R_1$$


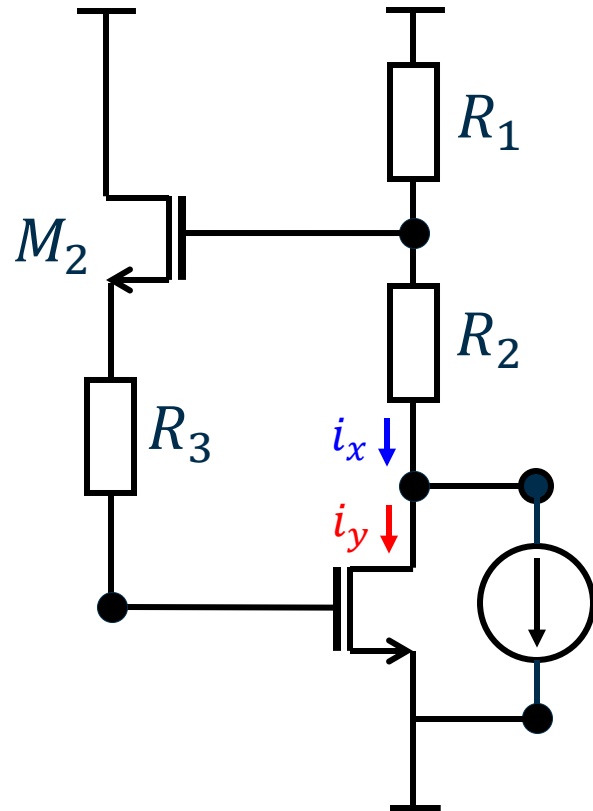
# Advanced Example: Cherry-Hooper Amplifier



$$i_x R_1 = v_{G2} = v_{G1} \quad (\text{M2 is common drain})$$

$$T = -\frac{i_y}{i_x} = g_{m1} R_1$$


$$H = H_\infty \frac{T}{1 + T} + H_0 \frac{1}{1 + T}$$

$$H = -\left(R_3 + \frac{1}{g_{m2}}\right)\left(1 + \frac{R_2}{R_1}\right)\frac{g_{m1} R_1}{1 + g_{m1} R_1}$$

$$H \approx -R_3 \left(1 + \frac{R_2}{R_1}\right)$$

# Advanced Example: Cherry-Hooper Amplifier

- With input and output capacitors

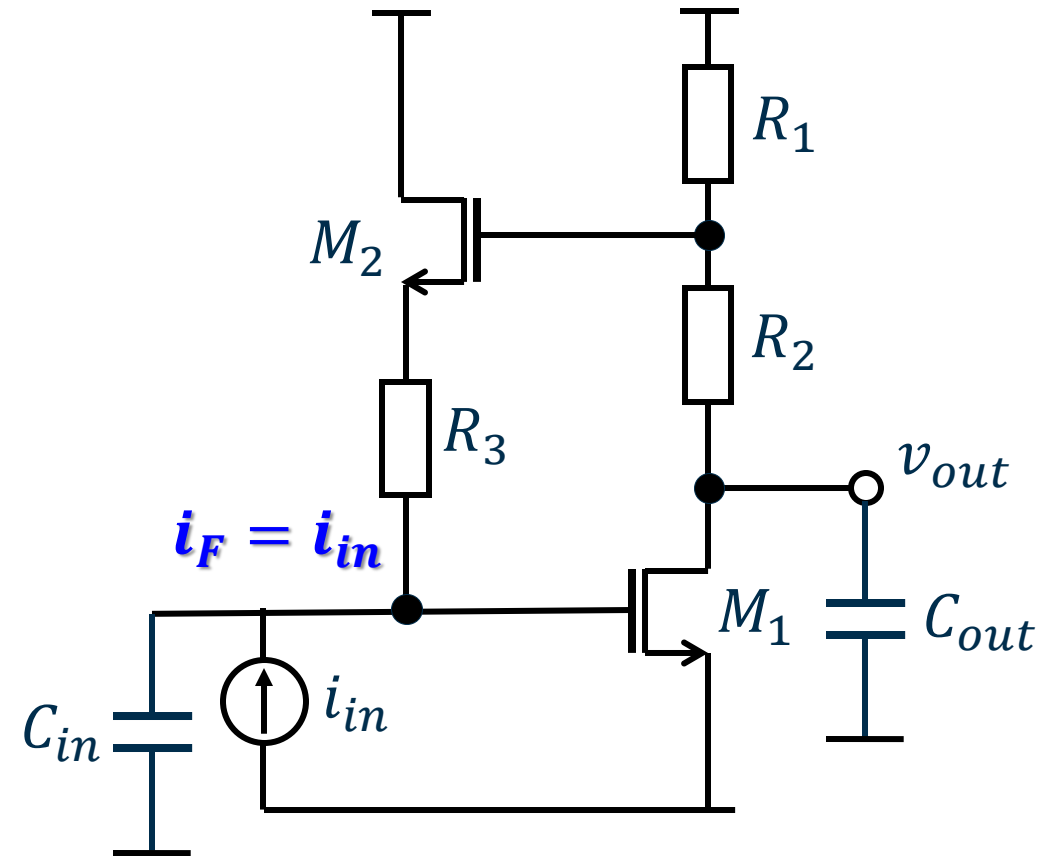


$$H_{\infty} = \left. \frac{v_{out}}{i_{in}} \right|_{g_{m1}=\infty} = - \left( R_3 + \frac{1}{g_{m2}} \right) \left( 1 + \frac{R_2}{R_1} \right)$$

$$H_0 = \left. \frac{v_{out}}{i_{in}} \right|_{g_{m1}=0} = 0$$

- ! Asymptotic gain expressions do not change, because  $H_{\infty}$  forces  $v_{in}$  to 0, and  $C_{out}$  has no influence in the  $v_{out}$  expression
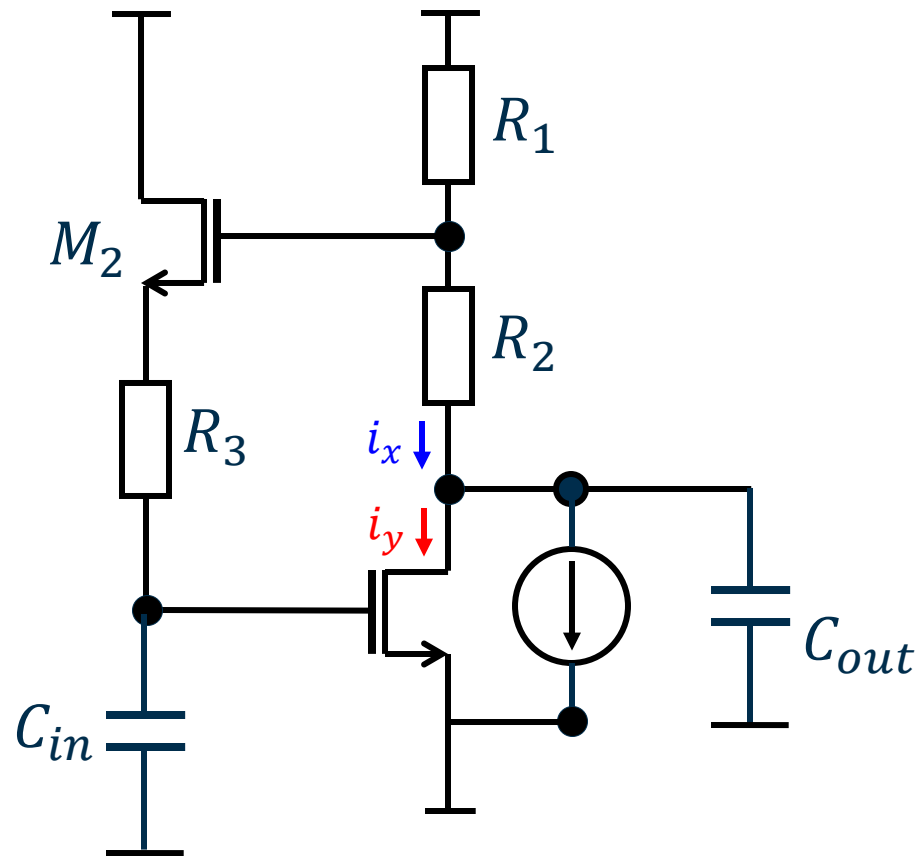
# Advanced Example: Cherry-Hooper Amplifier



$$T = -\frac{i_y}{i_x}$$

- The capacitors will impact return ratio with two independent time constants:

$$T = -\frac{i_y}{i_x} = T_0 \frac{1}{(1 + \tau_1 j\omega)(1 + \tau_2 j\omega)}$$

$$\tau_1 = \left( R_3 + \frac{1}{g_{m2}} \right) C_1$$

$$\tau_2 = (R_1 + R_2) C_2$$


# Advanced Example: Cherry-Hooper Amplifier

$$\frac{T}{1+T} = \frac{T_0}{1+T_0} \frac{1}{1 + \frac{\tau_1 + \tau_2}{1+T_0}s + \frac{\tau_1\tau_2}{1+T_0}s^2}$$

- We have a second-order response, where we can control the damping factor as desired!
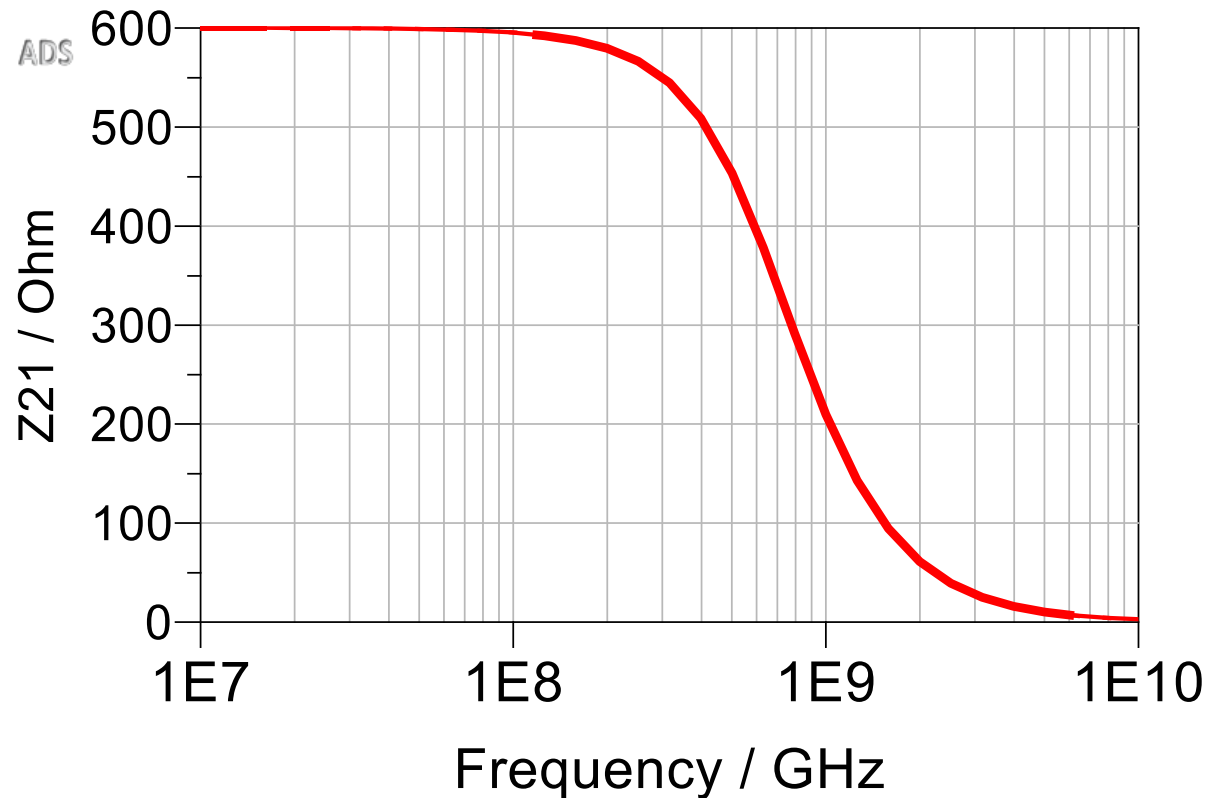
# Advanced Example: Cherry-Hooper Amplifier

- Simulations with
  - $C_{1,2} = 1 \text{ pF}$ ,  $R_{3,1} = 100 \text{ } \Omega$ ,  $R_2 = 500 \text{ } \Omega$ ,  $g_{m1,2} = 10 \text{ mS}$




$$\tau_1 = 0.2 \text{ nsec}$$

$$\tau_2 = 0.6 \text{ nsec}$$

- !3-dB bandwidth should be 200 MHz
- Simulated bandwidth is 700 MHz !!

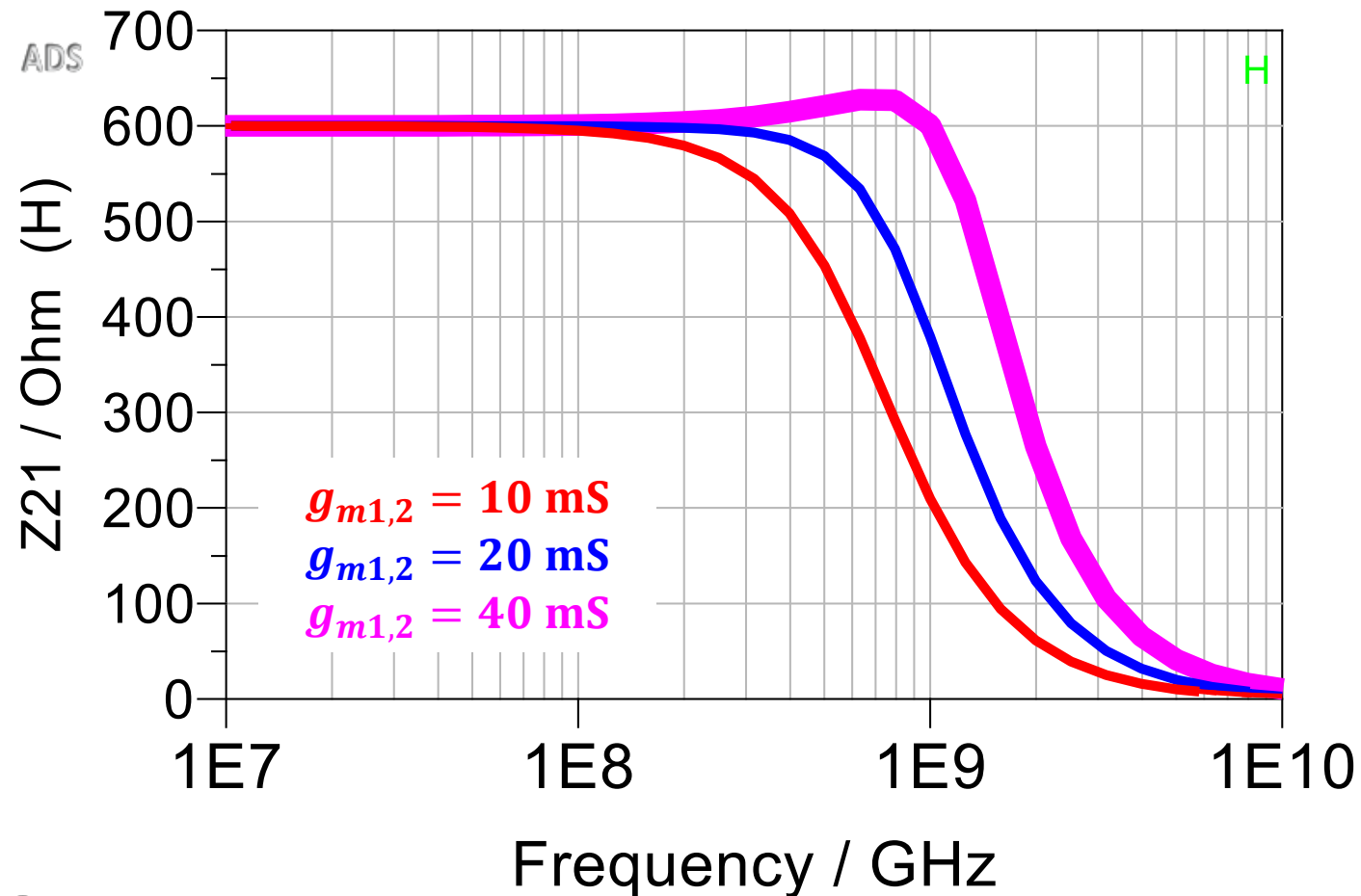
# Advanced Example: Cherry-Hooper Amplifier

- Simulations with
  - $C_{1,2} = 1 \text{ pF}$ ,  $R_{3,1} = 100 \text{ } \Omega$ ,  $R_2 = 500 \text{ } \Omega$ ,  $g_{m1,2} = 10 \text{ mS}$



# Advanced Example: Cherry-Hooper Amplifier

- Loop gain

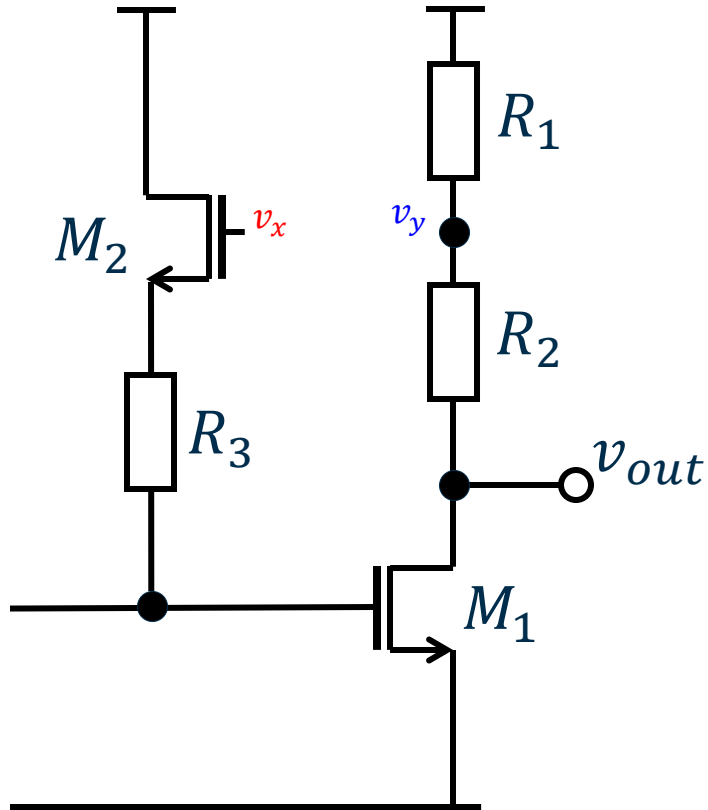


$$v_{out} = g_{m1} v_x$$

$$v_y = \frac{v_{out}}{R_1 + R_2} R_1$$

$$A_{vop} = - \left. \frac{v_y}{v_x} \right|_{i_y=0} = \frac{g_{m1} R_1}{R_1 + R_2}$$

# Advanced Example: Cherry-Hooper Amplifier

- Loop gain

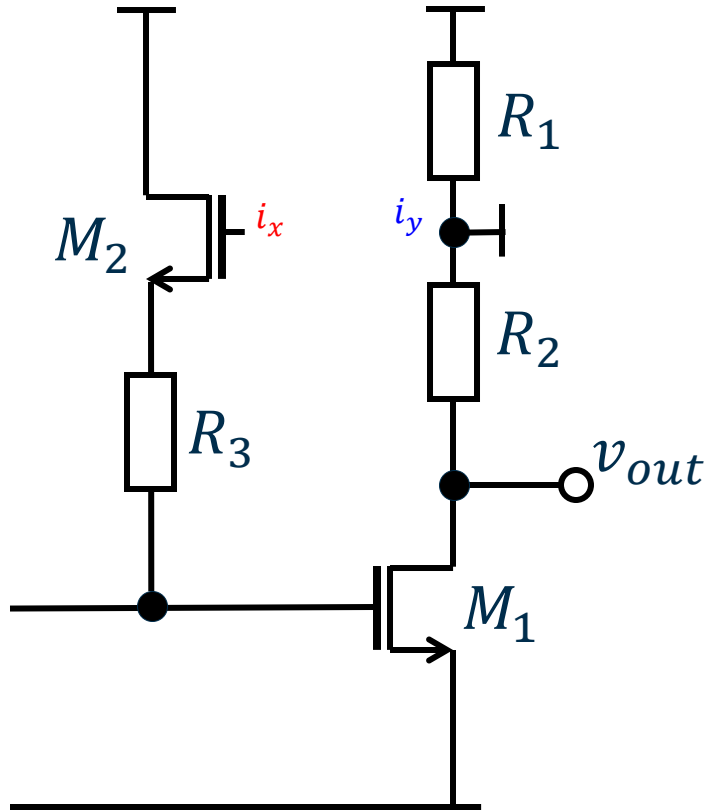


$$H_{os} = -\frac{i_y}{i_x} \Big|_{v_y=0} = \infty$$

$$AF = \frac{g_{m1} R_1}{R_1 + R_2}$$



# Advanced Example: Cherry-Hooper Amplifier


## ■ Input Impedance

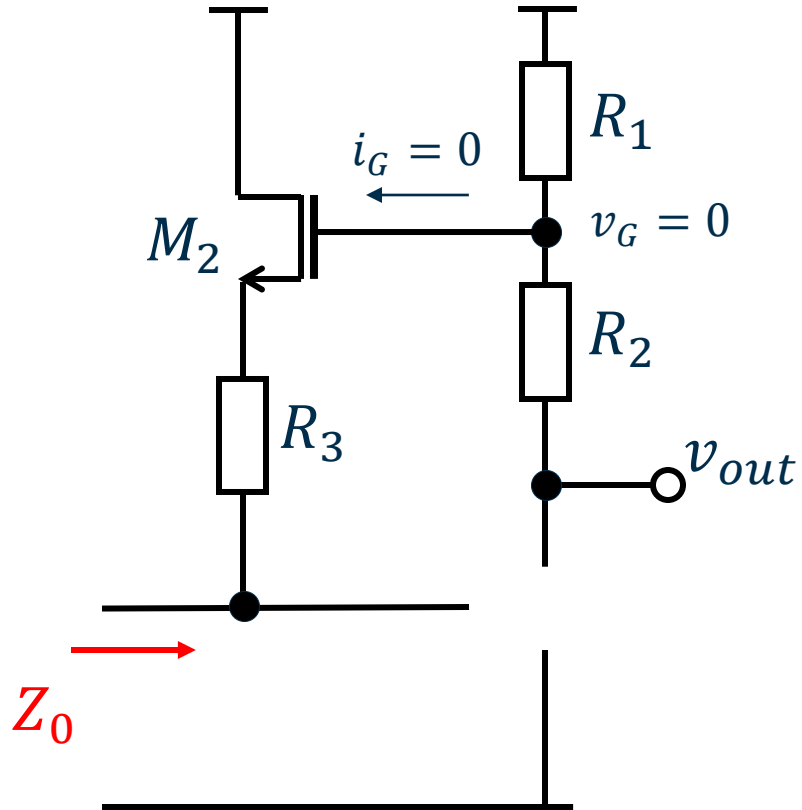

$$Z_0 = R_3 + \frac{1}{g_{m2}}$$

# Advanced Example: Cherry-Hooper Amplifier

■  $T_{short}$

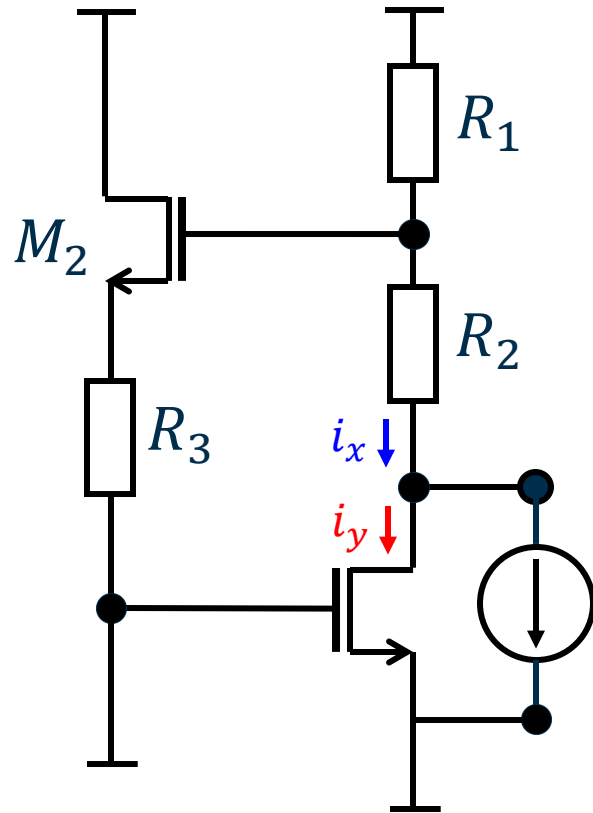

$$T_{short} = -\frac{i_y}{i_x} = 0$$

$$T_{open} = T = -\frac{i_y}{i_x} = g_{m1}R_1$$


$$Z = Z_0 \frac{1 + T_{short}}{1 + T_{open}}$$

$$Z = \left( R_3 + \frac{1}{g_{m2}} \right) \frac{1}{1 + g_{m1}R_1}$$

$$Z_{in} \approx \frac{1}{g_m} \left( \frac{R_3}{R_1} \right)$$

# Advanced Example: Cherry-Hooper Amplifier


- Output Impedance

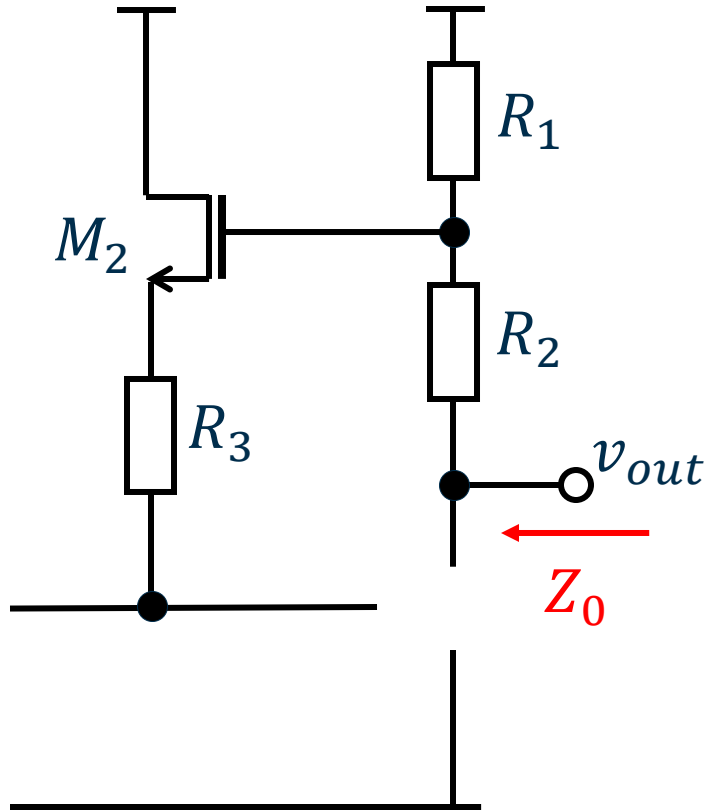

$$Z_0 = R_2 + R_1$$

# Advanced Example: Cherry-Hooper Amplifier

■  $T_{short}$

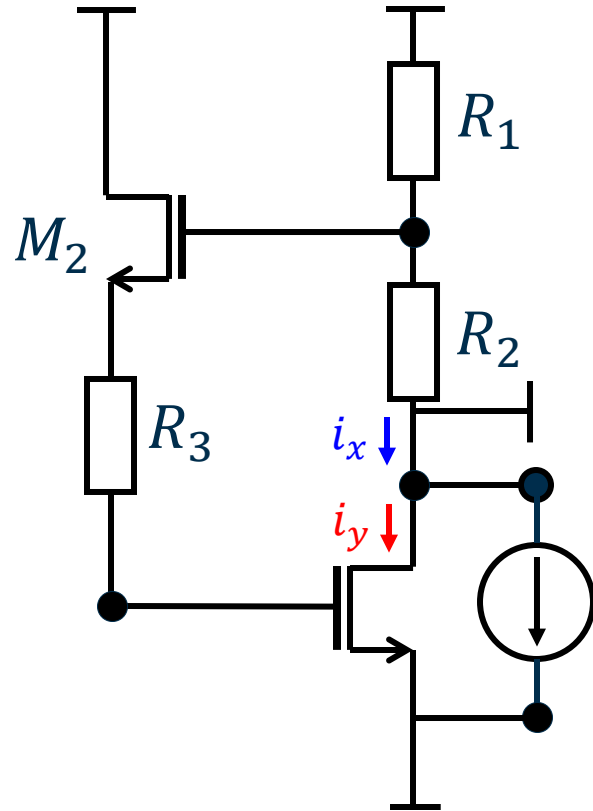

$$T_{short} = 0$$

$$T_{open} = T = -\frac{i_y}{i_x} = g_{m1}R_1$$

$$Z = Z_0 \frac{1 + T_{short}}{1 + T_{open}}$$

$$Z_{out} = \frac{R_1 + R_2}{1 + g_{m1}R_1}$$