

Mikroelektronische Schaltungen und Systeme

Übung 1


Ahmed Aksu

Institut für Hochfrequenztechnik und Elektronik (IHE)



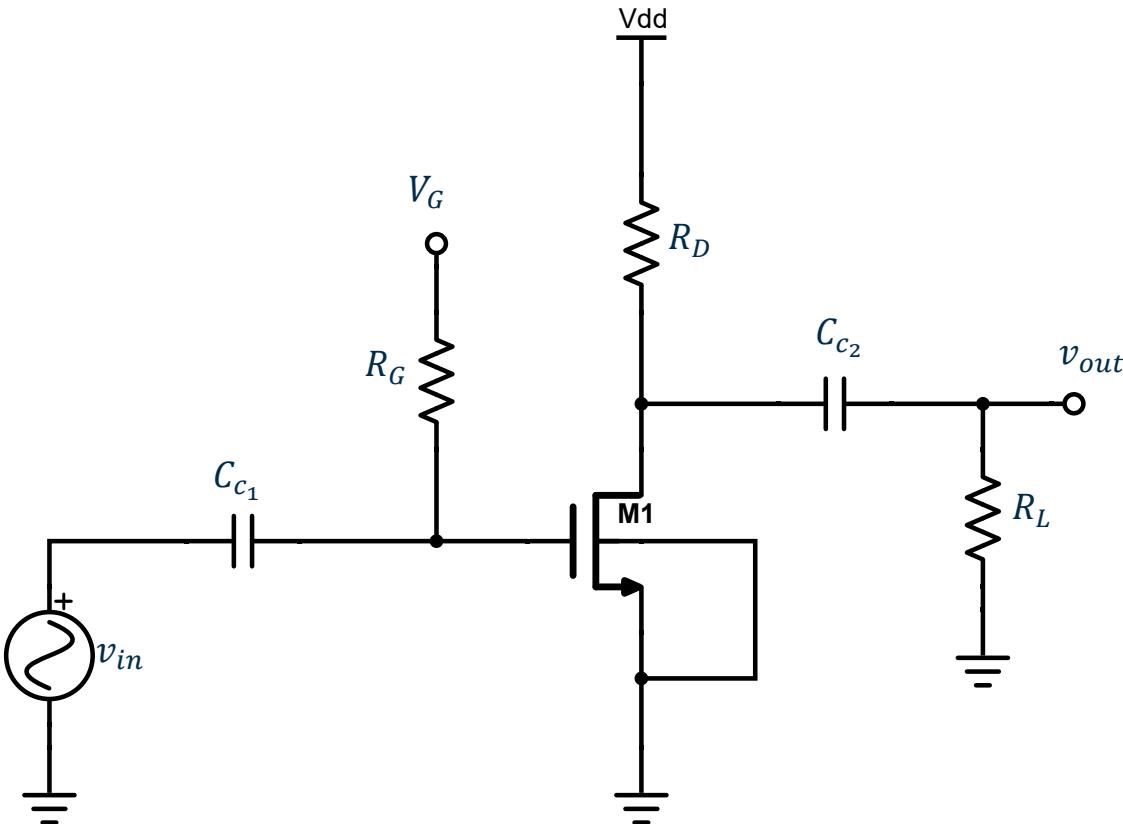Task 1.1

In the circuit below following MOSFET and circuit parameters are provided:



- $V_{TH} = 0.7V$ ▪ $R_L = 6k\Omega$
- $V_{ov} = V_{GS} - V_{TH} = 0.5 V$ ▪ $R_G \rightarrow \infty, C_{c_{1,2}} \rightarrow \infty$
- $\mu_n C_{ox} = 200 \frac{\mu A}{V^2} = k_n = \beta$ ▪ $L = 200nm$
- $I_D = 1mA$ ▪ $A_v = \frac{v_{out}}{v_{in}} = -4$

Channel-length modulation can be ignored.

- a) Calculate g_m , transistor width W , and R_D .
- b) Find the minimum supply voltage $V_{DD_{min}}$ to keep the transistor in saturation and determine the DC power consumption P_{DC} .

a)

Slide 1 P.53

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})$$

$$g_m = \sqrt{2I_D \mu_n C_{ox} \frac{W}{L}}$$

$$g_m = \frac{2I_D}{V_{GS} - V_{TH}}$$

$$I_D = \frac{1}{2} \underbrace{\mu_n C_{ox}}_{\text{given}} \frac{W}{L} \left(V_{GS} - V_{TH} \right)^2$$

$$g_m = \frac{2I_D}{V_{GS}} = \frac{2 \text{ mA}}{0.5 \text{ V}} = 4 \text{ mS}$$

$$1 \text{ mA} = \frac{1}{2} 200 \frac{\mu\text{A}}{\text{V}^2} \frac{W}{200n} (0.5)^2$$

Leave W alone.

$$W = \frac{(1 \times 10^{-3}) \times (200 \times 10^{-9})}{(200 \times 10^{-6}) \times (0.5)^2} = 8 \text{ MM}$$


$\frac{W}{2} = \frac{8 \text{ MM}}{200n}$

$$A_V = -g_m R_{out} = -4 \text{ V} \quad R_{out} = R_D || R_L$$

$$g_m = 4 \text{ mS} \Rightarrow R_{out} = 1 \text{ k}\Omega$$


$$R_D = \left(\frac{1}{7k} + \frac{1}{6k} \right)^{-1} = \frac{6k}{5} = 1.2 \text{ k}\Omega$$

b)

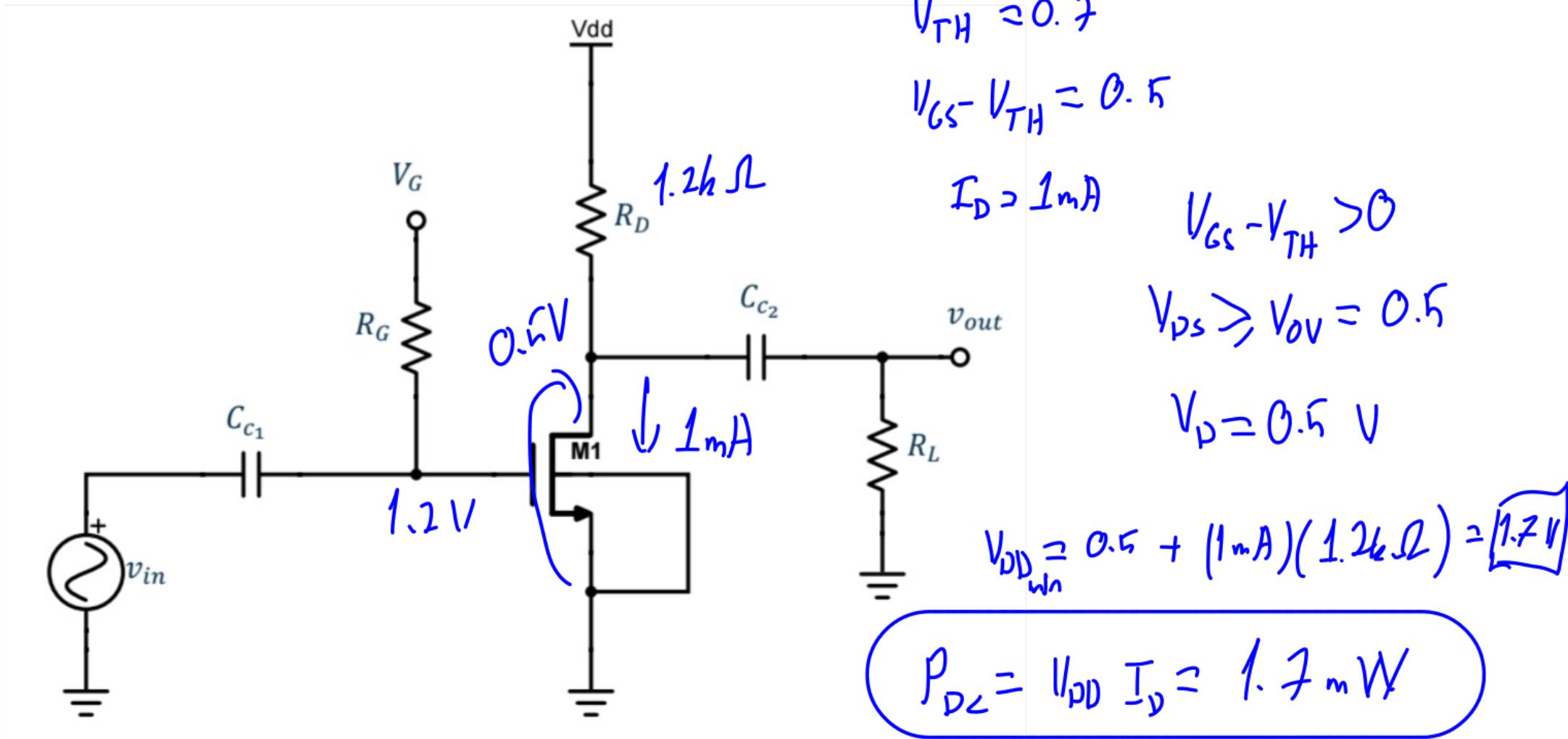

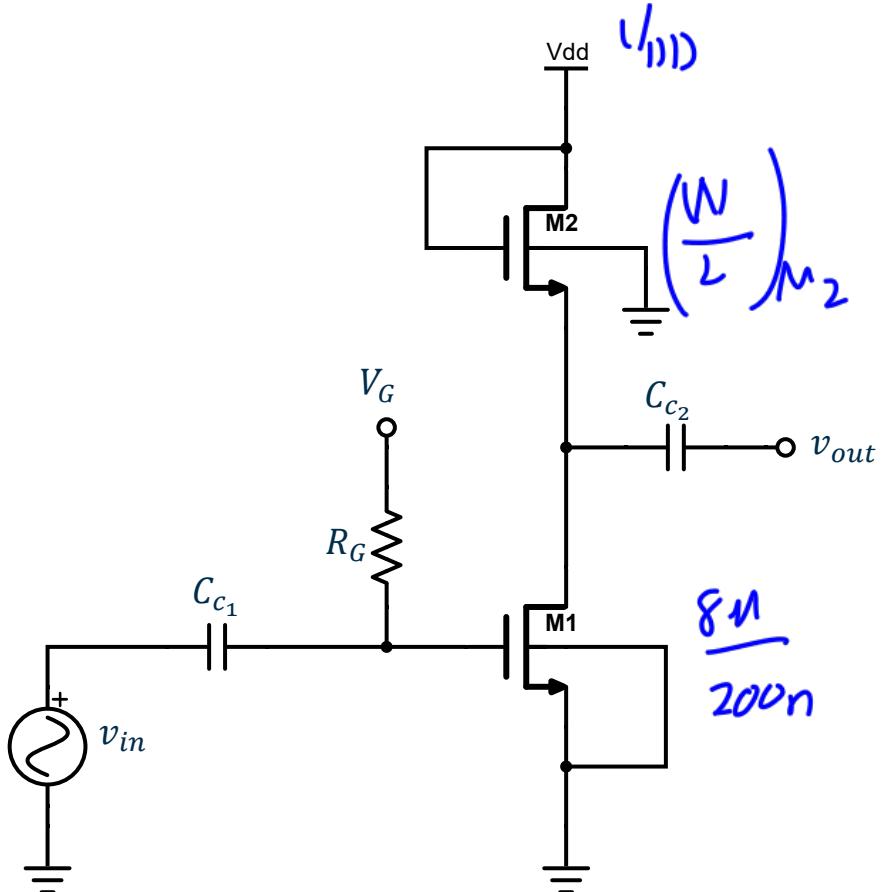Task 1.2

The circuit from Task 1.1 will be changed as following:



- R_L is removed and R_D is replaced with a diode-connected NMOS transistor. All parameters of M1 remains the same.

- a) Determine the required $(W/L)_{M2}$ to achieve the same voltage gain magnitude $|A_v| = 4$, and calculate the new DC power consumption P_{DC} .

$$I_D = 1\text{mA} \quad V_{OV} = 0.5 \quad g_n = 2\text{nS}$$

Lecture Slide 1 P.10

- Assuming both transistors have the same $\mu_n C_{ox}$ and operate at equal drain currents, the voltage gain can be expressed as:

$$A_v = -\frac{g_{m_1}}{g_{m_2}} \frac{1}{(1+\eta)} = -\sqrt{\frac{2I_D \mu_n C_{ox} \left(\frac{W}{L}\right)_1}{2I_D \mu_n C_{ox} \left(\frac{W}{L}\right)_2}} \frac{1}{(1+\eta)} = -\sqrt{\frac{\left(\frac{W}{L}\right)_1}{\left(\frac{W}{L}\right)_2}} \frac{1}{(1+\eta)}$$

$$A_v = -4 = -\sqrt{\frac{\left(\frac{W}{L}\right)_1}{\left(\frac{W}{L}\right)_2}}$$

Bulk transconductance omitted

$$\left(\frac{W}{L}\right)_2 = \frac{\left(\frac{W}{L}\right)_1}{16}$$


$$L = 200 \text{ nm}$$

$W_2 = 500 \text{ nm}$

$$\left(\frac{W}{L}\right)_1 = \frac{500 \text{ nm}}{200 \text{ nm}}$$

$$I_D = \frac{1}{2} \mu_n C_{Ox} \frac{W}{L} (V_{GS} - V_{TH})^2 = 1 \text{ mA}$$

$V_{DD} = 0.5$

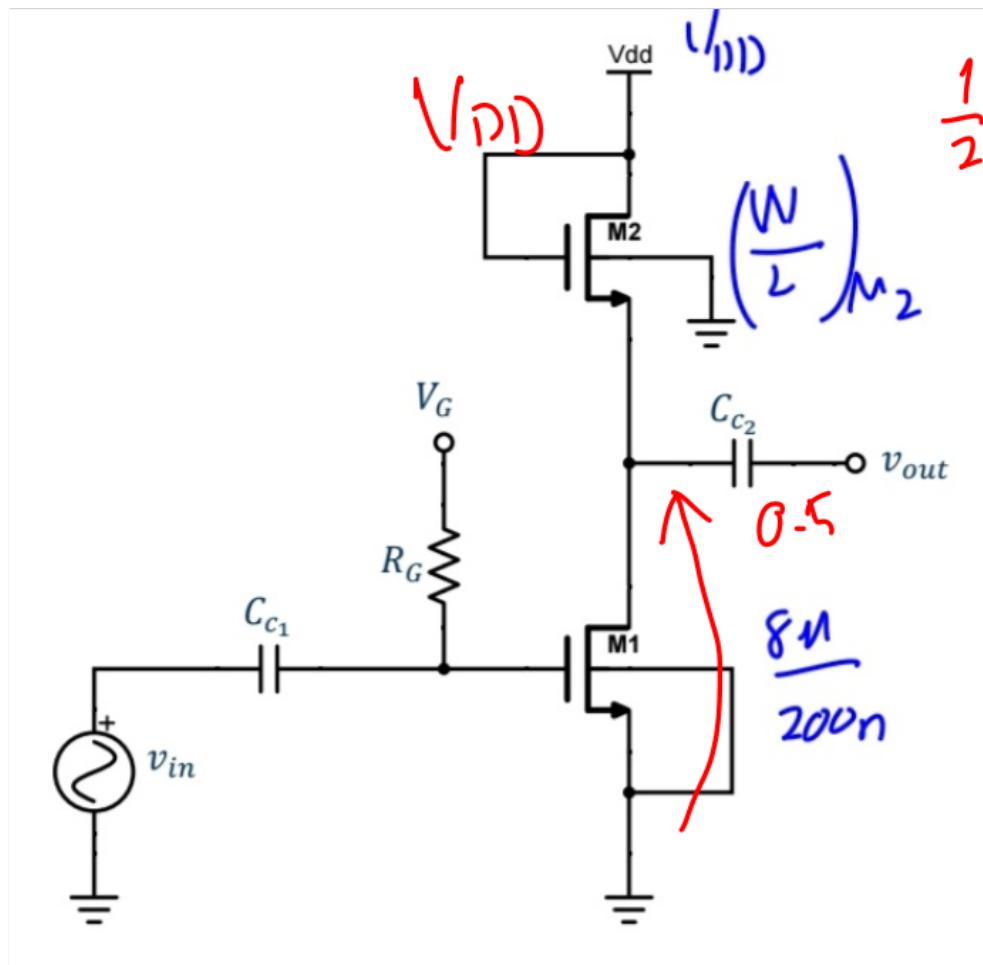

$$\frac{1}{2} \left(\frac{200 \text{nF}}{V_2} \right) (1.5) \left(V_{DD} - 0.5 - 0.7 \right)^2 = 1 \text{ mA}$$

Leave V_{DD} alone


$$V_{DD} = 3.2 \text{ V}$$

$$P_{PC} = 3.2 \text{ mW}$$

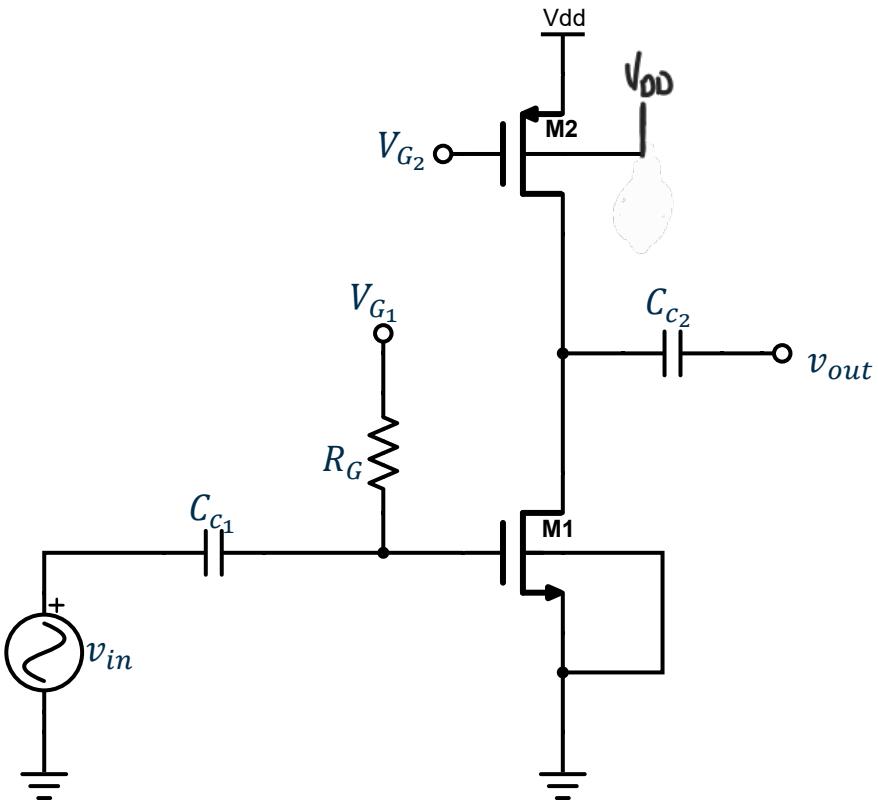Task 1.3


The circuit from Task 1.2 is further modified:

- Replace the diode-connected load with a **current-source PMOS load** with following parameters (M1 remains the same):



- $|V_{TH_P}| = 0.5V$
- $\mu_p C_{ox} = 50 \frac{\mu A}{V^2}$
- $\lambda_n = \lambda_p = 0.1 V^{-1}$
- $|V_{ov}| = 0.5V$

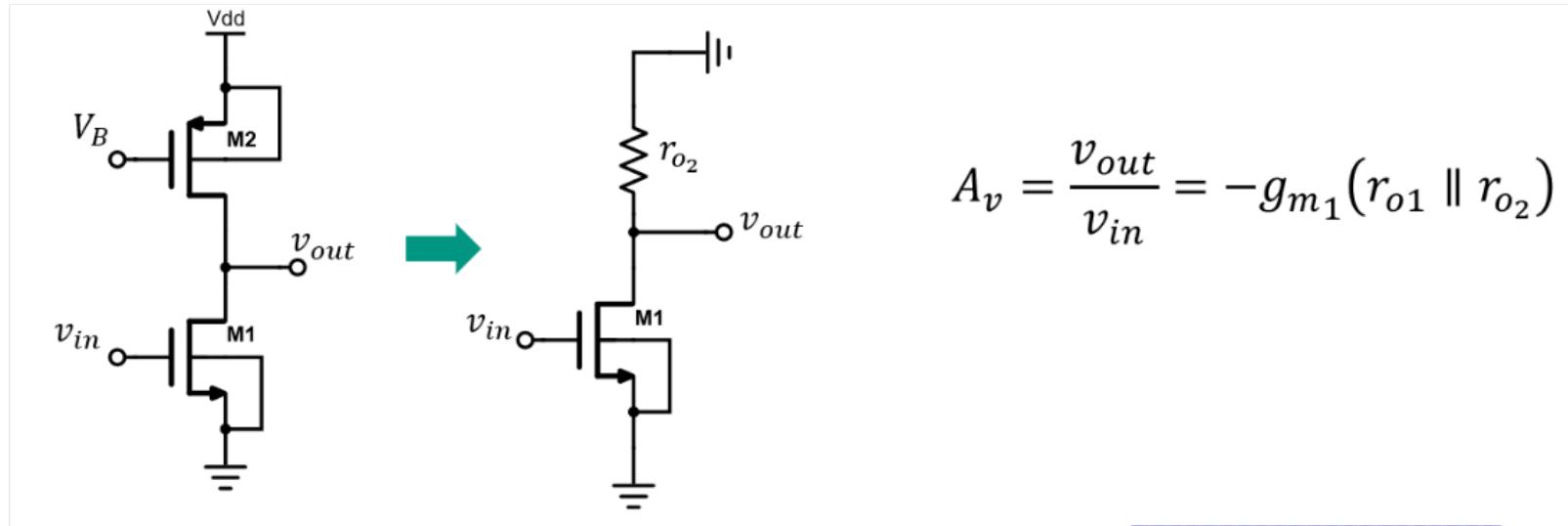- Calculate the small-signal gain A_v .
- Determine the required gate bias voltage V_{G_2} , and calculate the DC power consumption P_{DC} .



$$I_D = \frac{1}{2} \underbrace{\mu_n C_{ox} \left(\frac{W}{L} \right)}_{200\mu \frac{8\mu}{200n}} \left(\frac{V_{GS} - V_{THN}}{V_{OV}} \right)^2 \left(1 + \lambda \frac{V_{DS}}{V_{OV}} \right) = 1.05 \text{ mA}$$

$$I_{D_{M_2}} = I_D = \frac{1}{2} \underbrace{\mu_p C_{ox} \left(\frac{W}{L} \right)}_{50\mu} \left(\frac{V_{SG} - |V_{TH}|}{V_{OV}} \right)^2 \left(1 + \lambda \frac{V_{SD}}{V_{OV}} \right) = 1.05 \text{ mA}$$


$$\frac{(W/L)_2}{(W/L)_1} = \frac{\mu_n C_{ox}}{\mu_p C_{ox}} = 4 \Rightarrow \left(\frac{W}{L}\right)_2 = \frac{32 \mu m}{200 nm}$$

$$g_m = g_{m_1} = g_{m_2} = \frac{2 I_D}{V_{ov}} = \frac{2 \cdot 1 mA}{0.5 V} = 4.2 mS$$

$$r_o = r_{o_1} = r_{o_2} = \frac{1}{\lambda I_D} = \frac{1}{(0.1 V^{-1})(1.05 nA)} \approx 9.52 k\Omega$$

$$A_V = g_{m_1} \left(r_{o_1} // r_{o_2} \right) = \frac{g_m r_o}{2} \approx 20 V/V = 26 dB$$
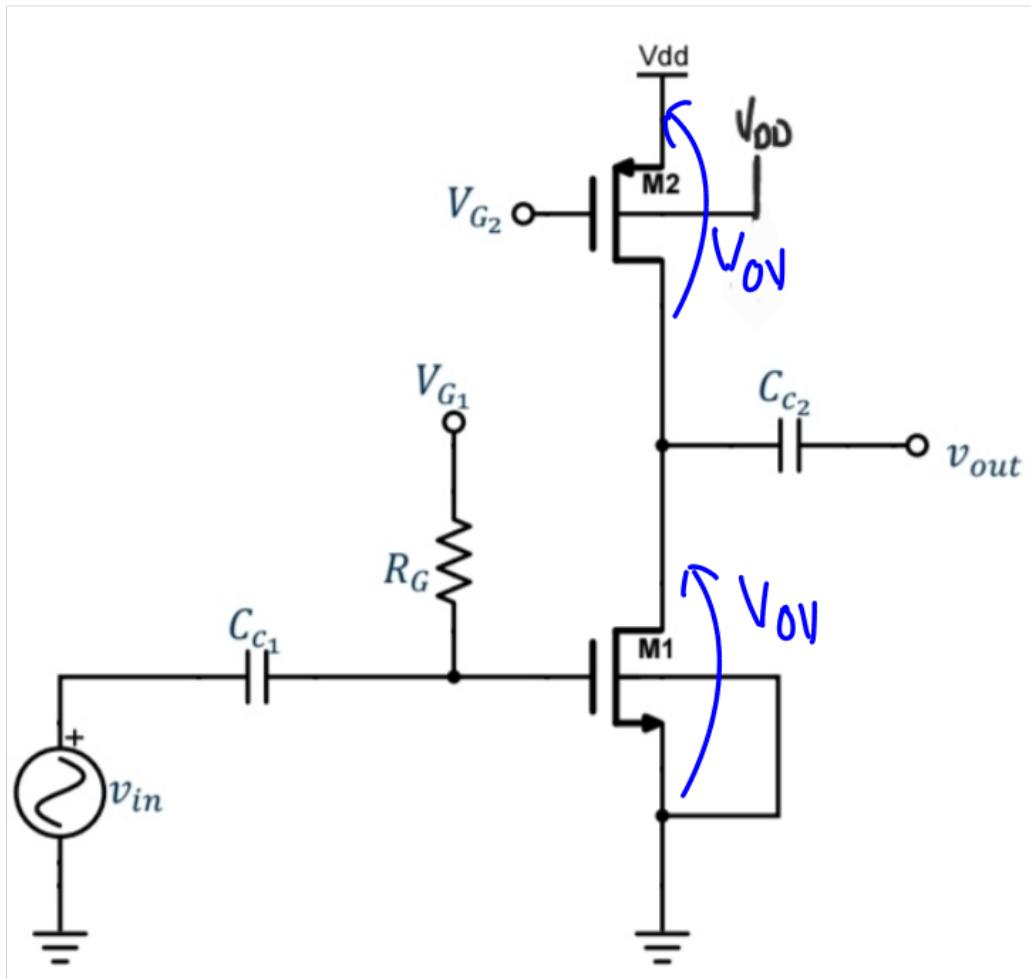
$$V_{TH_N} = 0.7 \text{ V}, \quad V_{TH_P} = -0.5 \text{ V}, \quad V_{ov} = 0.5 \text{ V}$$



$$V_{G_1} - V_{TH_N} = 0.5 \text{ V} \Rightarrow V_{G_1} = 1.2 \text{ V}$$


$$V_{DD} - V_{G_2} - |V_{TH_P}| = 0.5 \text{ V}$$

$$V_{DD} = 2 V_{ov} = 1 \text{ V} \Rightarrow V_{G_2} = 0 \text{ V}$$

$$P_{DC} = \underbrace{(1 \text{ V})}_{V_{DD}} \left(\underbrace{1.05 \text{ mA}}_{I_D} \right) = 1.05 \text{ mW}$$

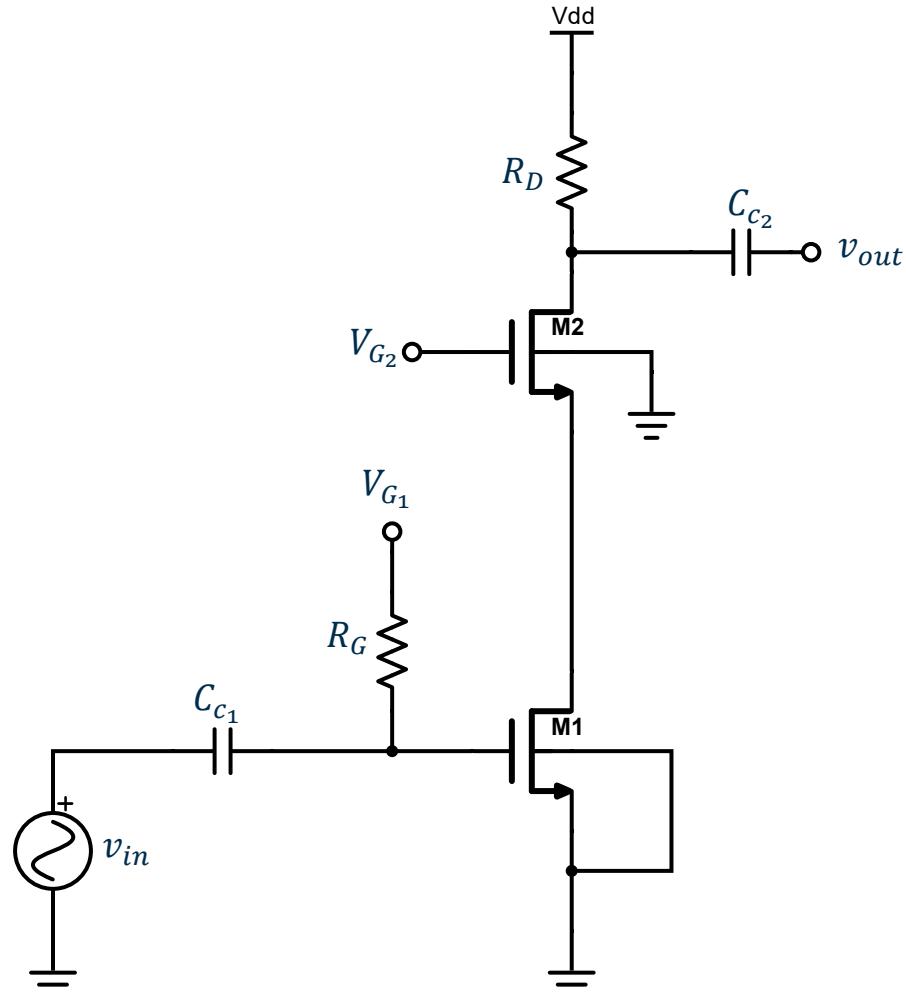Task 2.1

For the cascode amplifier below following circuit parameters are provided:



- $V_{TH} = 0.7V$ ▪ $R_D = 1k\Omega$
- $V_{ov} = V_{GS} - V_{TH} = 1 V$ ▪ $R_G \rightarrow \infty, C_{c_{1,2}} \rightarrow \infty$
- $\mu_n C_{ox} = 200 \frac{\mu A}{V^2}$ ▪ $L = 200nm$
- $I_D = 1mA$ ▪ $\lambda_n = 0.01 V^{-1}$


- a) Calculate g_{m_1}, g_{m_2} . ✓
- b) Determine transistor width W_1, W_2 . ✓
- c) Find the minimum V_{DD} to keep both transistors in saturation. ✓
- d) Calculate the small-signal gain A_v .

a) $g_m = g_{m_1} = g_{m_2} = \frac{2 I_D}{V_{ov}} = 2 \text{ mS}$

b) $g_m = M_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) \Rightarrow W = \frac{2 \text{ mS}}{\frac{M_n C_{ox} (V_{GS} - V_{TH})}{200 \mu\text{A/V}^2}}$

$$W = W_1 = W_2 = 2 \mu\text{m}$$

C)

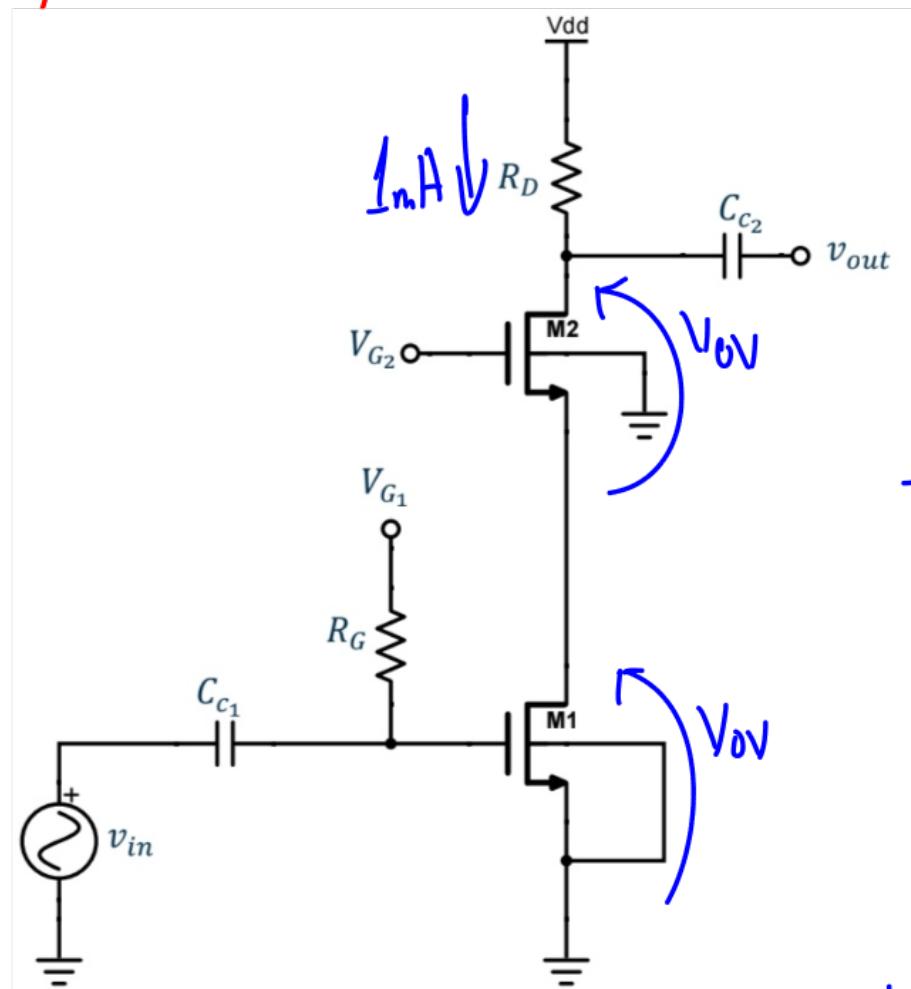

Please note that both I_D and λ were given in the question.
Since λ is too low, it is excluded in I_D calculation but will be used in R_0 calculation.

$$\frac{1}{2} M_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 = 1 \text{ mA}$$

$V_{OV} = 1 \text{ V}$


$$V_{G_1} - 0.7 \text{ V} = 1 \text{ V} \Rightarrow V_{G_1} = 1.7 \text{ V}$$

$$V_{G_2} - 1 \text{ V} - 0.7 \text{ V} = 1 \text{ V} \Rightarrow V_{G_2} = 2.7 \text{ V}$$

$$V_{DD} = 2 V_{OV} + I_D R_D = 3 \text{ V}$$

$\downarrow 1 \text{ V}$ $\downarrow 1 \text{ mA}$ $\downarrow 1 \text{ k}\Omega$

c)

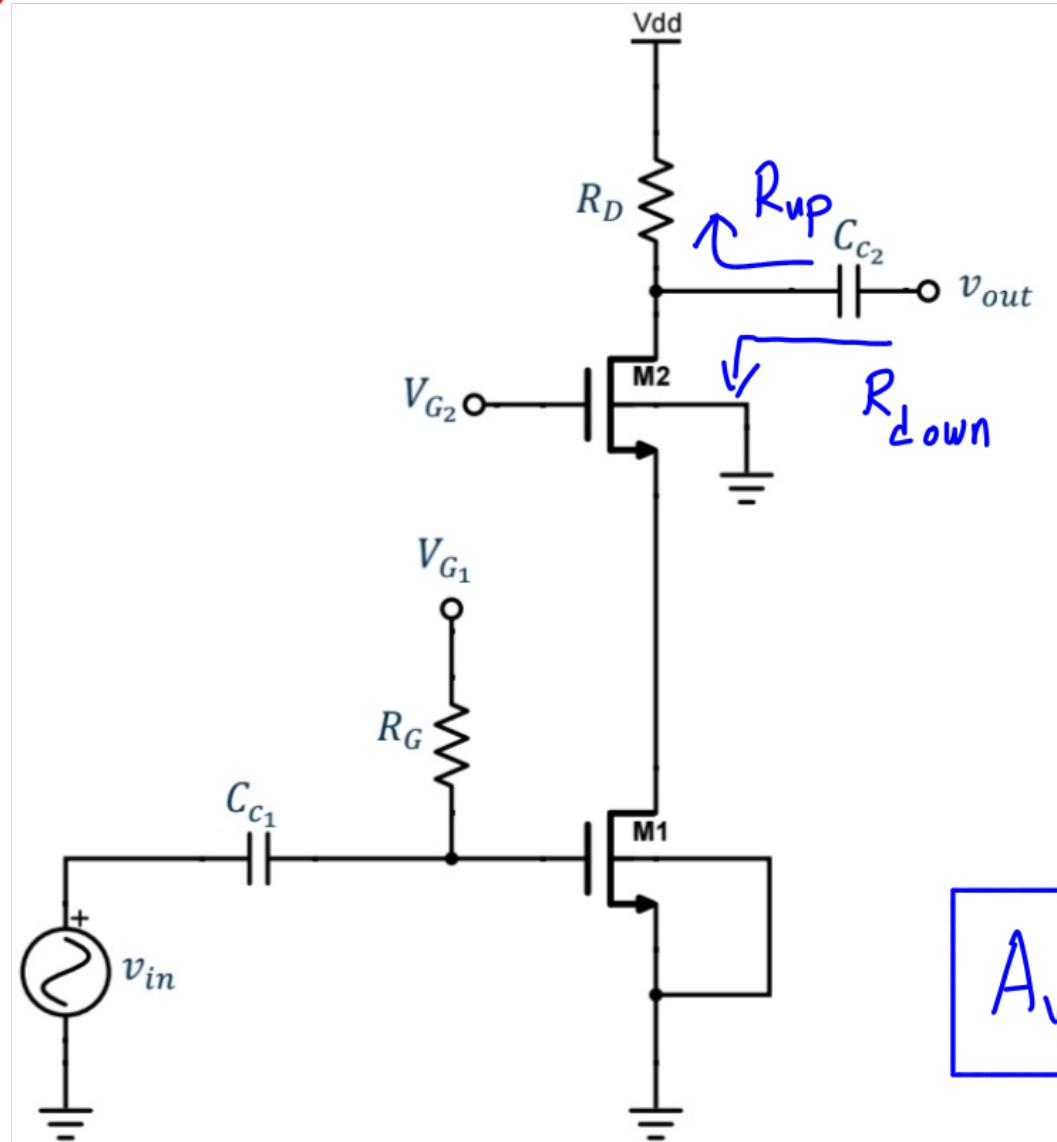

$$R_{\text{down}} \approx g_m r_{o_2} r_{o_1} \quad (\text{Cascade Rout})$$

$$R_{\text{up}} = R_D$$

$$A_V = -g_m (R_{\text{up}} // R_{\text{down}})$$

$$r_o = r_{o_1} = r_{o_2} = \frac{1}{\lambda I_D} = 100k \Omega$$


$$R_{\text{down}} = (2 \mu S)(100k \Omega)^2 = 20M \Omega$$

$$R_{\text{up}} = R_D = 1k \Omega \longrightarrow R_{\text{up}} // R_{\text{down}} \approx R_{\text{up}} = 1k \Omega$$

$$A_V = -g_m R_{\text{up}} = -2 \text{ V/V} \quad (6 \text{ dB})$$

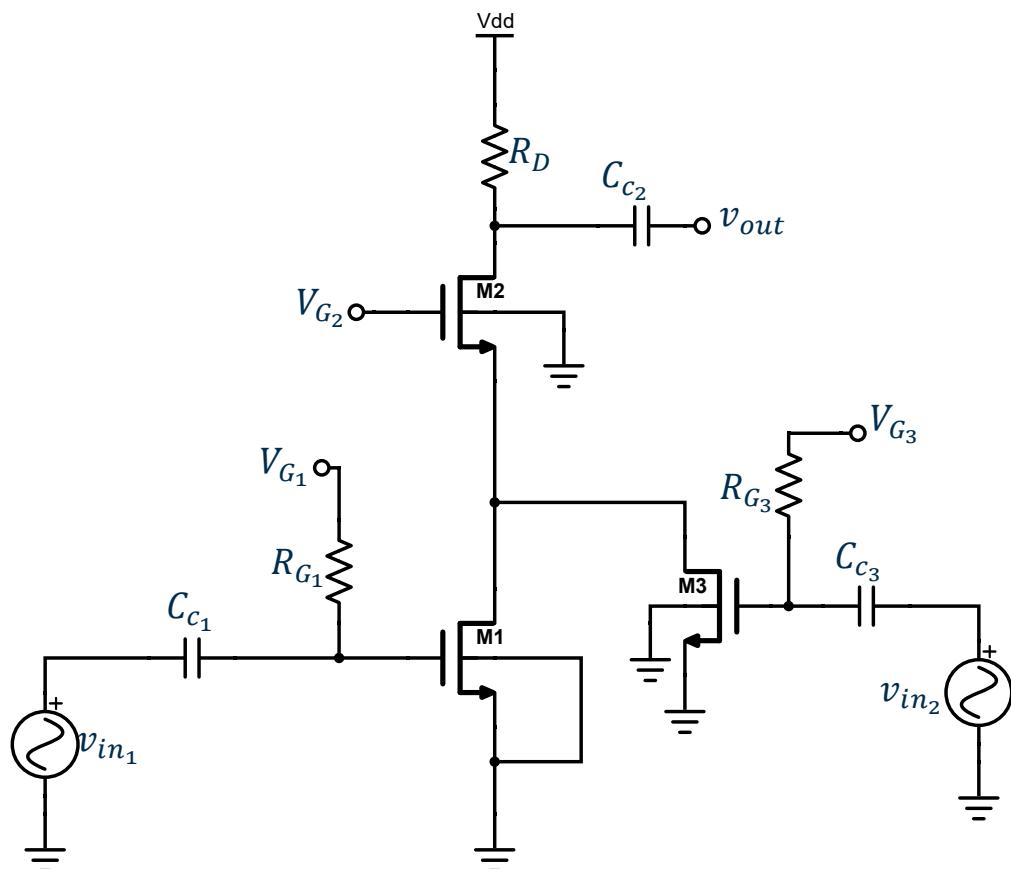Task 2.2

The amplifier from Task 2.1 is modified as following by include a second input stage.
Following circuit parameters are provided with M1 and M3 being identical:




- $V_{TH} = 0.7V$
- $V_{ov} = V_{GS} - V_{TH} = 1V$
- $\mu_n C_{ox} = 200 \frac{\mu A}{V^2}$
- $I_{D_1} = I_{D_3} = 1mA$
- $R_D = 1k\Omega$
- $R_{G_{1,3}} \rightarrow \infty, C_{c_{1,2,3}} \rightarrow \infty$
- $L = 200nm$

The two input signals are:

- $v_{in_1}(t) = 1\mu V \cos(2\pi 10^6 t + 5^\circ)$
- $v_{in_2}(t) = 5\mu V \cos(2\pi 10^6 t + 35^\circ)$.

a) Determine $v_{out}(t)$.

First check the DC Performance

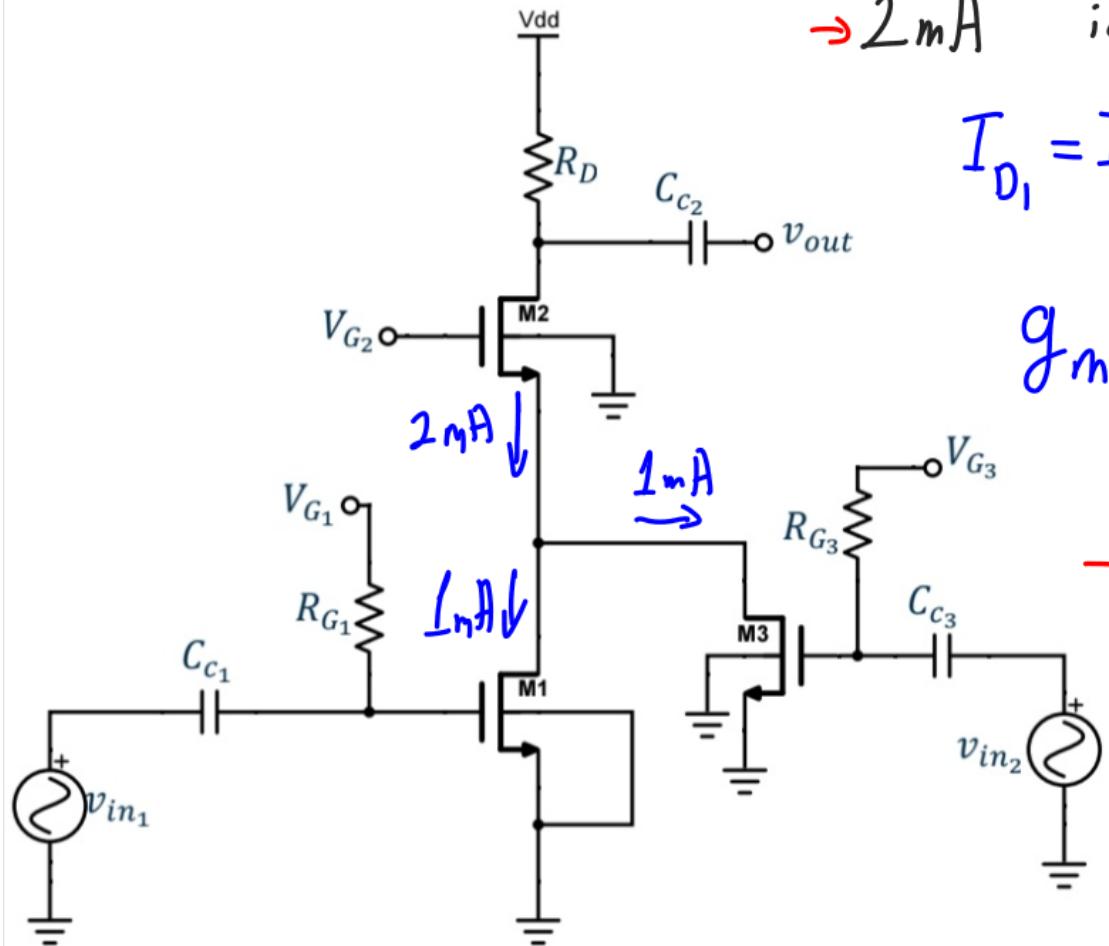


$$I_{D1} = I_{D3} \Rightarrow \left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_3 \Rightarrow V_{G1} = V_{G3} = 1.7V$$

$$g_{m_1} = g_{m_3} = \frac{2 \times 1\text{mA}}{1\text{V}} = 2\text{mS} \quad g_{m_2} = 2g_{m_1,2} = 4\text{mS}$$

\rightarrow The current flowing through M_2 is doubled.
It could maybe adjusted by changing V_{GS_2} .
However, it'd effect the whole circuit.
Doubling $\frac{W}{L}$ is more efficient.

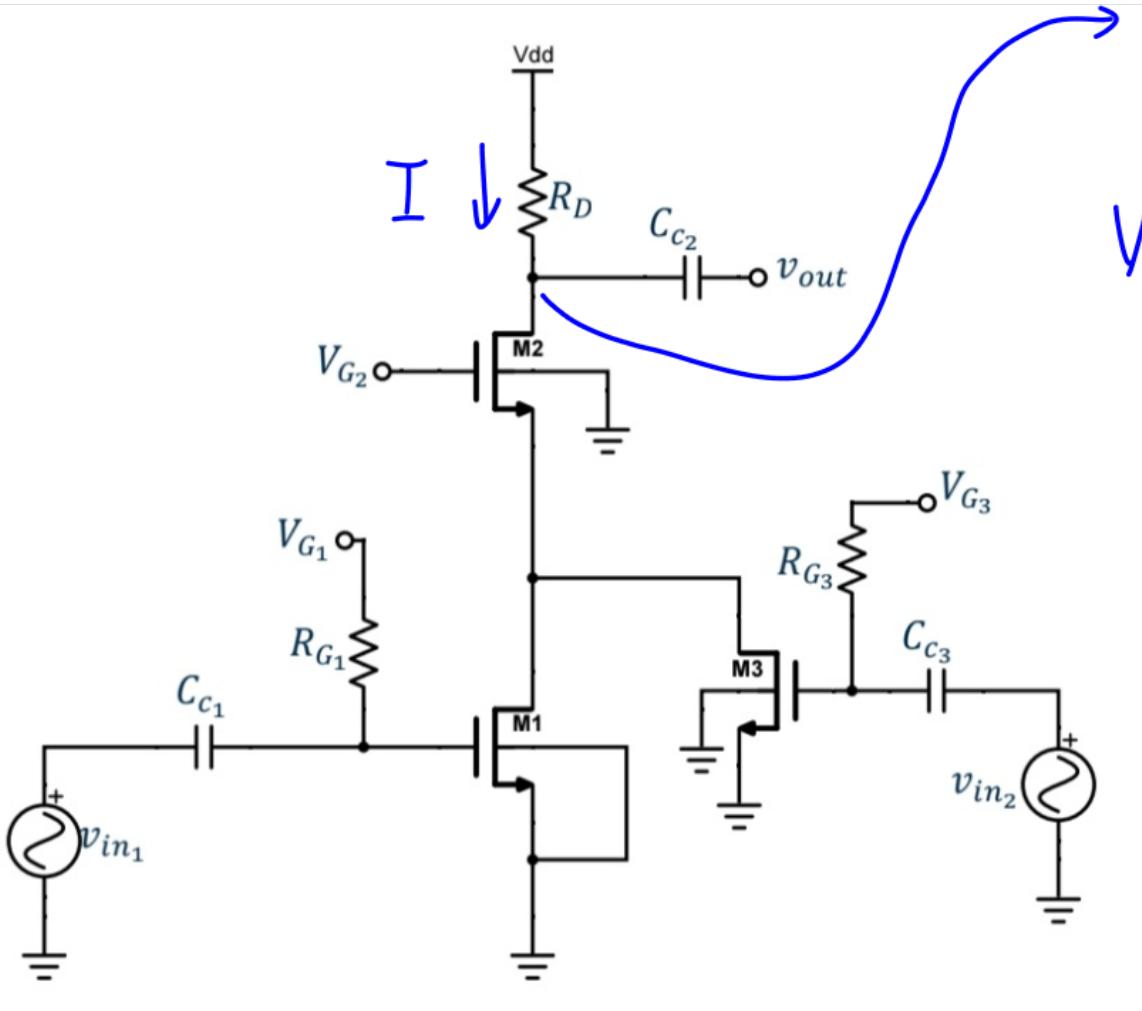
$$\left(\frac{W}{L}\right)_2 = 2 \left(\frac{W}{L}\right)_1 = 2 \left(\frac{W}{L}\right)_2$$



$$V_{D_{M_2}} = 2 V_{ov} = 2V, \quad R_D = 1k\Omega, \quad I = 2mA$$

$$V_{DD} = 2V + (2mA)(1k\Omega) = \boxed{4V}$$

Using superposition. V_{in_2} shorted.

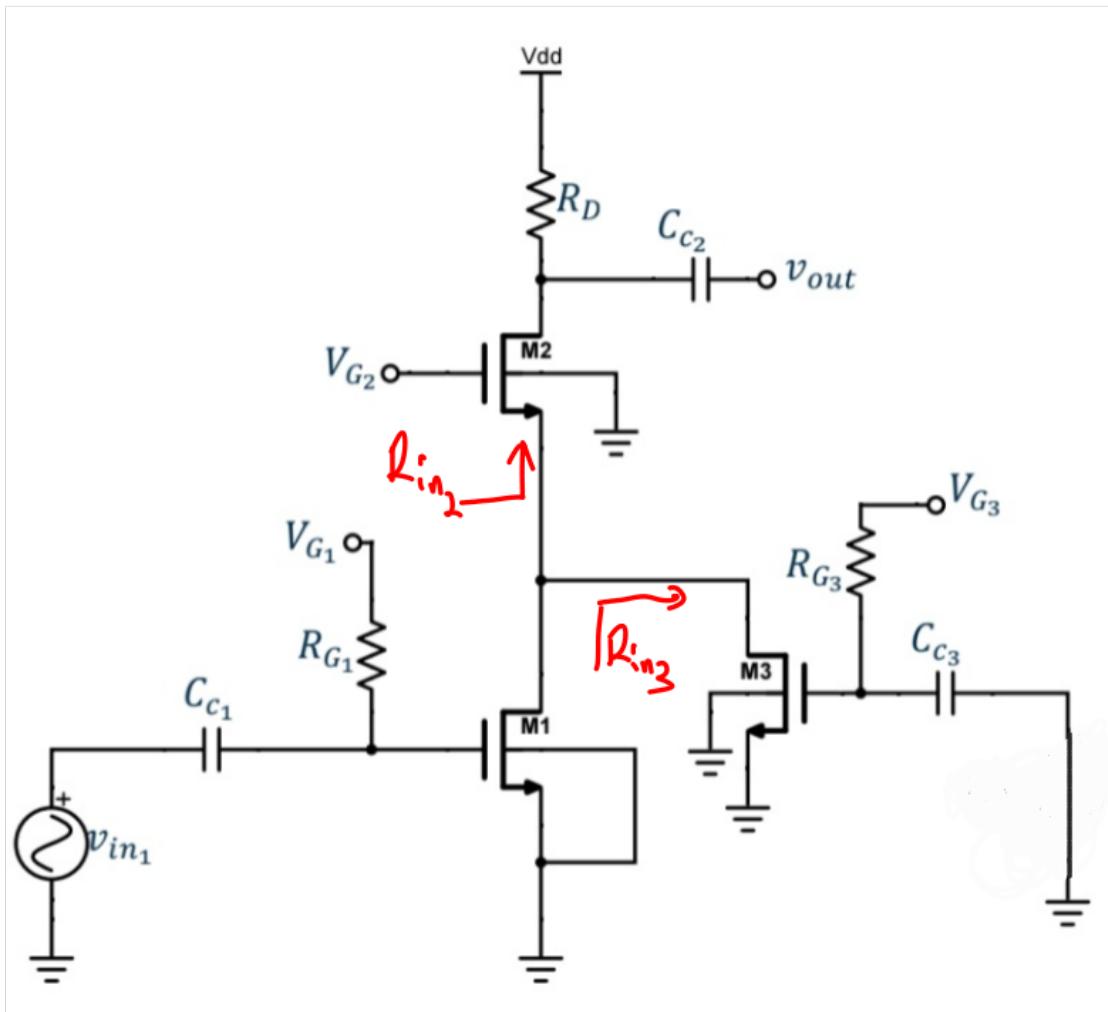


$$R_{in_2} \approx \frac{1}{g_{m_2}} \ll R_{in_3} = r_{o_2}$$

So, due to its higher impedance R_{in_3} can be considered as open circuit. Then standard cascode amplifier remains left.

$$A_V \approx -g_{m_1} R_D = -2V/V$$

$$\left| \frac{v_{out_1}}{v_{in_1}} \right| = 2 \text{ mV} \cos(2\pi 10^6 t + 185^\circ)$$

v_{in_1} Shorted

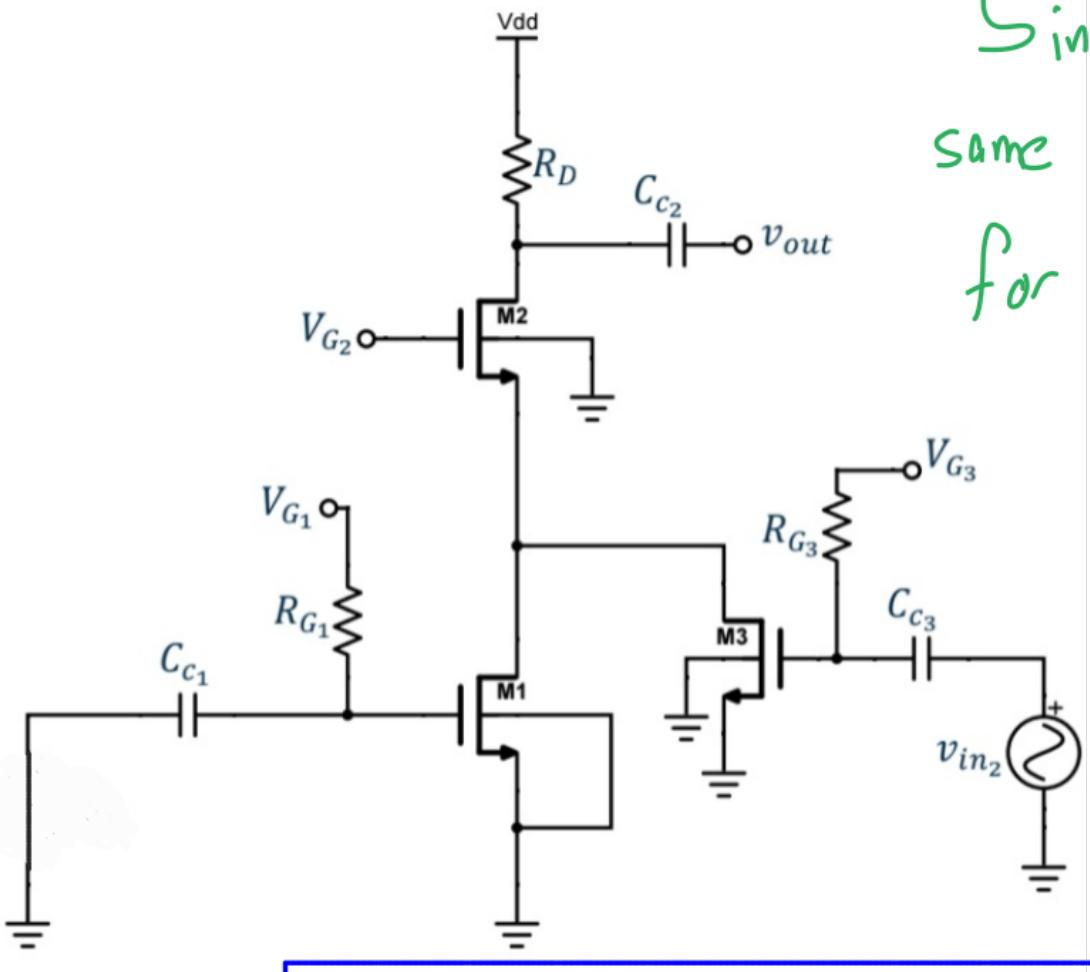


Since M1 and M3 are equivalent, the same principle will apply for v_{in_2} . No need for repeating the calculation.

$$\frac{v_{out_2}}{v_{in_2}} = 10 \text{ mV} \cos(2\pi 10^6 t + 215^\circ)$$

$$v_{out} = v_{out_1} + v_{out_2} = 2 \text{ mV} \cos(2\pi 10^6 t + 185^\circ) + 10 \text{ mV} \cos(2\pi 10^6 t + 215^\circ)$$

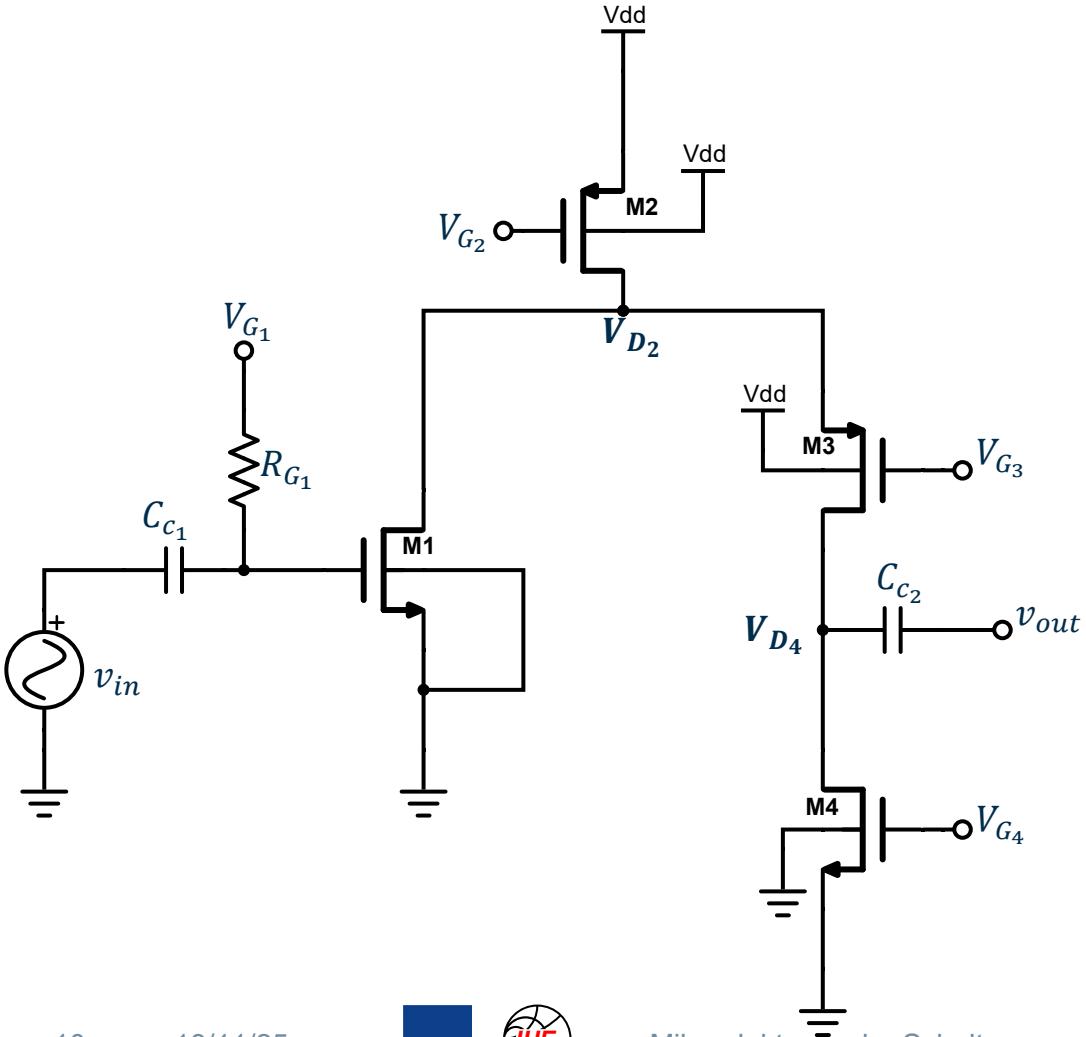Task 2.3


For the circuit below, following circuit parameters are provided:



- $V_{TH_N} = |V_{TH_P}| = 0.4V$
- $V_{ov} = |V_{GS}| - |V_{TH}| = 0.6 V$
- $\mu_n C_{ox} = 200 \frac{\mu A}{V^2}$
- $\mu_p C_{ox} = 50 \frac{\mu A}{V^2}$
- $I_{D_1} = I_{D_{3,4}} = 1mA$
- $R_{G_1} \rightarrow \infty, C_{c_{1,2}} \rightarrow \infty$
- $L = 200nm$
- $\lambda_N = \lambda_P = 0.05V^{-1}$

Furthermore, assume $V_{D_4} = 0.6V$, $V_{D_2} = 1.2V$

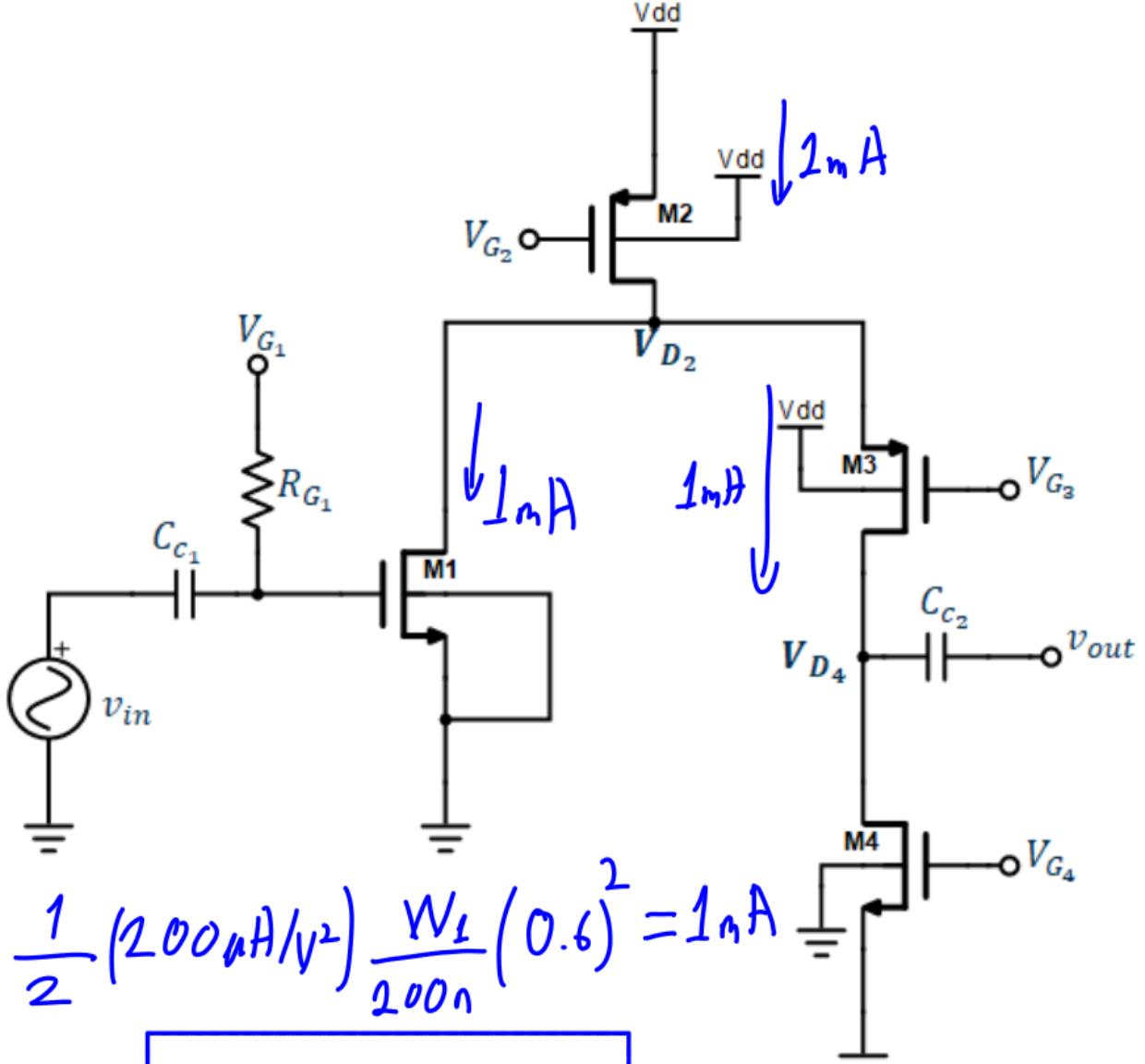- a) Calculate DC operating points of each transistor and calculate the small-signal gain A_v .



$$\frac{1}{2} \left(200 \mu\text{A}/\text{V}^2 \right) \frac{W_1}{200 n} (0.6)^2 = 1 \text{nA}$$

$$W_1 \approx 5.55 \mu\text{m}$$

$$W_1 = W_4 = \frac{W_3}{4} = \frac{W_2}{8} \quad \left(\frac{\mu_n C_{ox}}{\mu_p C_{ox}} = 4 \right)$$

$$V_{G_1} - 0.4V = 0.6V \Rightarrow V_{G_1} = 1V$$

$$V_{G_4} - 0.4V = 0.6V \Rightarrow V_{G_4} = 1V$$

$$1.2 - V_{G_3} - 0.4V = 0.6V \Rightarrow V_{G_3} = 0.2V$$

$$V_{DD} = V_{D_2} + V_{ov} = 1.8V$$


$$1.8V - V_{G_2} - 0.4V = 0.6V \Rightarrow V_{G_2} = 0.8V$$

All transistors operate in saturation region.

$$g_m = g_{m_1} = \frac{g_{m_2}}{2} = g_{m_3} = g_{m_4} = \frac{2 + 1mA}{0.6V} = 3.33mS$$

$$r_o = r_{o_1} = 2r_{o_2} = r_{o_3} = r_{o_4} = \frac{1}{\lambda(1mA)} = 20k\Omega$$

Folded Cascode Gain Slide 2 P.44

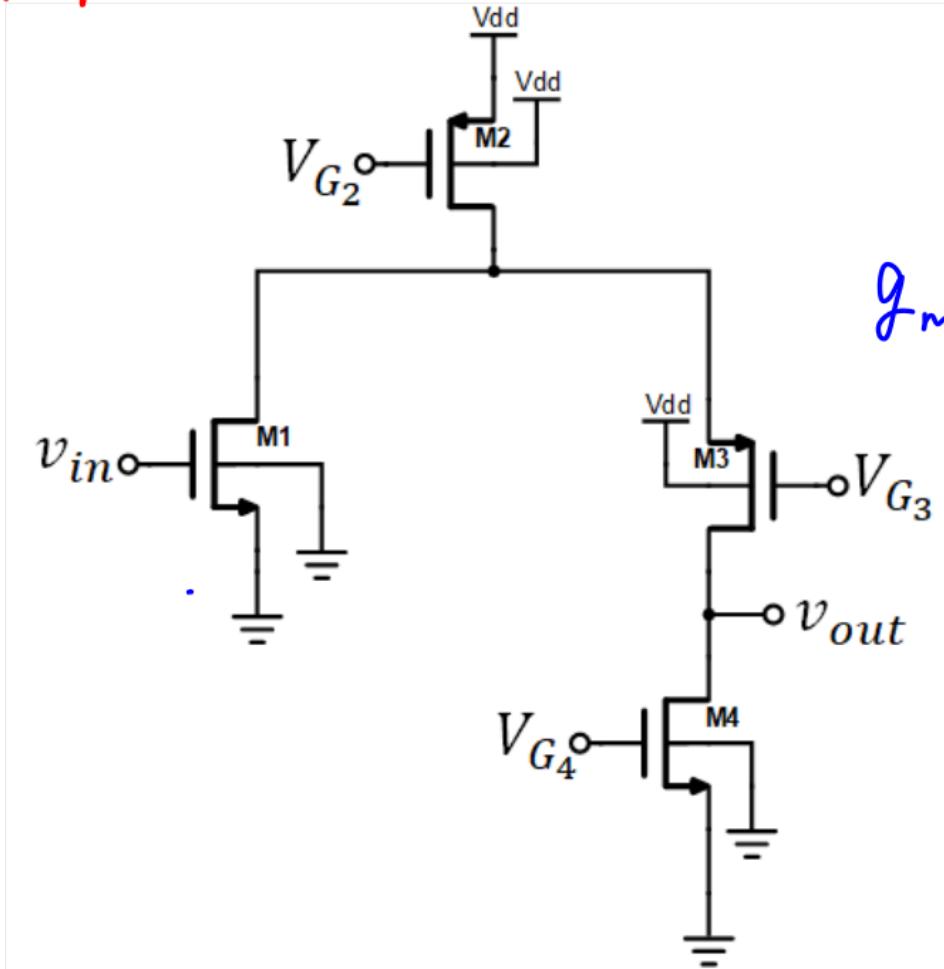

$$A_v = -g_{m_1} \left([g_{m_3} r_{o_3} (r_{o_1} \parallel r_{o_2})] \parallel r_{o_4} \right)$$

$g_{m_3} r_{o_3} (r_{o_1} \parallel r_{o_2}) = g_m \frac{r_o^2}{3} = 444 k\Omega$


$(444 k\Omega) \parallel 20 k\Omega \approx 19 k\Omega$

$$A_V = -g_m (19 k\Omega) = -(3.33 mS) (19 k\Omega)$$

$$A_v \approx 63 V/V$$

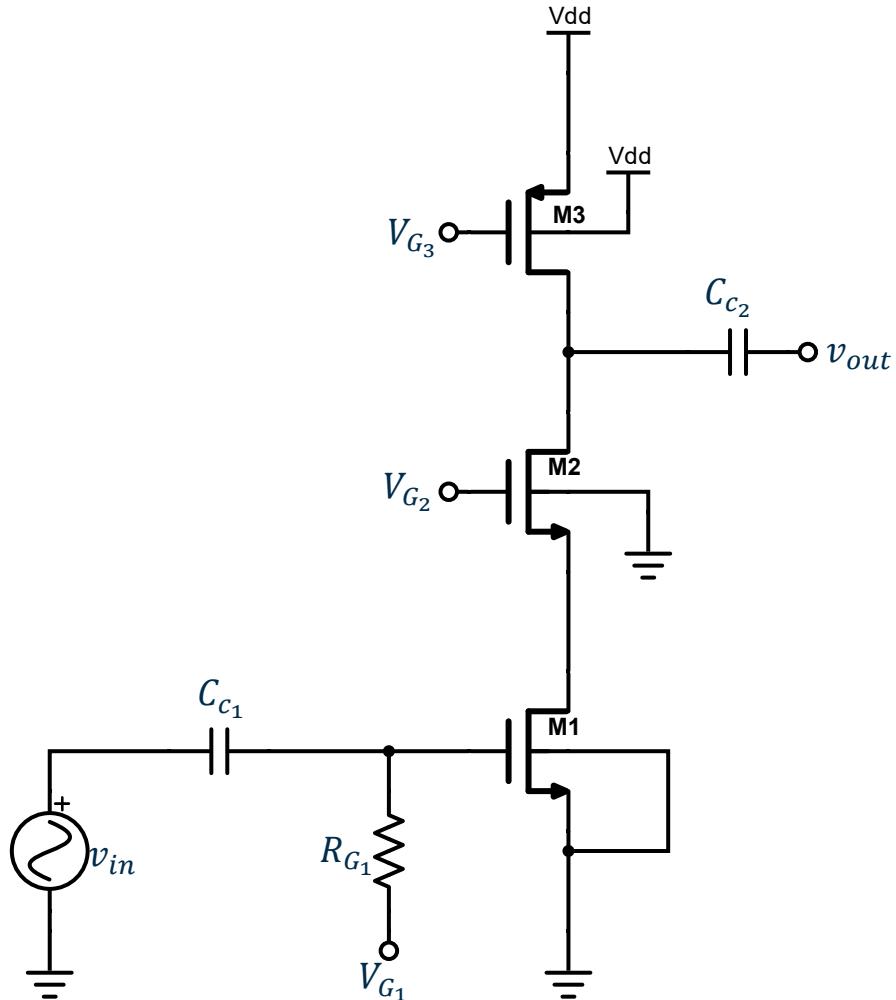Task 3

For the circuit below, following parameters are provided:



- $V_{TH_N} = |V_{TH_P}| = 0.2V$ ▪ $I_D = 4mA$
- $V_{ov} = |V_{GS}| - |V_{TH}| = 0.4 V$ ▪ $R_{G_1} \rightarrow \infty, C_{c_{1,2}} \rightarrow \infty$
- $\mu_n C_{ox} = 200 \frac{\mu A}{V^2}$ ▪ $L = 200nm$
- $\mu_p C_{ox} = 50 \frac{\mu A}{V^2}$ ▪ $\lambda_N = \lambda_P = 0.01V^{-1}$

It can be assumed that all transistors are operated in saturation region.

- Calculate the output noise voltage density and input-referred noise voltage density.
- Compare the noise performance of this amplifier to that of a single-ended common-source amplifier with a current-source load (i.e., without M2).

$$I_D = I_{D_{M_1}} = I_{D_{M_2}} = I_{D_{M_3}} = 4 \text{ mA}$$

$$g_m = \frac{2 I_D}{V_{ov}} = 20 \text{ mS}$$


$$V_{ov} = V_{ov_{M_1}} = V_{ov_{M_2}} = V_{ov_{M_3}} = 0.4 \text{ V}$$

$$r_o = \frac{1}{\lambda I_D} = 25 \text{ k}\Omega$$


$$A_V = -g_m \left(g_{m_2} r_{o_2} r_{o_1} \parallel r_{o_3} \right) \approx -g_m r_o = -500 \text{ V/V}$$

Each transistor generates thermal noise.

CURRENT NOISE EQUIVALENT

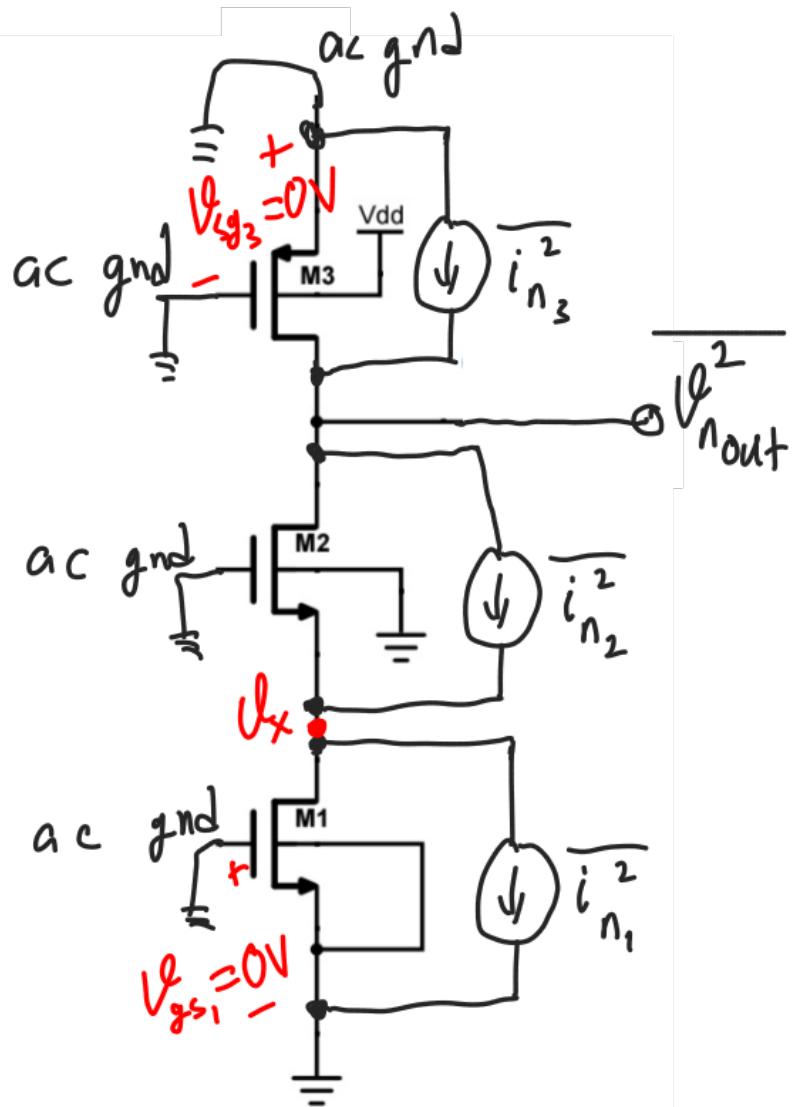


VOLTAGE NOISE EQUIVALENT

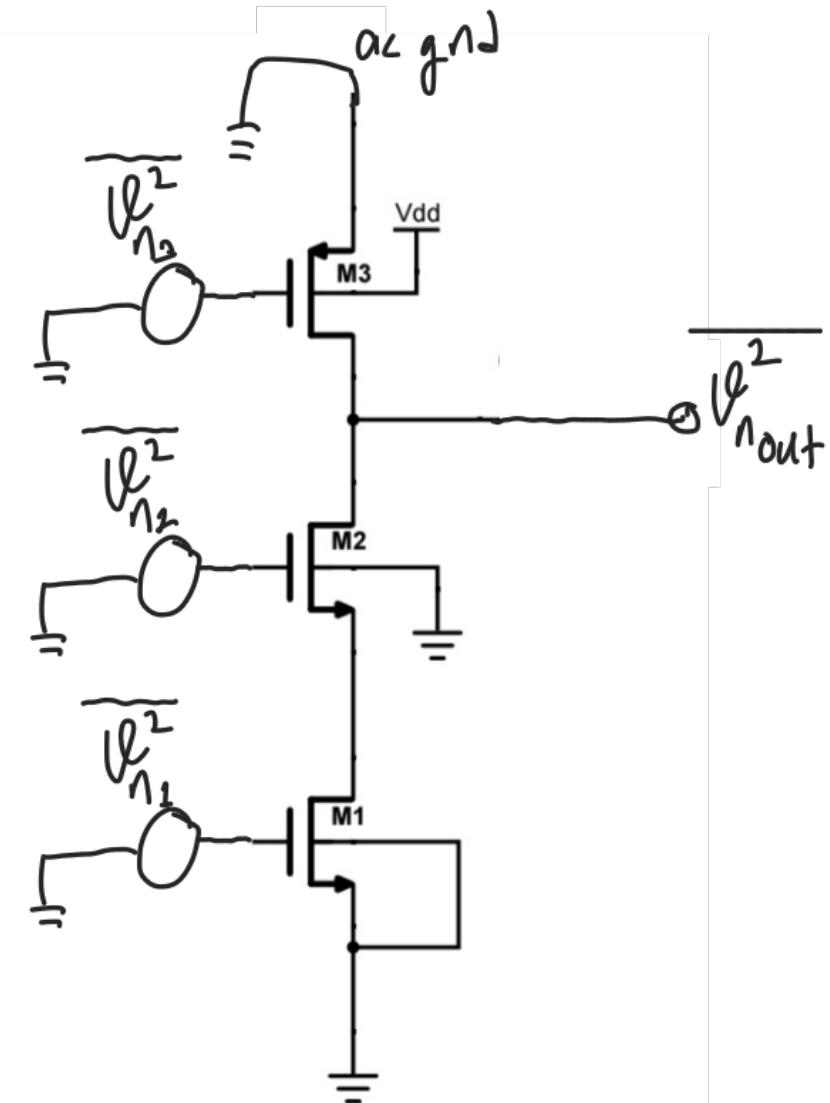

Apply superposition & draw small-signal model:

i_{n_1}

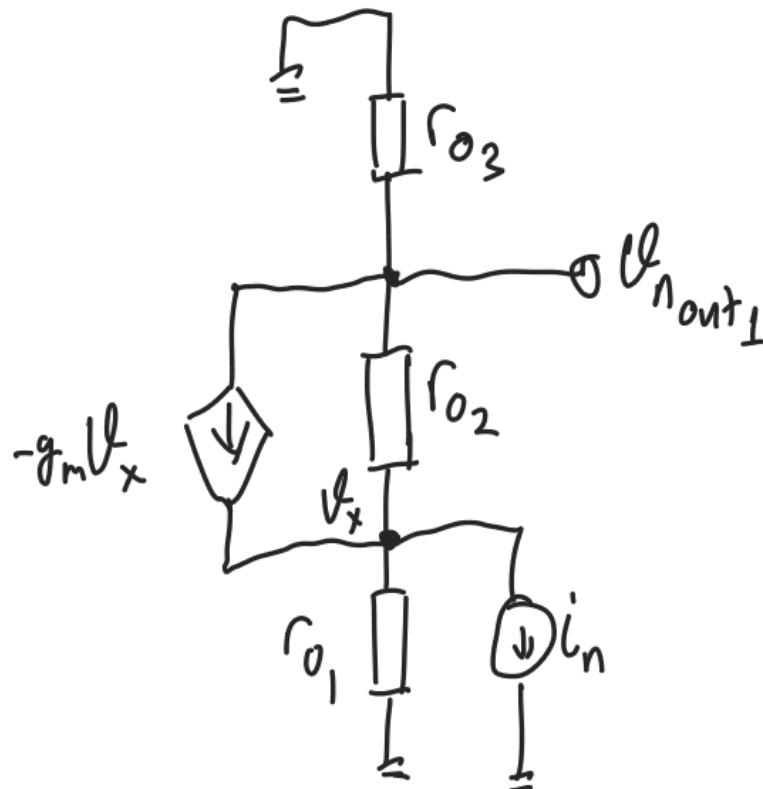


$$\begin{aligned}
&\textcircled{1} \quad -\frac{V_{nout1}}{R_{O3}} = -g_m V_x + \frac{V_{nout1} - V_x}{R_{O2}} = \frac{V_x}{R_{O1}} + i_n \\
&\textcircled{2} \quad V_x = V_{nout1} \frac{\frac{1}{R_{O3}} + \frac{1}{R_{O2}}}{g_m + \frac{1}{R_{O2}}} \\
&\textcircled{3} \quad -V_{nout1} \left(\frac{1}{R_{O3}} + \frac{\frac{1}{R_{O3}} + \frac{1}{R_{O2}}}{g_m + \frac{1}{R_{O2}}} \frac{1}{R_{O1}} \right) = i_n \\
&\qquad\qquad\qquad \frac{1}{R_{eq1}}
\end{aligned}$$

$$\overline{V_{n_{out_1}}^2} = \overline{i_{n_1}^2} R_{eq_1}^2$$

Please note that calculating M1's noise contribution through its voltage noise equivalent is way more easier!

$$\overline{V_{n_{out_1}}^2} = \overline{V_{n_1}^2} |A_{uf}|^2$$

i_{n_2} :

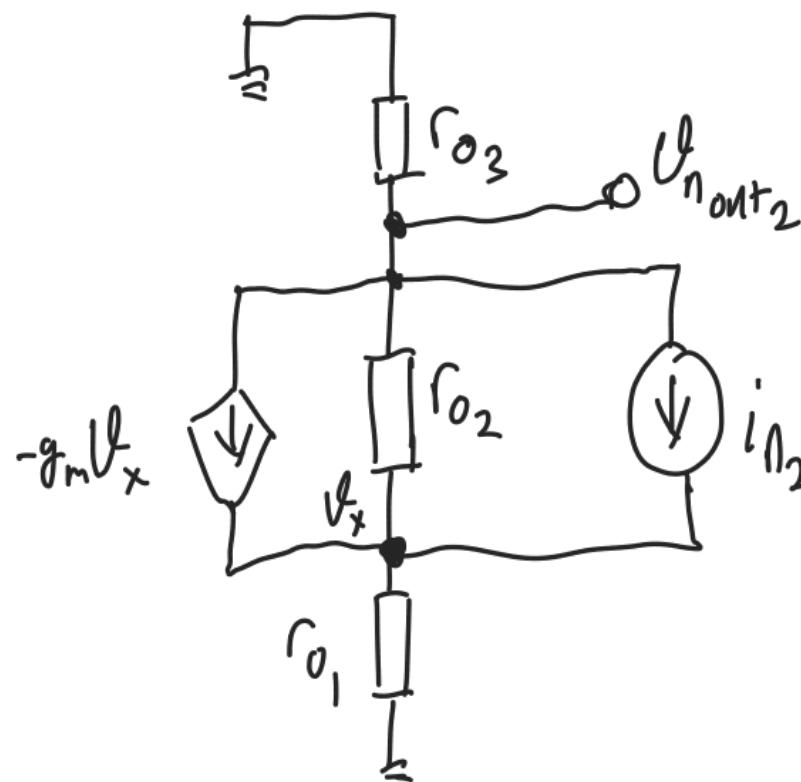

$$\frac{-V_{n_{out2}}}{r_{o_3}} = -g_m V_x + \frac{V_{n_{out2}} - V_x}{r_{o_2}} + i_{n_2} = \frac{V_x}{r_{o_1}}$$

①

$$V_x = -\frac{r_{o_1}}{r_{o_3}} V_{n_{out2}}$$

②


$$-V_{n_{out2}} \left(g_n \frac{r_{o_1}}{r_{o_3}} + \frac{r_{o_1}}{r_{o_2}} + \frac{1}{r_{o_2}} + \frac{1}{r_{o_3}} \right) = i_{n_2}$$

③

$$V_{n_{out2}} = -\frac{r_{o_2} r_{o_3}}{g_n r_{o_1} r_{o_2} + r_{o_1} + r_{o_2} + r_{o_3}} i_{n_2}$$

$$\boxed{V_{n_{out2}}^2 = \left(\frac{r_{o_2} r_{o_3}}{g_n r_{o_1} r_{o_2} + r_{o_1} + r_{o_2} + r_{o_3}} \right)^2 i_{n_2}^2}$$

i_{n_3} :

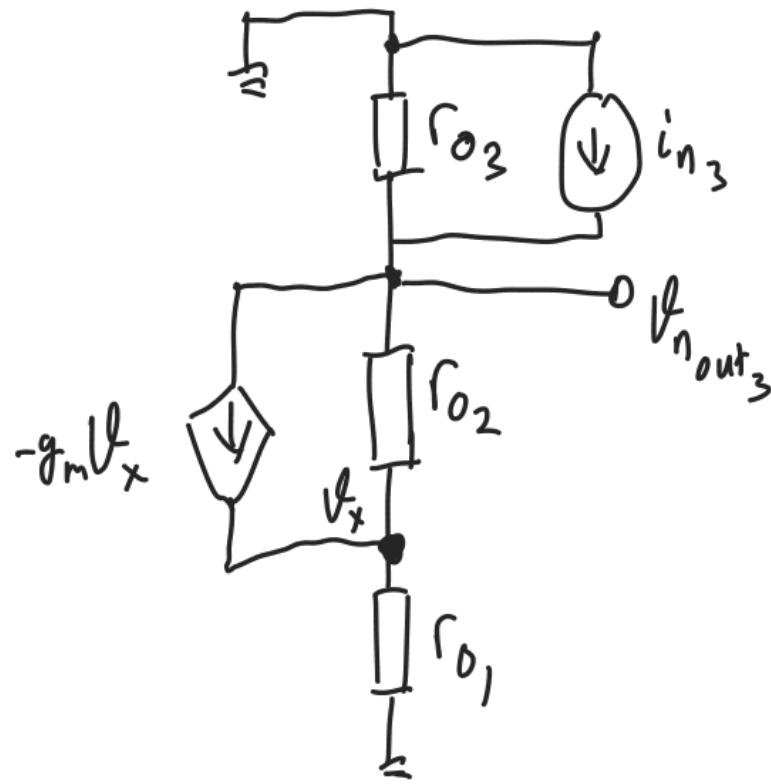

$$\frac{-V_{n_{out3}}}{R_{O3}} + i_{n_3} = -g_m V_x + \frac{V_{n_{out3}} - V_x}{R_{O2}} = \frac{V_x}{R_{O1}}$$

(1)

\downarrow

$$V_{n_{out3}} \frac{1}{R_{O2}} \left(\frac{1}{R_{O1}} + \frac{1}{R_{O2}} + g_m \right) = V_x$$

(2)

\downarrow

$$i_{n_3} = V_{n_{out3}} \left[\frac{1}{R_{O3}} + \frac{1}{R_{O1} R_{O2}} \left(\frac{1}{g_m} \parallel R_{O1} \parallel R_{O2} \right) \right]$$

$\approx \frac{1}{g_m}$

$\frac{1}{g_m} \ll R_O$

(3)

$$\overline{V_{n_{out3}}}^2 = \overline{i_{n_3}}^2 \left(R_{O3} \parallel g_m R_{O1} R_{O2} \right)^2$$

$$\overline{V_{n_{out_1}}^2} = \overline{V_{n_1}^2} |A_V|^2 = \frac{4kT\gamma}{g_m} \left(g_m r_0 \right)^2 = \boxed{4kT\gamma g_m r_0^2}$$

$$\overline{V_{n_{out_2}}^2} = \left(\frac{r_{0_2} r_{0_3}}{g_m r_{0_1} r_{0_2} + r_{0_1} + r_{0_2} + r_{0_3}} \right) \overline{i_{n_2}^2} = \boxed{4kT\gamma g_m \left(\frac{r_0^2}{g_m r_0^2 + 3r_0} \right)^2}$$

$$\overline{V_{n_{out_3}}^2} = \overline{i_{n_3}^2} \left(r_{0_3} // g_m r_{0_1} r_{0_2} \right)^2 \approx \boxed{4kT g_m r_0^2}$$

$$r_0 \ll g_m r_0^2$$

$$k = 1.38 \times 10^{-23} \text{ J/K}$$

$$T = 300 \text{ K} \quad \gamma = 2/3$$

$$\overline{\mathcal{V}_{n_{out_1}}^2} = \overline{\mathcal{V}_{n_{out_3}}^2} = 138.06 \text{ fV}^2/\text{Hz}$$

$$\overline{\mathcal{V}_{n_{out_2}}^2} = 545.69 \text{ zV}^2/\text{Hz}$$

$(z=10^{-21})$

$$\overline{\mathcal{V}_{n_{out}}^2} = \overline{\mathcal{V}_{n_{out_1}}^2} + \overline{\mathcal{V}_{n_{out_2}}^2} + \overline{\mathcal{V}_{n_{out_3}}^2} = 276.13 \text{ fV}^2/\text{Hz}$$

$$\text{Output Noise Voltage Density} = \sqrt{\overline{\mathcal{V}_{n_{out}}^2}} = 524.43 \text{ V}/\text{Hz}$$

$$\text{Input-referred Noise Voltage Density} = \sqrt{\frac{V^2}{n_{out}}} = 1.05 \text{ nV}/\sqrt{\text{Hz}}$$



Note that the common-gate device M2 contributes negligibly to the total noise.

The dominant noise sources are the input transistor M1, and the PMOS load M3.

As a result, a cascode amplifier typically exhibits higher output noise, simply because it has a higher voltage gain than a common-source amplifier with a current-source load.

However, the input-referred noise remains almost the same for both amplifiers, since input-referred noise is independent of the amplifier gain.