

Mikroelektronische Schaltungen und Systeme

Lect.8 Stability

Prof. Dr.-Ing. Ahmet Cagri Ulusoy
Institut für Hochfrequenztechnik und Elektronik (IHE)



Mikroelektronische Schaltungen und Systeme

Lect.1

Intro/CMOS Basics

Lect.2

Single Stage
Amplifiers

Lect.3

Noise

Lect.4

Differential
Amplifiers

Lect.5

Current Sources

Lect.6

Frequency
Response

Lect.7

Feedback

Lect.8

Operational Amplifiers

Lect.9

Stability and
Frequency
Compensation

Lect.10

Switched-Capacitor
Circuits

Lect.11

Introduction to Data
Converters

Lect.12

Combinational Logic
Circuits

Lect.13

Sequential Circuits

Lect.14

Timing of Sequential
Circuits

Lect.15

Digital Building
Blocks

Lect.16

Memory

Lect.17

Technology
Mapping

Lect.18

FPGA

Lect.19

Physical Design I

Lect.20

Physical Design II

Lect.21

Q&A





001011110110100
... (conf_addr = 0);
... (conf_addr, r.conf_addr
... 0); ...
... v.conf.wb.wr
... (7 downto 0)
... sel(0) & wb_b
... (15 downto 0)

Introduction

- We have seen that amplifiers with second-order response can result in an oscillatory behavior,
- We would like to take a deeper look into this phenomena,
- Understand unstable behavior, how to assess it and how to eliminate it.

2nd Order Amplifiers

- The second-order system will be described with the characteristic equation in the denominator


$$s^2 + s \frac{\omega_0}{Q} + \omega_0^2 = 0$$

- In terms of the time constants

$$1 + s(\tau_1 + \tau_2) + s^2 \tau_1 \tau_2$$

2nd Order Amplifiers

- The behavior we have previously seen

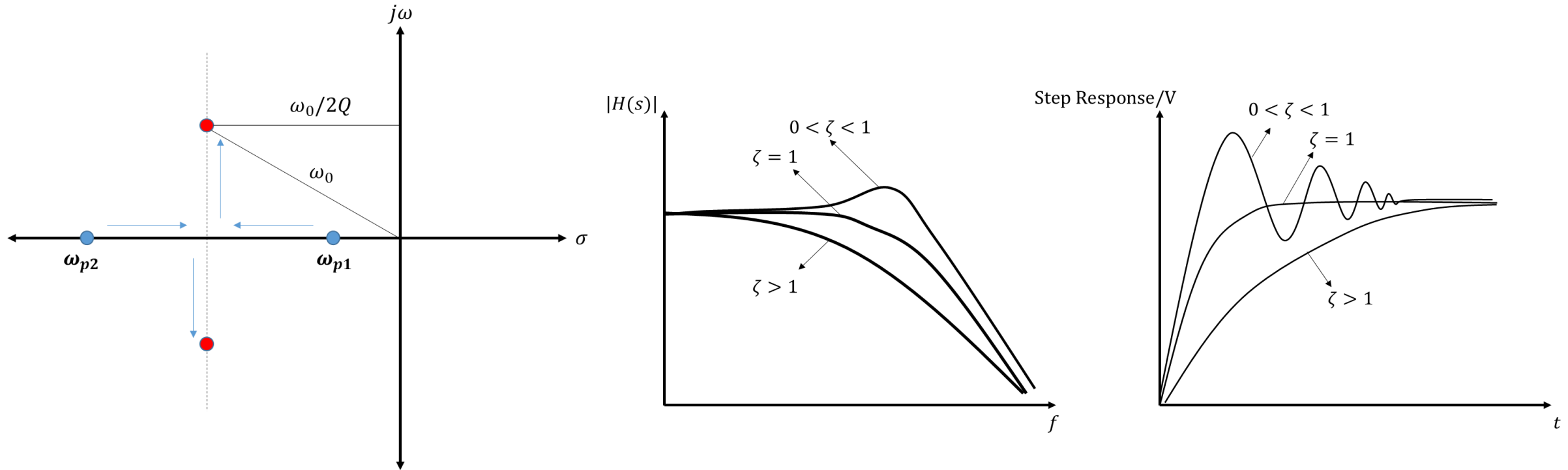

- is observed, when the roots of the characteristic function are complex conjugates

2nd Order Amplifiers

- Quadratic equation:

$$1 + s(\tau_1 + \tau_2) + s^2\tau_1\tau_2$$
$$c + sb + s^2a$$

- The solution of the quadratic equation:

$$s = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

- s here of course being the Laplace parameter with $s = \sigma + j\omega$ ($\sigma = 0$ is steady state)
- The roots will be complex conjugate if $b^2 < 4ac$

2nd Order Amplifiers

- In terms of circuit parameters:

$$1 + s(\tau_1 + \tau_2) + s^2\tau_1\tau_2$$

$$a = \tau_1\tau_2$$

$$b = \tau_1 + \tau_2$$

$$c = 1$$


- For complex roots:

$$(\tau_1 + \tau_2)^2 < 4\tau_1\tau_2$$

- This typically requires some kind of feedback, or interaction between reactive components beyond a simple second-order response

Sallen-Key Filter

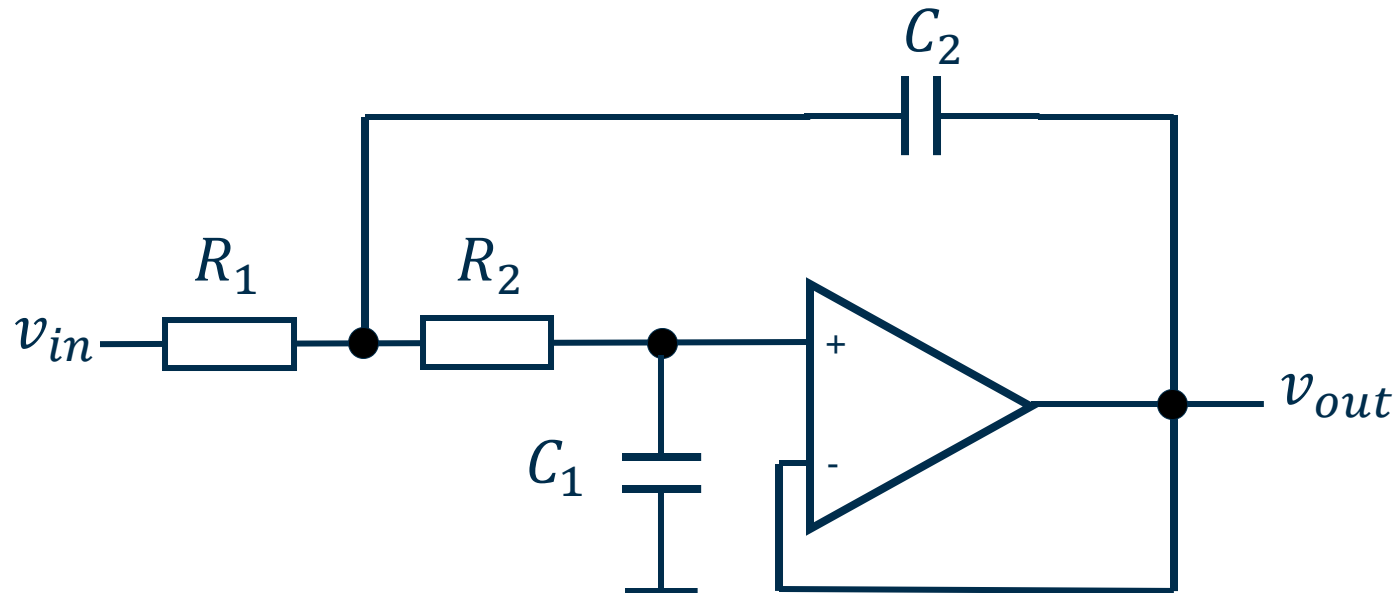
- We can observe this effect with a well-know circuit architecture: the Sallen-Key filter



- We will focus on asymptotic transfer function H_{∞} . In this example this is quite accurate, considering $H_0 = 0$ for output open and a high OPAMP gain


Sallen-Key Filter

- In the asymptotic case (ideal OPAMP):

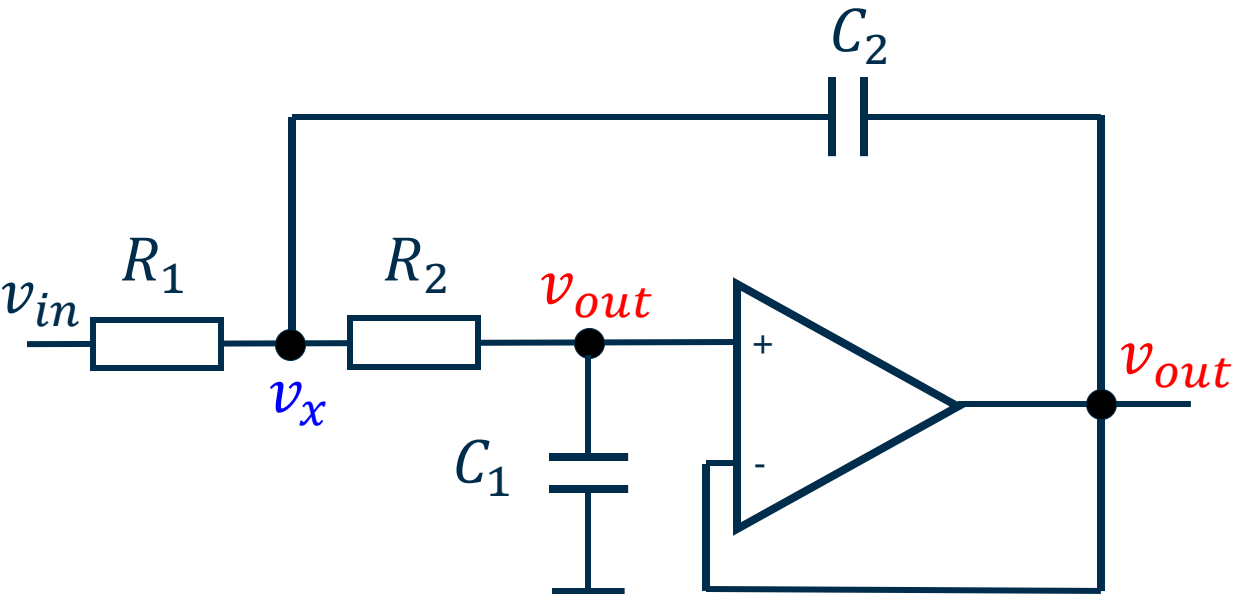

Sallen-Key Filter


- In the asymptotic case (ideal OPAMP):

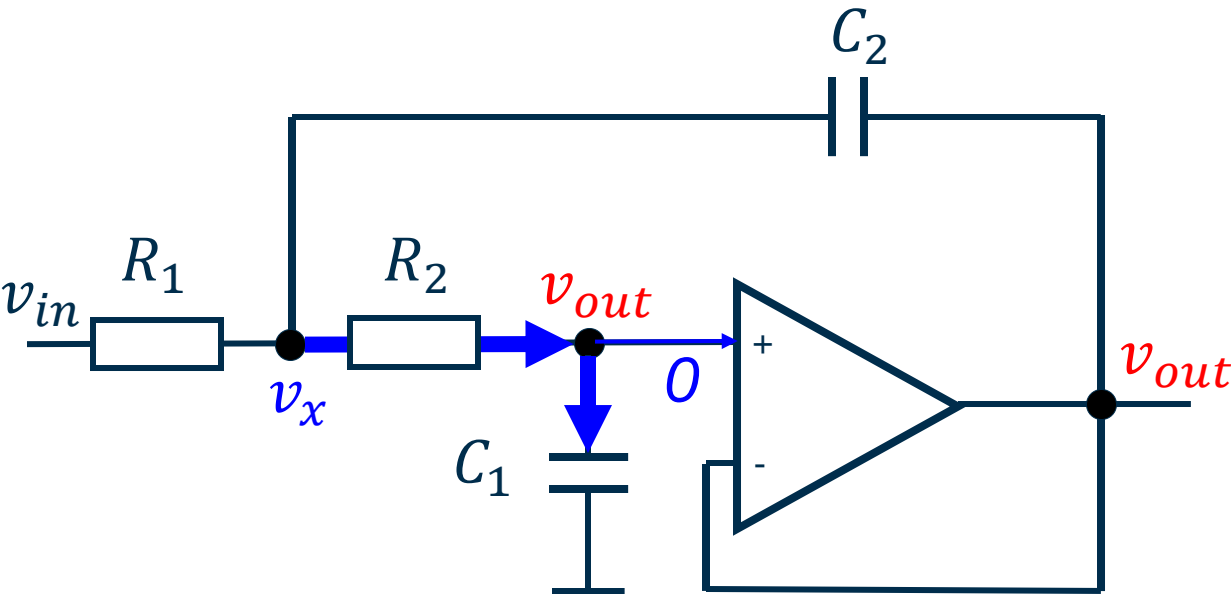

$$\frac{v_x - v_{out}}{R_2} = sC_1 v_{out} \rightarrow v_x = v_{out} (1 + sR_2 C_1)$$

Sallen-Key Filter

- In the asymptotic case (ideal OPAMP):

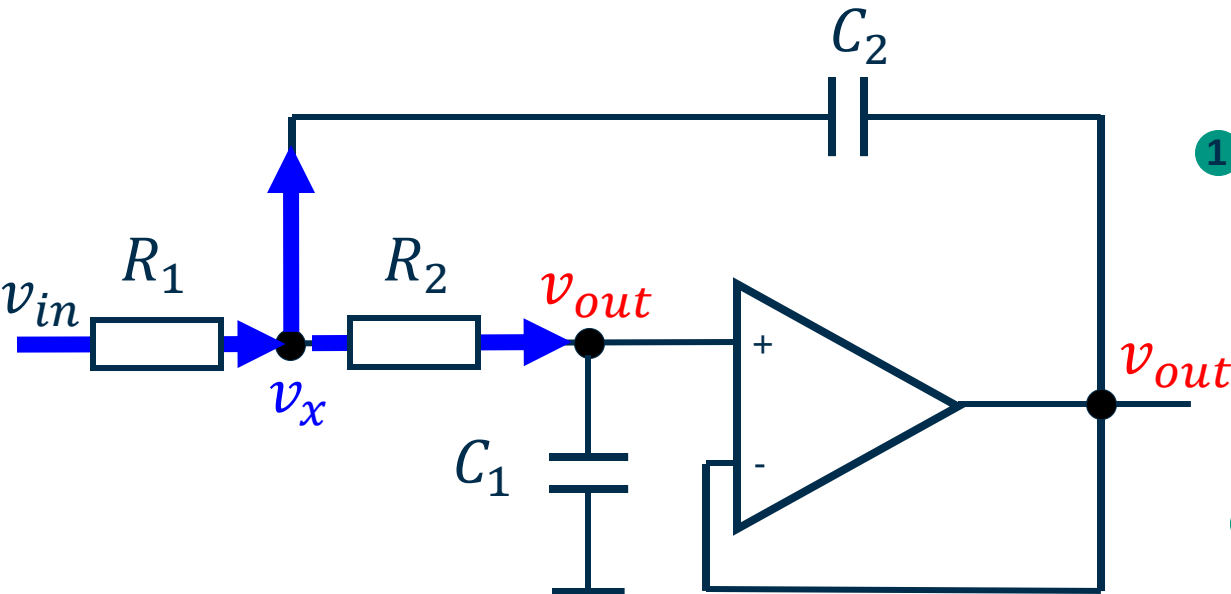


$$① \quad \frac{v_x - v_{out}}{R_2} = sC_1 v_{out} \rightarrow v_x = v_{out} (1 + sR_2 C_1)$$

$$② \quad \frac{v_{in} - v_x}{R_1} = (v_x - v_{out})sC_2 + \frac{v_x - v_{out}}{R_2}$$

Sallen-Key Filter

- In the asymptotic case (ideal OPAMP):

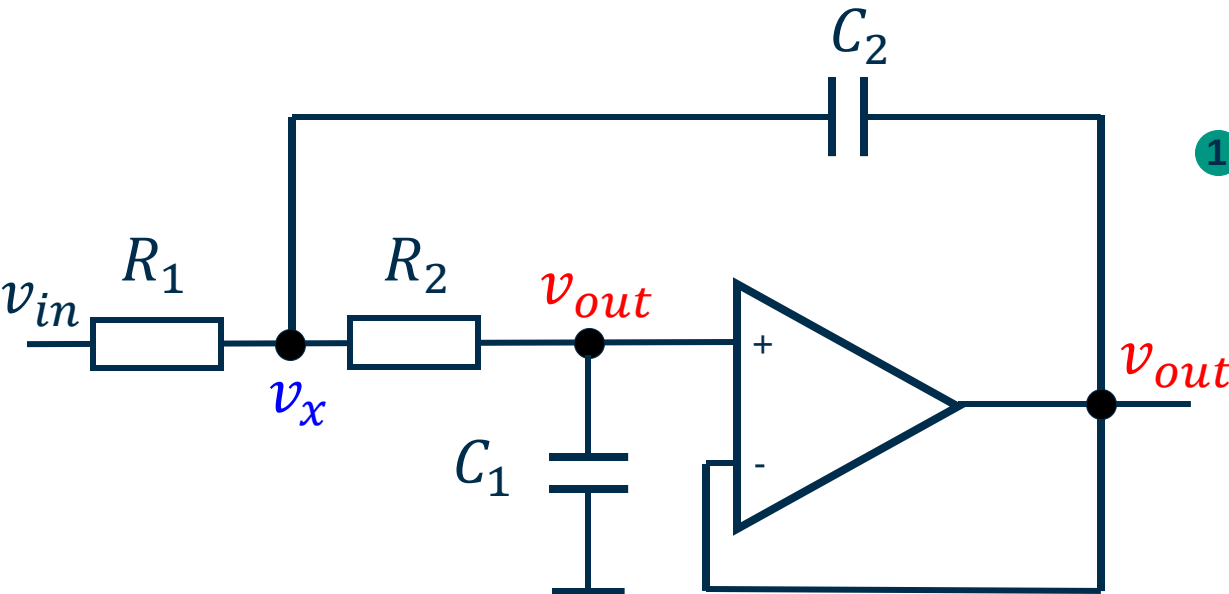

$$① \quad \frac{v_x - v_{out}}{R_2} = sC_1 v_{out} \rightarrow v_x = v_{out} (1 + sR_2 C_1)$$

$$② \quad \frac{v_{in} - v_x}{R_1} = (v_x - v_{out})sC_2 + \frac{v_x - v_{out}}{R_2}$$

$$v_{in} - v_{out} (1 + sR_2 C_1) = v_{out} s^2 R_2 R_1 C_1 C_2 + v_{out} s R_1 C_1$$

$$\frac{v_{out}}{v_{in}} = \frac{1}{s^2 R_2 R_1 C_2 C_1 + s(R_1 C_1 + R_2 C_1) + 1}$$


Sallen-Key Filter

- Here, we see that C_2 allows us to adjust a and b coefficients independently

$$\frac{v_{out}}{v_{in}} = \frac{1}{s^2 R_2 R_1 C_2 C_1 + s(R_1 C_1 + R_2 C_1) + 1}$$


$$\frac{v_{out}}{v_{in}} = \frac{1}{s^2 + s \frac{R_1 C_1 + R_2 C_1}{R_2 R_1 C_2 C_1} + R_2 R_1 C_2 C_1}$$

Sallen-Key Filter

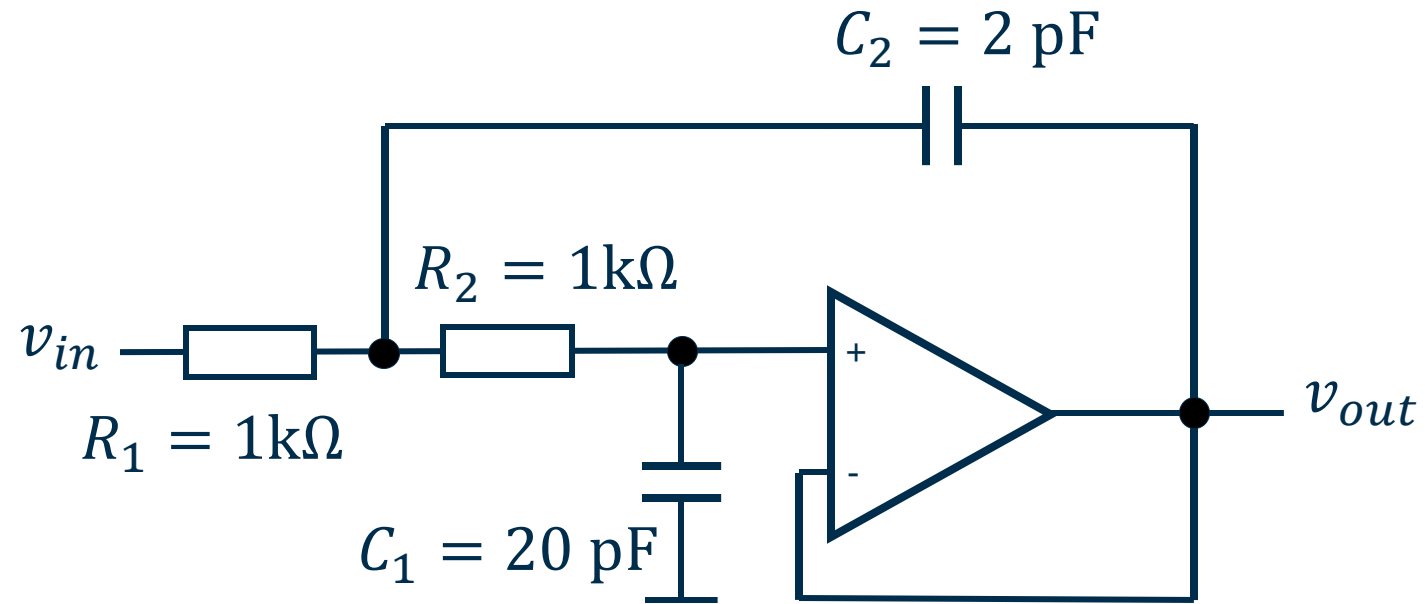

$$R_2 R_1 C_2 C_1 = 40\text{ ns}^2 = \frac{1}{\omega_0^2} \rightarrow f_0 = 25\text{ MHz}$$


Sallen-Key Filter

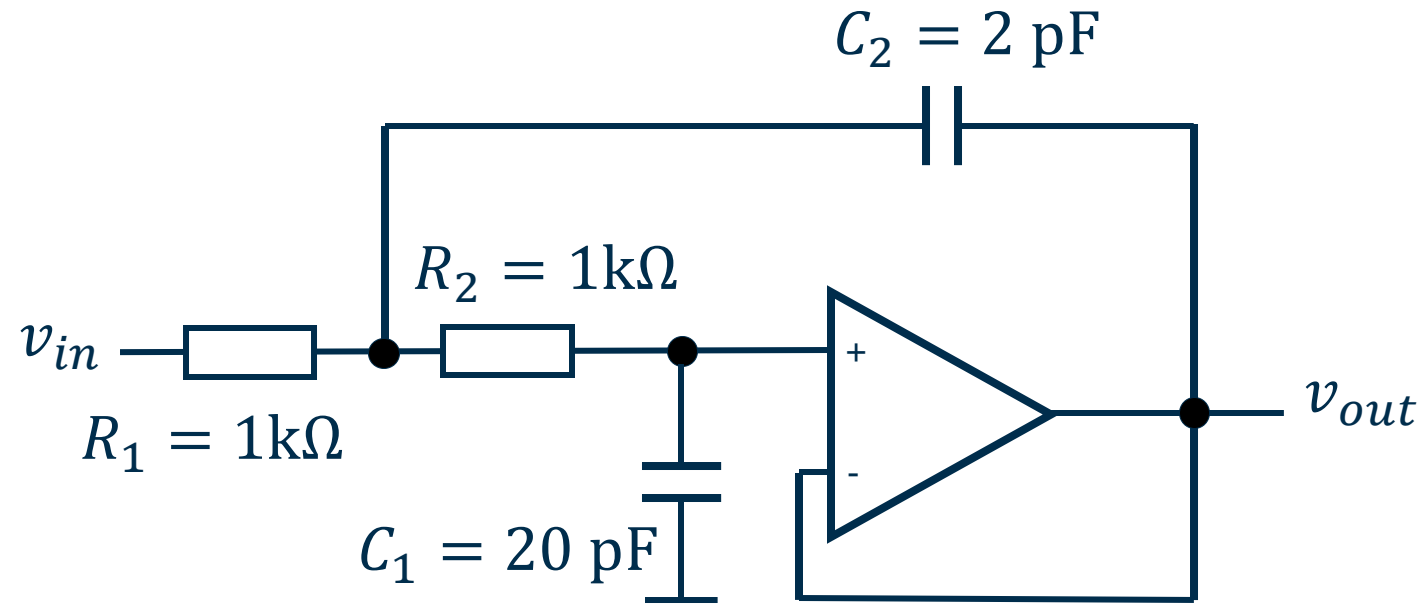

$$R_2 R_1 C_2 C_1 \rightarrow f_0 = 25\text{ MHz}$$

$$(R_1 + R_2) C_1 = b = 40\text{ ns} \rightarrow f_{3dB} \cong 3.98\text{ MHz (in case of a dominant pole)}$$

Sallen-Key Filter

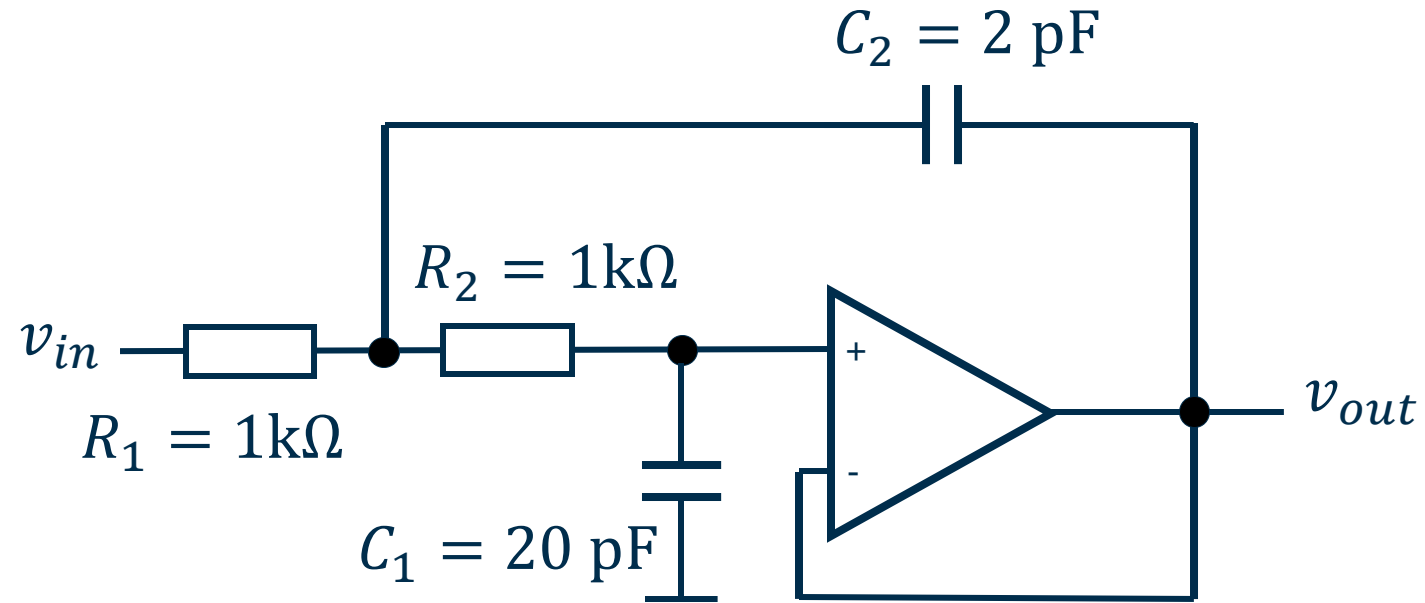


$$R_2 R_1 C_2 C_1 \rightarrow f_0 = 25 \text{ MHz}$$

$$(R_1 + R_2) C_1 = b = 40 \text{ ns} \rightarrow f_{3dB} \cong 3.98 \text{ MHz}$$

$$\tau_2 = C_2 (R_1 \parallel R_2) = 1 \text{ ns} \rightarrow \text{second pole around } 160 \text{ MHz}$$

Sallen-Key Filter


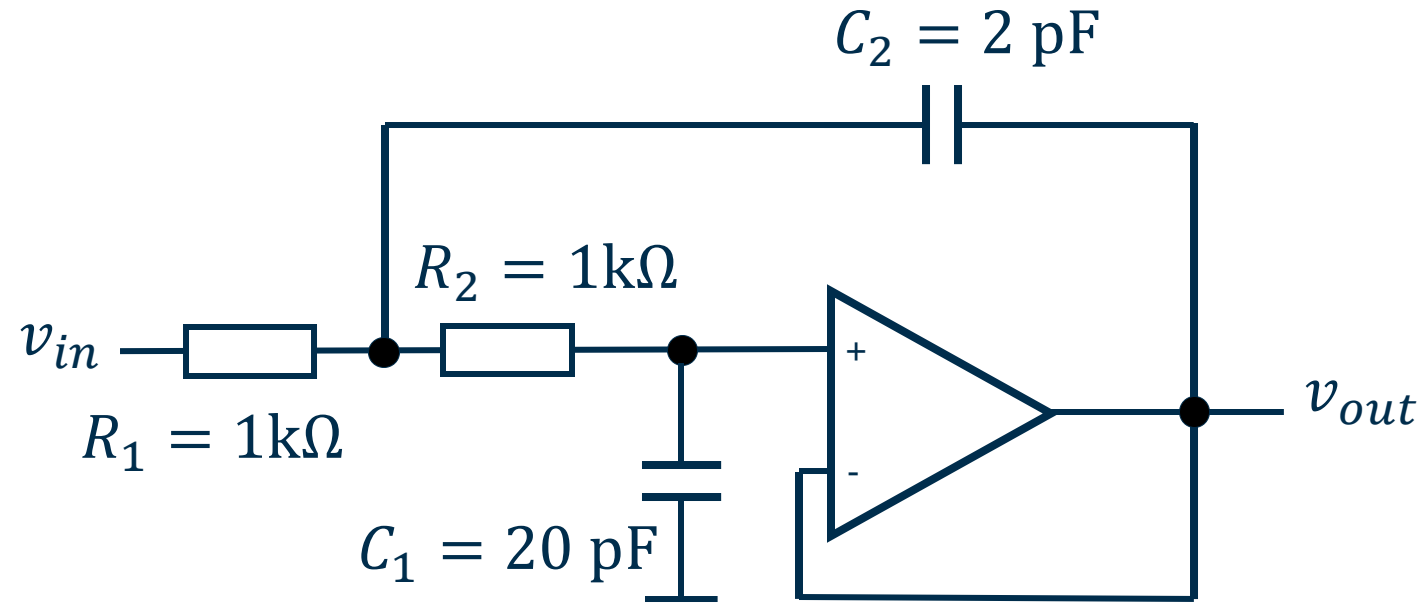


$$R_2 R_1 C_2 C_1 \rightarrow f_0 = 25\text{ MHz}$$


$$R_1 C_1 + R_2 C_1 \rightarrow f_{3dB} \cong 3.98\text{ MHz}$$

$$\frac{R_1 C_1 + R_2 C_1}{R_2 R_1 C_2 C_1} = 1\text{ Gs} = \frac{\omega_0}{Q} \rightarrow Q = 0.156 \rightarrow \zeta = 12.7$$


Sallen-Key Filter ($C_2 = 2 \text{ pF}$)

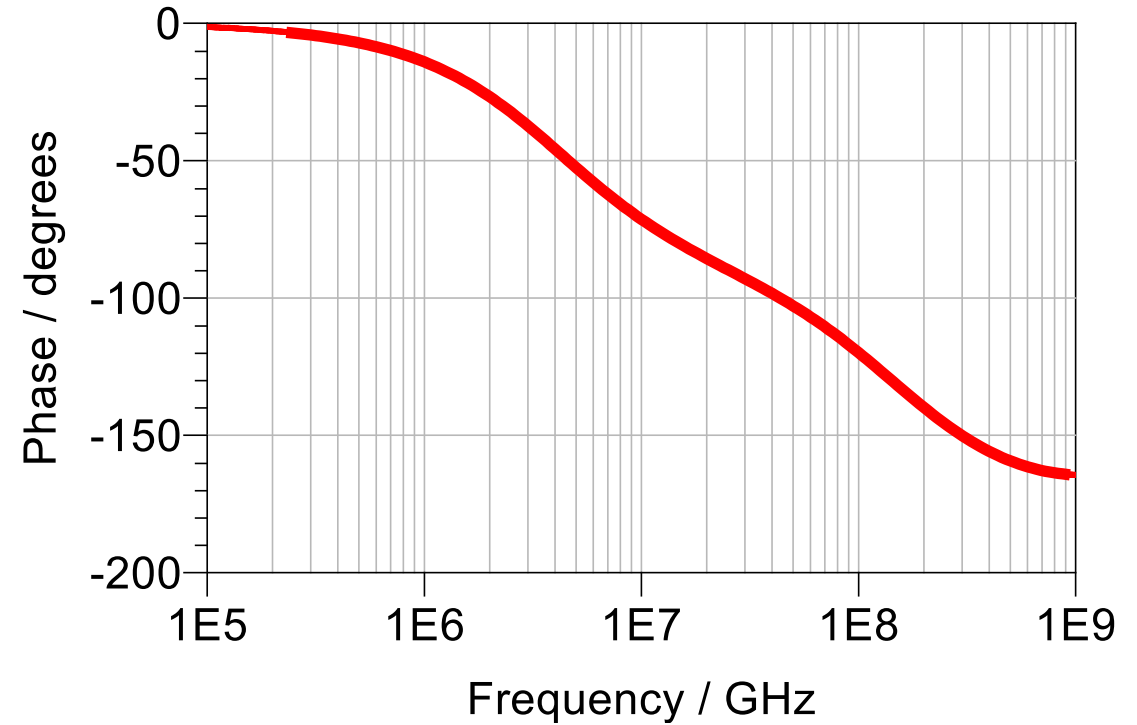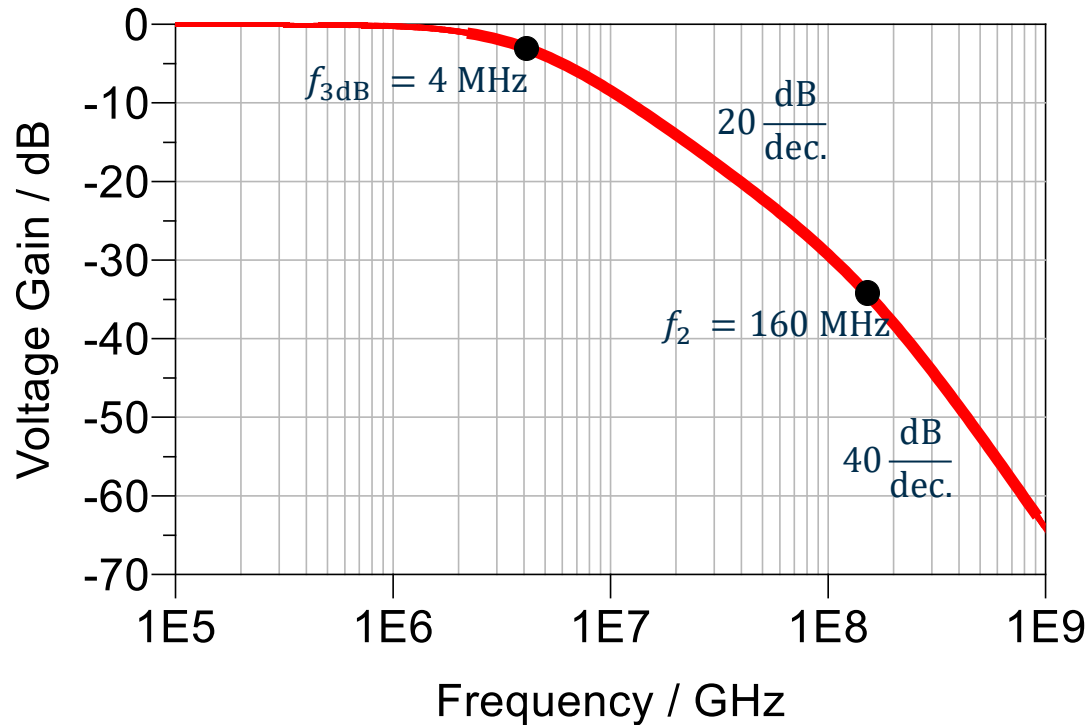

Sallen-Key Filter ($C_2 = 2 \text{ pF}$)

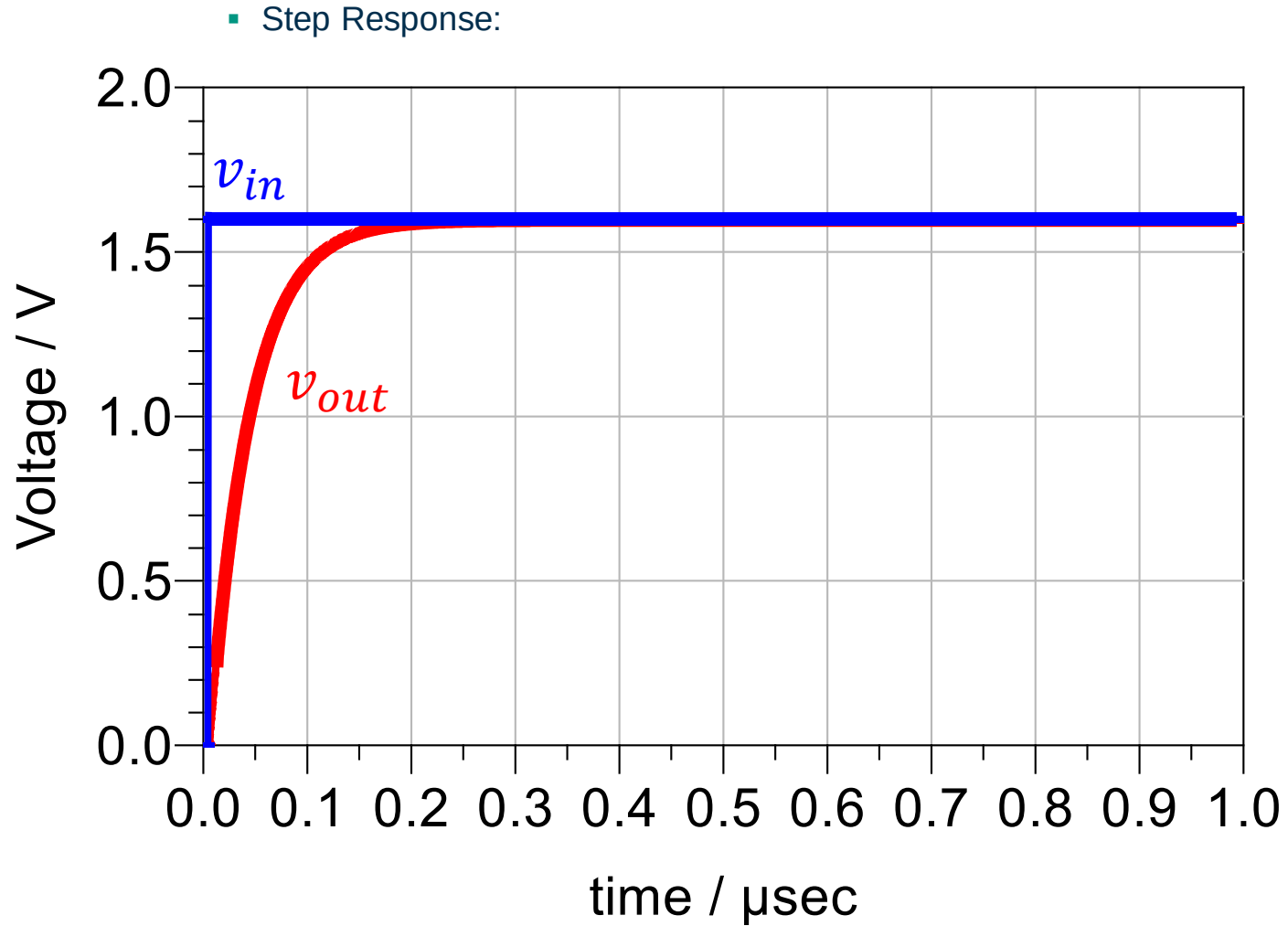

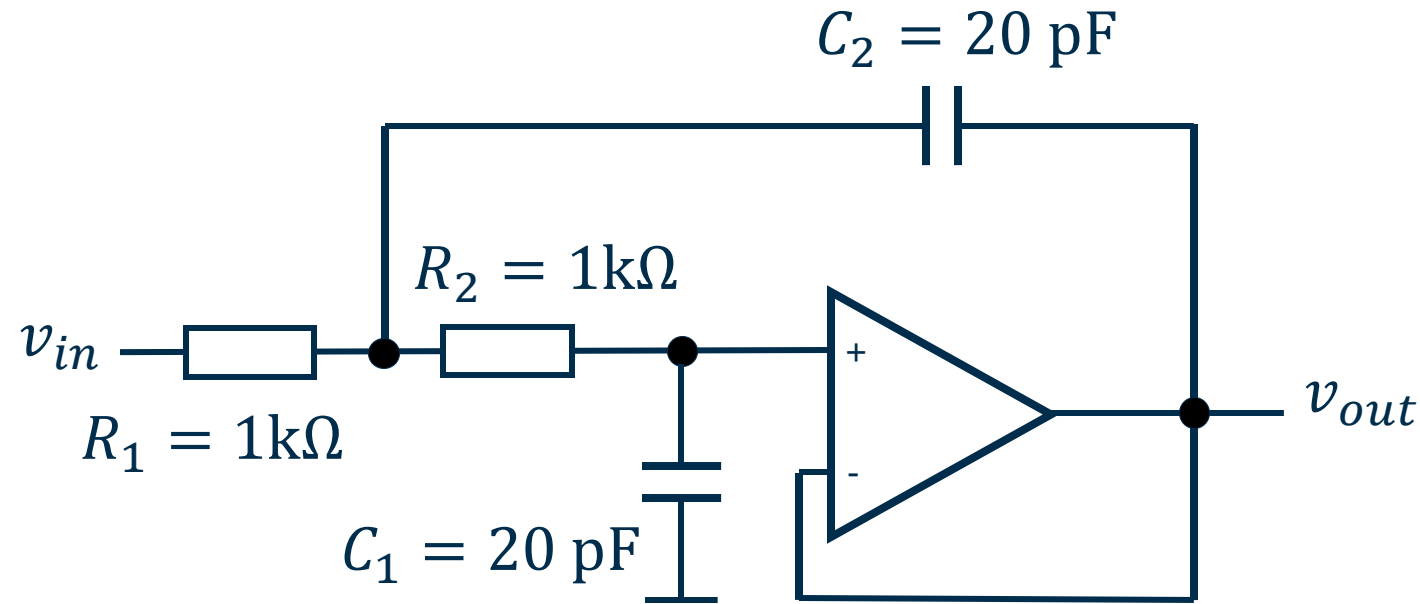Sallen-Key Filter ($C_2 = 20 \text{ pF}$)





$$R_2 R_1 C_2 C_1 = 4.0 \times 10^{-16} \text{ s} \rightarrow \omega_0 = 50 \text{ MHz} \rightarrow 7.9 \text{ MHz}$$

$$R_1 C_1 + R_2 C_1 = 40 \text{ ns} \rightarrow f_{3dB} \neq 3.98 \text{ MHz}$$

$$\frac{R_1 C_1 + R_2 C_1}{R_2 R_1 C_2 C_1} \rightarrow Q \sim 0.5 \rightarrow \zeta \sim 1$$

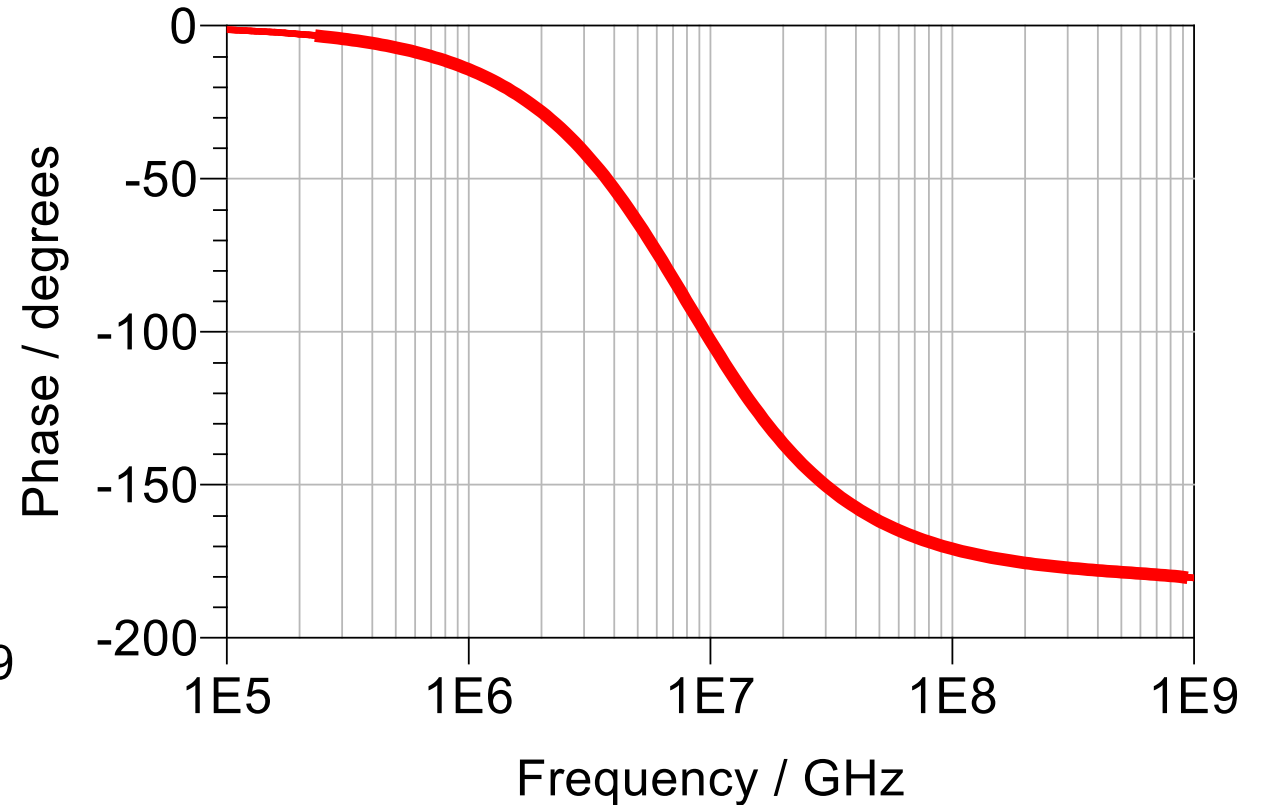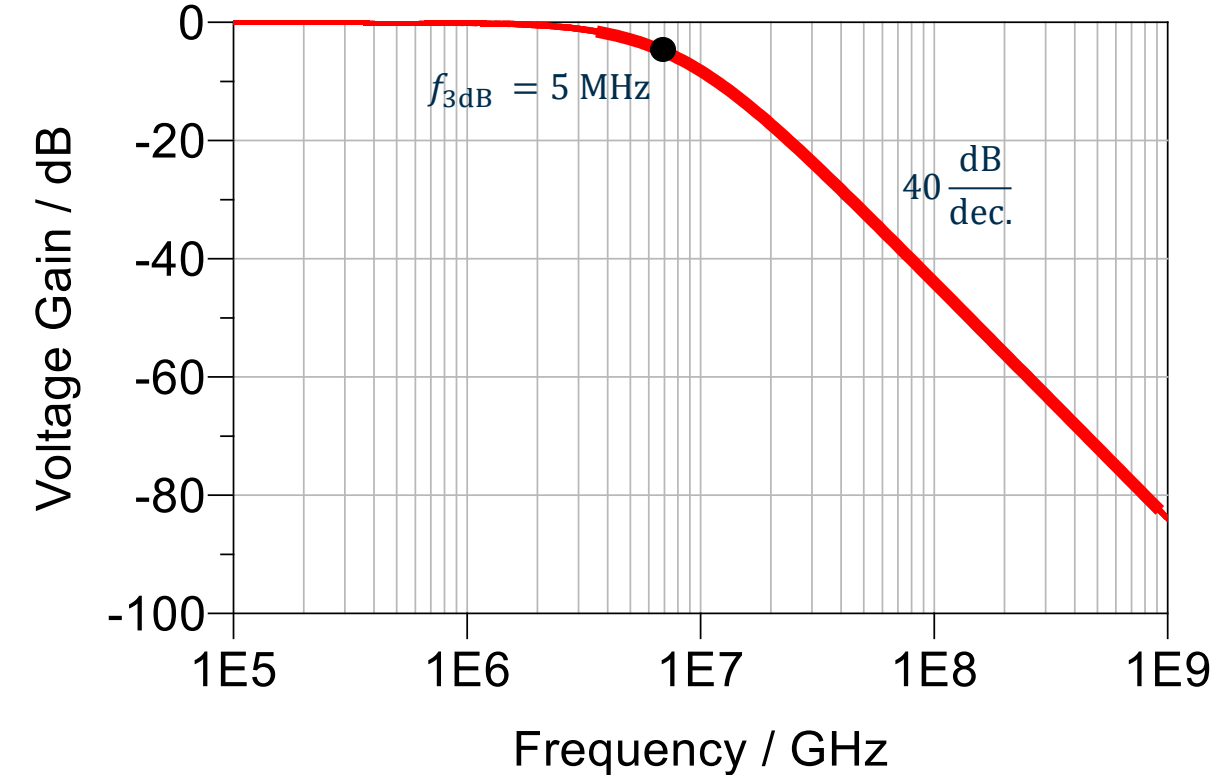Sallen-Key Filter ($C_2 = 20 \text{ pF}$)



Sallen-Key Filter ($C_2 = 20 \text{ pF}$)

- We reexamine the second-order transfer function

$$H(s) = \frac{\omega_0^2}{s^2 + 2\zeta\omega_0s + \omega_0^2}$$

- If we calculate the magnitude and derive the frequency, where the magnitude is reduced by $1/\sqrt{2}$, we find:

$$\omega_{3dB} = \omega_0 \sqrt{1 - 2\zeta^2 + \sqrt{(2\zeta^2 - 1)^2 + 1}}$$

- This is only relevant for ζ approaching 1 or lower, for all cases, dominant pole approximation holds

Sallen-Key Filter ($C_2 = 20 \text{ pF}$)

- We reexamine the second-order transfer function

$$H(s) = \frac{\omega_0^2}{s^2 + 2\zeta\omega_0s + \omega_0^2}$$


- If we calculate the magnitude and derive the frequency, where the magnitude is reduced by $1/\sqrt{2}$, we find:

$$\omega_{3dB} = \omega_0 \sqrt{1 - 2\zeta^2 + \sqrt{(2\zeta^2 - 1)^2 + 1}}$$


- For $\zeta = 1 \rightarrow \omega_{3dB} = 0.64\omega_0 \rightarrow f_0 = 5.05 \text{ MHz}$

Sallen-Key Filter ($C_2 = 20 \text{ pF}$)

■ Step Response:

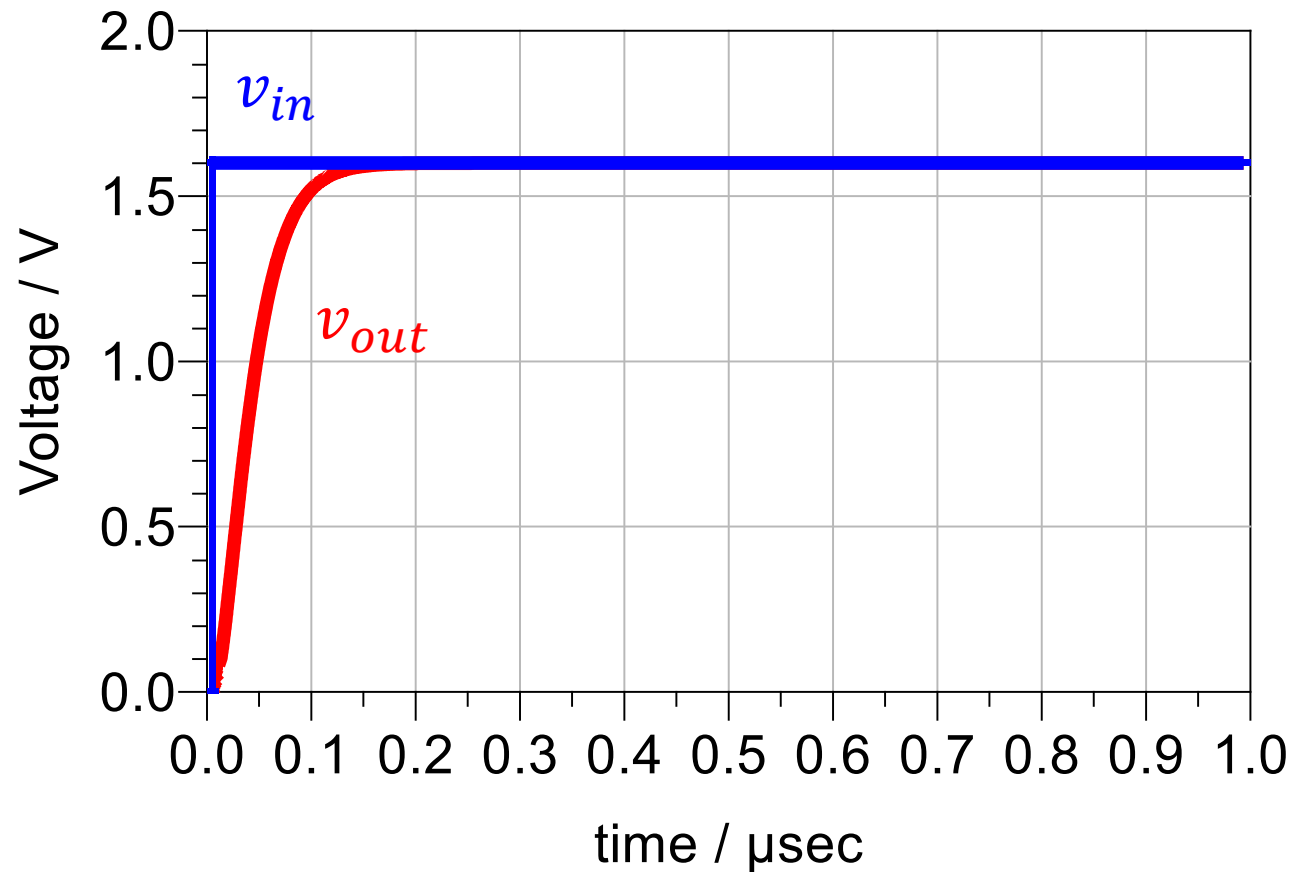

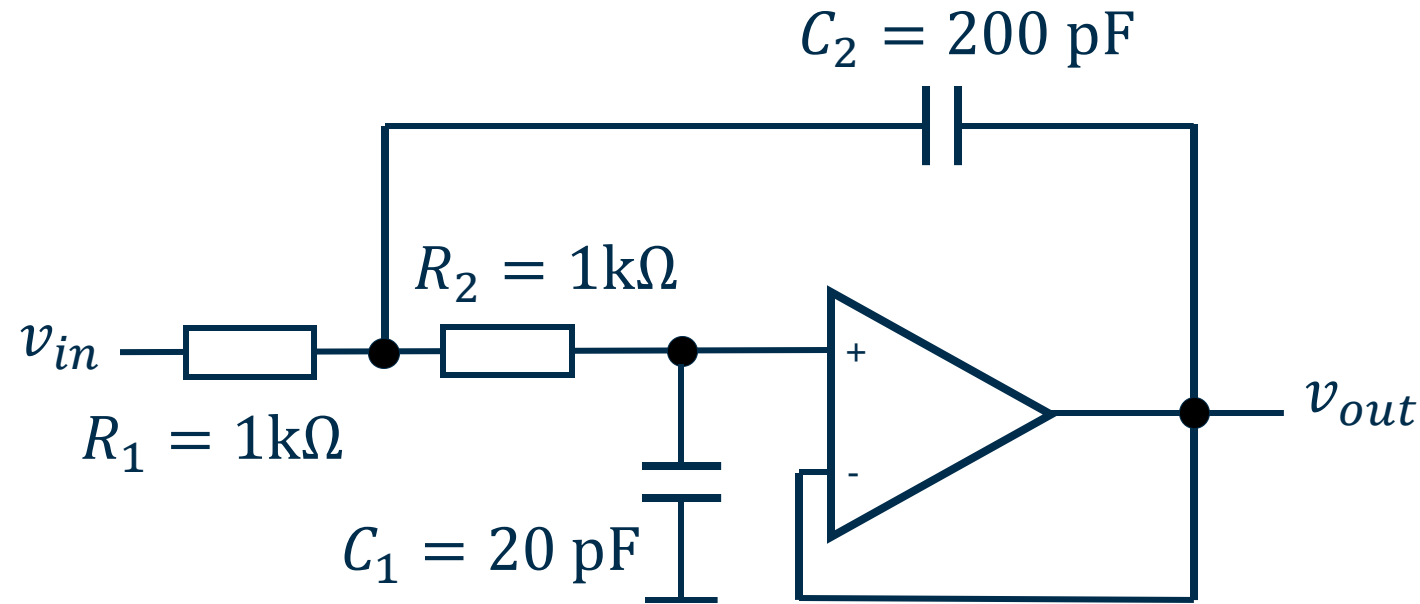Sallen-Key Filter ($C_2 = 200 \text{ pF}$)





$$R_2 R_1 C_2 C_1 = 4.0 \times 10^{-15} \text{ s} \rightarrow \omega_0 = 15 \text{ MHz} \rightarrow f_0 = 2.5 \text{ MHz}$$


$$\omega_{3dB} = 1.26 \omega_0 \rightarrow f_0 = 3.15 \text{ MHz}$$

$$\frac{R_1 C_1 + R_2 C_1}{R_2 R_1 C_2 C_1} \rightarrow Q = 1.5 \rightarrow \zeta = 0.33$$

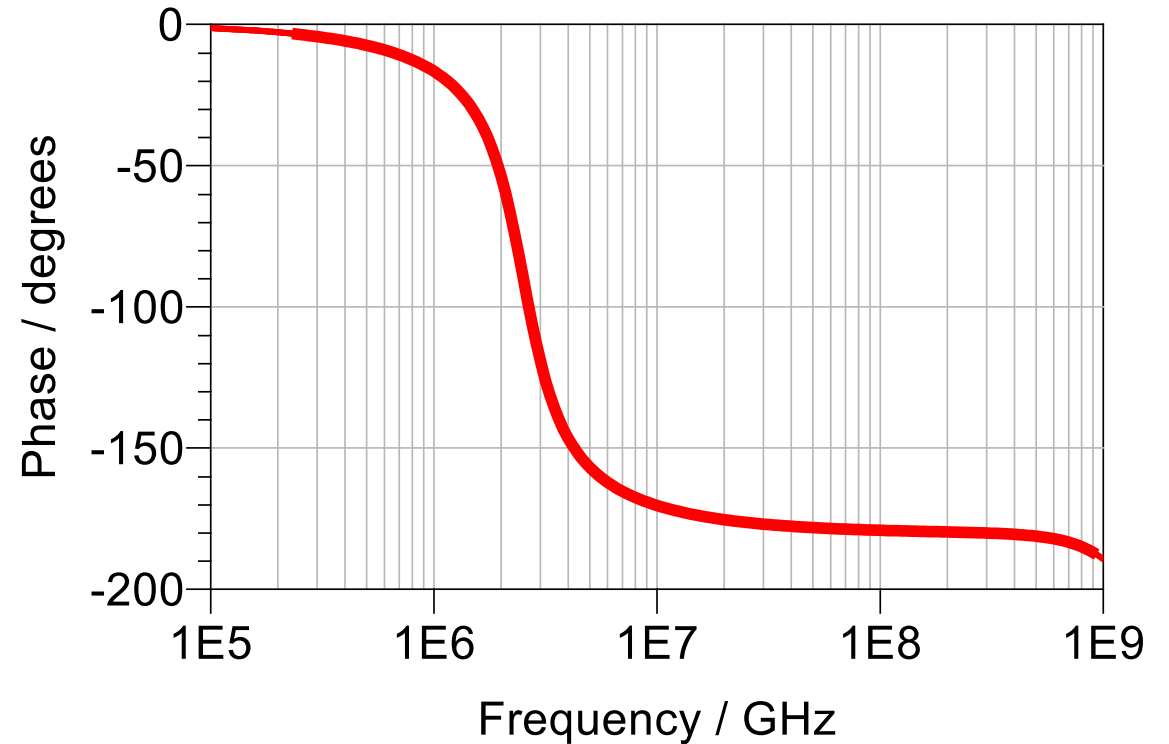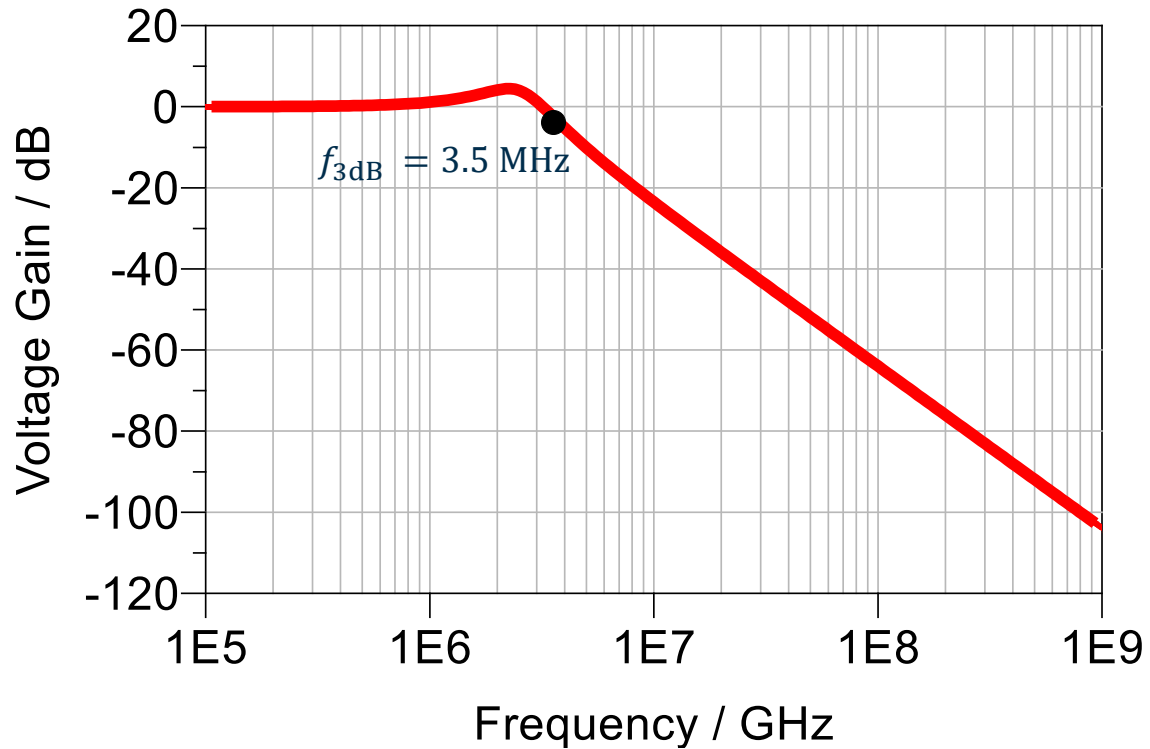Sallen-Key Filter ($C_2 = 200 \text{ pF}$)



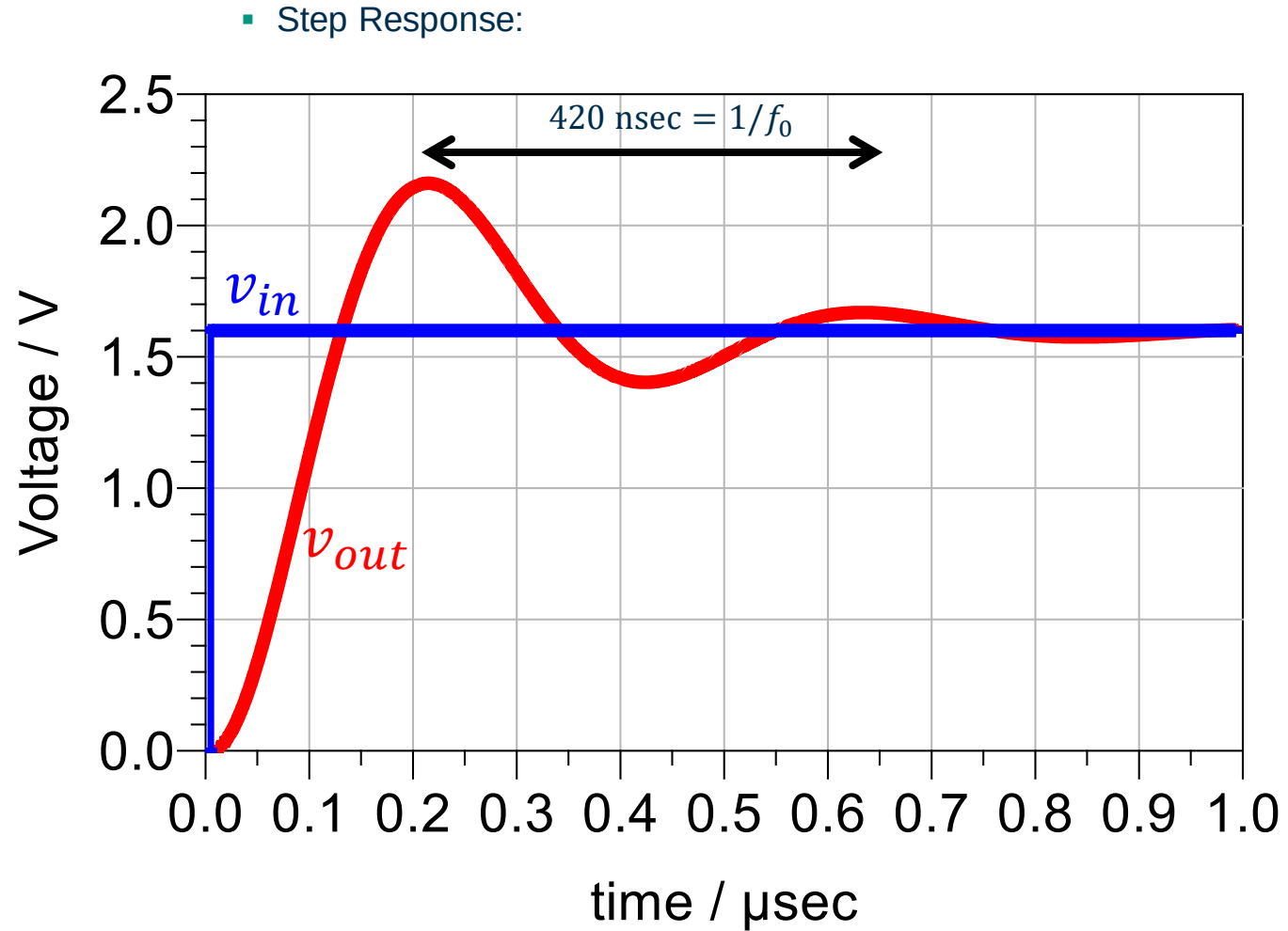Sallen-Key Filter ($C_2 = 200 \text{ pF}$)



2nd Order Response and Stability

- As seen, the interaction between poles (reactive components) in the circuit can lead to a second order response that can lead to an indirect relation of the 3-dB bandwidth, and ringing in the transient response
- This may sometimes be desired (e.g. Cherry-Hooper), but in other times is an undesired effect
- The complex conjugate root pair was so far assumed to have a negative real part, resulting in an exponentially decaying oscillatory behavior
- If the complex conjugate roots have positive real part, the oscillatory behavior will be exponentially growing → instability!
- Therefore, it is important to introduce a methodology that can spread the poles apart in a circuit, to avoid 2nd order ringing or unstable behavior

2nd Order Response and Stability

- For stability analysis, the previously introduced “Loop Gain” is the critical quantity we need to investigate

$$\frac{v_{out}}{v_{in}} = \frac{A(j\omega)}{1 + A(j\omega)F(j\omega)}$$

- For $|A(j\omega)F(j\omega)| = 1$ and $\angle A(j\omega)F(j\omega) = n180^\circ$, the denominator of the closed loop transfer function goes to zero, resulting in infinite voltage amplification → unstable behavior (Barkhausen Criteria)
- This indicates, we can assess stability of an amplifier examining the steady-state response of the Loop Gain!

2nd Order Response and Stability

- To understand how closed loop gain is affected by feedback, we will consider a second order $A(s)$ and a constant F

$$A(s) = \frac{A_0}{\left(1 + \frac{s}{\omega_{p1}}\right)\left(1 + \frac{s}{\omega_{p2}}\right)}$$

- The closed loop transfer function will be:

$$H(s) = \frac{A_0 \omega_{p1} \omega_{p2}}{s^2 + (\omega_{p1} + \omega_{p2})s + (1 + A_0 F) \omega_{p1} \omega_{p2}}$$

- with the roots


$$s_{1,2} = \frac{-(\omega_{p1} + \omega_{p2}) \mp \sqrt{(\omega_{p1} + \omega_{p2})^2 - 4(1 + A_0 F) \omega_{p1} \omega_{p2}}}{2}$$

2nd Order Response and Stability

- With no feedback ($F = 0$), the roots will be $-\omega_{p1}$ and $-\omega_{p2}$
- As, the feedback amount is increase ($F \nearrow$), the term under square-root decreases, reaching zero for critical value (having two equal real roots)

$$F_C = \frac{1}{A_0} \frac{(\omega_{p1} - \omega_{p2})^2}{4\omega_{p1}\omega_{p2}}$$

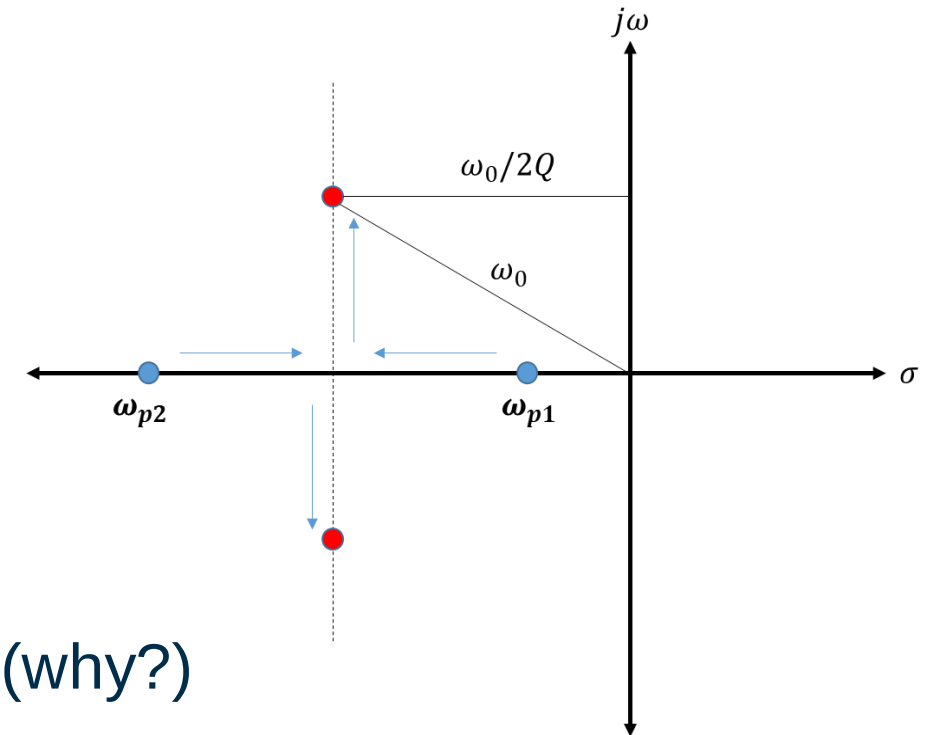
- Becoming complex conjugate beyond this point if F is further increased
- This is the process we have observed in the Sallen-Key circuit
- A second-order amplifier cannot become unstable (why?)



Stability and Loop Gain


- Let's examine a third-order OPAMP with poles at 100 kHz, 500 kHz and at 500 MHz

- open loop:

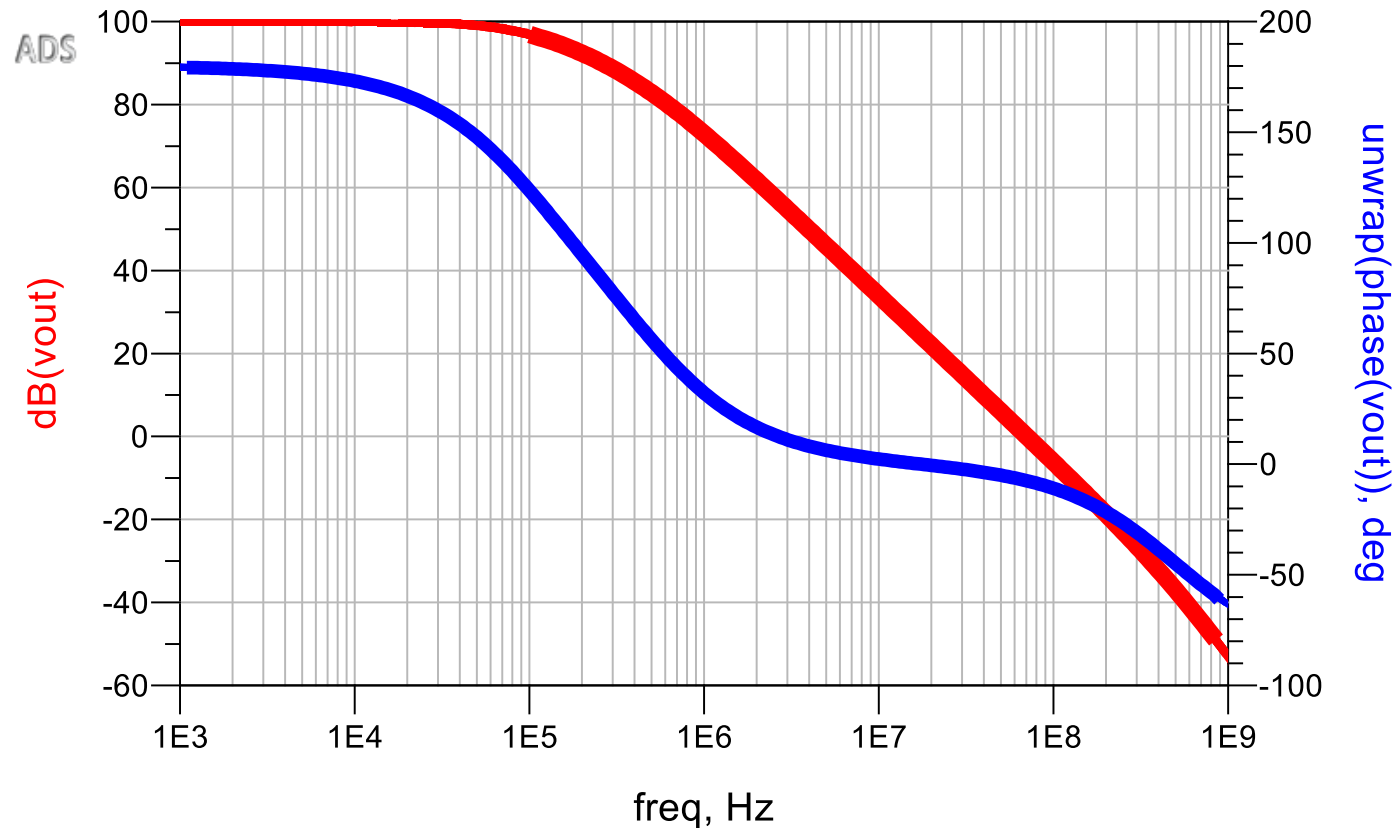

Stability and Loop Gain

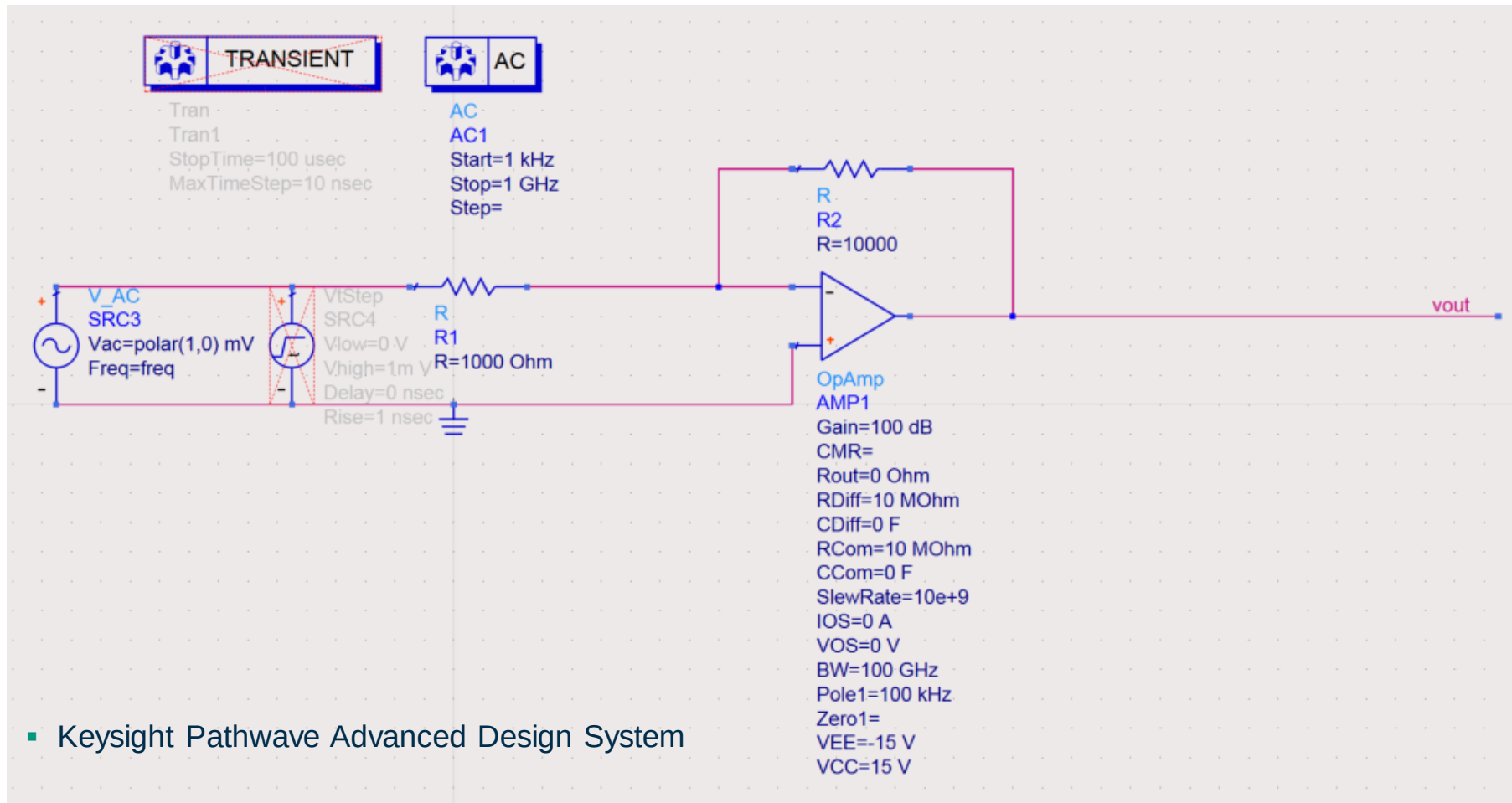
- Now, we build a feedback amplifier with a gain of 20 dB using this OPAMP



- Keysight Pathwave Advanced Design System



Stability and Loop Gain

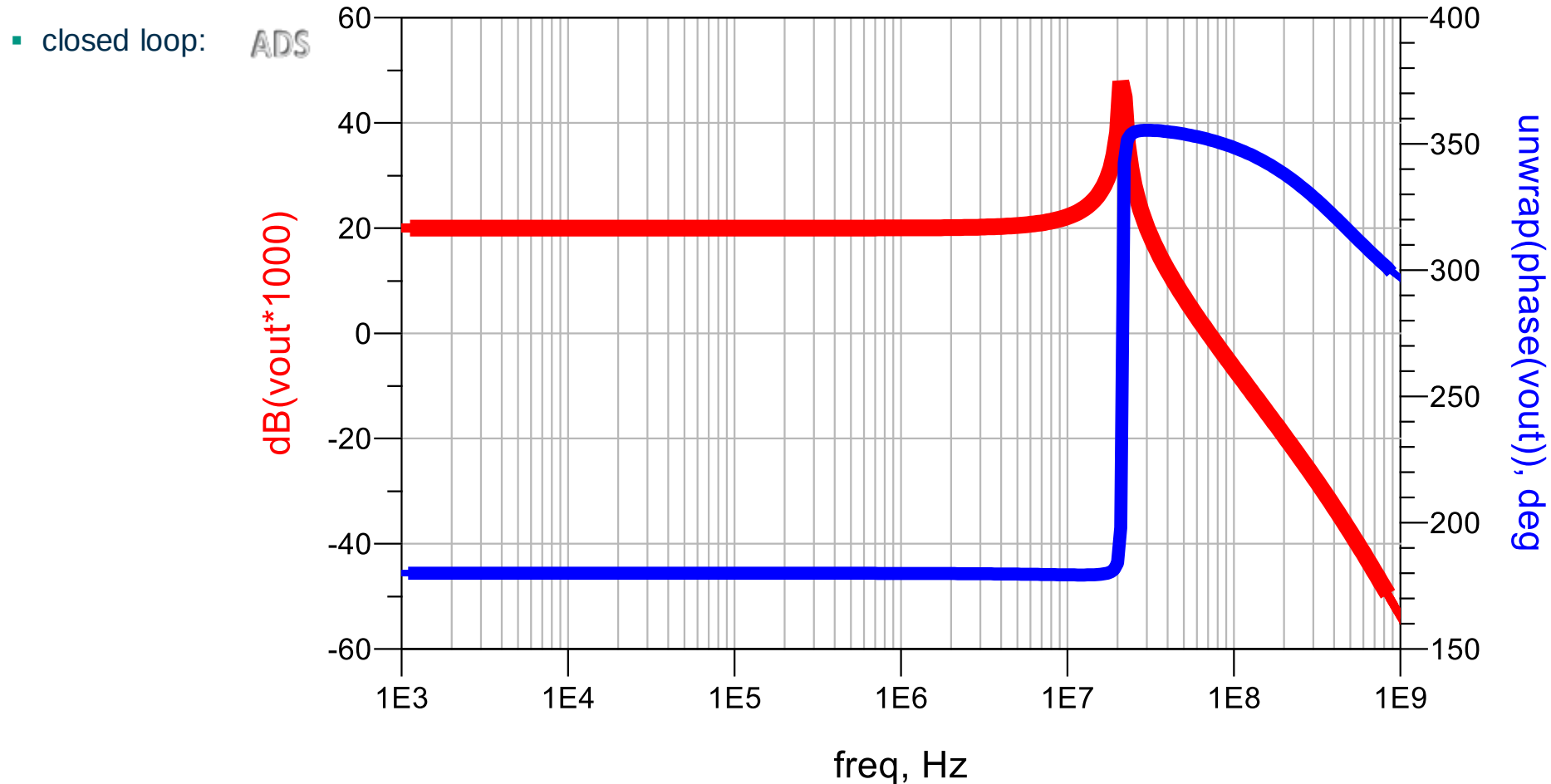- Now, we build a feedback amplifier with a gain of 20 dB, using this OPAMP



Stability and Loop Gain


■ Step Response:

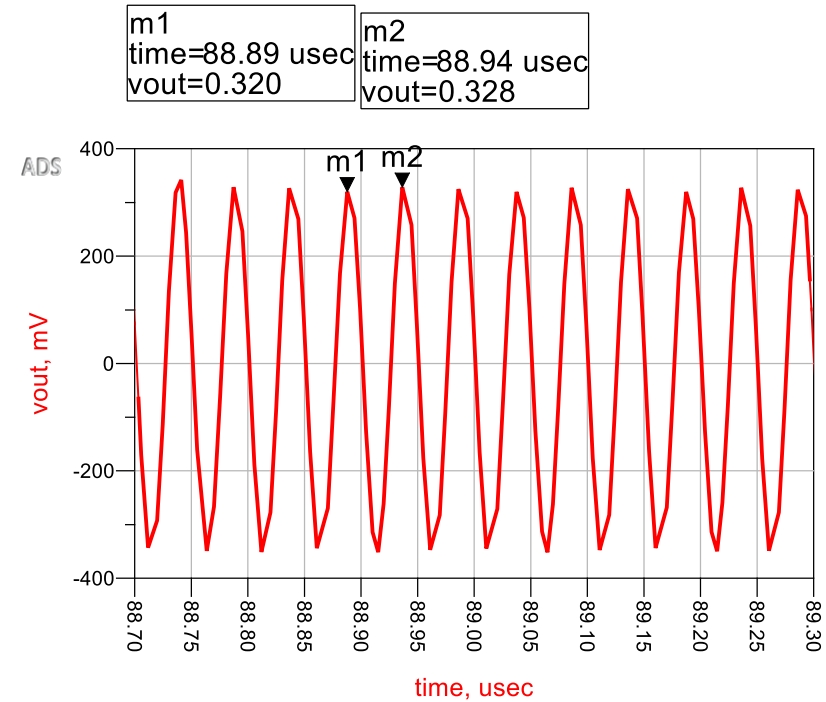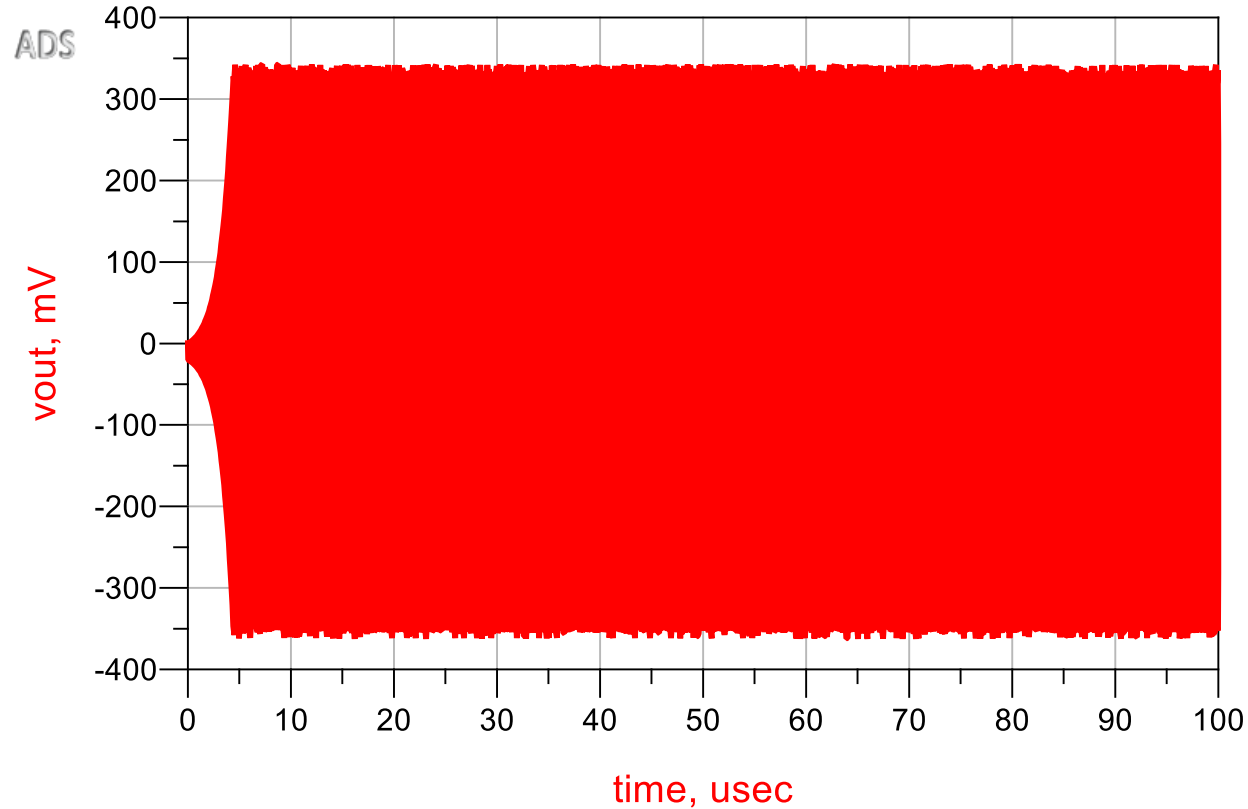

■ f_0 around 20 MHz


Stability and Loop Gain

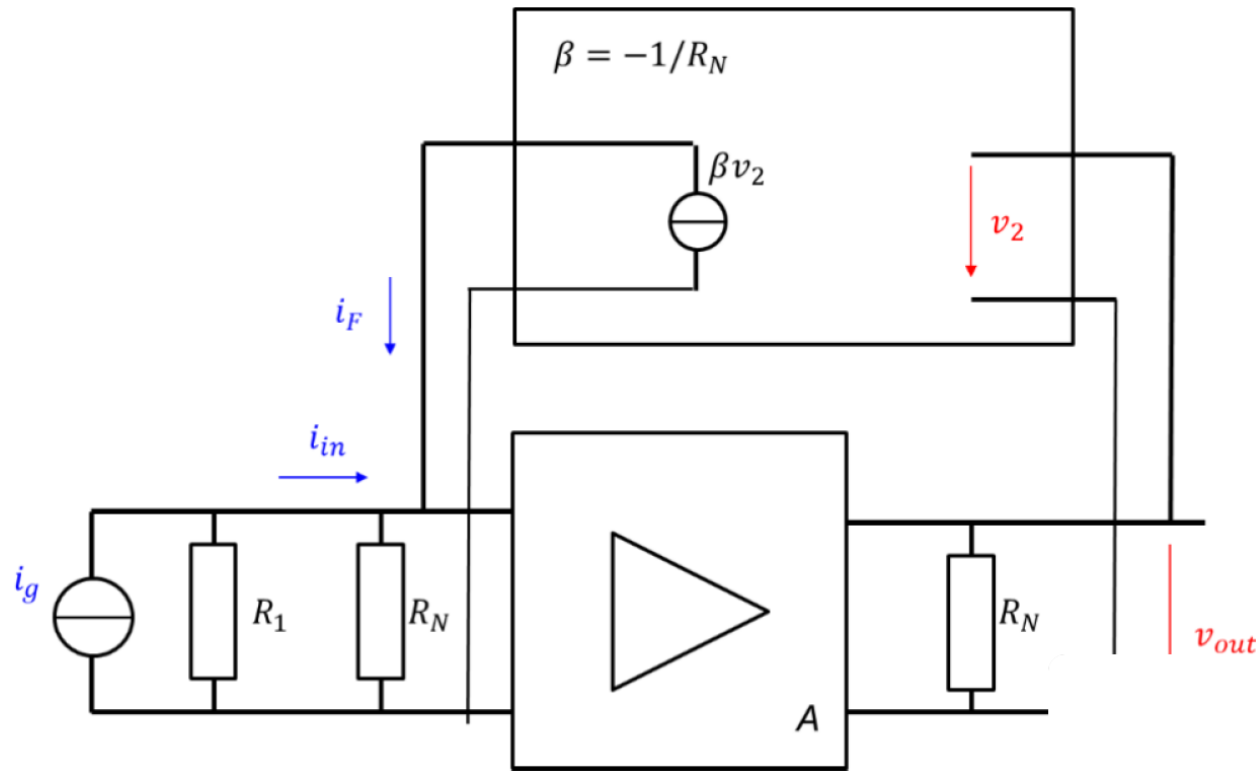- As seen, closed loop gain does not tell us necessarily whether the amplifier is stable or not, however if we examine the loop gain (here using classical method)




Stability and Loop Gain

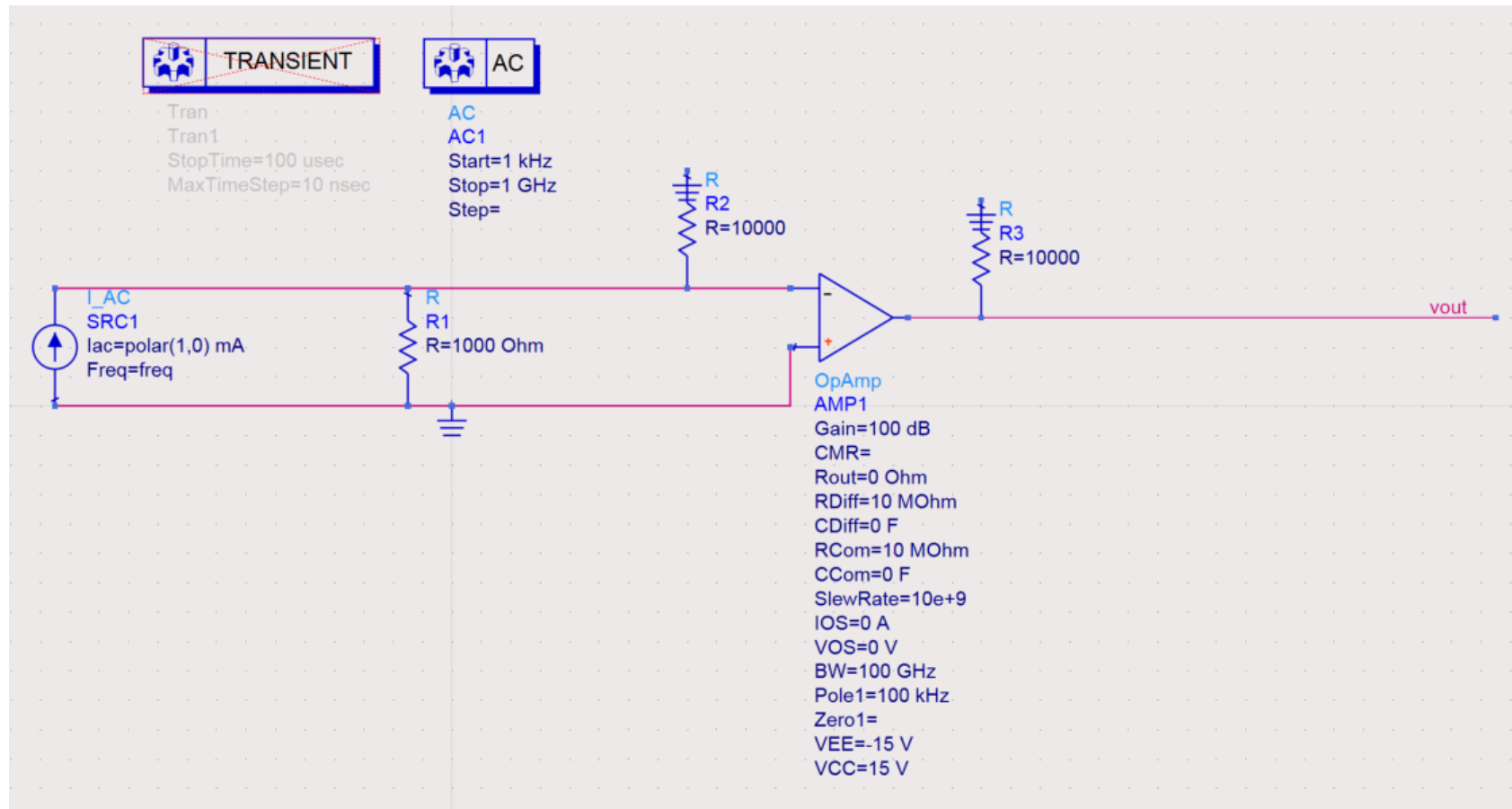- As seen, closed loop gain does not tell us necessarily whether the amplifier is stable or not, however if we examine the loop gain (here using classical method)




Stability and Loop Gain

- Loop Gain (A and F separate):

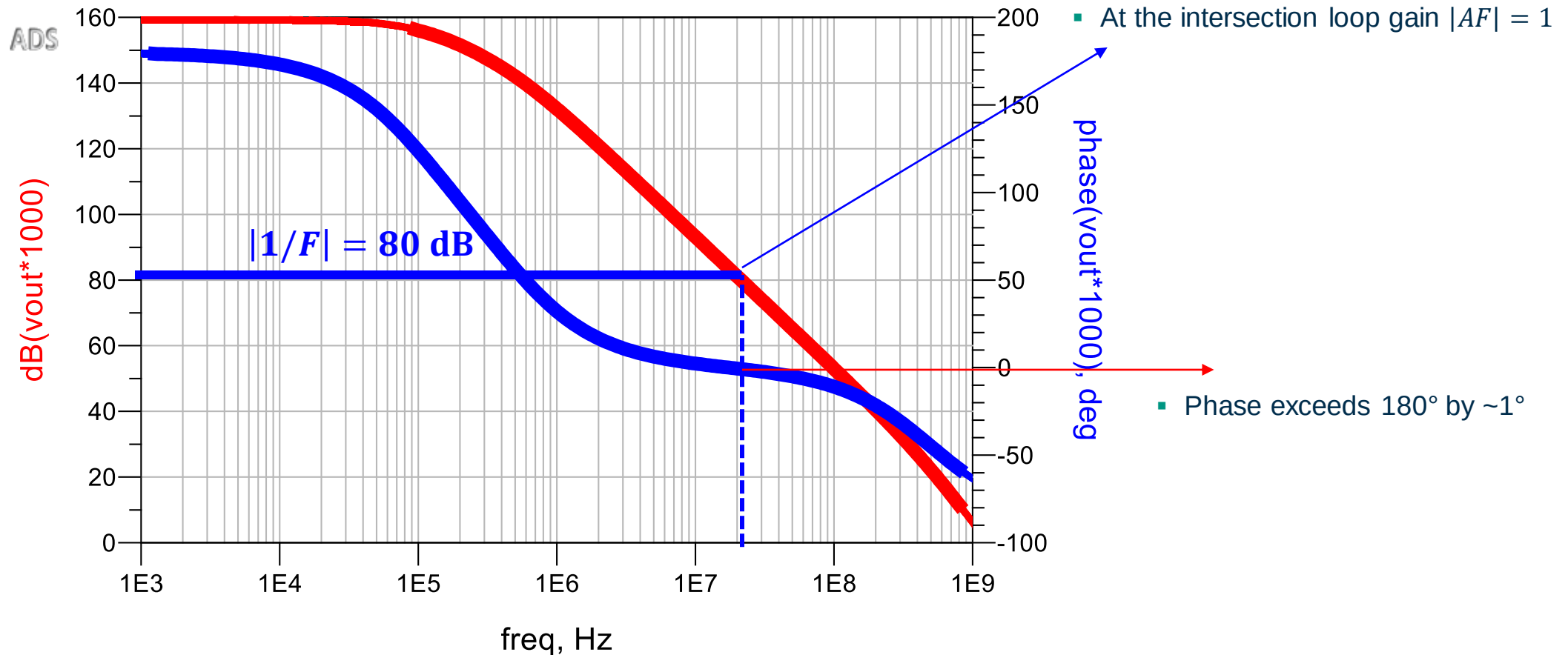


Stability and Loop Gain

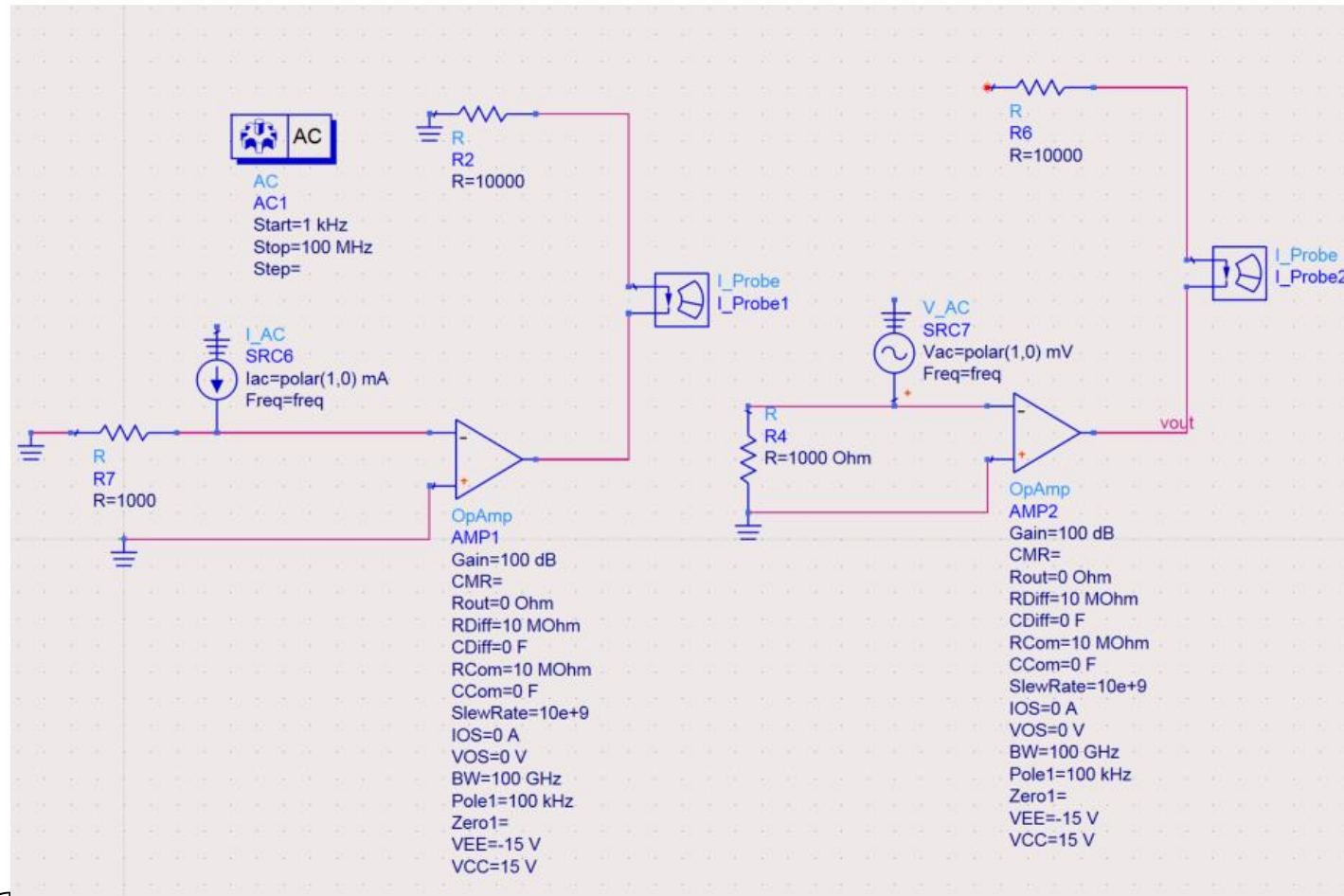- Loop gain assessed using: $\frac{1}{AF} = \frac{1}{A_{vop}} + \frac{1}{H_{os}}$




Stability and Loop Gain

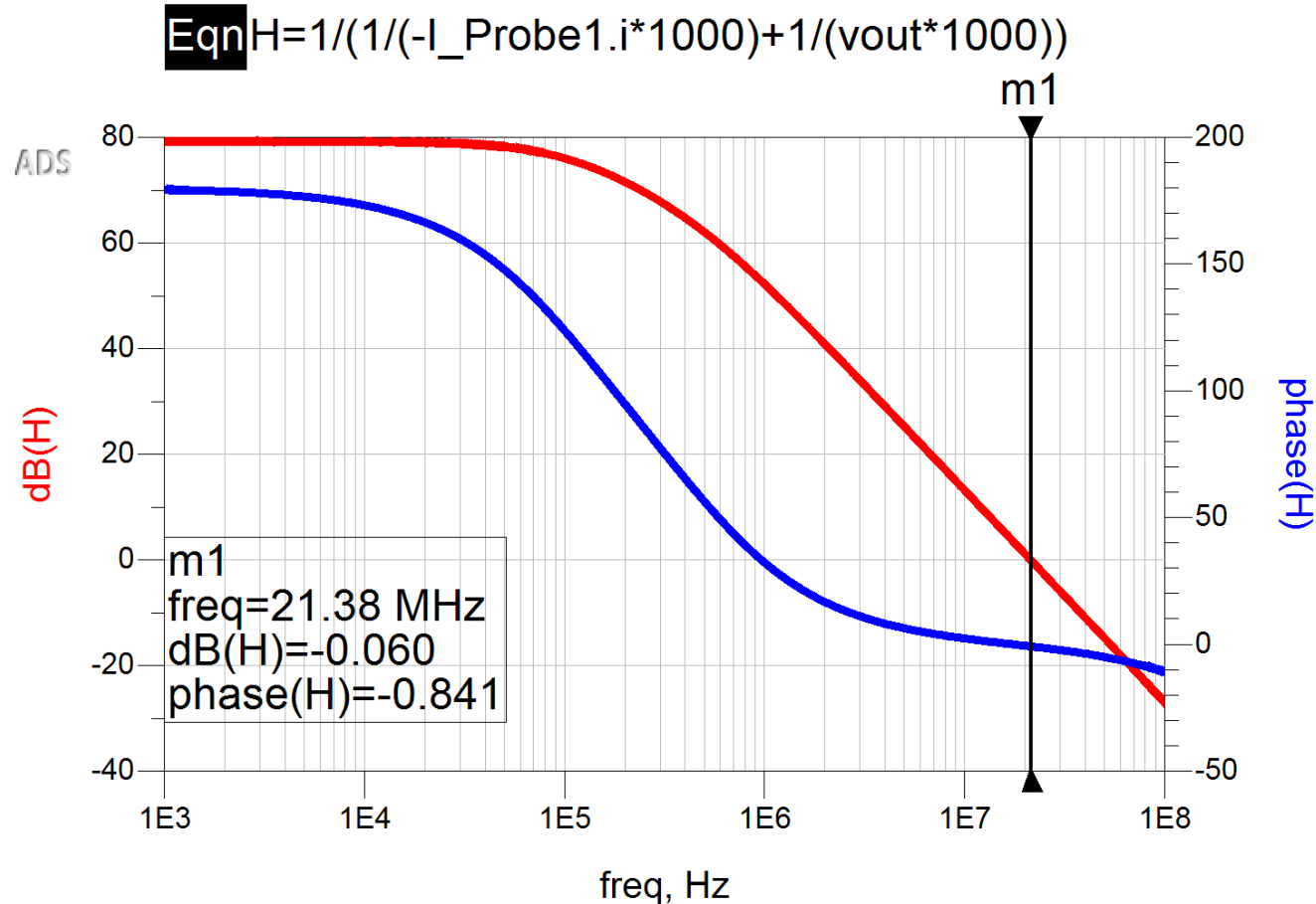- Loop gain assessed using: $\frac{1}{AF} = \frac{1}{A_{vop}} + \frac{1}{H_{os}}$



Phase Margin

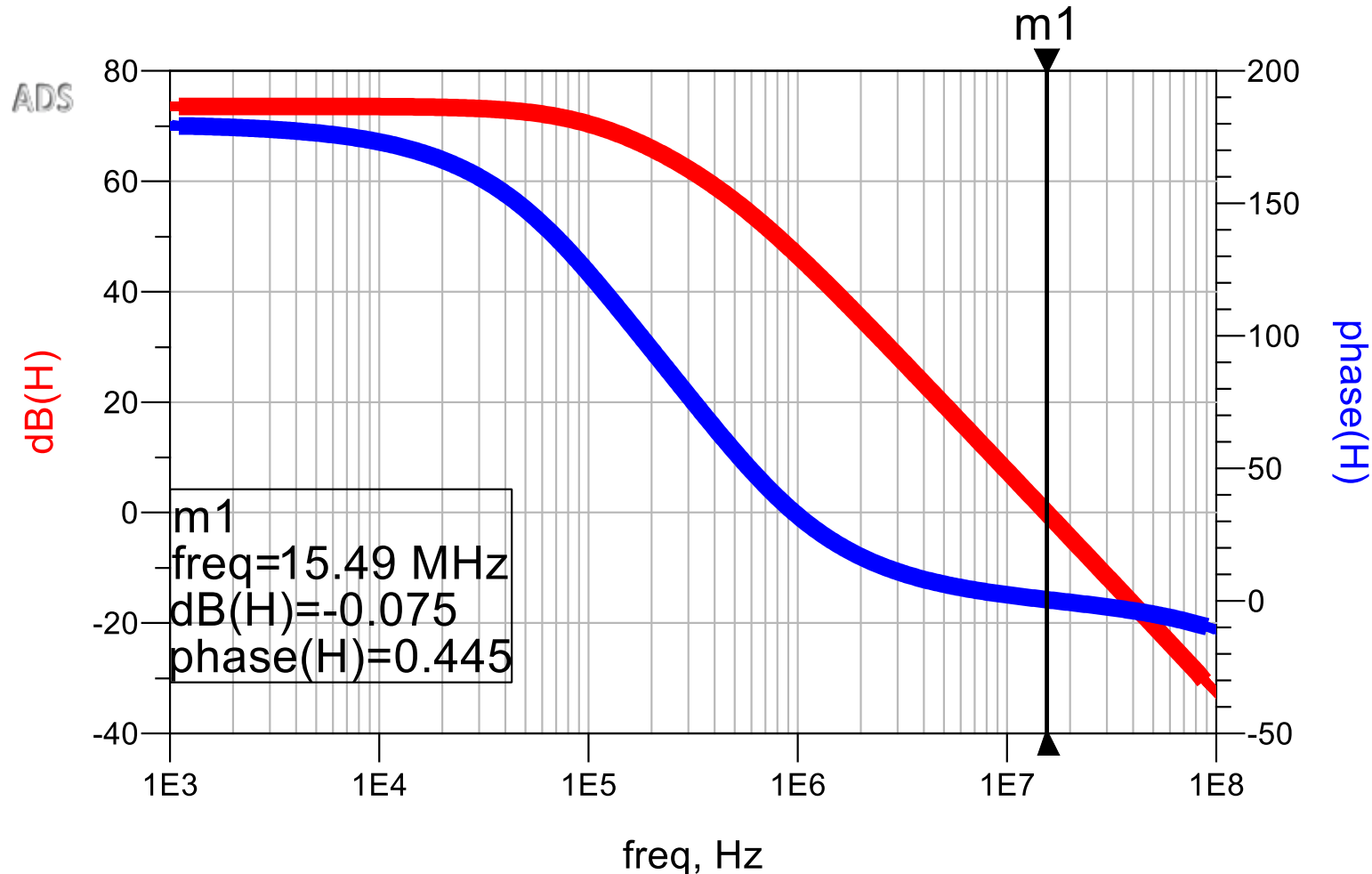
- Feedback resistance increased to 20 k Ω (less feedback, closed loop gain **increased**)



- When loop gain $|AF| = 0$ dB, the phase response is 0.5° below 180° of phase shift
- This is called the **phase margin**
- The magnitude at 180° phase shift is called the **amplitude margin**
- In this case the phase margin is only 0.5°

Phase Margin

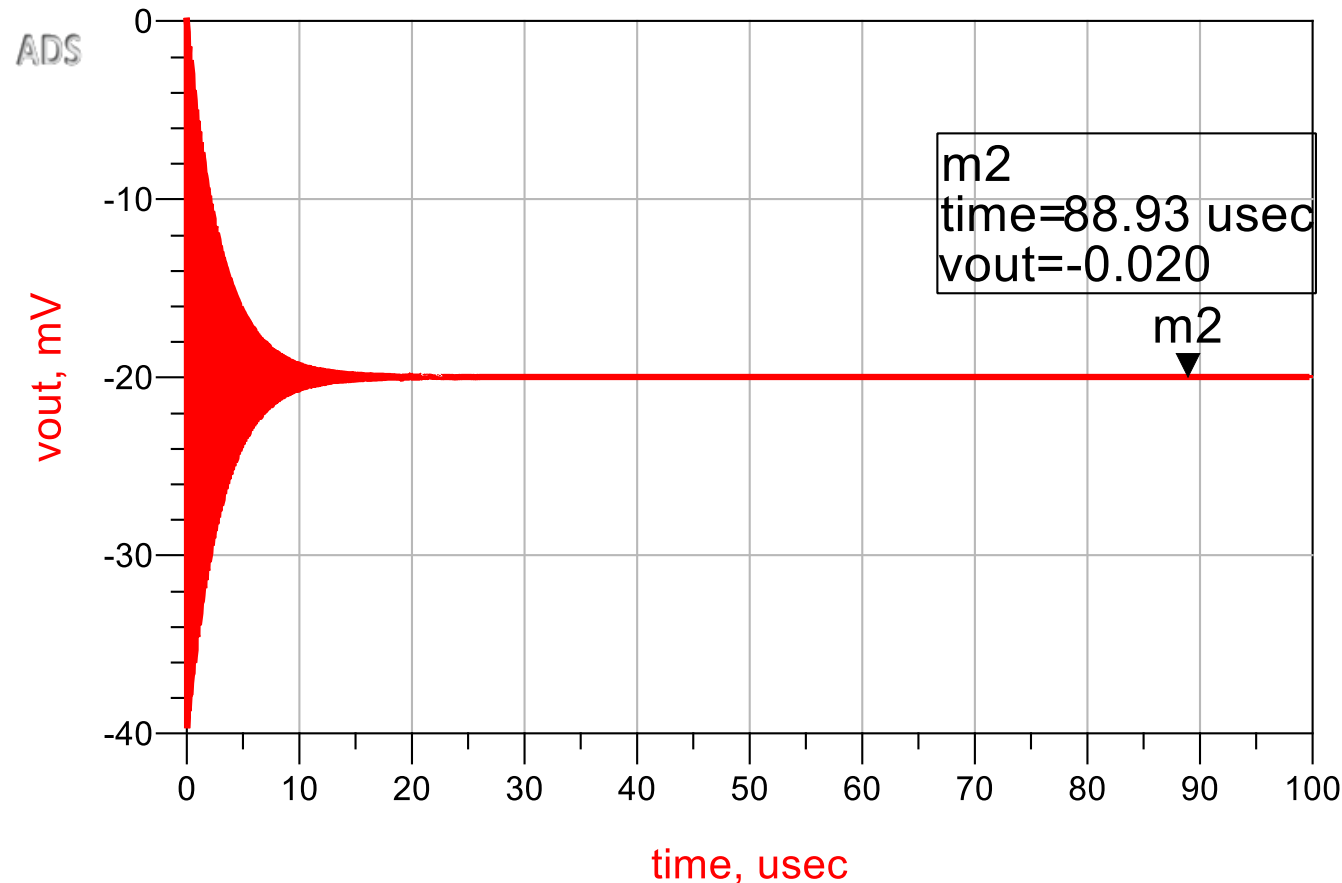- Step Response (closed loop with 20 k Ω):



- A gain of -20 as expected ($|v_{in}| = 1$ mV)
- A significant ringing response is observed, much stronger than the actual signal amplitude
- No sustained oscillation, the oscillation decays exponentially in steady state

Phase Margin

- How much phase margin is good enough?
- We observe the closed loop transfer function in the vicinity of $|A| = 1$ at frequency ω_1

$$H(j\omega_1) = \frac{A(j\omega_1)}{1 + A(j\omega_1)F}$$

Phase Margin

- An important question is, how much phase margin is good enough?
- We observe the closed loop transfer function in the vicinity of $|A| = 1$ at frequency ω_1

$$H(j\omega_1) = \frac{A(j\omega_1)}{1 + A(j\omega_1)F} \rightarrow \frac{\frac{1}{F} e^{-j179^\circ}}{1 + e^{-179^\circ}}$$

- For our example with a phase margin of 1° , $A(j\omega_1)F$, will have a magnitude of 1, and a phase of -179°

Phase Margin

- An important question is, how much phase margin is good enough?
- We observe the closed loop transfer function in the vicinity of $|A| = 1$ at frequency ω_1

$$H(j\omega_1) = \frac{A(j\omega_1)}{1 + A(j\omega_1)F} \rightarrow \frac{\frac{1}{F} e^{-j179^\circ}}{1 + e^{-179^\circ}} \rightarrow \frac{1}{F} \left(\frac{-0.997 - j0.0707}{0.003 - j0.0707} \right) \rightarrow |H| = \frac{14.1}{F}$$

- For our example with a phase margin of 1° , $A(j\omega_1)F$, will have a magnitude of 1, and a phase of -179°
- Compared to asymptotic response of $\frac{1}{F}$, we will observe a peaking of 24 dB at ω_1

Phase Margin

- An important question is, how much phase margin is good enough?
- We observe the closed loop transfer function in the vicinity of $|A| = 1$ at frequency ω_1

$$H(j\omega_1) = \frac{A(j\omega_1)}{1 + A(j\omega_1)F} \rightarrow \frac{\frac{1}{F} e^{-j179^\circ}}{1 + e^{-179^\circ}} \rightarrow \frac{1}{F} \left(\frac{-0.997 - j0.0707}{0.003 - j0.0707} \right) \rightarrow |H| = \frac{14.1}{F}$$


- For our example with a phase margin of 1° , $A(j\omega_1)F$, will have a magnitude of 1, and a phase of -179°
- Compared to asymptotic response of $\frac{1}{F}$, we will observe a peaking of 24 dB at ω_1
- At a **phase margin of 60°** , ringing behavior can be considered negligible
- At a phase margin of 45° , the peaking is around 2.2 dB, with still noticeable ringing

Frequency Compensation

- In order to increase phase margin, ideally we would like to build a circuit with as low number of poles as possible → reduce number of stages & reactive components
- If this is not possible, a typical approach would be to reduce the lowest pole frequency (making it dominant) so that the magnitude decays faster before reaching a phase shift of 180° → this means gain-bandwidth product will be lower
- In OPAMP designs this is a standard method, as typically multiple stages are required to reach sufficient gain, and frequency compensation is applied to create a dominant pole frequency

Frequency Compensation

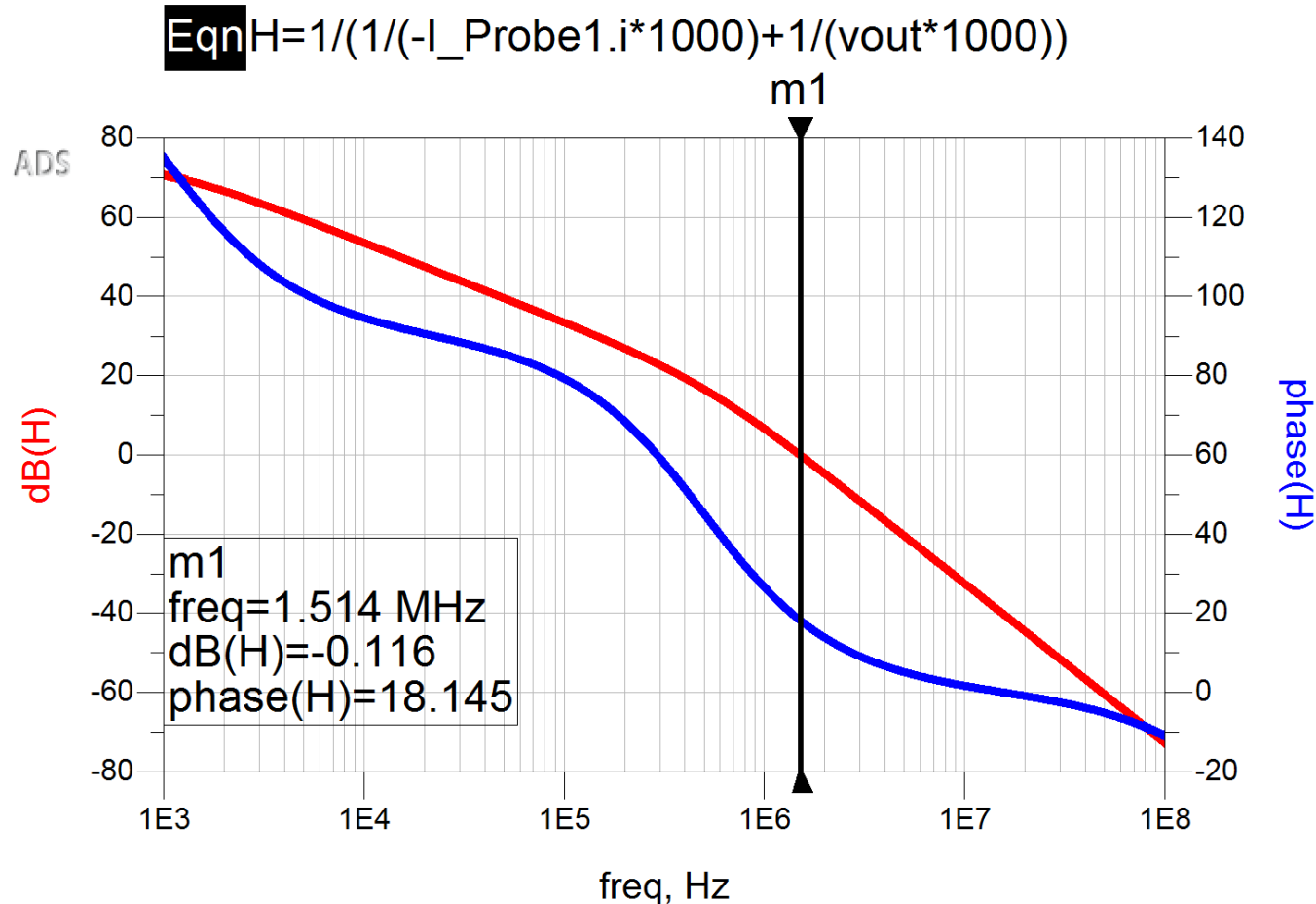
- In our previous example, first pole frequency is reduced to 1 kHz (from 100 kHz)



- In this case the phase margin is almost 20°
- How can a pole frequency be reduced?

Frequency Compensation


- In closed loop:

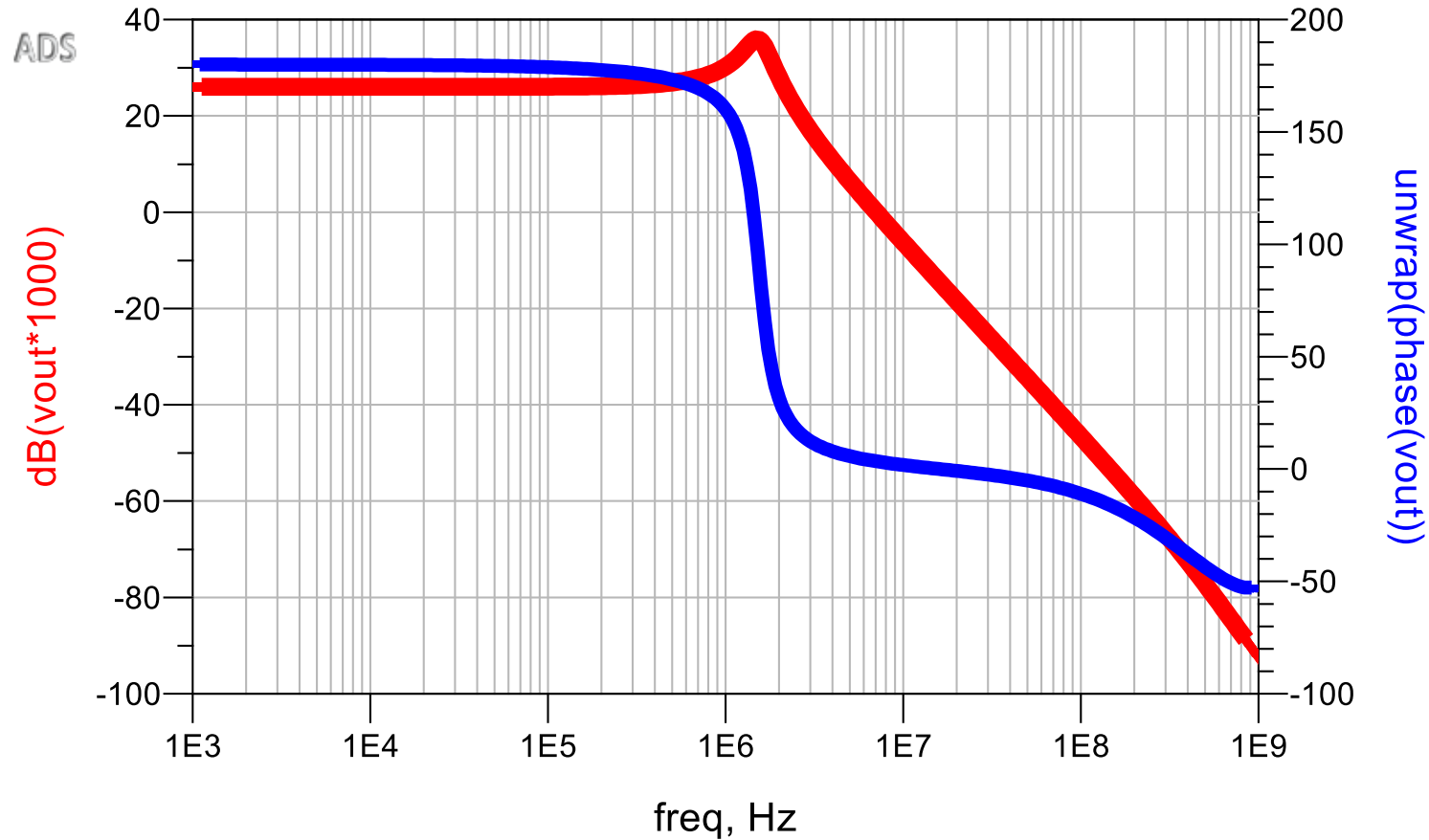

- Peaking is reduced to 9 dB


Frequency Compensation

- Ringing is reduced:

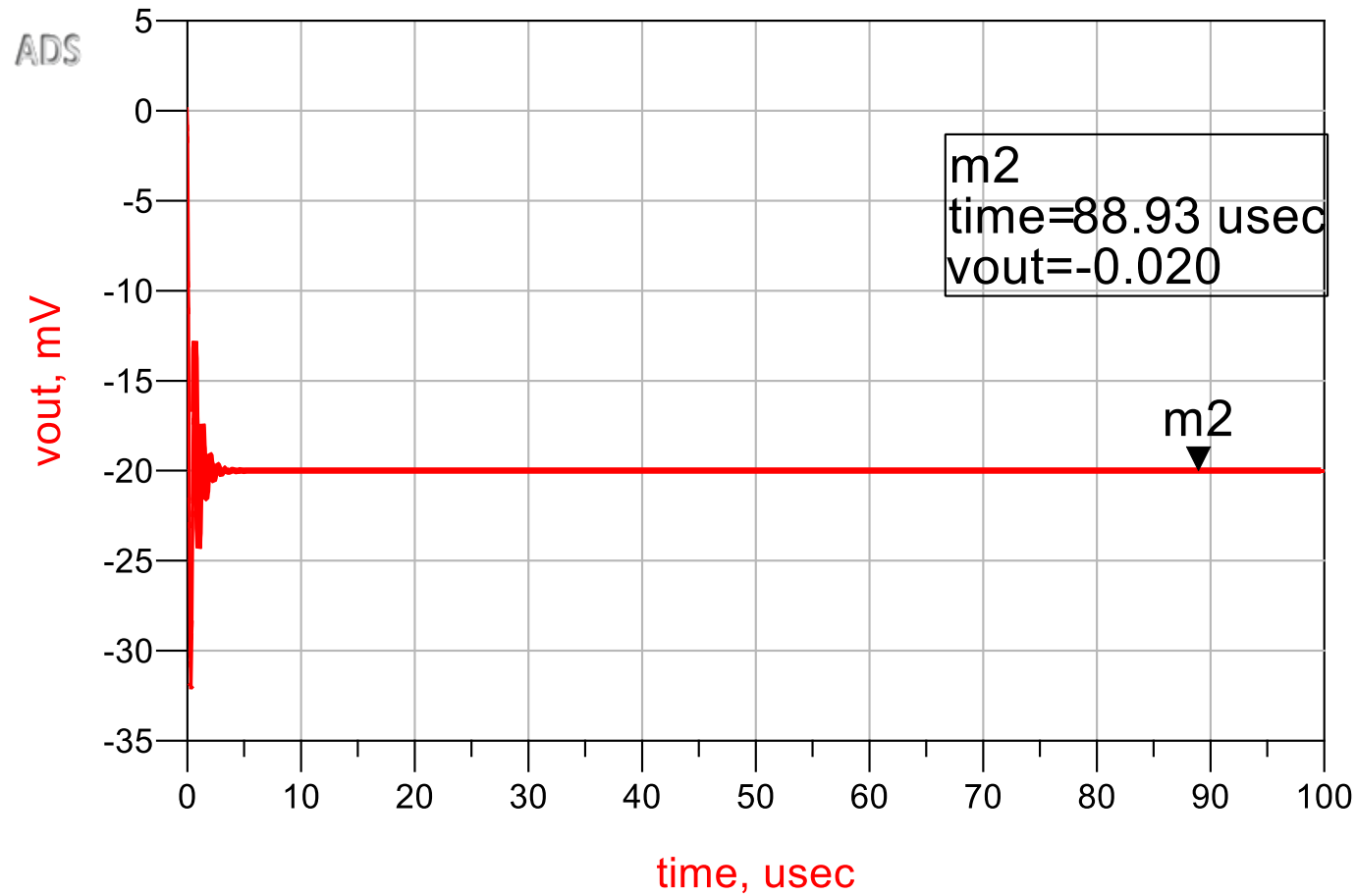

Miller Compensation

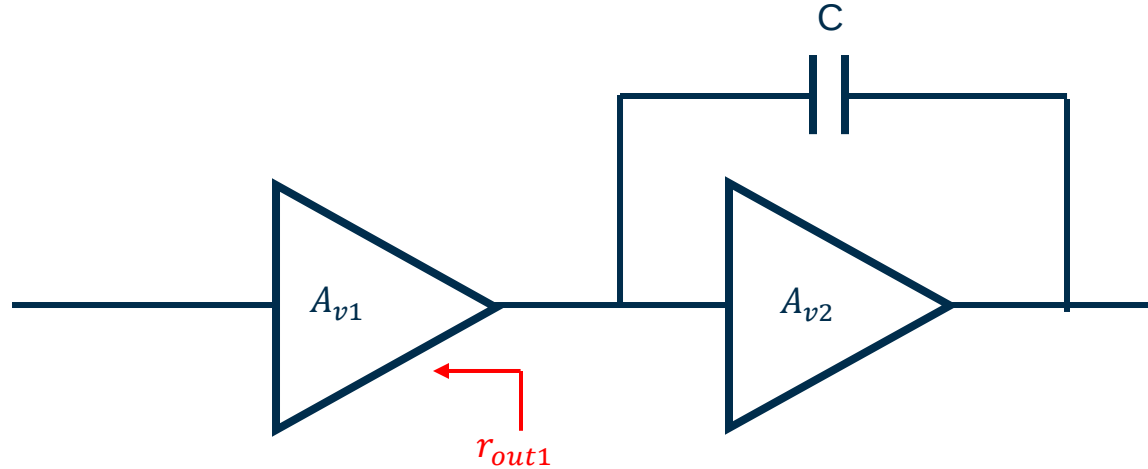- In multi-stage designs, we typically see this kind of configuration:



- The capacitance in Feedback will be enhanced by Miller effect:
- $(C \times (1 + A_{v2}))$, forming a time constant with r_{out1} (which is high), and lower the pole frequency at the input of the second stage significantly, which is typically the lowest pole frequency in the chain